

WORKSHOP ON LTSPICE



Fabrice WATEAU



What and why LTSPICE

- What ?
 - Analog part of pspice simulation software
 - Drawing interface and component library provide by LTC
- Why ?
 - Free download on www.linear.com/designtools/software/
 - Easy to use
 - But only analog analysis

Objective

- See the different ways to use this software
- Use LTSpice as an help during futur studys and projects

How do we work together ?

- 1st day :Presentation of the software and its possibilities
- From 2nd to 8th day :
 - First step with Ltspice
 - .OP, .DC, .TRAN and .AC simulation
 - ,STEP, .PARM and .MEAS add tools

For all simulations

- First we perform simulation together
- Second you try yourself on exercises
- The 9th day you try to use the new knowledges to resolve some small problems with Ltspice and my help,

OVERVIEW

Main simulation tools

- .OP : calculate the operating point of a circuit
- .DC : the same as .OP but for several values of one/several voltage(s) or current source. The result is given in a graph
- .TRAN : use simulator as a scope to see the timing diagram of different signals
- .AC : calculate the frequency response of circuit

OVERVIEW

Additional tools

- .STEP use with .PARAM command allows to perform analysis in which value of component can be varied .
- .MEAS allows to perform measurement on the result of the analysis (timing periode, frequency, max and min value of a curve, ...)

Analysis







Different steps to perform a simulation

1. Create a new sheet and save it on a folder specially created for all the files of the simulation
2. Drawing schematic
 - Place and move component. **Don't forget the ground**
 - Place wire to connect components
 - Place label to mark the most important node
3. Set the analysis (.OP, .DC, .TRAN or .AC)
4. Run simulation
5. Interpret results

Drawing schematic

Place and move component

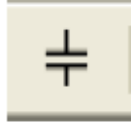
Select component by press a key or click on the correspondant pictures in the tool bar

Component	Press Key	Click	Component	Press Key	Click
Resistor	R		Diode	D	
Capacitor	C		Other component	F2 key	
Inductor	L		Ground	G	


Move the mouse until the position you want, and left click to place the component.

Drawing schematic

Place and move component

To move and rotate a component, it must be select (grey). It's not, select it with  and use « CTRL+R » to turn it, and mouse to move it.

Fixed component,
cannot move or
rotate

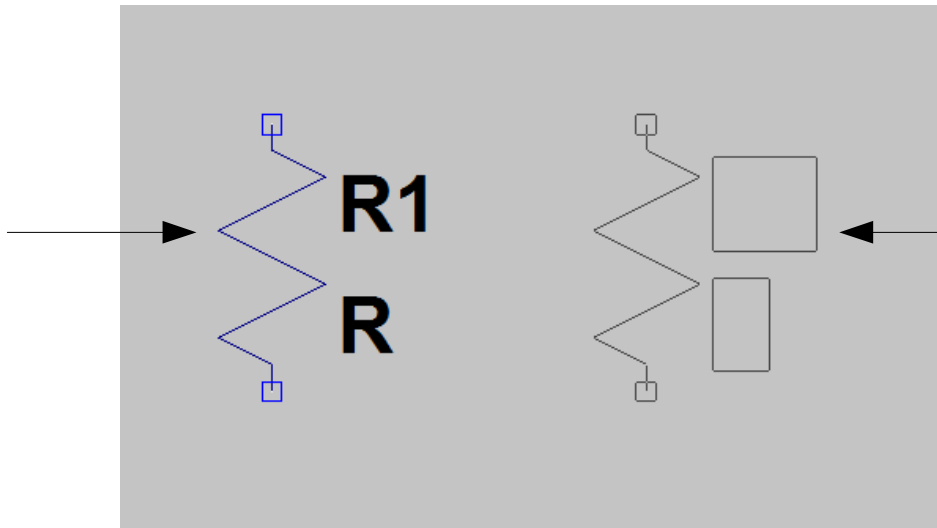

Not fixed component,
can move and rotate


Drawing schematic

Connect component : trace wire

Press « F3 » key or click on  to select wire tools.

Left click to change direction

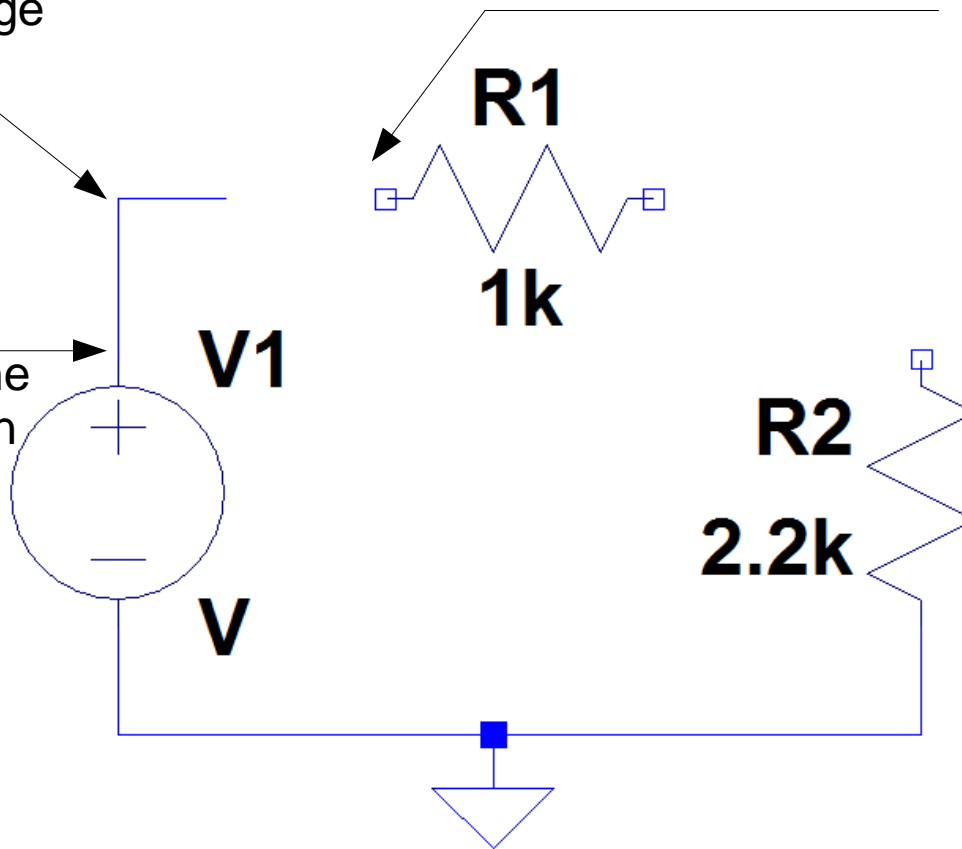
Left click on the terminal point of one component to begin




Left click on the terminal point of the other component what you want connect, or right click to finish the wire


Drawing schematic

Place label

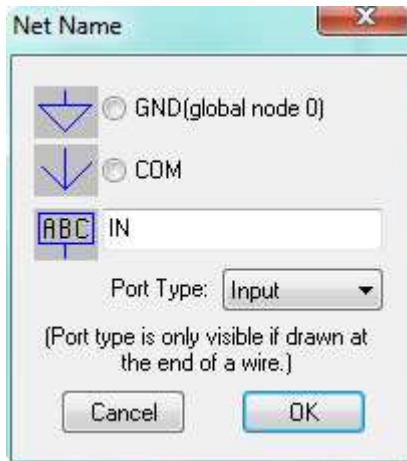Press « F4 » key or click on  to select label tools.



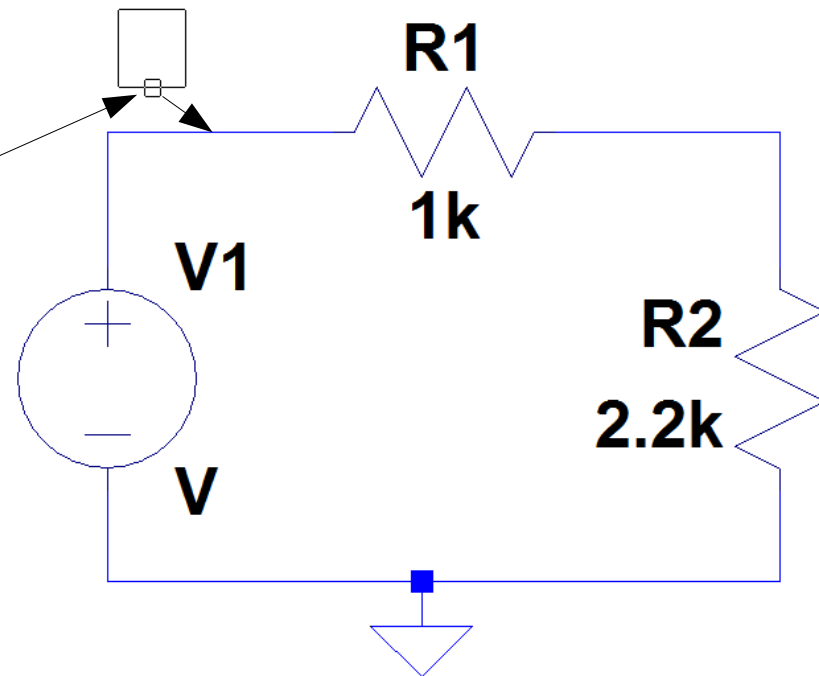
Place the node on the wire on what you want give name.




Comment : label can also be use to connect 2 nodes. Just give the same name at the 2 nodes

.OP analysis

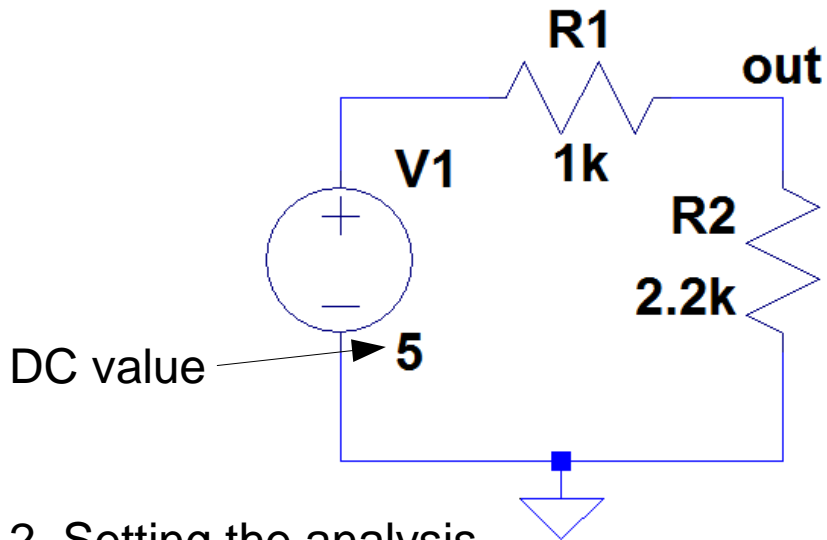1. Draw the schematic study, and modify (Right click on V) the DC voltage of V1




2. Setting the analysis

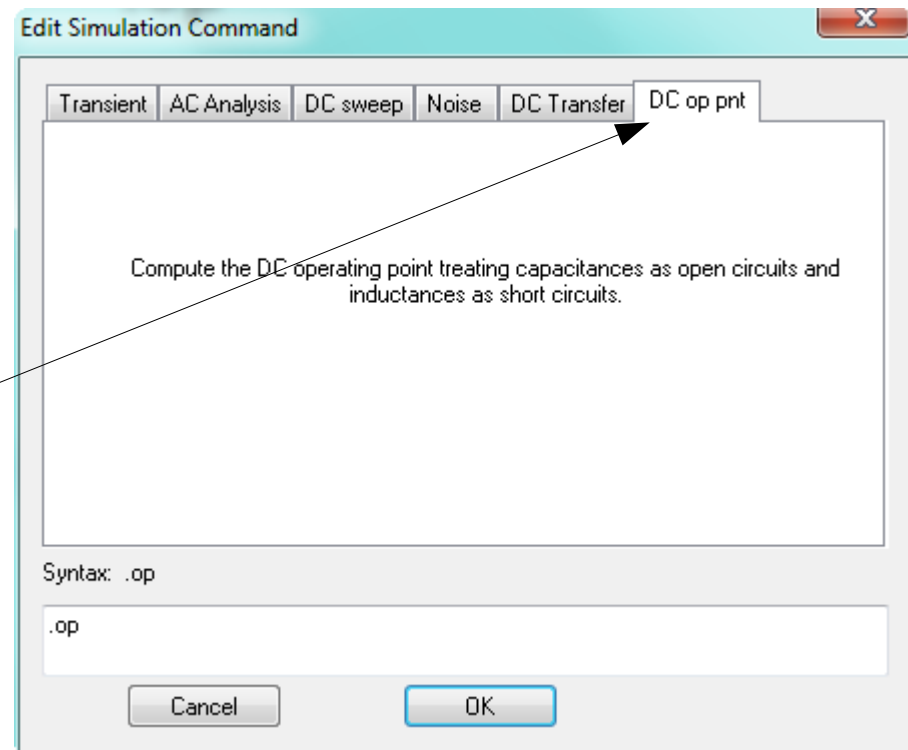


.OP analysis

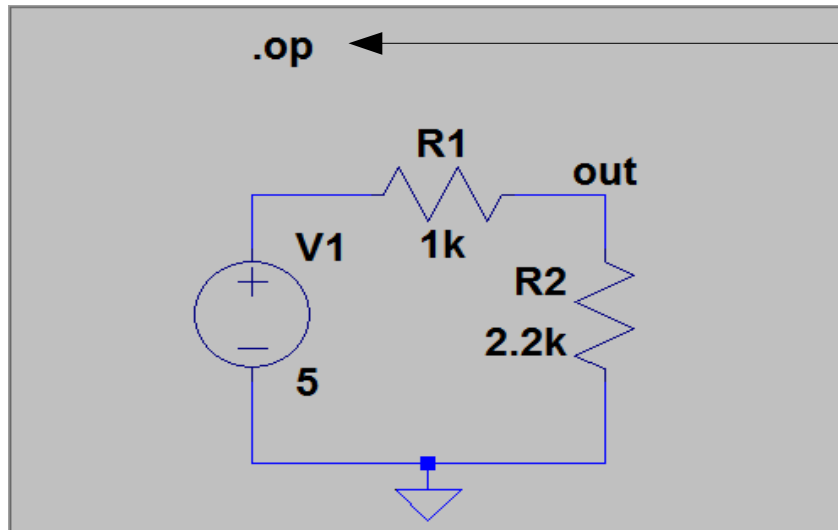
3. Click on schematic to valid your choice



left click on the schematic to put it

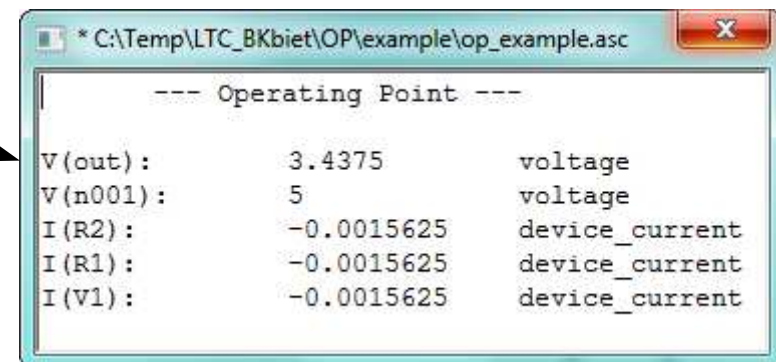4. Run the analysis 

A new window appears and contains the value of the operating point



A screenshot of a software window titled '* C:\Temp\LTC_BKbiet\OP\example\op_example.asc'. The window displays the following text:




```
--- Operating Point ---  
V(out):          3.4375      voltage  
V(n001):         5          voltage  
I(R2):           -0.0015625  device_current  
I(R1):           -0.0015625  device_current  
I(V1):           -0.0015625  device_current
```

.DC analysis

- Perform .op analysis for any value of one (or more) voltage (or current) source(s).
- Example: with the same circuit, we want to know how change the output voltage, if the input change.
- You need only change the analysis setting by choosing DC sweep

.DC analysis Setting


- Setting the DC sweep analysis

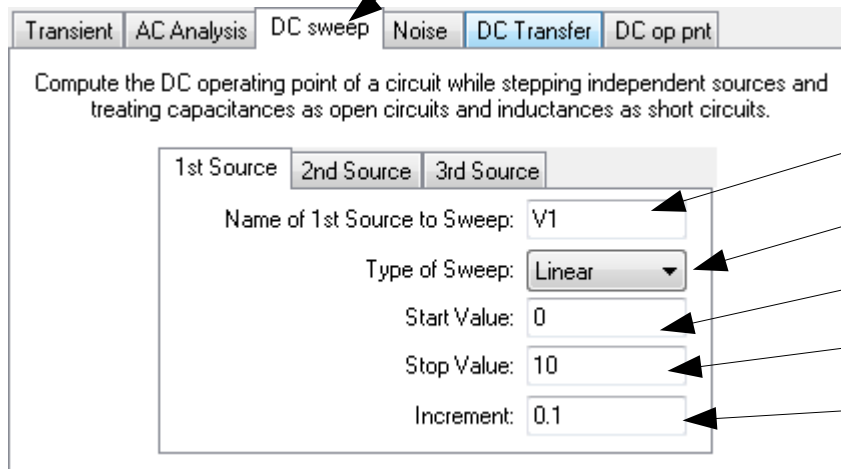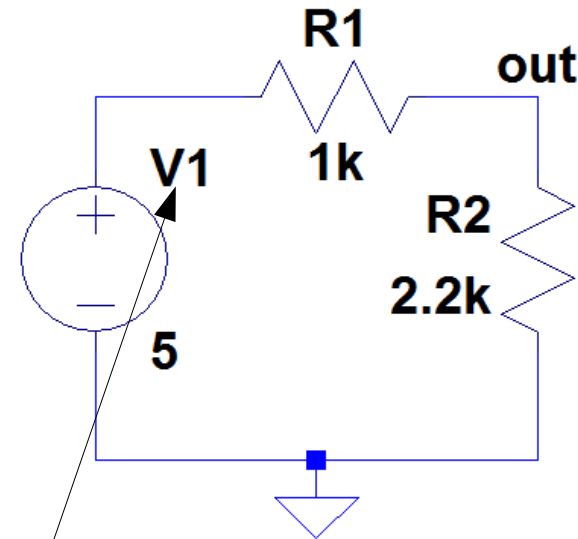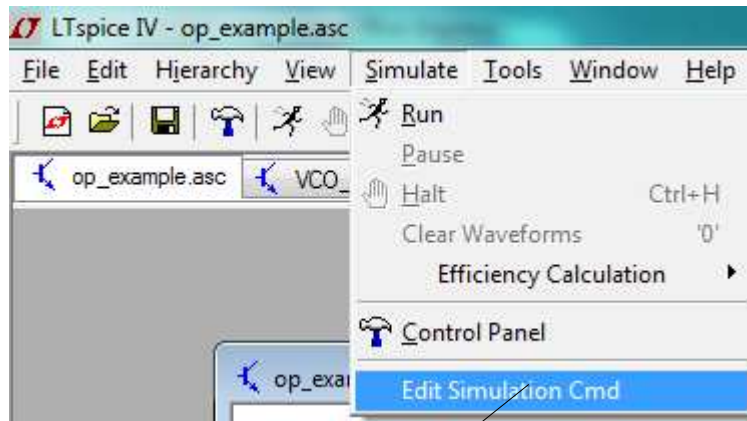

- Name of the source which change of value
- Linear, octave, decade or list of value
- First value simulate
- Last value simulate
- Voltage range between two simulation

.DC analysis Result

- Result is a graph :

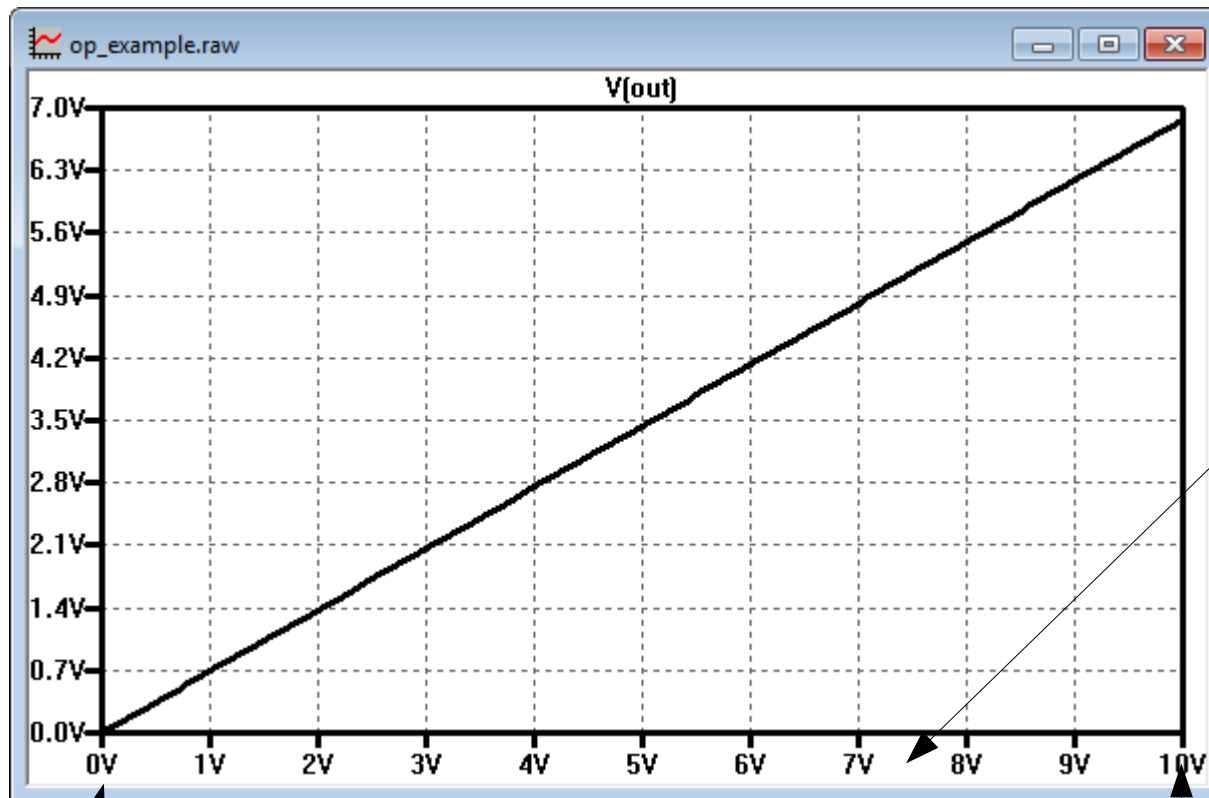

Linear scale

Horizontal axis : value of V1



Start value

Step between 2 values

Stop value

.DC analysis Example


- Load line

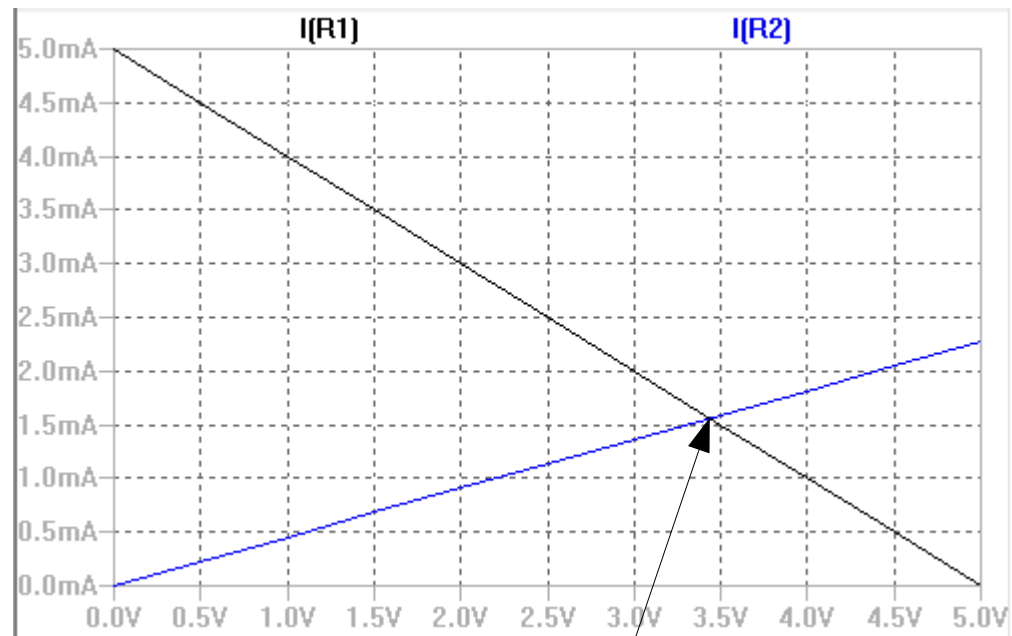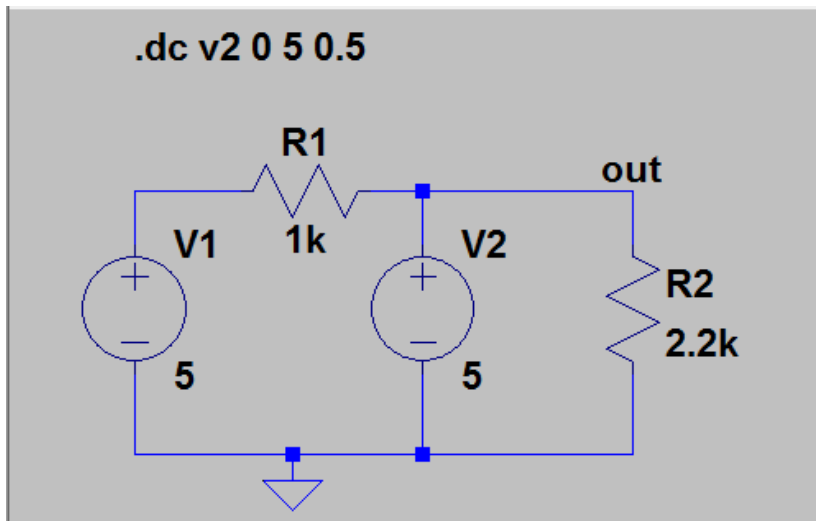

Operating point

.OP and .DC Training

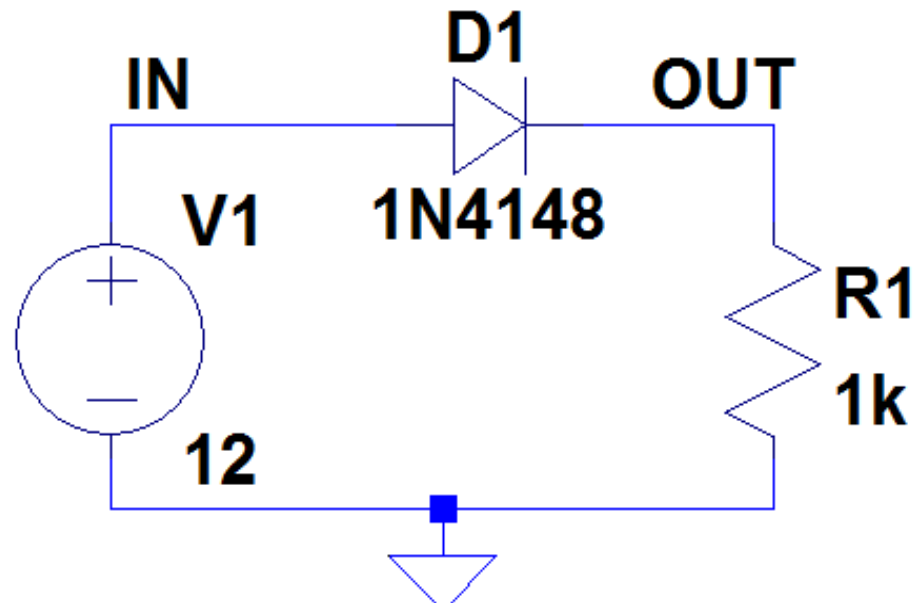1. Propose a simulation which give the operating point of the following circuit




2. Propose a new simulation which allows to have the same result by tracing diode and « generator+resistor » characteristics

.DC sweep

Training

- Propose analysis which allow you to plot the 3 characteristics of BJT (Bipolar Junction Transistor),
 1. $I_b = f(V_{be})$ for $V_{ce} = 6V$
 2. $I_c = f(I_b)$ for $V_{ce} = 6V$
 3. $I_c = f(V_{ce})$ for $0 < V_{ce} < 12V$ pour $I_b = 0$ to $100\mu A$ by step $10\mu A$

.TRAN analysis

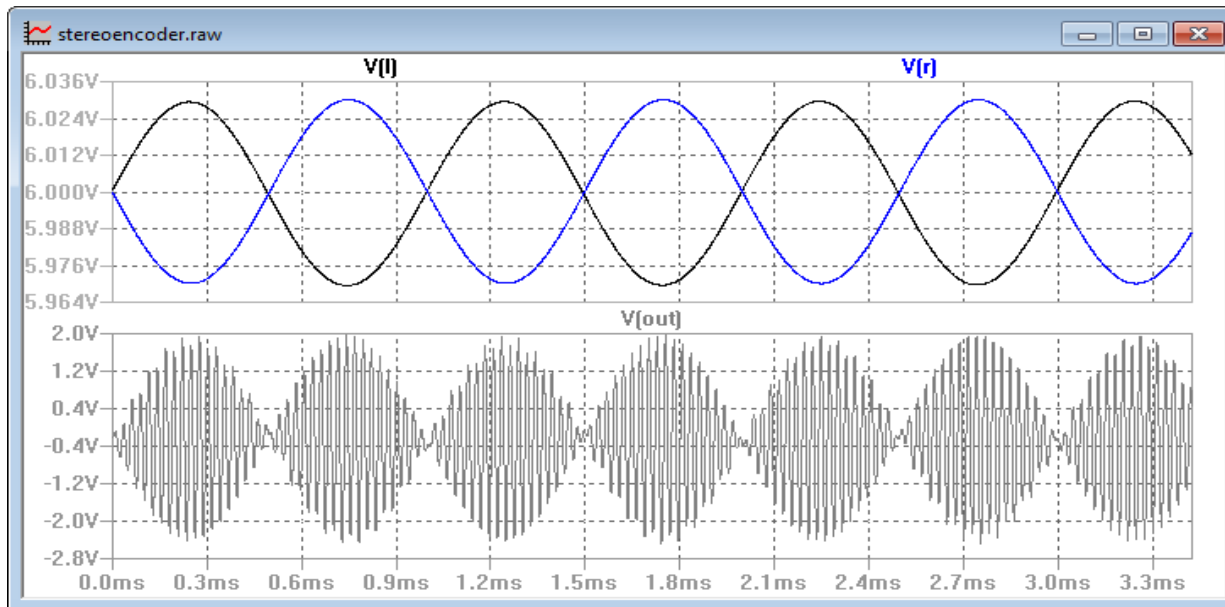


- Transient analysis is used when you want to see the timing diagram of the waveform (voltage and/or current) of a circuit.
- In practical, it's the same result as an scope

.TRAN analysis

Set up the voltage or current source

1
Right on the source symbol

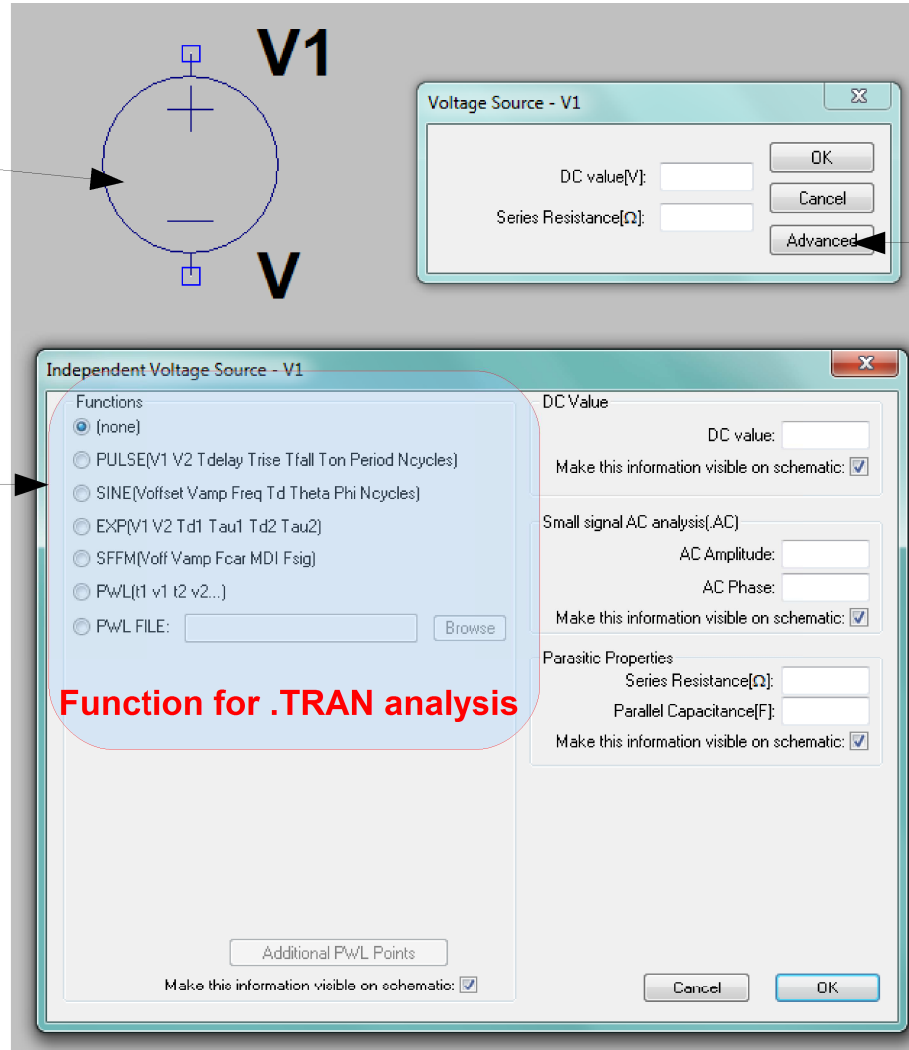3
Choose one of this function. Each are describe below.




2
Click on Advanced button

.TRAN analysis

PULSE DEFINITION

Von

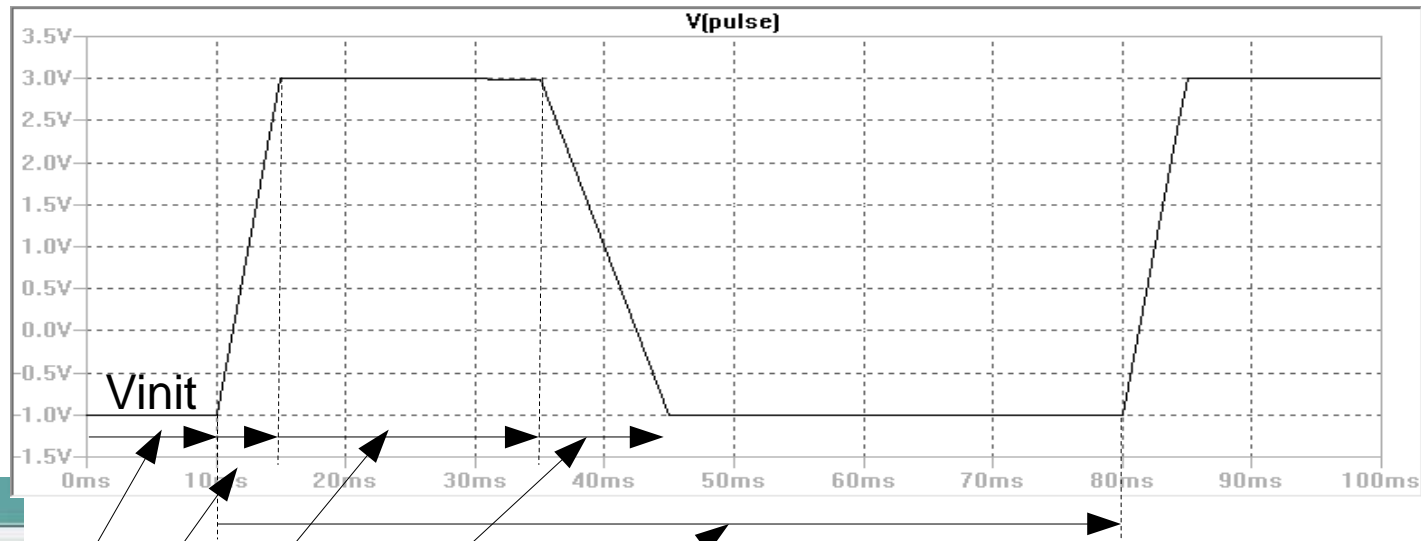

Independent Voltage Source - V1

Functions

- [none]
- PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- SFFM(Voff Vamp Fcar MDI Fsig)
- PWL(t1 v1 t2 v2...)
- PWL FILE:

Vinitial[V]: -1
Von[V]: 3
Tdelay[s]: 10m
Trise[s]: 5m
Tfall[s]: 10m
Ton[s]: 20m
Tperiod[s]: 70m
Ncycles: 3

.TRAN analysis

SINUS DEFINITION

Independent Voltage Source - V1

Functions

- (none)
- PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- SFFM(Voff Vamp Fcar MDI Fsig)
- PWL(t1 v1 t2 v2...)
- PWL FILE:

DC offset[V]:

Amplitude[V]:

Freq[Hz]:


Tdelay[s]:

Theta[1/s]:

Phi[deg]:



Ncycles:

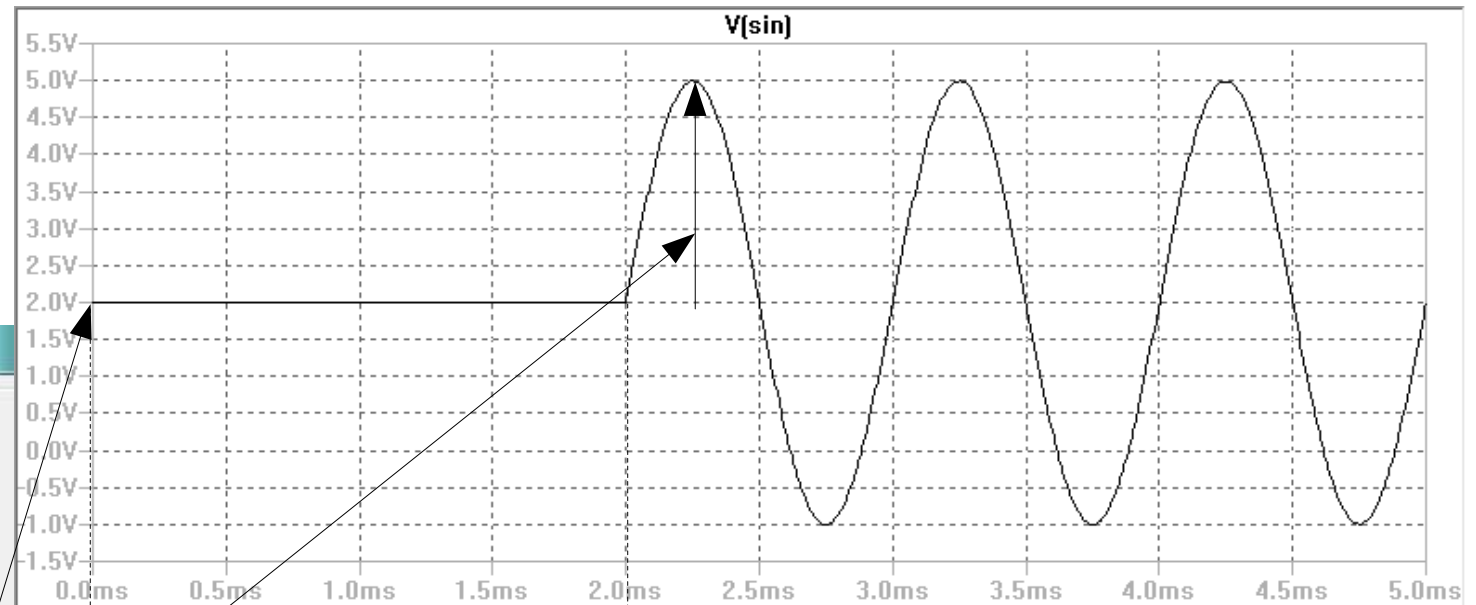Make this information visible on schematic:



.TRAN analysis



PWL (Piece Wire Linear) DEFINITION

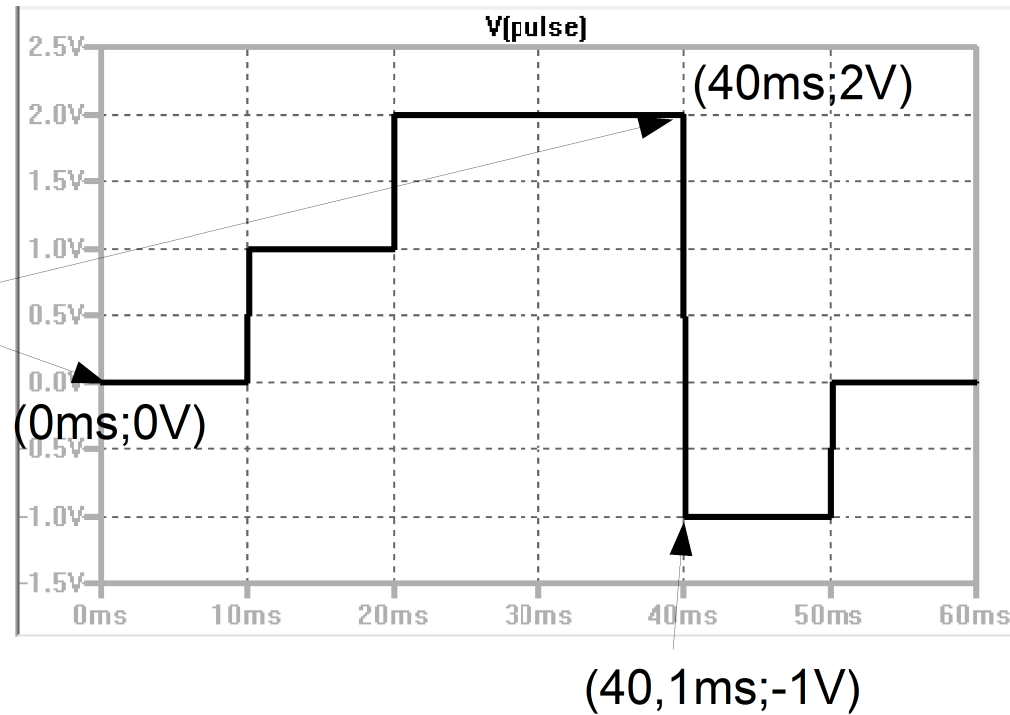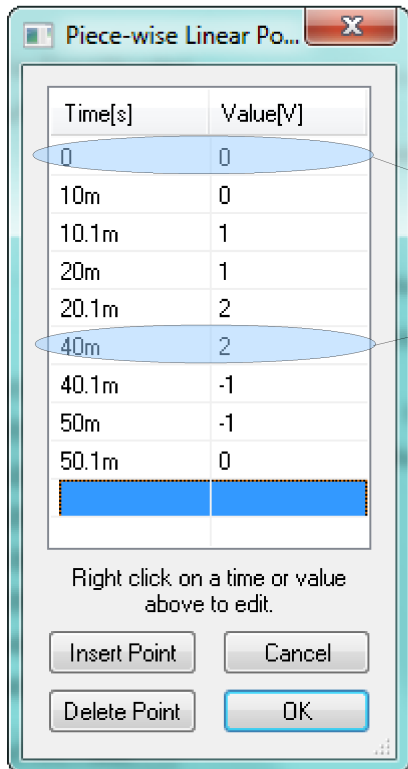

.TRAN analysis

Example : RC low pass filter

- Draw the circuit below :

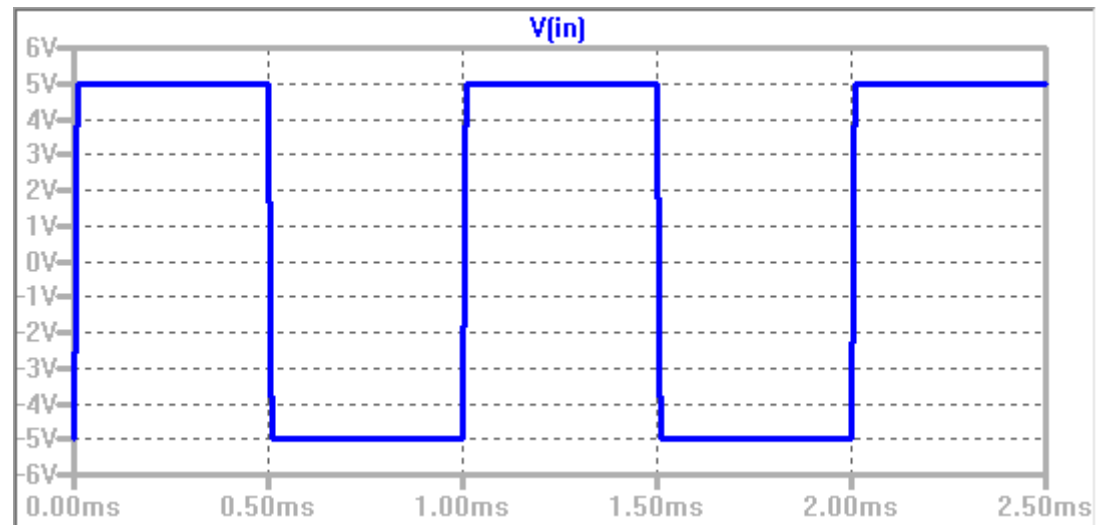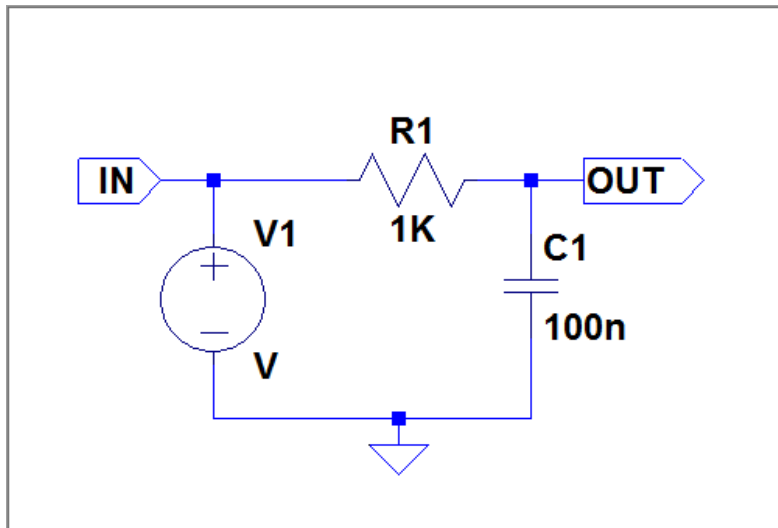

- Set the voltage source as it provides a square wave as defined above (at right)
- Set transient analysis to observe 10 periods of $V(IN)$ and $V(out)$.

.TRAN analysis

Example : RC low pass filter

- After drawing schematic, right click on the voltage source and set as below :

The image shows a configuration dialog box for a PULSE function. The 'Functions' section has several radio buttons, with 'PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)' selected. Below this, there are input fields for various parameters: Vinitial[V] (-5), Von[V] (5), Tdelay[s] (0), Trise[s] (0.01m), Tfall[s] (0.01m), Ton[s] (0.49m), Tperiod[s] (1m), and Ncycles (empty). There is also a 'Browse' button next to the 'PWL FILE:' field. At the bottom, there is a checkbox labeled 'Make this information visible on schematic:' which is checked.

Functions

(none)

PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)

SINE(Voffset Vamp Freq Td Theta Phi Ncycles)

EXP(V1 V2 Td1 Tau1 Td2 Tau2)

SFFM(Voff Vamp Fcar MDI Fsig)

PWL(t1 v1 t2 v2...)

PWL FILE:

Vinitial[V]:

Von[V]:

Tdelay[s]:

Trise[s]:

Tfall[s]:

Ton[s]:

Tperiod[s]:


Ncycles:

Make this information visible on schematic:

.TRAN analysis

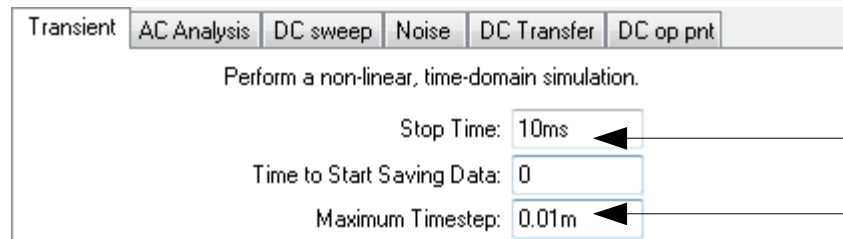Example : RC low pass filter


- After setting the source, set the analysis as below :




10periode => 10*1ms

As the rise and fall time in pulse definition

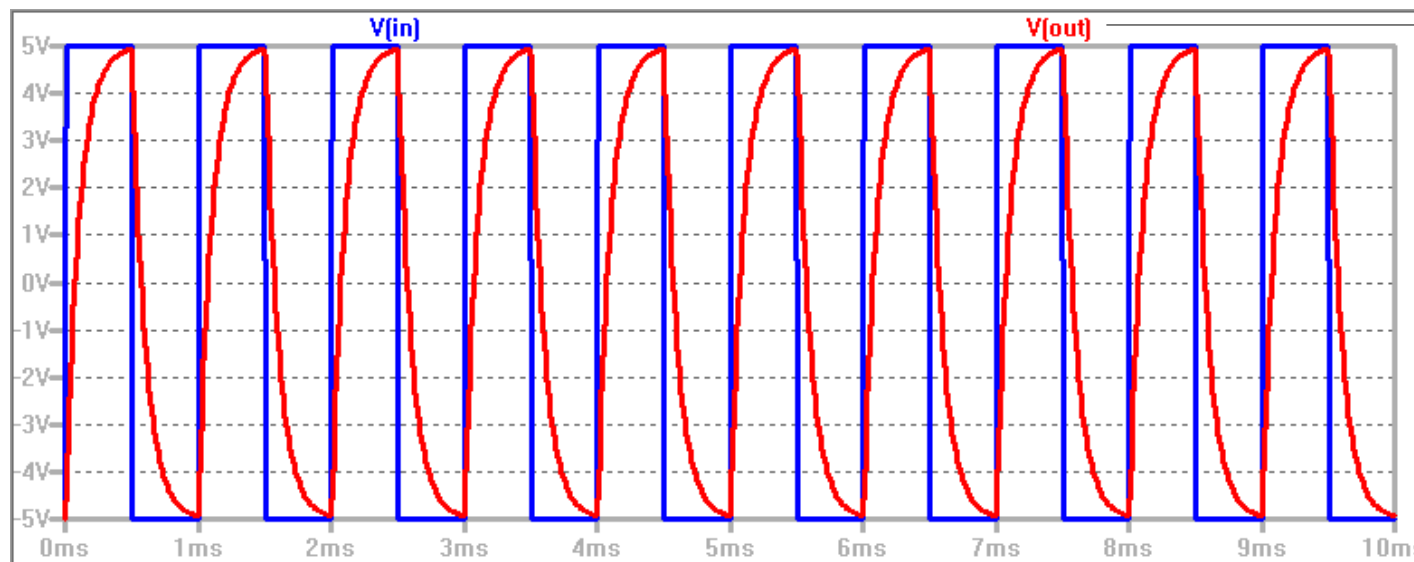- Run analysis and display v(IN) and V(out)




CRTL+click on the name

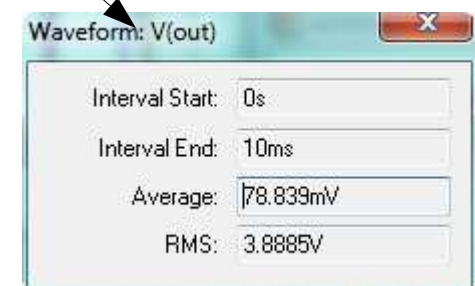

.TRAN analysis FFT

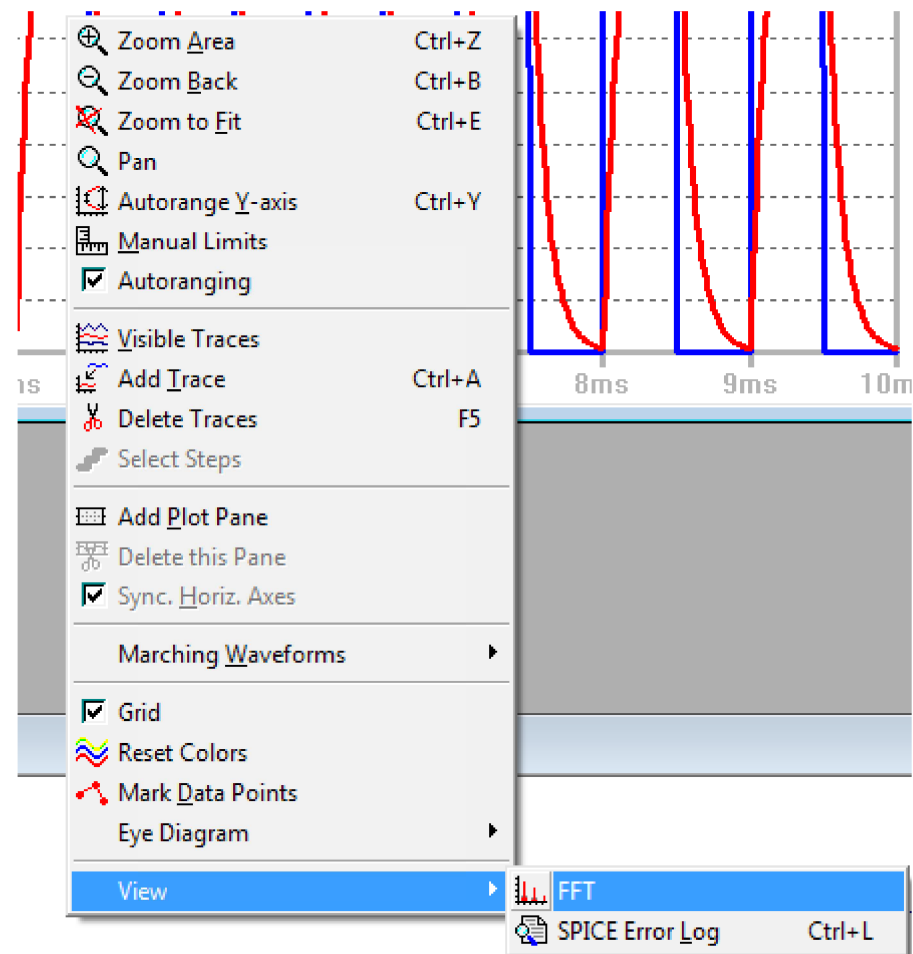
- You can see the spectrum of signal by right click on the probe windows and in the list choose « view », the « FFT » :



.TRAN analysis


FFT

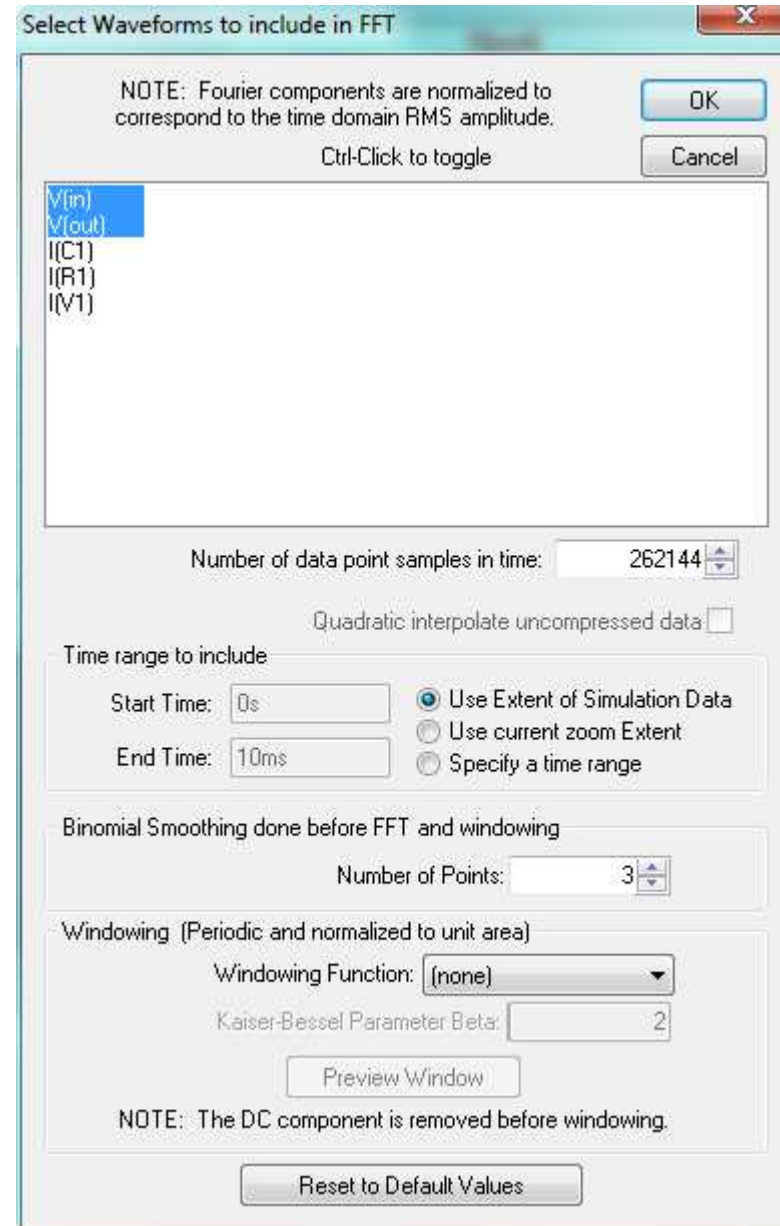- Select V(IN) and V(OUT) and click « OK » .
- In the new window select the both V(IN) and V(OUT) again and click Ok.




.TRAN analysis FFT


Modifie Y-Axis.

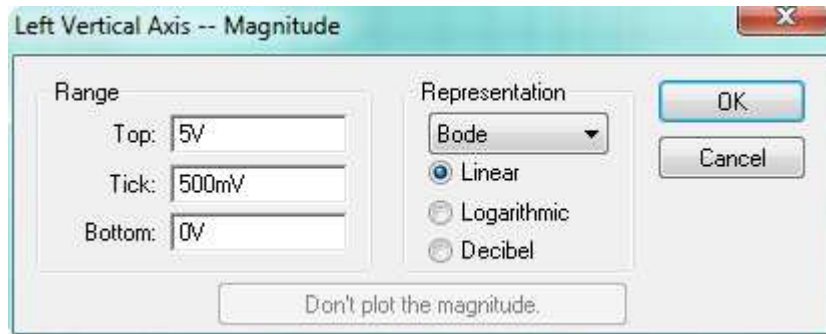

Modifie X-Axis.

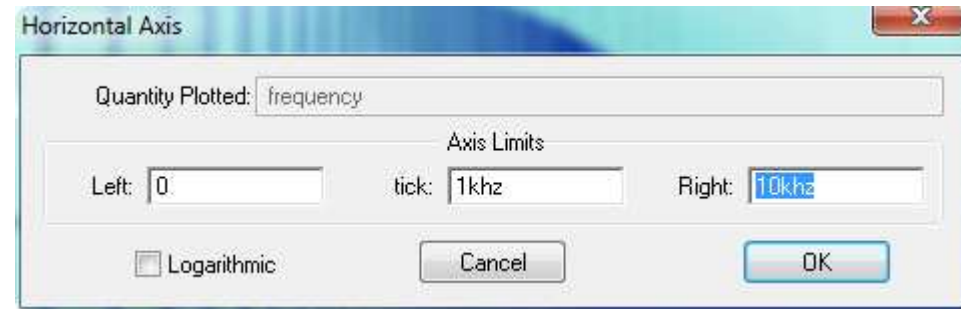

- You must have :

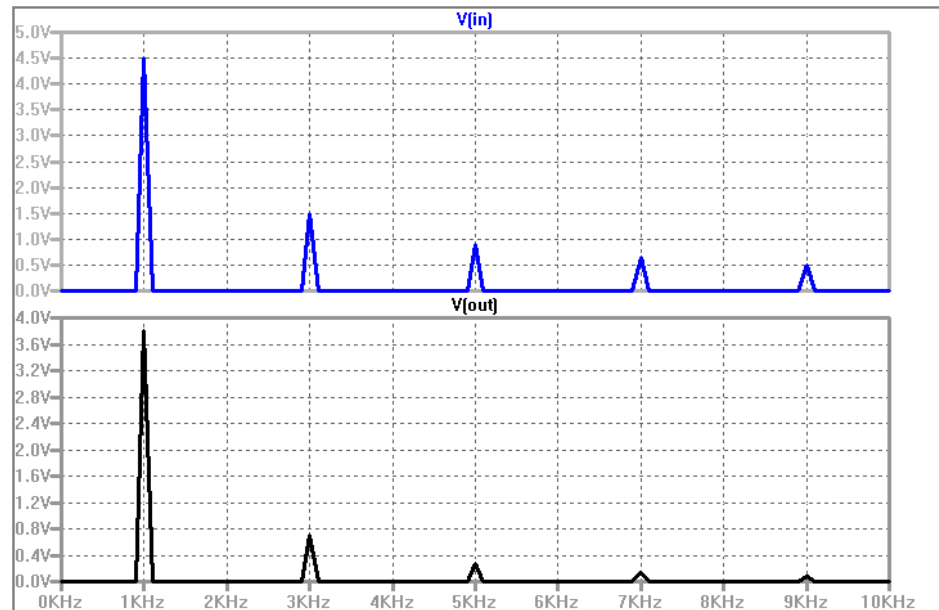


.TRAN analysis


Training : setting source

Place voltage source on a new schematic project, and set to the waveform as follow :

1

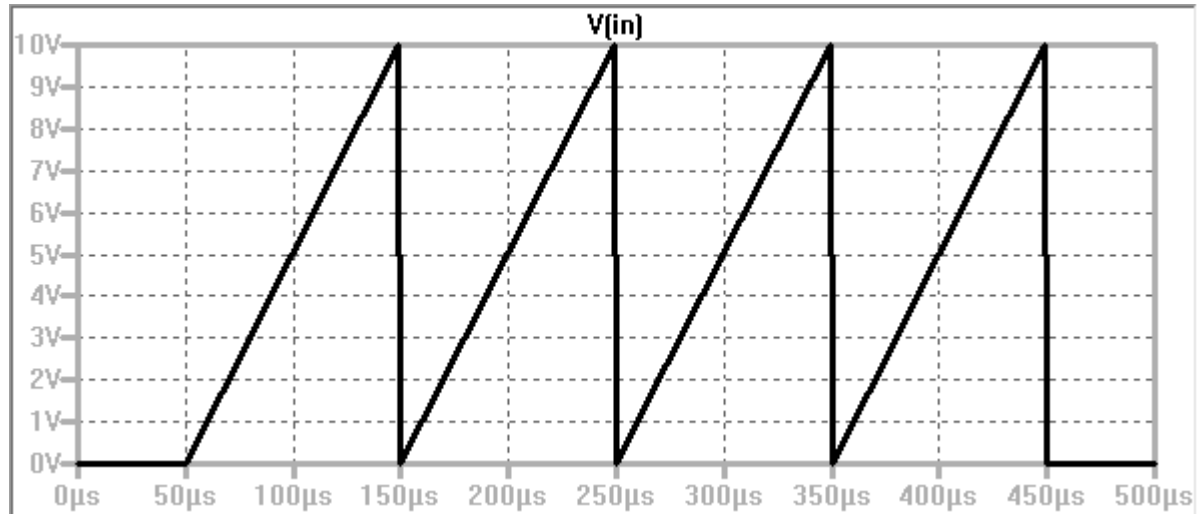

2

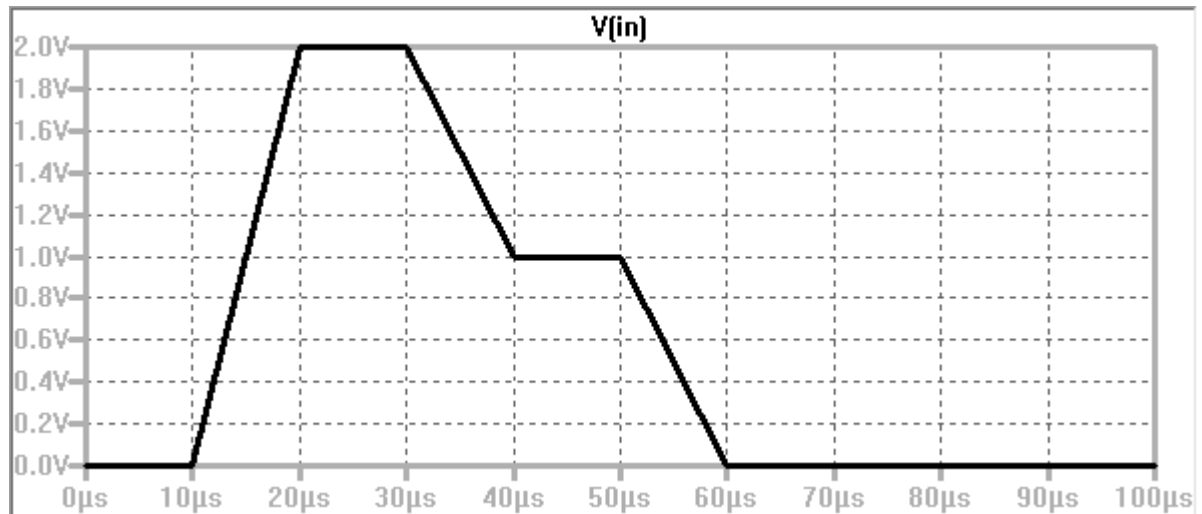


.TRAN analysis


Training : setting source

Place voltage source on a new schematic project, and set to the waveform as follow :

3

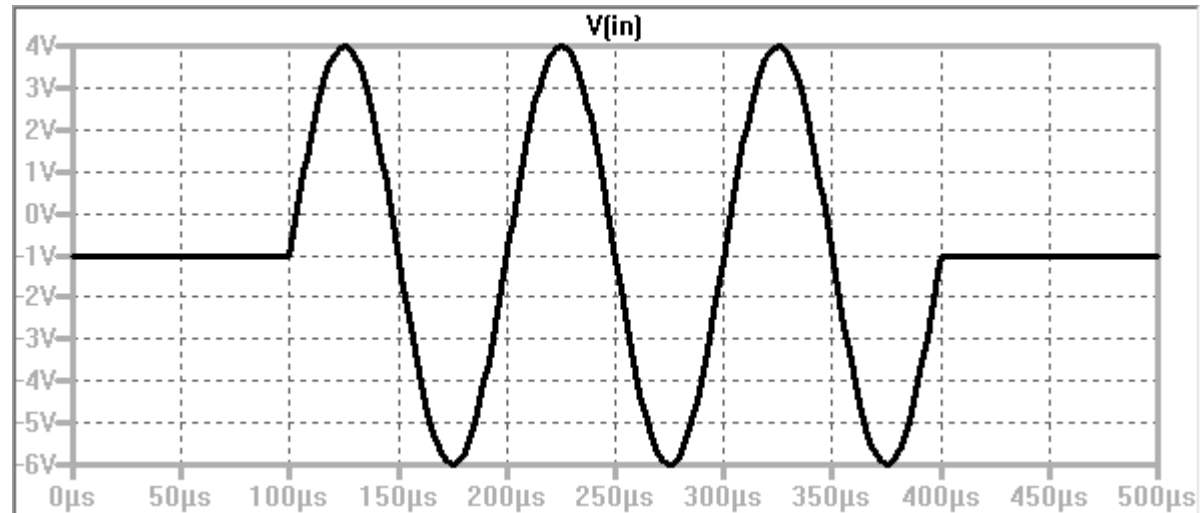



4

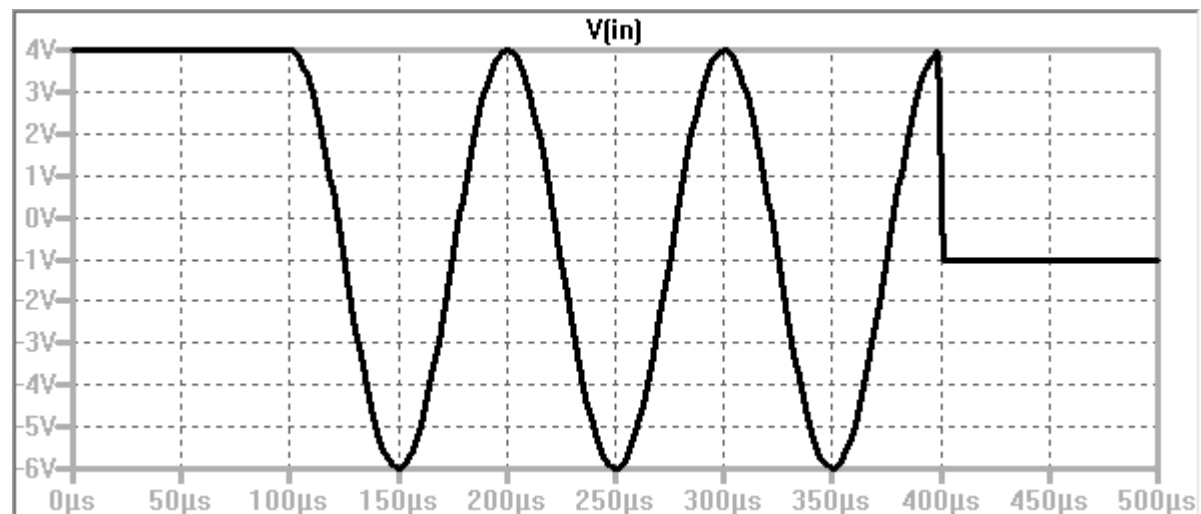


.TRAN analysis

Training : rectifier

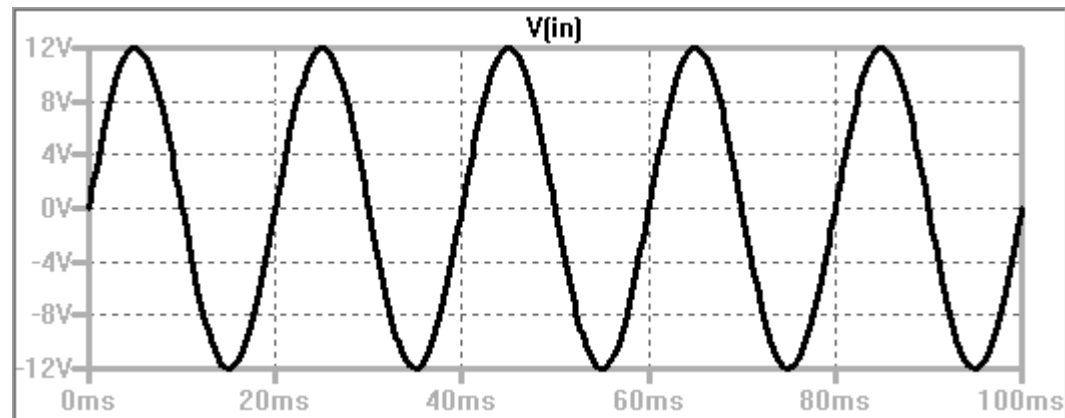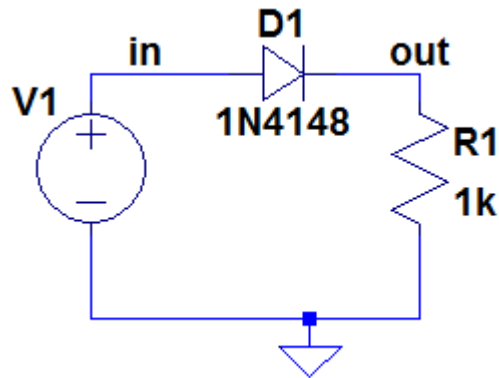
- Draw the schematic as below and perform a transient analysis for an sinus wave input as below, display V(in) and V(out), and I(D1) in an other pane:



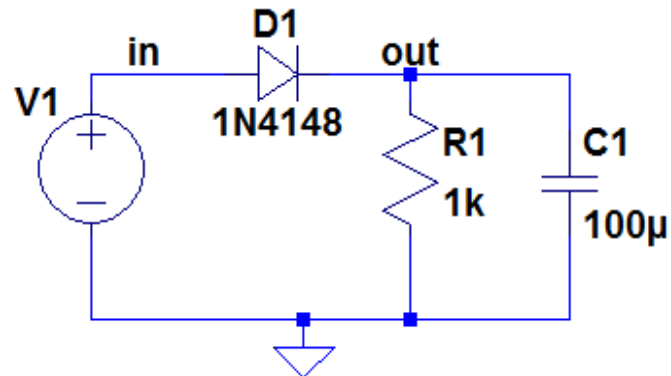- Modify the schematic as below and run again



.AC analysis

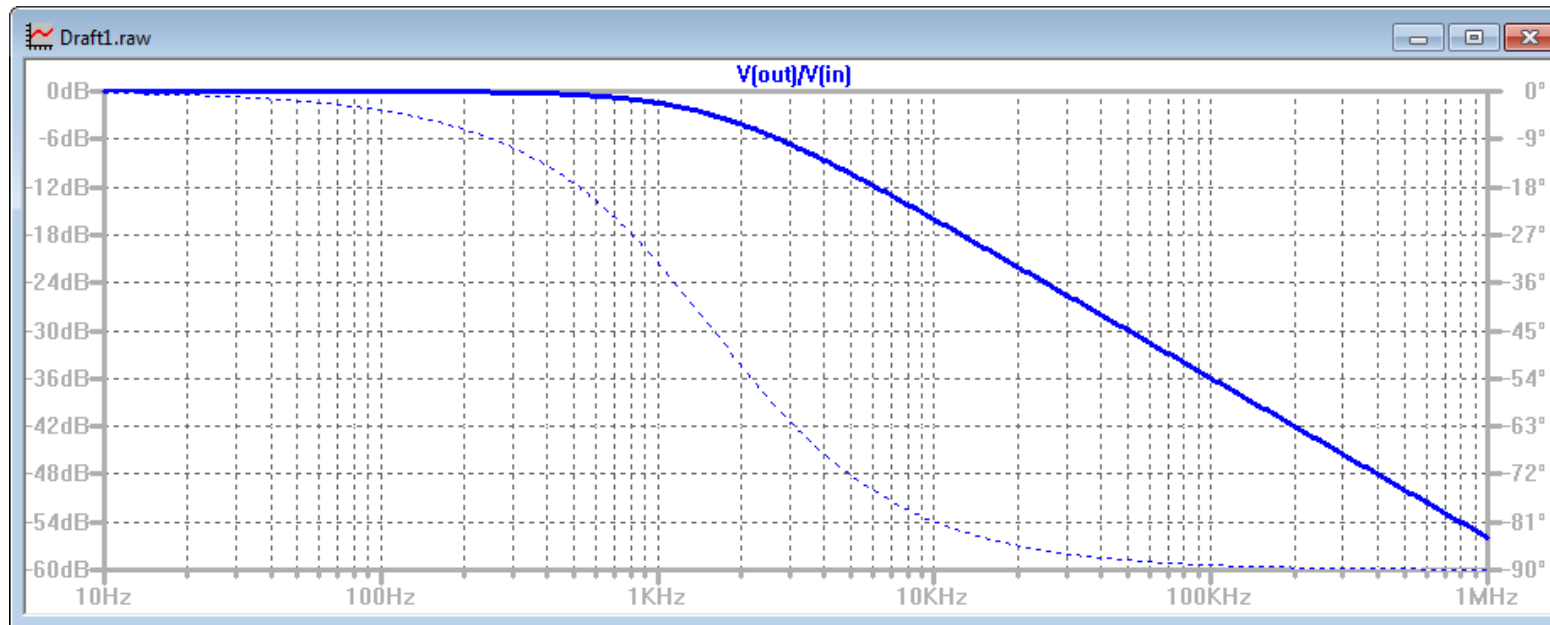


- Perform an Small Signal AC Analysis Linearized around the DC Operating Point and display the diagram of magnitude and phase functions of frequency, impedance versus frequency,...
- This mode of analysis is useful for filters, networks, stability analyses, and noise considerations.

.AC analysis

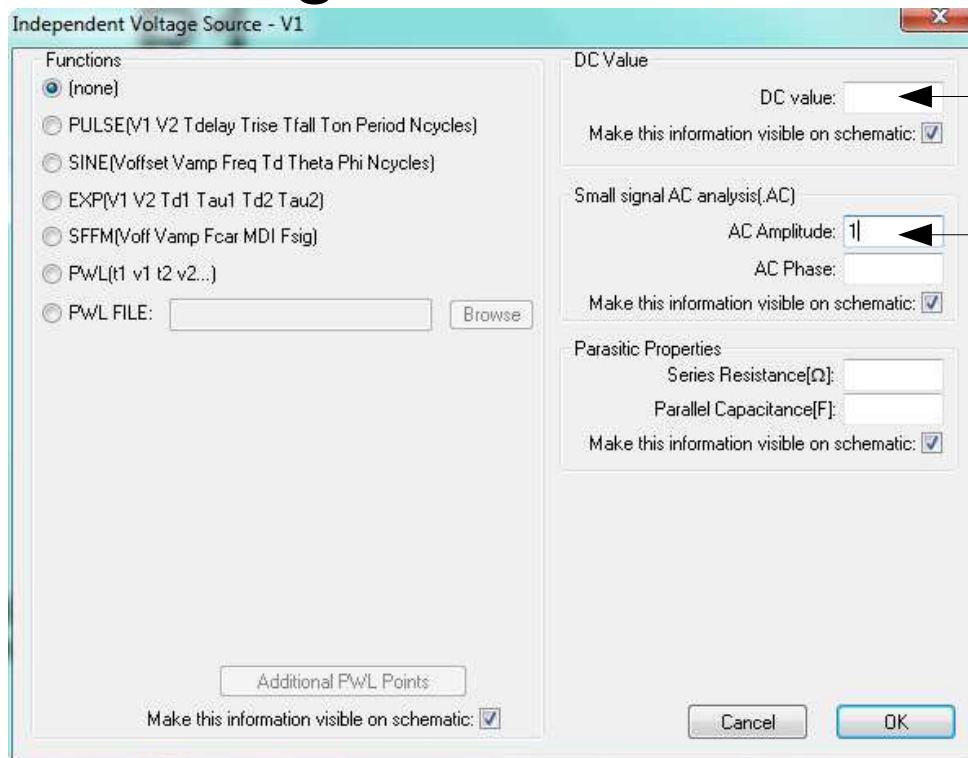Example : RC low pass filter


- After drawing schematic, right click on the voltage source and set as below :



Use by the software to calculate the operating point before linearization (0 if empty)

Amplitude of the sine wave used to drive the circuit


Circuit study

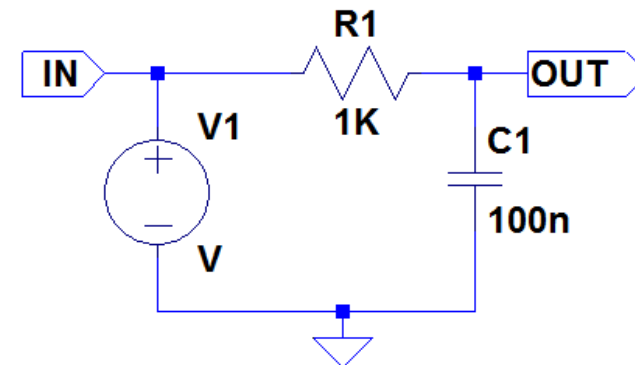

.AC analysis

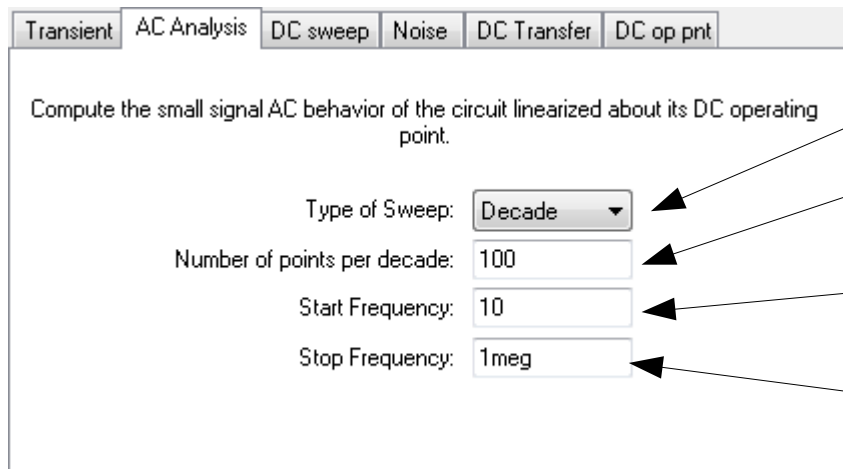Example : RC low pass filter

- After set voltage source, set analysis as below :




Decade, octave or linear

Take sufficient point if you want smooth curves

At least 1 decade lower than the theoretical low cut off frequency

At least 1 decade higher than the theoretical low cut off frequency

Reminder :

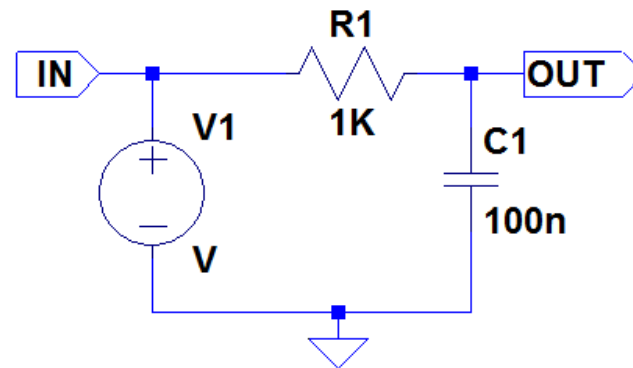

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + r_1 C_1 s}$$

$$f_{cutoff} = \frac{1}{2 * \pi * R_1 * C_1}$$


- Run analysis

.AC analysis

Example : RC low pass filter

- result :


Left click on the name to modify

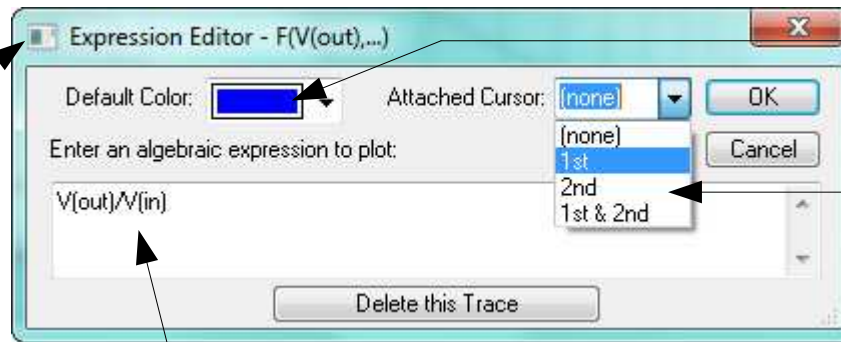

Change color

To use cursor on the curve


Enter the expression you want to display

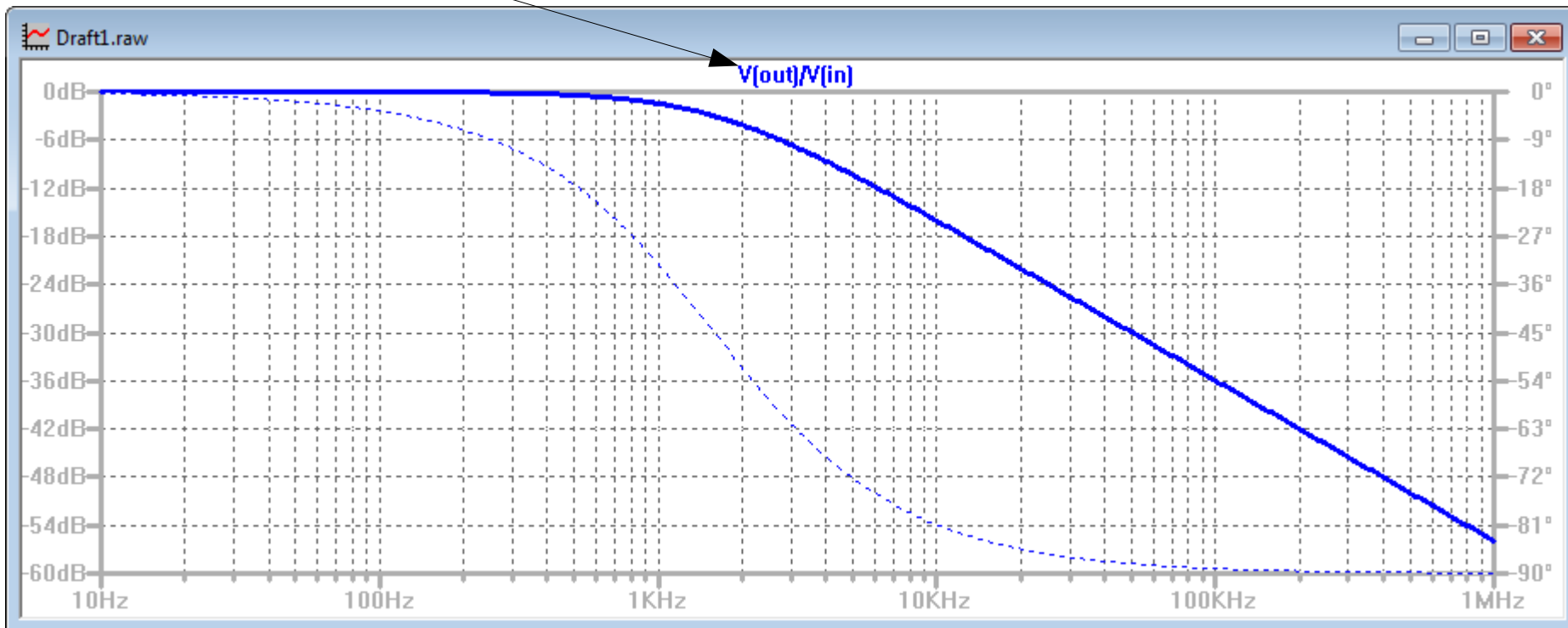

.AC analysis

Training : laplace function

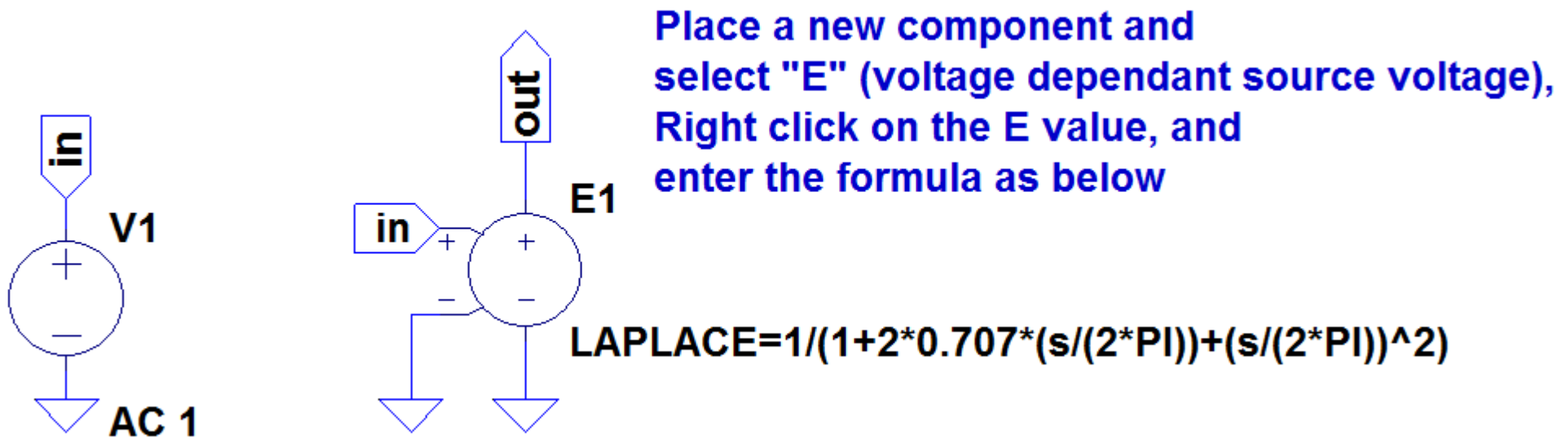
- Create a new schematic and draw as follow



- Set an AC analysis in decade between 0.1 and 10 hz, and run simulation.(you can change the value 0,707 of the damping factor to see its effect)

Additional tools

.PARAM .STEP

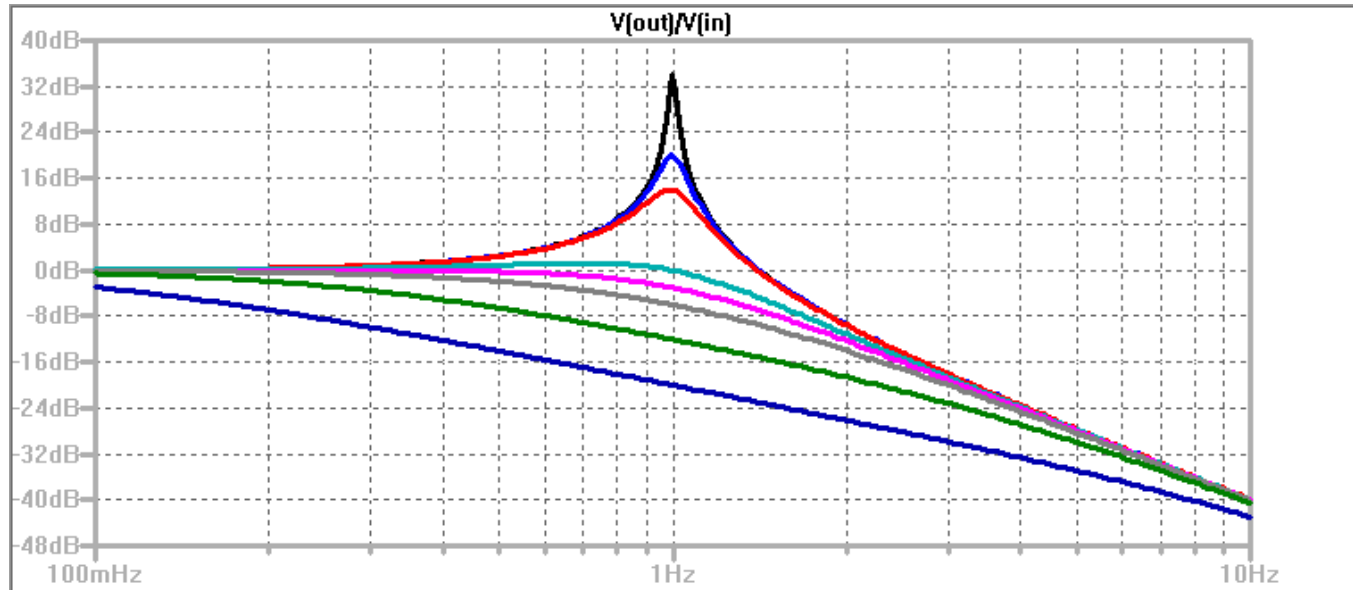




- Directive .PARAM allow you to create one or any user defined variable that you can use in place of component value, or for calculate an other parameter.
- Directive .STEP allow you to change the value of parameter step by step, then allow to repeat analysis for various values of parameters or component.

Additional tools

.PARAM .STEP : how to use

- How to simulate Potentiometer

Reminder : what is potentiometer ?

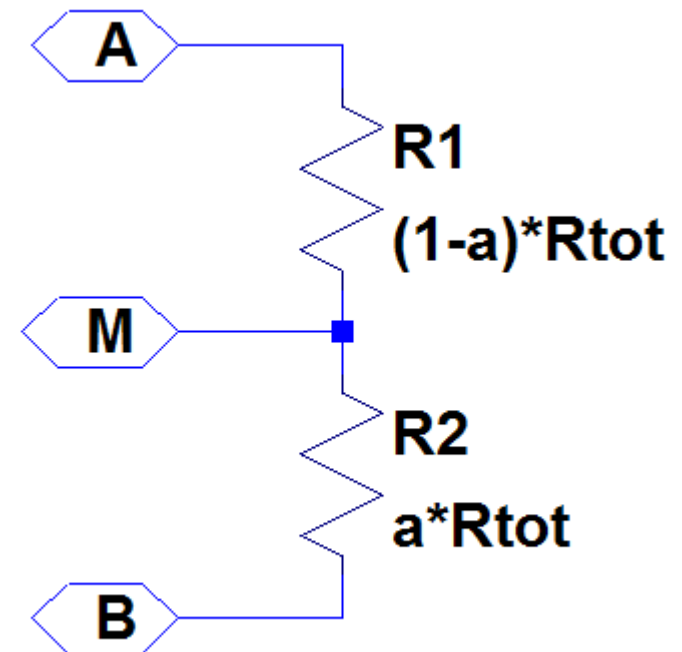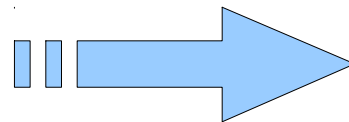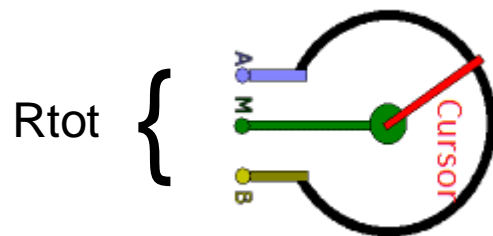

R_{tot} : value of the total resistor measure between nodes A en B. When you move cursor, resistor between A en M, and between M and B varied, with this relation :

$$R_{tot} = R_{AM} + R_{MB}$$

a : parameter which represent the cursor position :

$$0 < a < 1$$

We need 2 parameters :

- **R_{tot} : total resistor between nodes A and B**
- **a : cursor position**

Additional tools

.PARAM .STEP : how to use


- Create parameter : click on `.op` and write in the text box.

Syntax : `.param param_name=default_value`

Ex : `.param Rtot=10k, .param a=0.5`

- Affect to a component : Replace the value of the component by a relation between curly braces.

Ex : `10k => {(1-a)*Rtot+10m}`

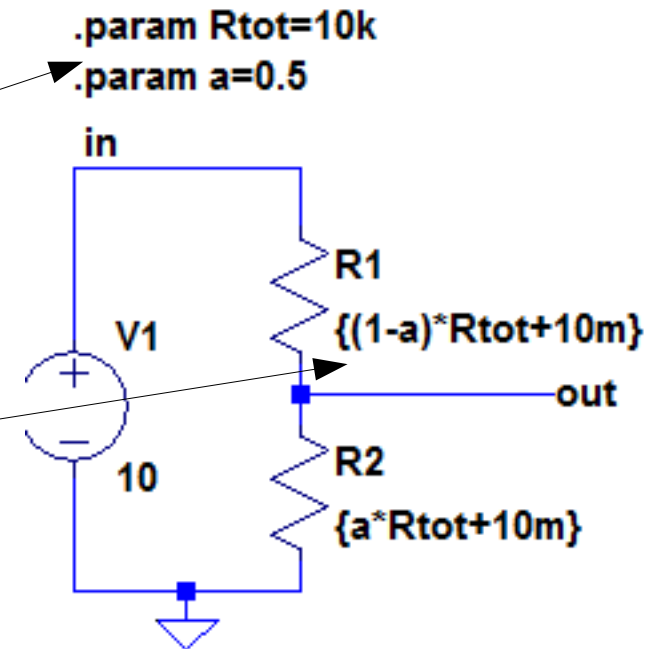

- Do vary : use the `.STEP` directive as follow :

`.STEP param param_name init Stop Step`

`.step param a 0 1 0.1`

`.op`

Name of parameter

Start value


Stop value

Step between 2 values

Additional tools

.PARAM .STEP : how to use


```
.param Rtot=10k  
.param a=0.5
```

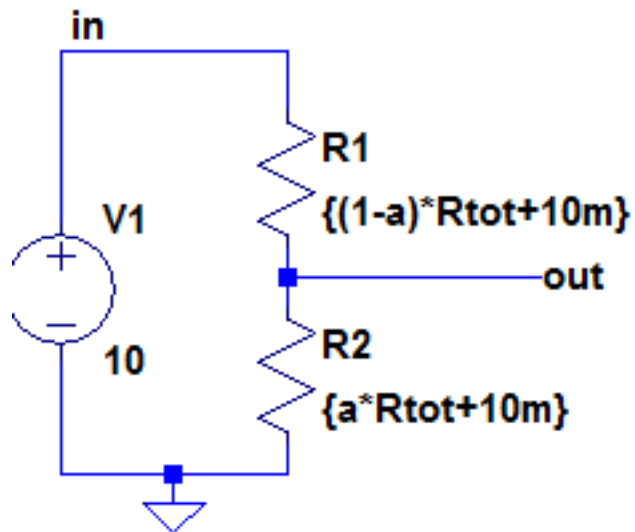

```
.step param a 0 1 0.1  
.op
```

The result is a curve which give the .OP analysis result for each value of the parameter a,


$V_{out}=f(a)$

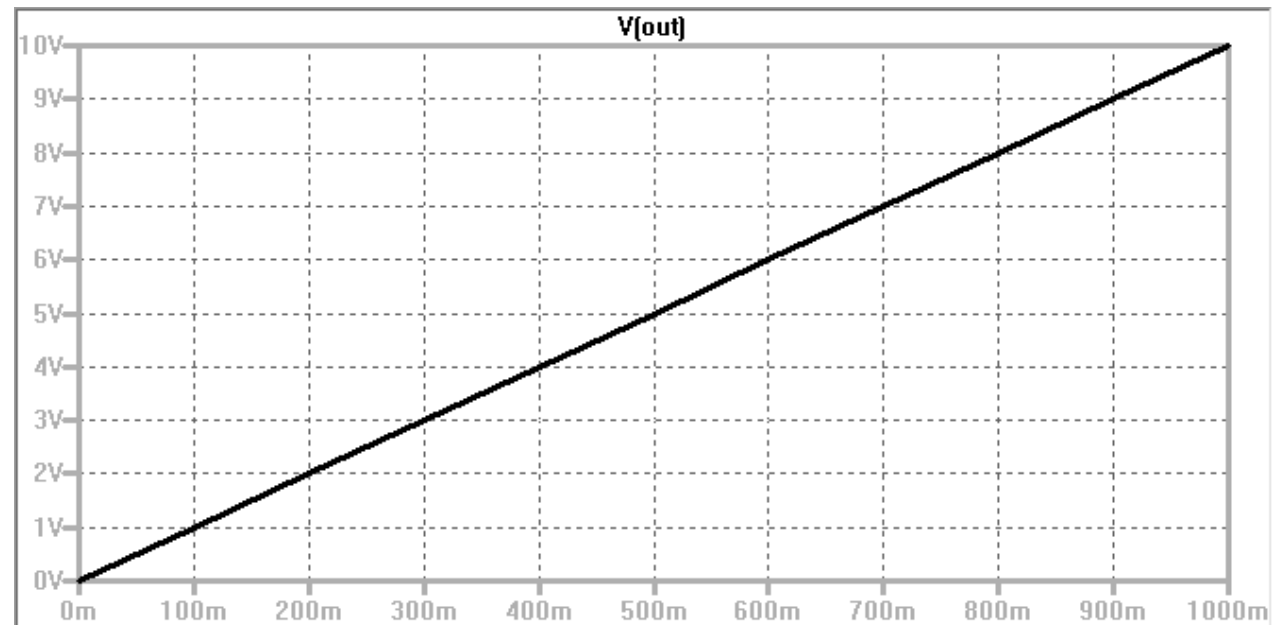

axis=>a parameter

Additional tools

`.PARAM .STEP` : try yourself

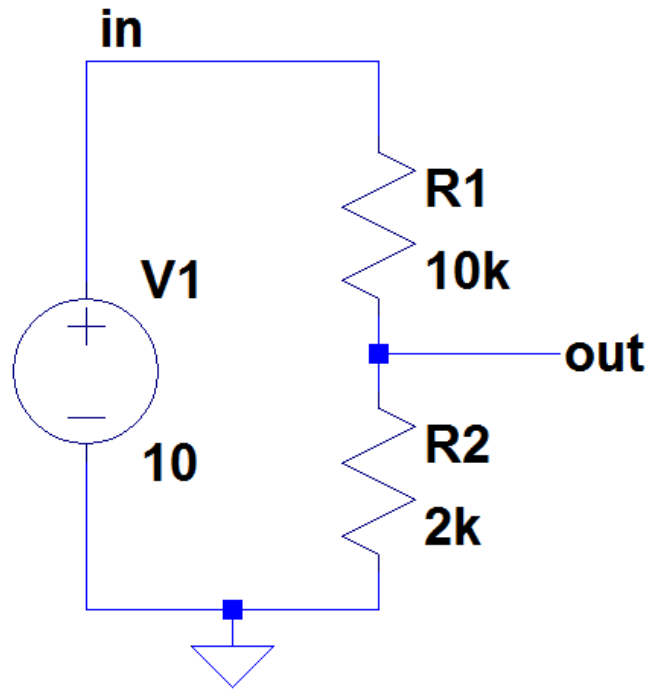



By using PARAM and STEP propose an analysis which allow to see how vary power consumed by R2 in fonction of R2.

For what value of R2 the power is max ?

Additional tools

.PARAM .STEP : try yourself

- Resume this schematic and analysis

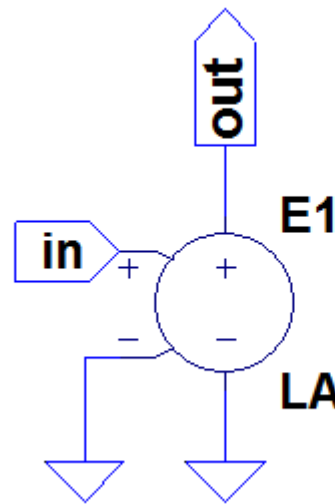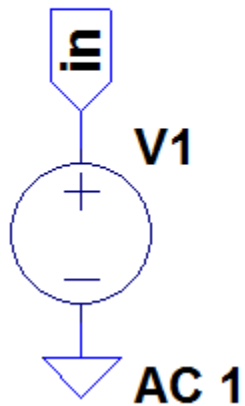

Place a new component and select "E" (voltage dependant source voltage), Right click on the E value, and enter the formula as below

$$\text{LAPLACE}=1/(1+2*0.707*(s/(2*PI))+(s/(2*PI))^2)$$

Damping Factor

- Propose modification to see the influence of the damping factor (0.707 in the formula) on the magnitude curve.

Additional tools

.MEAS


- When simulation is completed, it's possible to perform measurement on data point file using the directive .MEAS.
- MEAS allow :
 - to find a particular point at particular value of the x axis, or when a condition is met...
 - to find maximum value, minimum value, peak to peak value, RMS value, ...
 - To measure a range on a x axis between to particular point,...

Additional tools


.MEAS - Example

- RC circuit : Step response

Schematic :

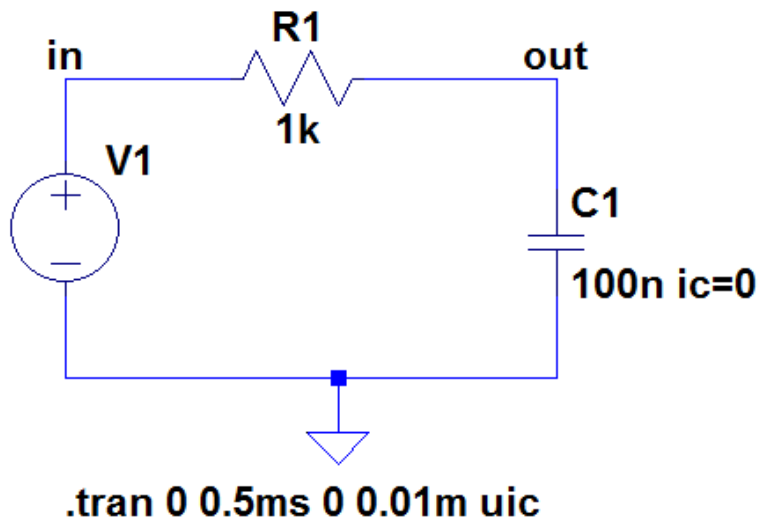

Result :

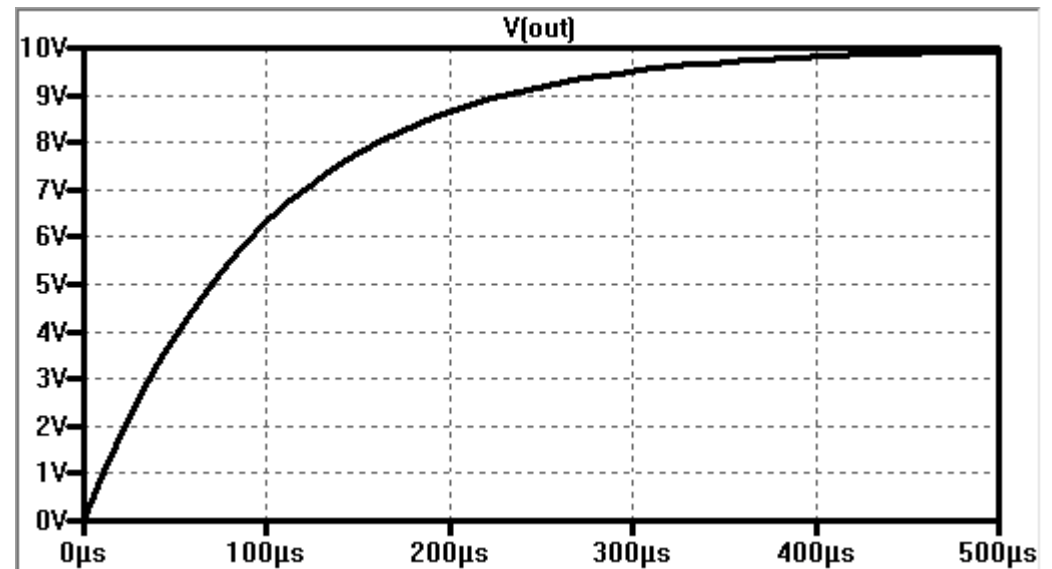


We want to know : what's the value of V(out) for time = $R1 * C1 = 100\mu s$

Additional tools

.MEAS - Example

- RC circuit : Step response

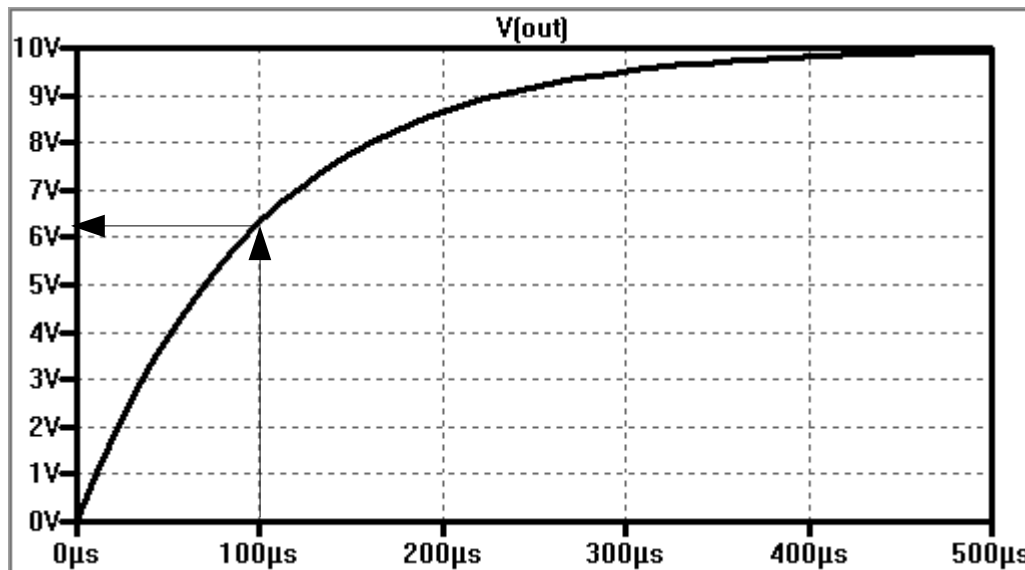We want to know : what's the value of $V(\text{out})$ for time = $R1 \cdot C1 = 100\mu\text{s}$



Using the `.op` button, we add on the schematic the follow directive :

```
.meas tran vrc find v(out) AT=100u
```

At $t=100\mu\text{s}$

Measure on the result of the transient analysis

Name of the user defined param it receive the result



On which measure is done

Vsr recieve the value of $v(\text{out})$ at $t=100\mu\text{s}$


Additional tools

.MEAS - Example

- RC circuit : Step response

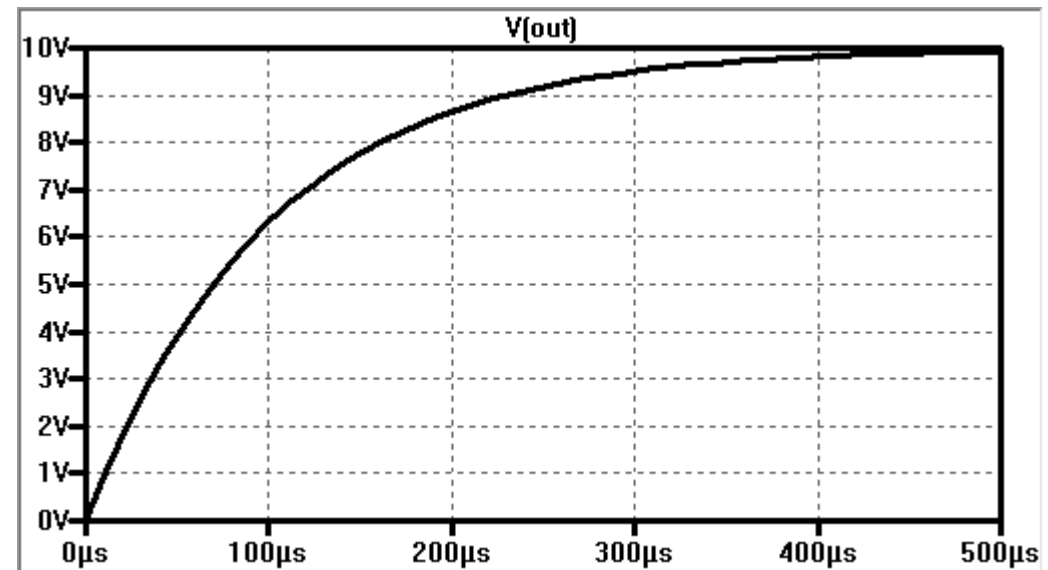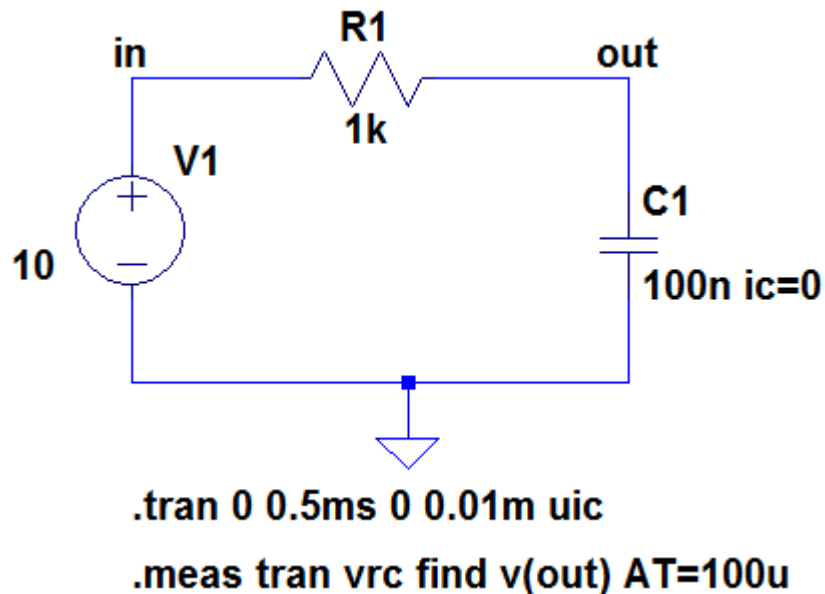

View => spice error log

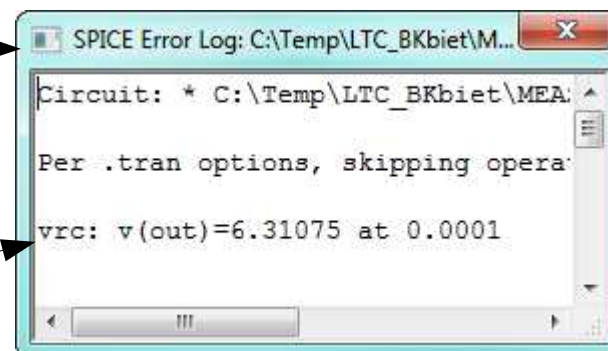


Vsr recieve the value of v(out) at t=100us

Additional tools

.MEAS - Example

- RC circuit : Step response

Schematic :

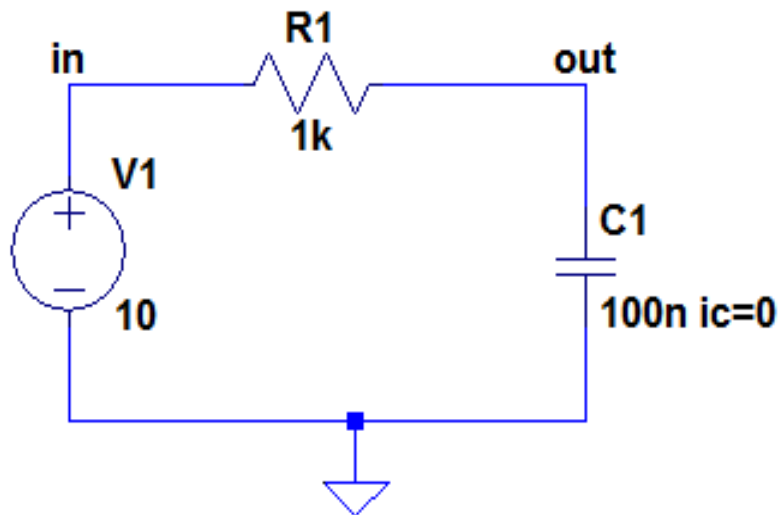

```
.tran 0 0.5ms 0 0.01m uic
```

```
.meas tran vrc find v(out) AT=100u
```

```
.meas vmax MAX v(out)
```

```
.meas tran ratio param (vrc/vmax)*100
```

View => spice error log

```
SPICE Error Log: C:\Temp\LTC_BKbiet\MEAS\MEAS_tran_R...  
Circuit: * C:\Temp\LTC_BKbiet\MEAS\MEAS_tran_  
Per .tran options, skipping operating point f  
vrc: v(out)=6.31075 at 0.0001  
vmax: MAX(v(out))=9.93289 FROM 0 TO 0.0005  
ratio: (vrc/vmax)*100=63.5339
```

Additional tools


.MEAS - Example

- Potentiometer : find the a value for which

$$v(\text{out}) = 0,5 * V(\text{in})$$

Schematic :
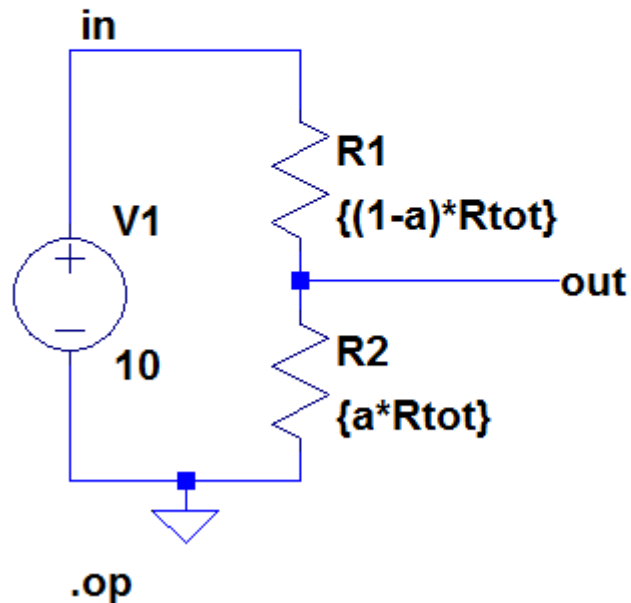
```
.param Rtot=10k
.param a=0.5
.step param a 0.1 0.9 0.1
.meas op alpha when v(out) = 0.5*v(in)
```



View => spice error log

```
SPICE Error Log: C:\Temp\LTC_BKbiet\MEAS\meas_alp
Circuit: * C:\Temp\LTC_BKbiet\MEAS\mea
Direct Newton iteration for .op point
alpha: v(out)=0.5*v(in) AT 0.5
```


Additional tools

.MEAS - Example

- Potentiometer : find the range on a for which $0,3 \cdot v(\text{IN}) < v(\text{out}) < 0,7 \cdot V(\text{in})$

Schematic :
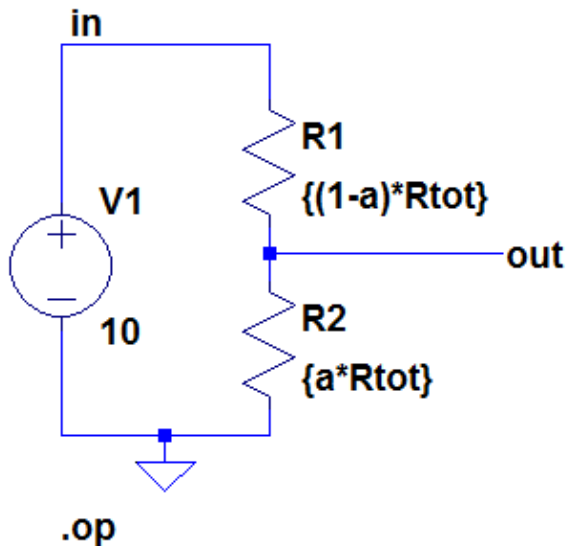
```
.param Rtot=10k
.param a=0.5
.step param a 0.1 0.9 0.1
.meas a_range trig v(out) val=0.3*v(in)
+ targ v(out) val=0.7*v(in)
```



View => spice error log

```
SPICE Error Log: C:\Temp\LTC_BKbiet\MEA
Circuit: * C:\Temp\LTC_BKbiet\ME
Direct Newton iteration for .op
a_range=0.4 FROM 0.3 TO 0.7
```

.meas a_range trig v(out) val=0.3*v(in) targ v(out) val=0.7*v(in)

From $V(\text{out}) = 0,3 \cdot V(\text{in})$

To $V(\text{out}) = 0,7 \cdot V(\text{in})$


Additional tools

.MEAS - Example

- Potentiometer : find the range on a for which $0,3 \cdot v(\text{IN}) < v(\text{out}) < 0,7 \cdot V(\text{in})$

Schematic :
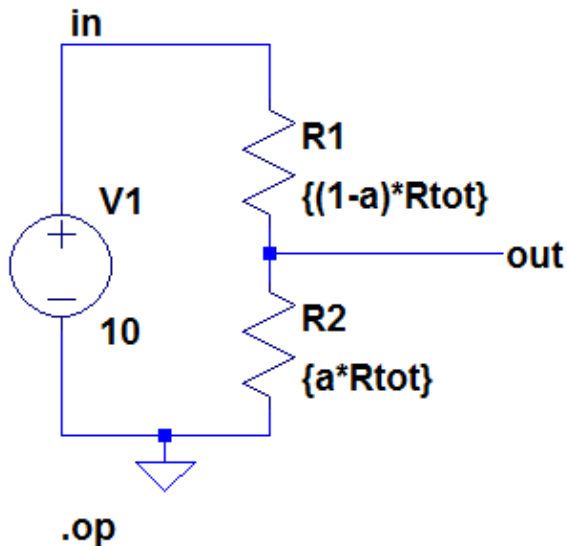
```
.param Rtot=10k  
.param a=0.5  
.step param a 0.1 0.9 0.1  
.meas a_range trig v(out) val=0.3*v(in)  
+ targ v(out) val=0.7*v(in)
```



View => spice error log

```
SPICE Error Log: C:\Temp\LTC_BKbiet\MEA  
Circuit: * C:\Temp\LTC_BKbiet\  
Direct Newton iteration for .op  
a_range=0.4 FROM 0.3 TO 0.7
```

.meas a_range trig v(out) val=0.3*v(in) targ v(out) val=0.7*v(in)

From $V(\text{out}) = 0,3 \cdot V(\text{in})$

To $V(\text{out}) = 0,7 \cdot V(\text{in})$

Additional tools

.MEAS - Example

- Amplifier : find the bandwidth
- Definition : bandwidth is the frequency range for which magnitude G is between G_{max} and $\frac{G_{max}}{\sqrt{2}}$

.measure tmp max mag(V(out)) Tmp receive the max value mag(V(out)) where mag(V(out)) is the real part of V(out)

.measure BW trig mag(V(out))=tmp/sqrt(2) **rise=1 targ** mag(V(out))=tmp/sqrt(2) **fall=last**



BW receive the frequency range **FROM** which mag(V(out)) cross the value $\frac{G_{max}}{\sqrt{2}}$ for the **first time** by rising (rise =1) **TO** mag(V(out)) cross the value $\frac{G_{max}}{\sqrt{2}}$ for the **last time** by falling (fall =1).

Comment : for more examples, see the help file, press F1 keys.

Summary

Training 1

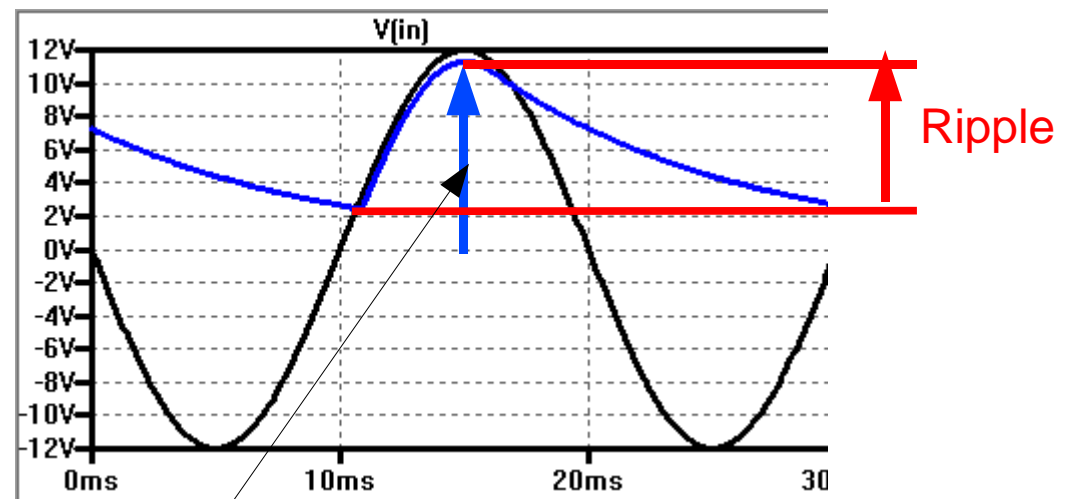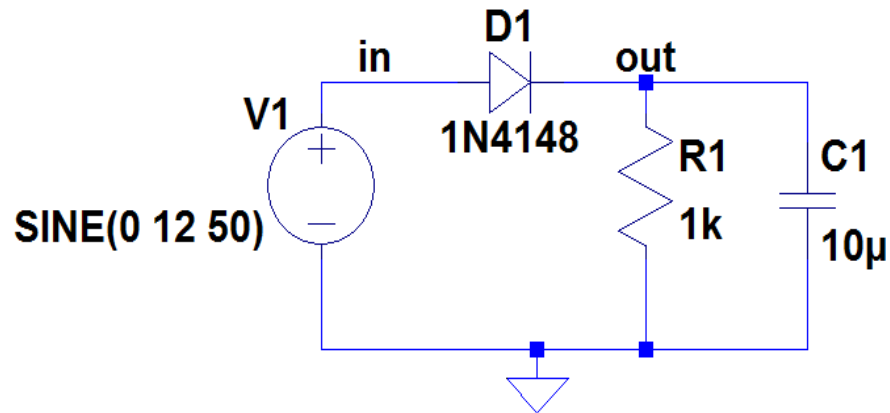- Take again and modify the rectifier analysis to perform the measurement of the ripple ratio in function of the value of the capacitor




$$\text{Ripple ratio} = \frac{\text{Ripple}}{V_{max}}$$

Summary

Training 1

Expected result :

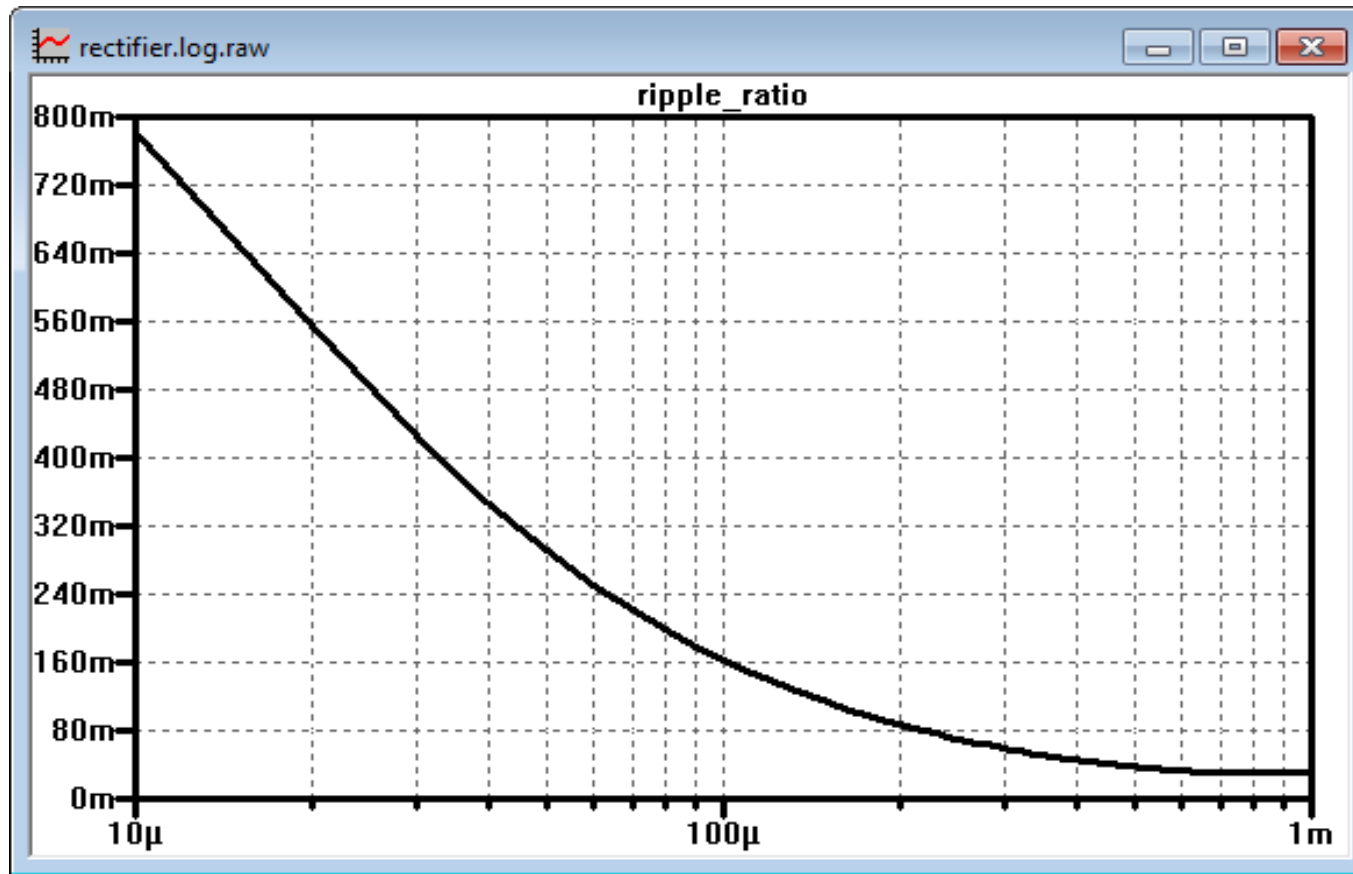


Valeur de C1

Summary

Training 1

Correct :
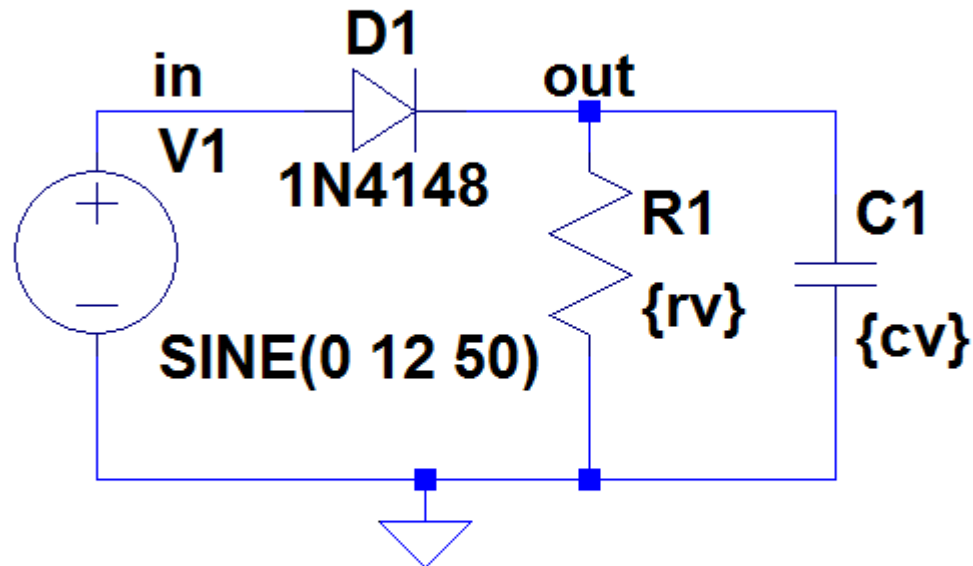
```
.param cv 100n  
.param rv 1k  
.step param cv 10u 1000u 10u
```



```
.tran 0 200m 10m 0.1m
```

```
.meas vmax MAX(v(out))
```

```
.meas ripple pp v(out)
```

```
.meas ripple_ratio param ripple/vmax
```


Summary


Training 2 : frequency measurement

- Open the file
« c:\programmeFiles\LTC\example\educational\Wien.asc »
and run it.
- Modify the schematic for change the value of C1 and C2
from 0,01uF to 0,1uT by step of 0,01uF
- Add .measure statement to measure the frequency of the
signal at output of the Opamp
- Trace the graph frequency versus the value of the 2
capacitor.

Summary

Training 2 : frequency measurement


- Expected result

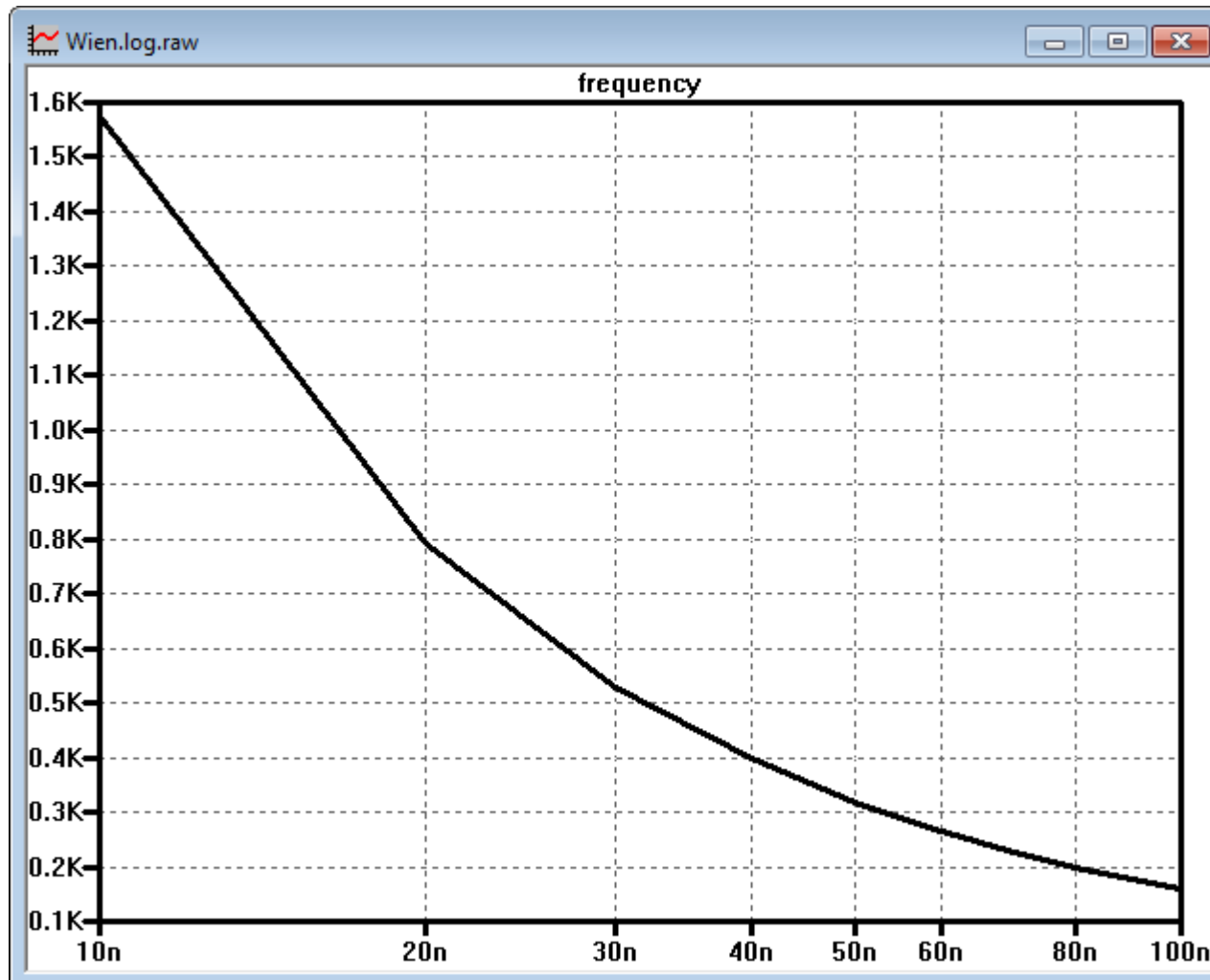

Summary

Training 2 : frequency measurement

- Correct :

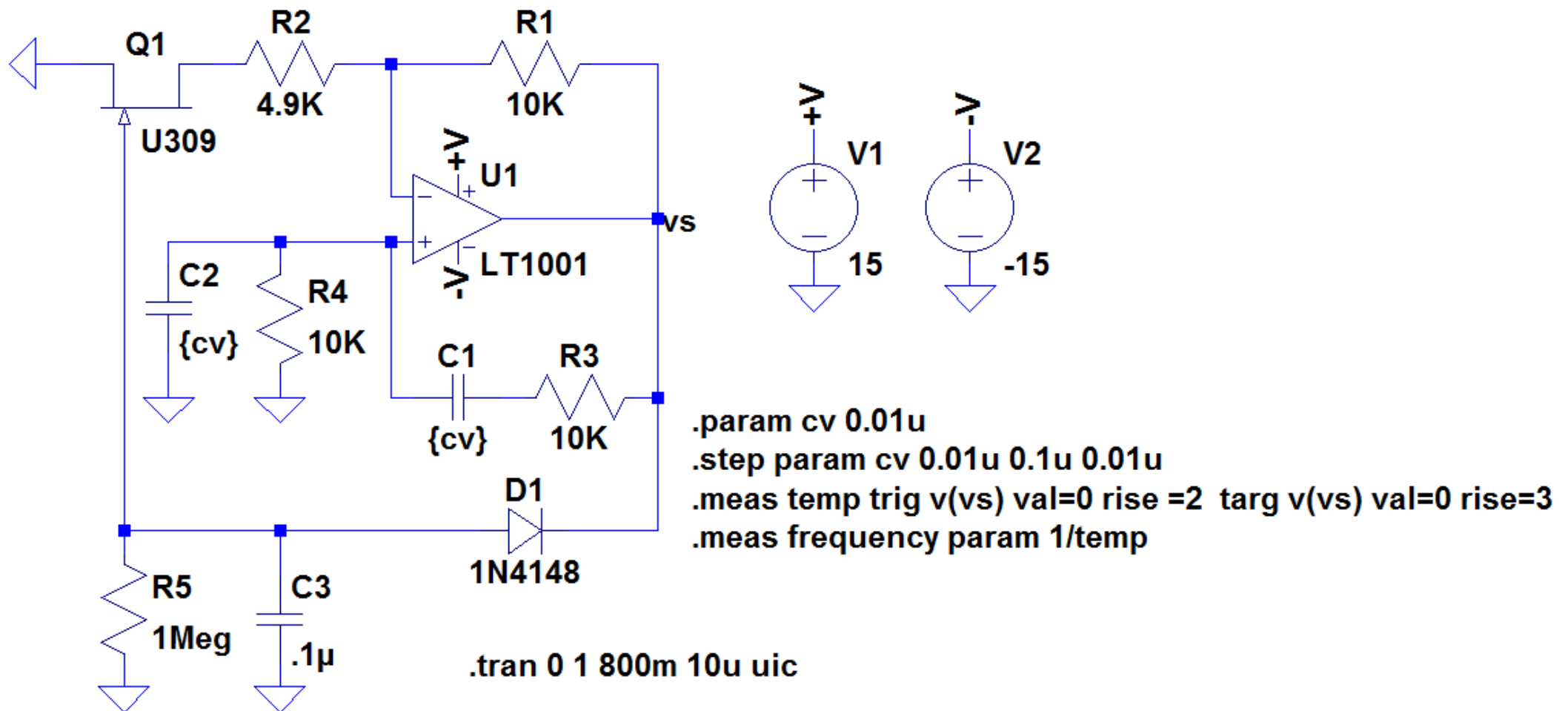

Web Link

- Power Point tutorial

www.ltspice.linear.com/software/LTspiceGettingStartedGuide.pdf

- Complete documentation

www.ltspice.linear.com/software/scad3.pdf