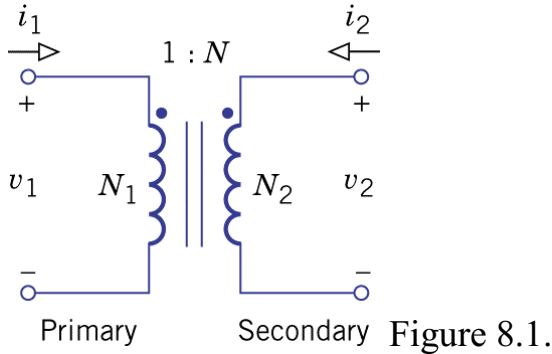


Chapter 8 Transformers and Mutual Inductance

8.1 Ideal Transformers

- Transformers consist of magnetically coupled coils the respond only when driven by time-varying excitations.
- Ideal transformers vs. real transformers.



- N_1 : primary winding, N_2 : secondary winding.
- Reference direction: both currents into the upper terminals.
- Dot convention: polarity is the same at both windings.
- Coils have zero resistance and are short circuits at dc steady state.
- Time varying excitation activates magnetic coupling and induces voltage at the other winding.
- Turns ratio: $N \equiv N_2 / N_1$.
- $v_2(t) = Nv_1(t)$, $i_2(t) = -i_1(t)/N$.
- With $N = 1$, a transformer becomes an isolation transformer that decouples the dc potential levels without affecting the time-varying quantities.
- An ideal transformer does not dissipate power ($p = v_1i_1 + v_2i_2 = 0$).
- Controlled source models (VCVS and CCCS)


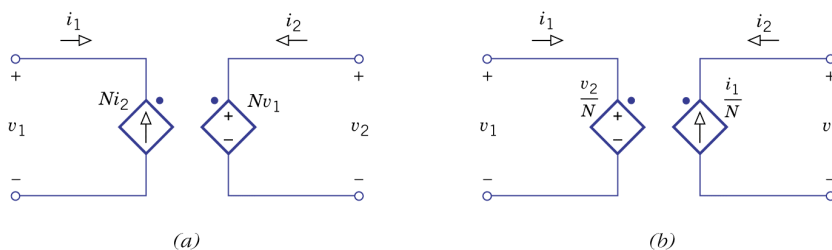


Figure 8.2.

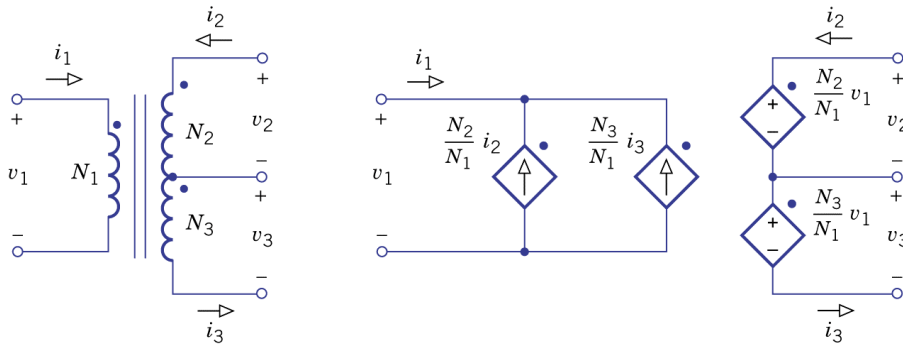- Transformers with three or more windings:




(a) Ideal transformer with tapped secondary

(b) Controlled-source model

Figure 8.3.

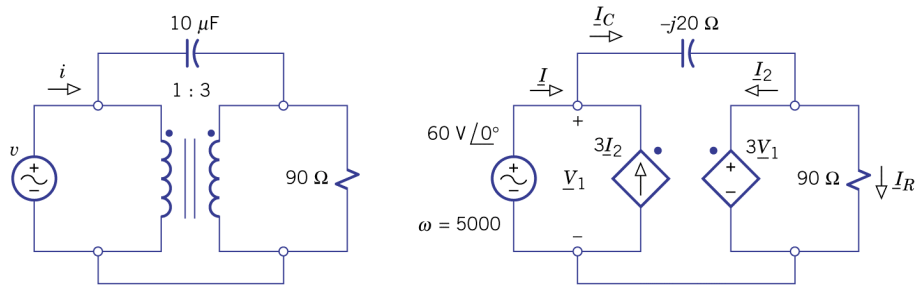Example 8.1: Analysis of a Transformer Circuit




(a) Circuit with an ideal transformer


(b) Frequency-domain diagram

Figure 8.4.

- Referred networks:

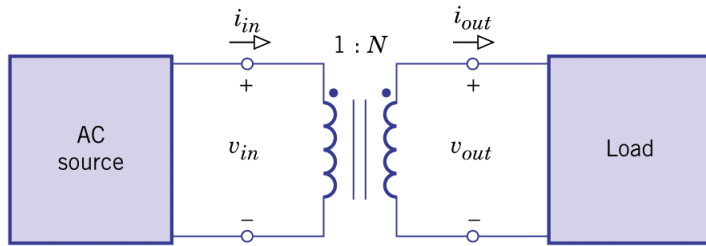

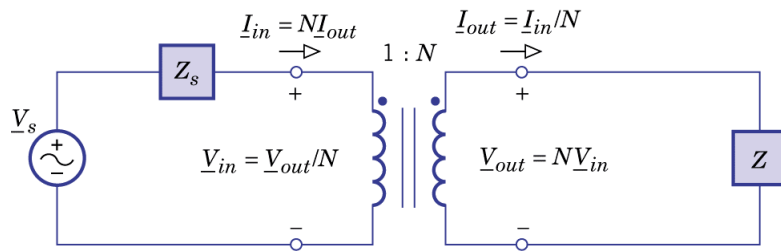(a) Ideal transformer interfacing a source and a load




(b) Frequency-domain diagram


Figure 8.6.

- Referred load network and referred source network.

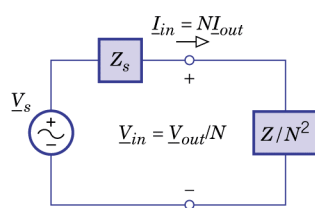- Referred load network: R and L divided by N^2 and C multiplied by N^2 .



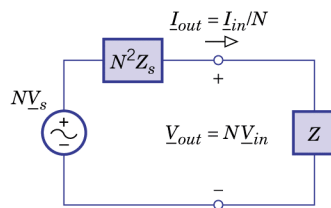(a) Referred load impedance in the primary



(b) Referred source network in the secondary

Figure 8.7.

- Referred source network: voltage multiplied by N , impedance multiplied by N^2 and current divided by N .

Example 8.2 Power Transmission with Transformers



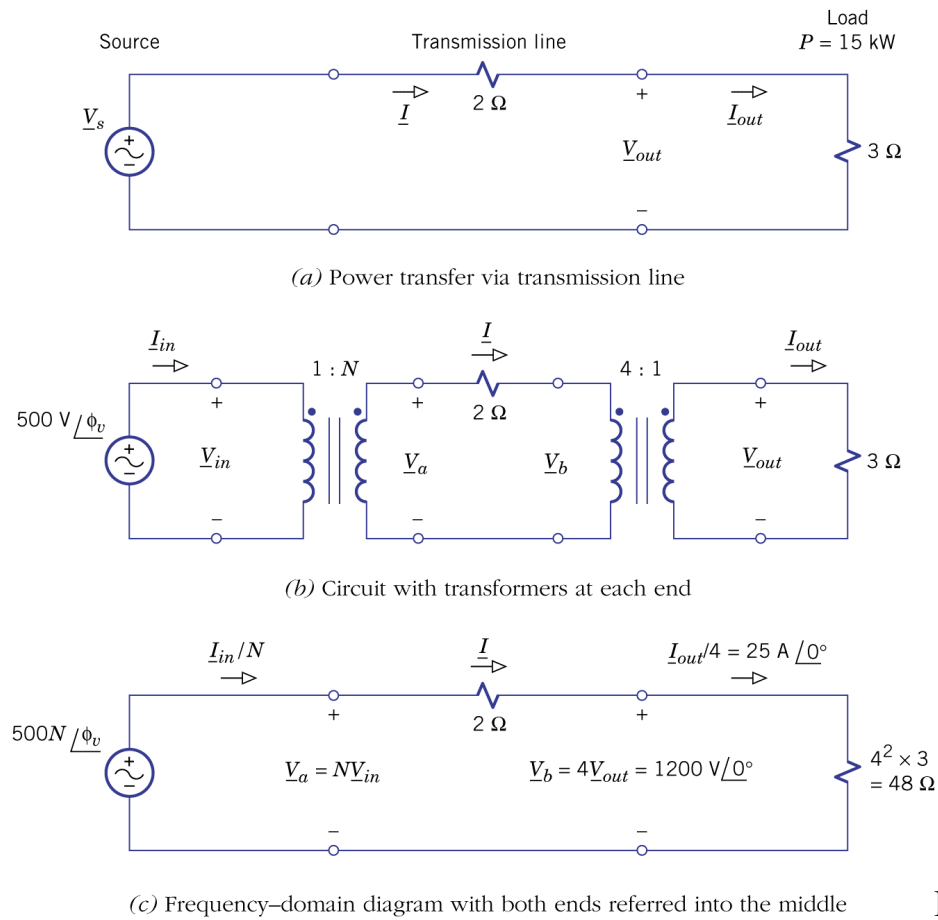


Figure 8.8.

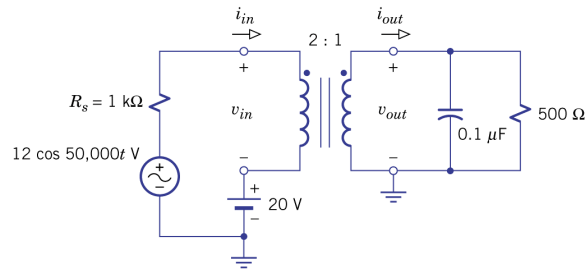Example 8.3 Transformer-Coupled Oscillator



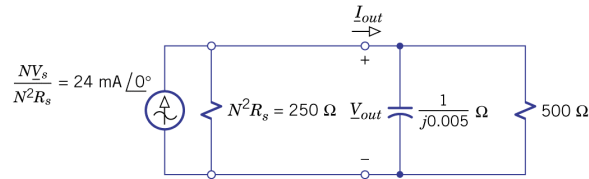(a) Transformer circuit with ac and dc sources




(b) Frequency-domain diagram with referred source network in the secondary


Figure 8.9.

- Impedance matching (refer to Figure 8.6b).

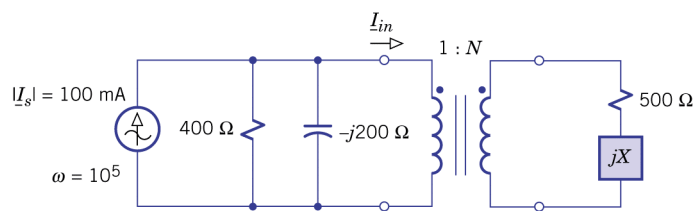Example 8.4 Impedance Matching with a Transformer



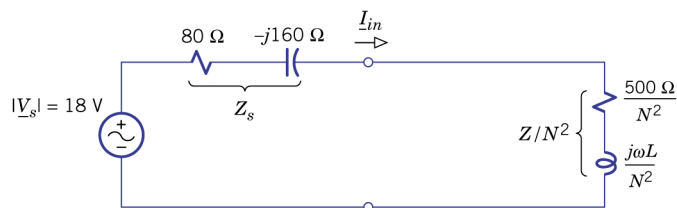(a) Model of amplifier with impedance-matching transformer




(b) Referred load in the primary

Figure 8.10.

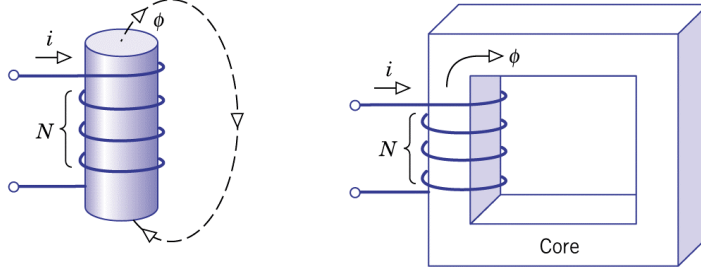8.2 Magnetic Coupling and Mutual Inductance

- Magnetic circuits: N turns, magnetic flux ϕ and current i (with right-hand rule).



(a) Coil with cylindrical core

(b) Magnetic circuit

Figure 8.11.

- Magnetomotive force (mmf): $F=Ni$.
- Reluctance: $R=l/\mu_r\mu_0A$.
- $F=R\phi$.


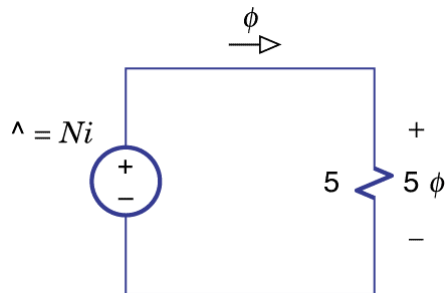


Figure 8.12.

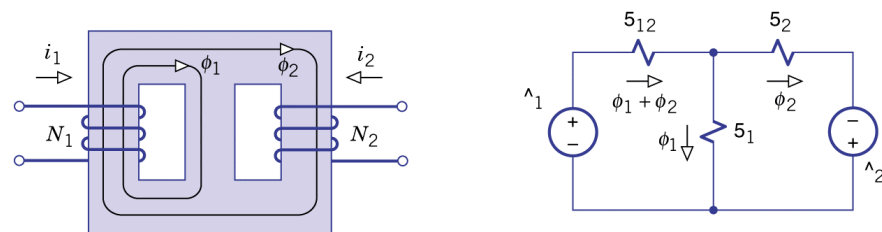

(a) Magnetic core with two flux loops

(b) Magnetic circuit diagram

Figure 8.13.

- Self-inductance and mutual inductance.

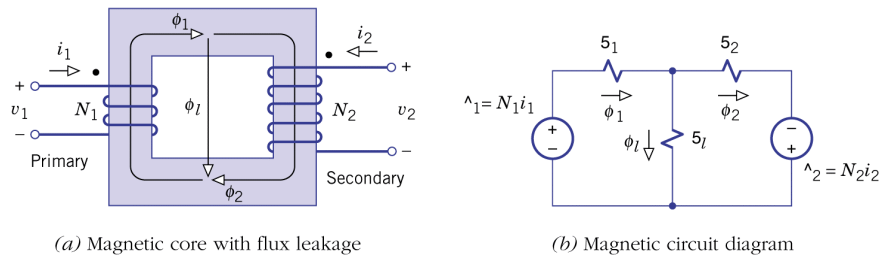


Figure 8.14.

- Currents entering the dotted ends of both windings produce flux in the same direction.
- Leakage flux, self-inductance, mutual inductance and coupling coefficient.

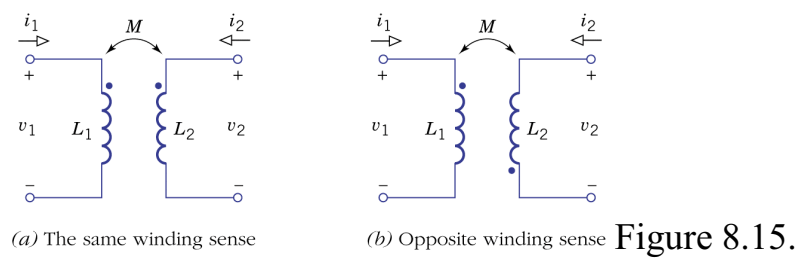


Figure 8.15.

Example 8.5: Series Equivalent Inductance

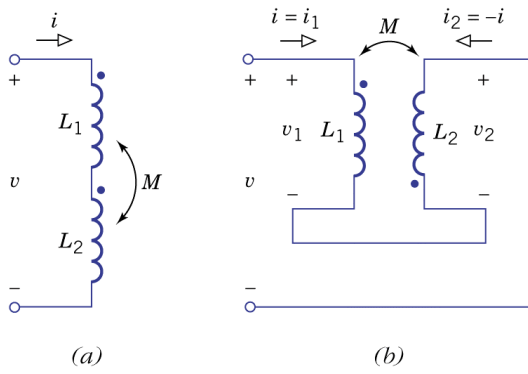


Figure 8.16.

- Stored energy:


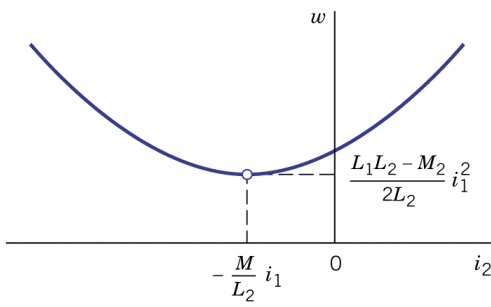


Figure 8.18.


- Unity coupling:

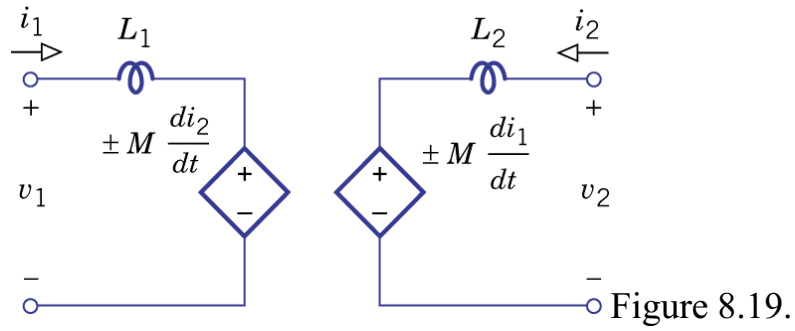
8.3 Circuits with Mutual Inductance

- Mutual inductance represented by controlled sources:




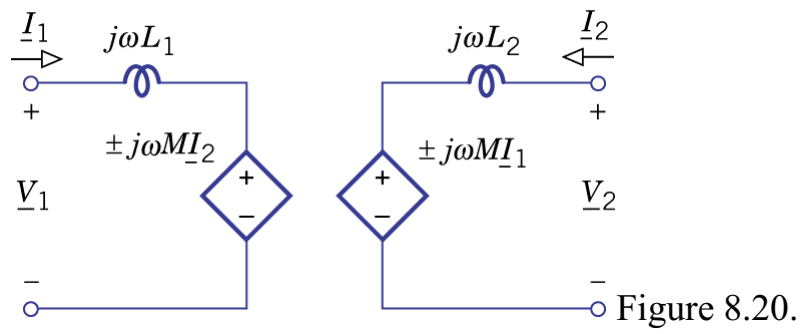- Frequency domain model of self- and mutual inductances:



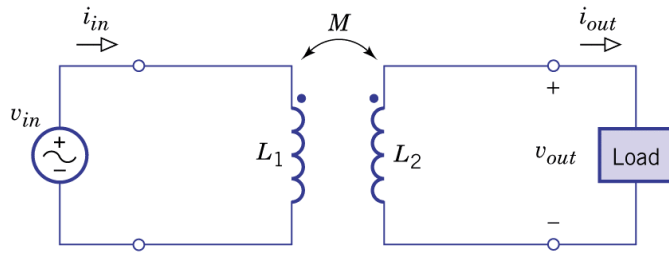

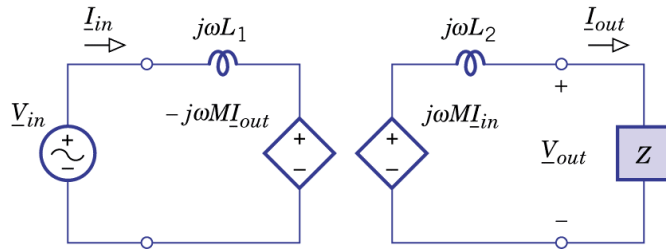
(a) Transformer interfacing a source and a load



(b) Frequency-domain diagram with controlled sources **Figure 8.21.**

Example 8.6: Comparison of a real and ideal transformer

- Equivalent tee (T) networks:

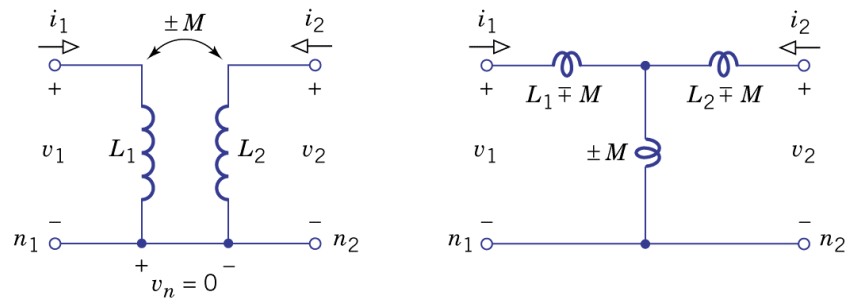

(a) Magnetically coupled coils

(b) Equivalent tee (T) network **Figure 8.23.**

- Equivalent pi (Π) networks:



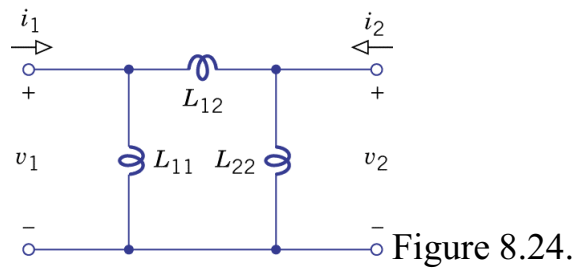


Figure 8.24.

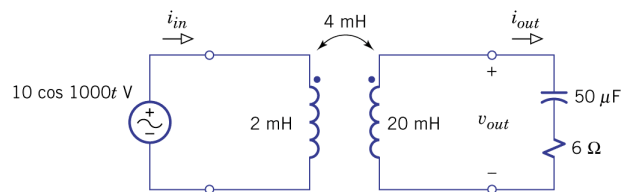Example 8.7: Transformer circuit analysis with a tee network



(a) Circuit with magnetic coupling

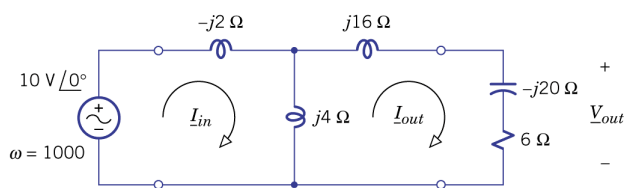

(b) Frequency-domain diagram with the equivalent tee network

Figure 8.25.

Example 8.8: Step-Up Autotransformer

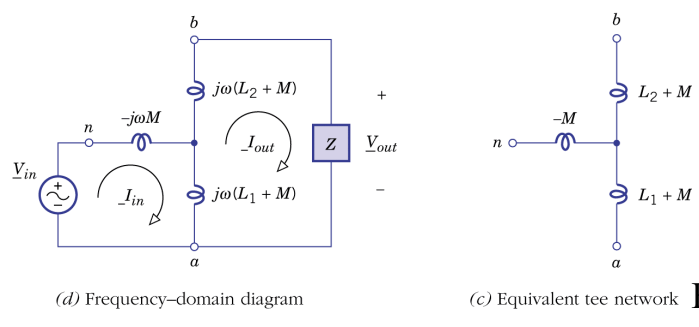
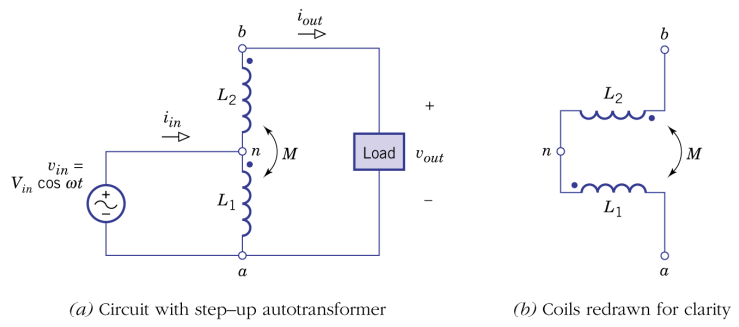


Figure 8.26.

- Equivalent networks with an ideal transformer to represent mutual inductance.



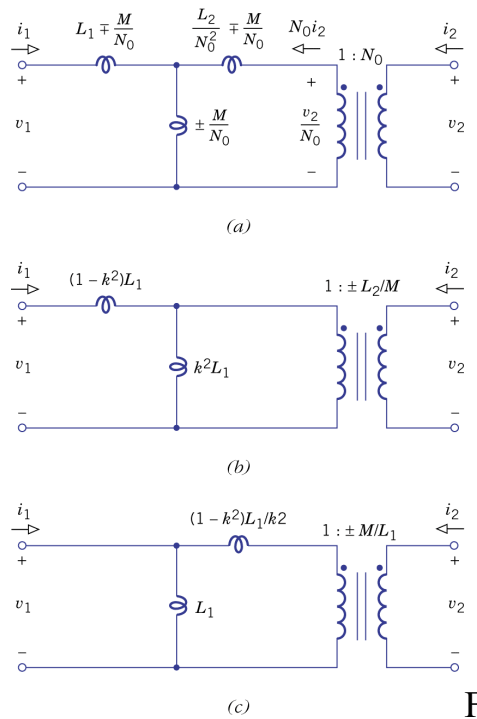


Figure 8.27.


Example 8.9: Design of a Tuned Amplifier

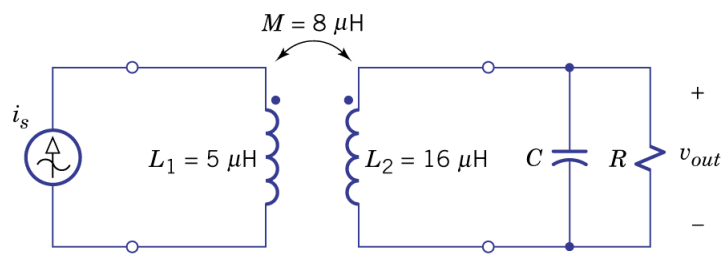

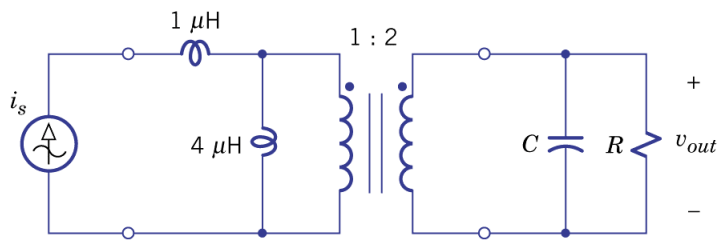(a) Model of “tuned” transistor amplifier



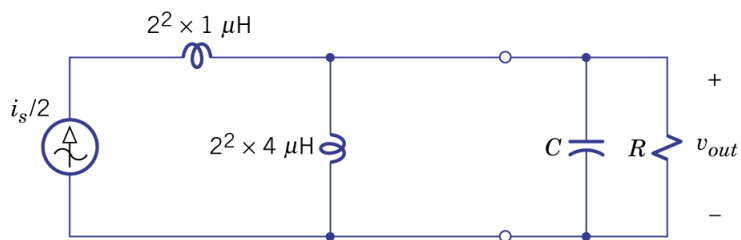(b) Equivalent circuit with an ideal transformer



(c) Referred source network in the secondary

Figure 8.28.