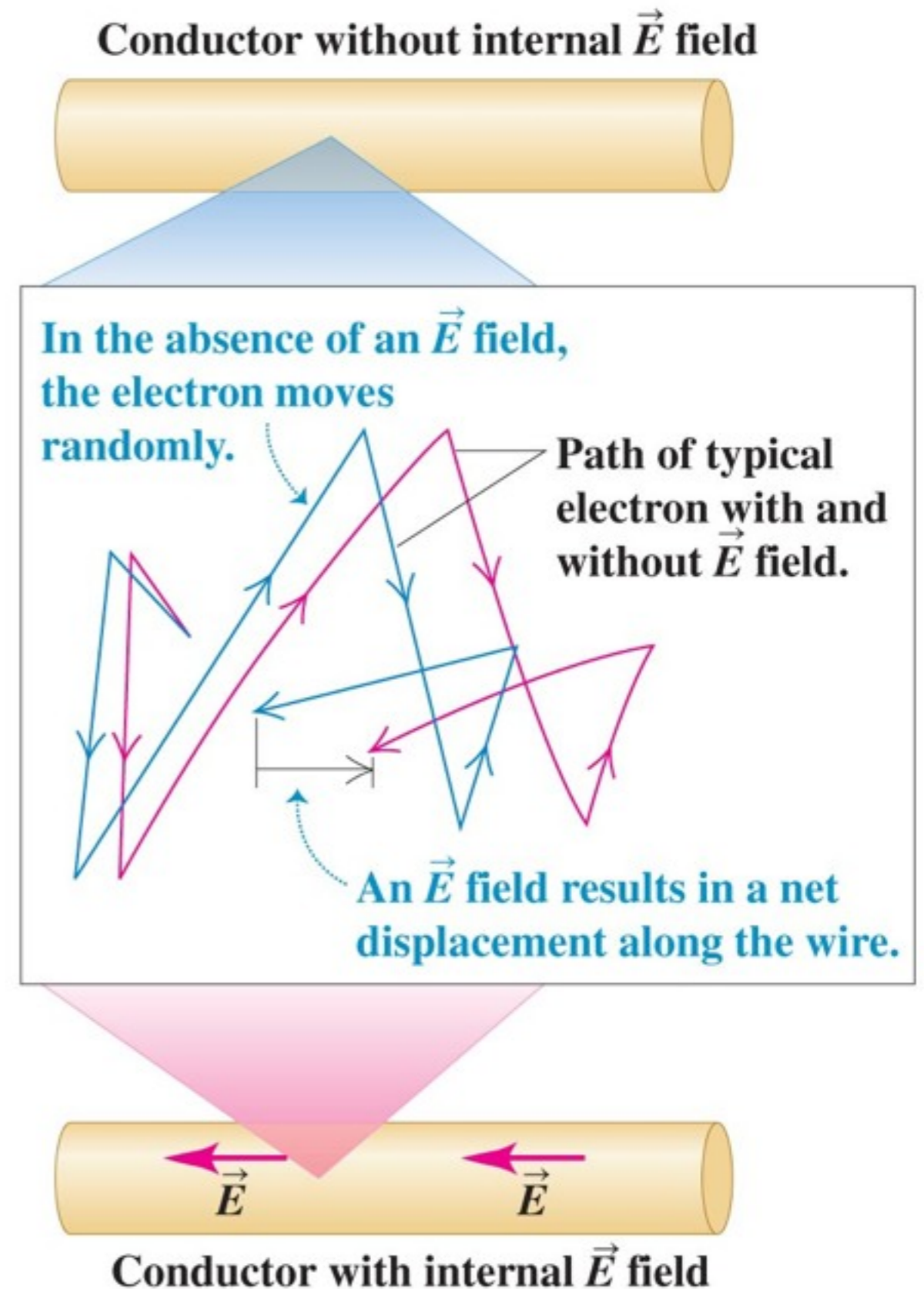
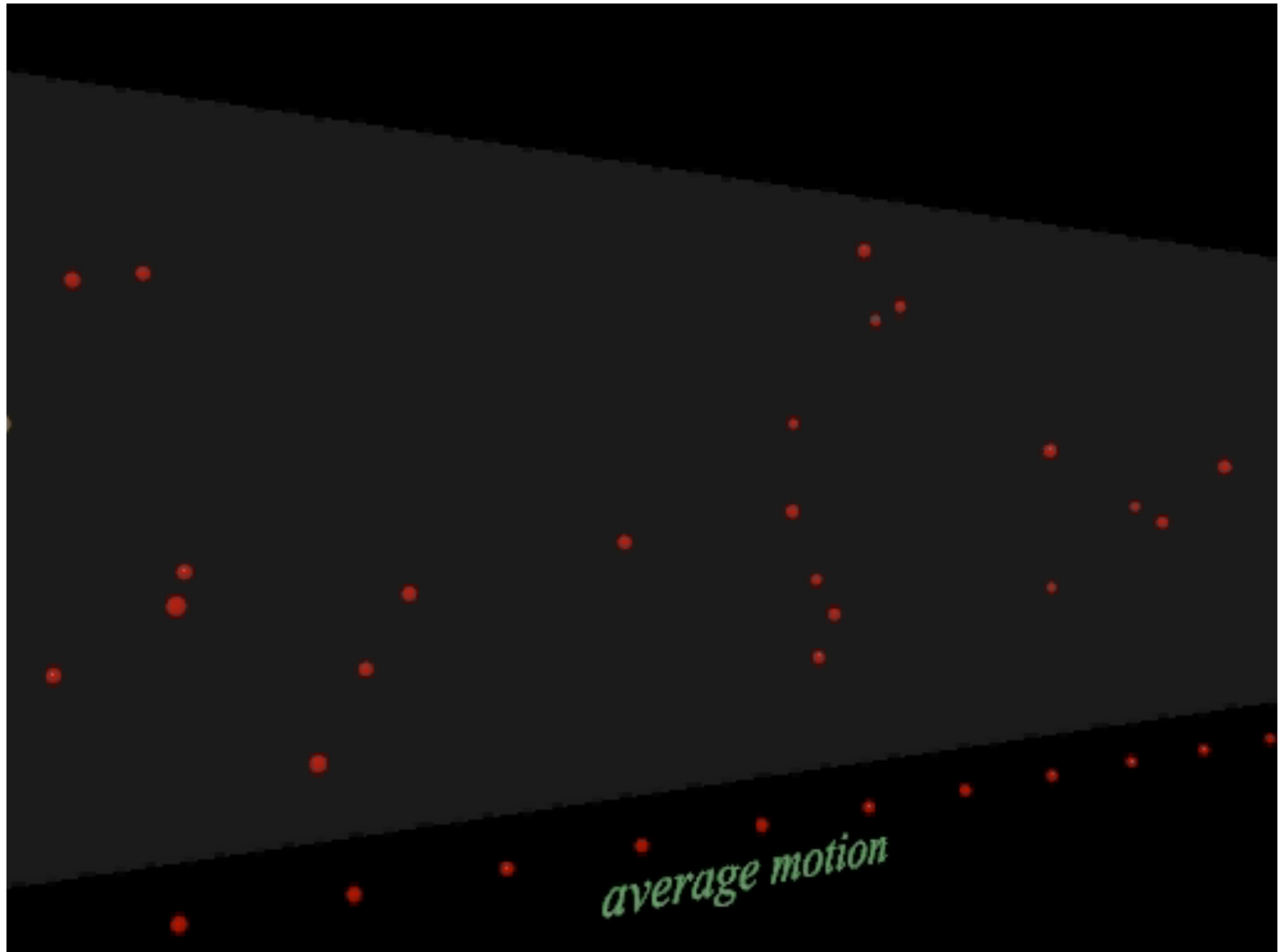

current, resistance and dc circuits

current

- rate of flow of charge is uniform throughout a conductor, else charge would accumulate in certain areas
- at non-zero temperature, electrons in a metal move a lot without any applied field
- although the drift velocity of electrons is rather slow $\sim 10^{-4}$ m/s, the electric fields propagate through the metal at close to the speed of light, so we never notice a delay when 'switching on'







current

- what determines how much current we get for a given applied electric field or potential difference ?
- properties of the conductor determine the “resistance”

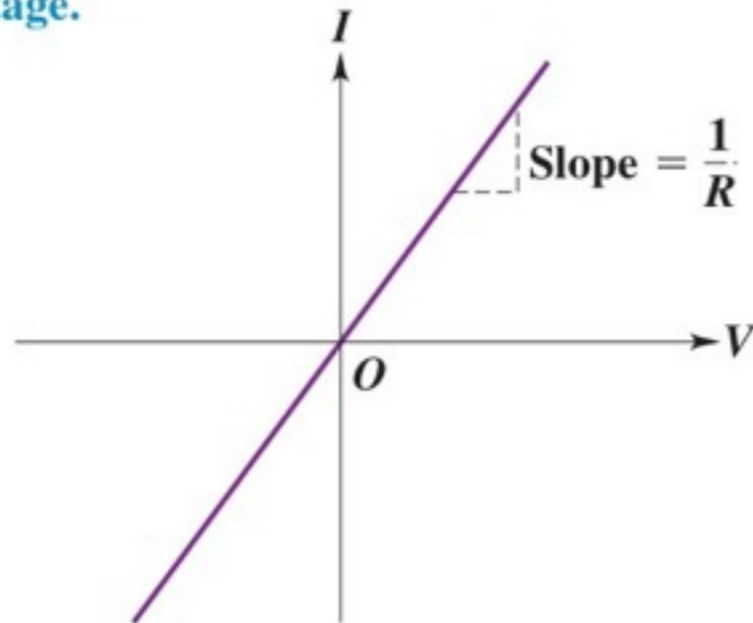Ohmic resistor (e.g., typical metal wire): At a given temperature, current is proportional to voltage.



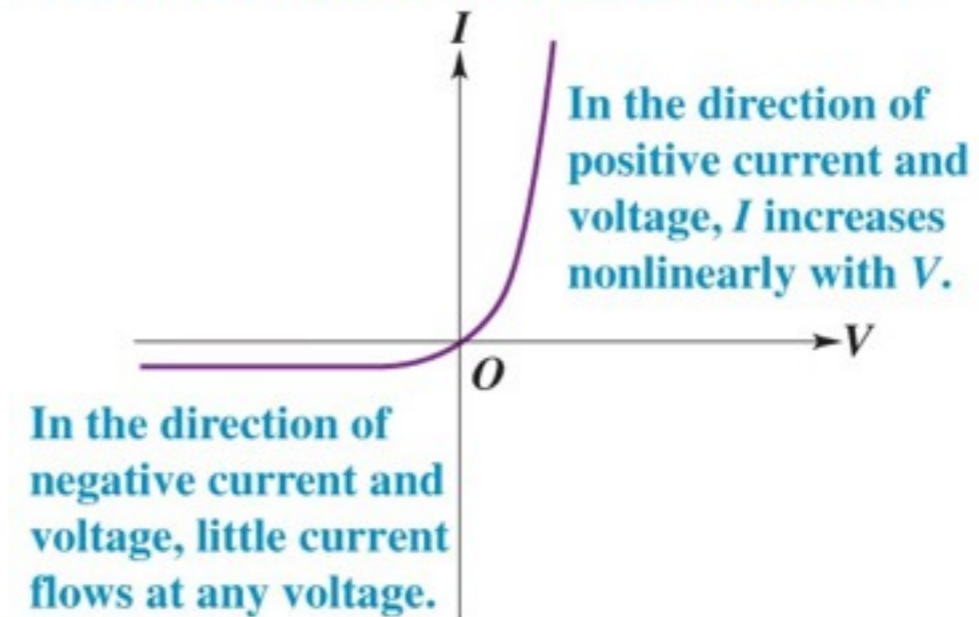Semiconductor diode: a non-ohmic resistor



Ohm's law

→ what determines how much current we get for a given applied electric field or potential difference ?

→ properties of the conductor determine the “resistance”

→ (conventional) current flows from a point of high potential to a point of lower potential along the direction of the \mathbf{E} -field

→ the current is proportional to the drift velocity of the charges in the conductor

→ in experiments, for many materials over a range of temperature, the drift velocity is approximately proportional to the electric field magnitude \mathbf{E} and hence to the potential difference V

→ from this follows the empirical Ohm's law

$$V = IR \quad \text{with } R \text{ a constant}$$

resistance, R ,
measured in
Ohms, $\Omega = \text{V/A}$

*if you like mysteries think about
whether this agrees with $F=ma$*

resistance of a wire

→ we find that the resistance of a cylindrical ‘wire’

→ increases with increasing length of wire
(charge has further to “push through”)

→ decreases with increasing cross-sectional area of wire
(charge has more possible paths through the wire)



→ depends upon the material the wire is made of

$$R = \rho \frac{L}{A}$$

ρ is the **resistivity** which is a property of the material at a given temperature


TABLE 19.1 Resistivities at room temperature

Substance	ρ ($\Omega \cdot \text{m}$)	Substance	ρ ($\Omega \cdot \text{m}$)
Conductors:		Mercury	95×10^{-8}
Silver	1.47×10^{-8}	Nichrome alloy	100×10^{-8}
Copper	1.72×10^{-8}	Insulators:	
Gold	2.44×10^{-8}	Glass	$10^{10} - 10^{14}$
Aluminum	2.63×10^{-8}	Lucite	$> 10^{13}$
Tungsten	5.51×10^{-8}	Quartz (fused)	75×10^{16}
Steel	20×10^{-8}	Teflon®	$> 10^{13}$
Lead	22×10^{-8}	Wood	$10^8 - 10^{11}$

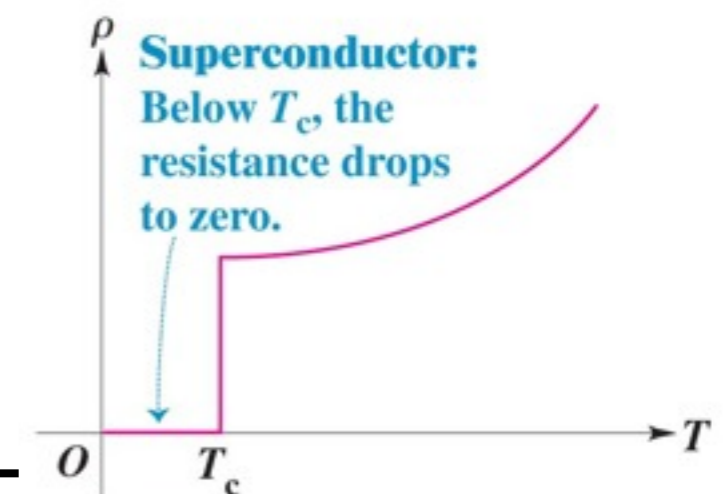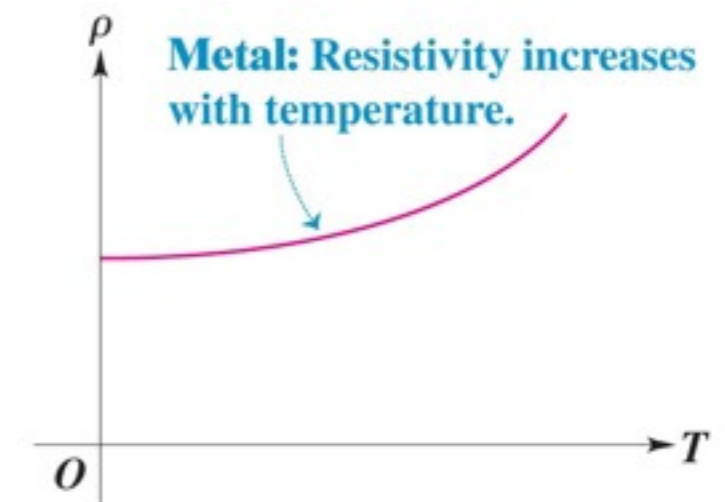


electromotive force

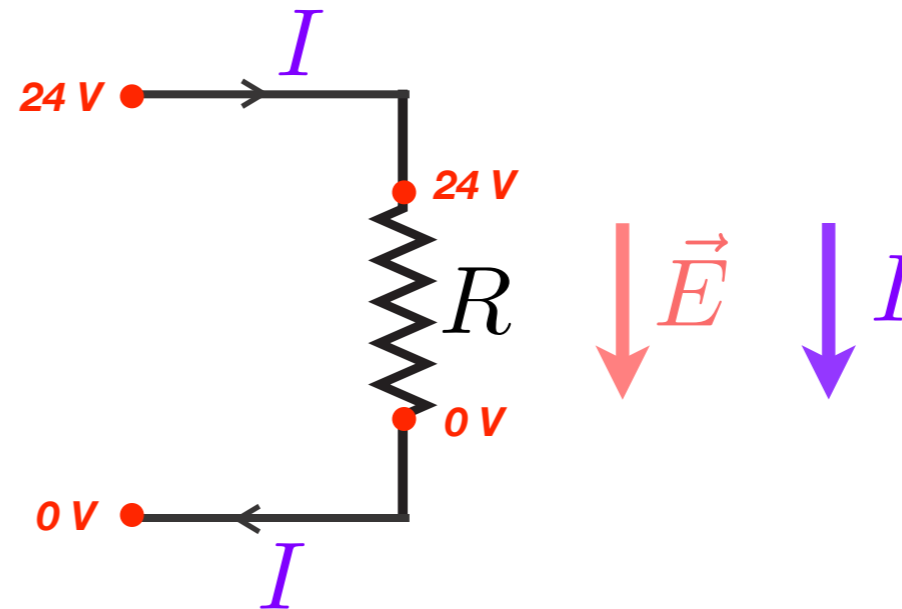current will always 'flow' from high potential to lower potential - along the direction of the electric field



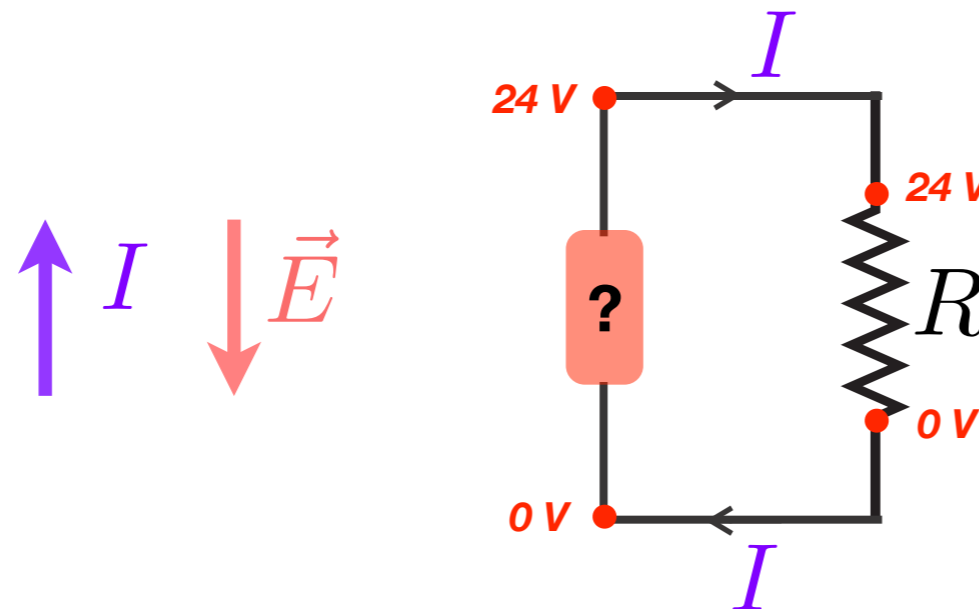if we want a complete circuit with resistance we will need a device in which current can flow from lower to higher potential **against the direction of the electric field**





electromotive force

this is called an “electromotive force”

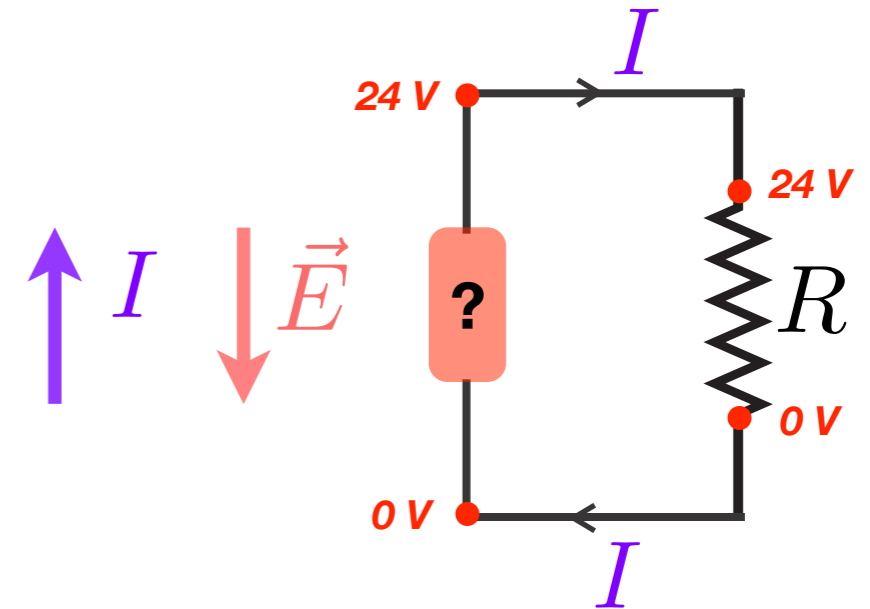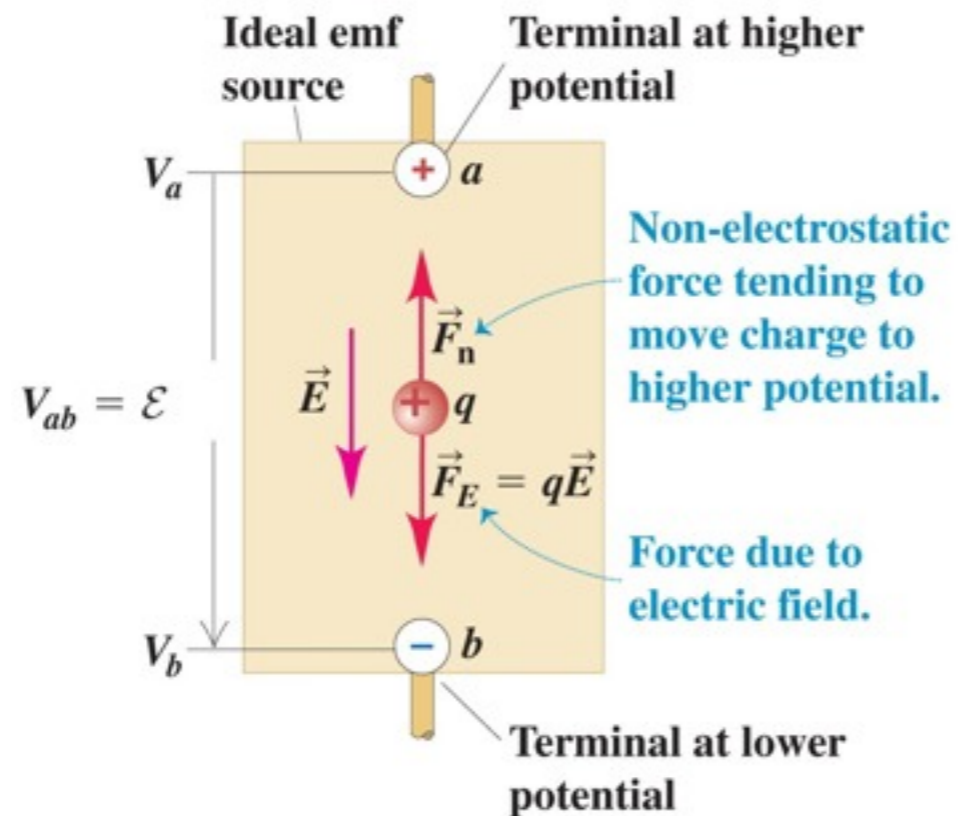examples include batteries, electric generators, solar cells, thermocouples ...

ideal emf sources maintain a constant potential difference between the terminals



the device uses a force other than $\vec{F} = q\vec{E}$ to move charges from low to high potential

real emf sources


→ real sources of emf have an internal resistance experienced by the current as it flows through the source.

we denote this by a lower case r

→ hence the potential difference between the terminals is reduced and depends upon the current flowing


$$V = \mathcal{E} - Ir$$

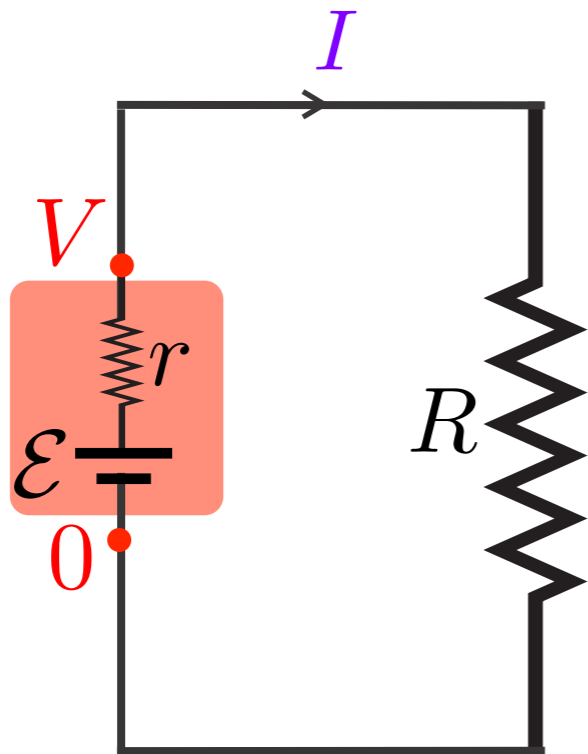→ so connected in a circuit with a resistor we have






$$V = IR$$

$$I = \frac{\mathcal{E}}{r + R}$$

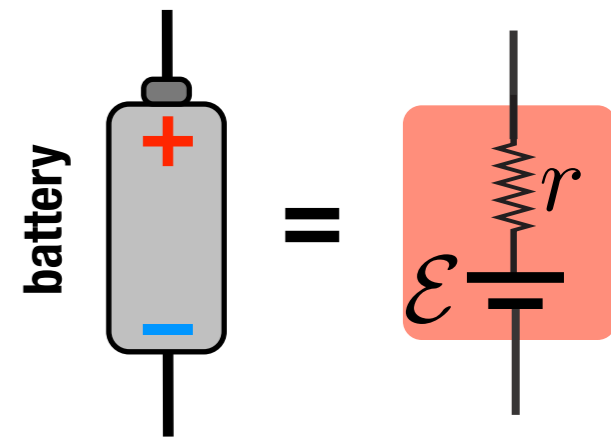


dimming bulb

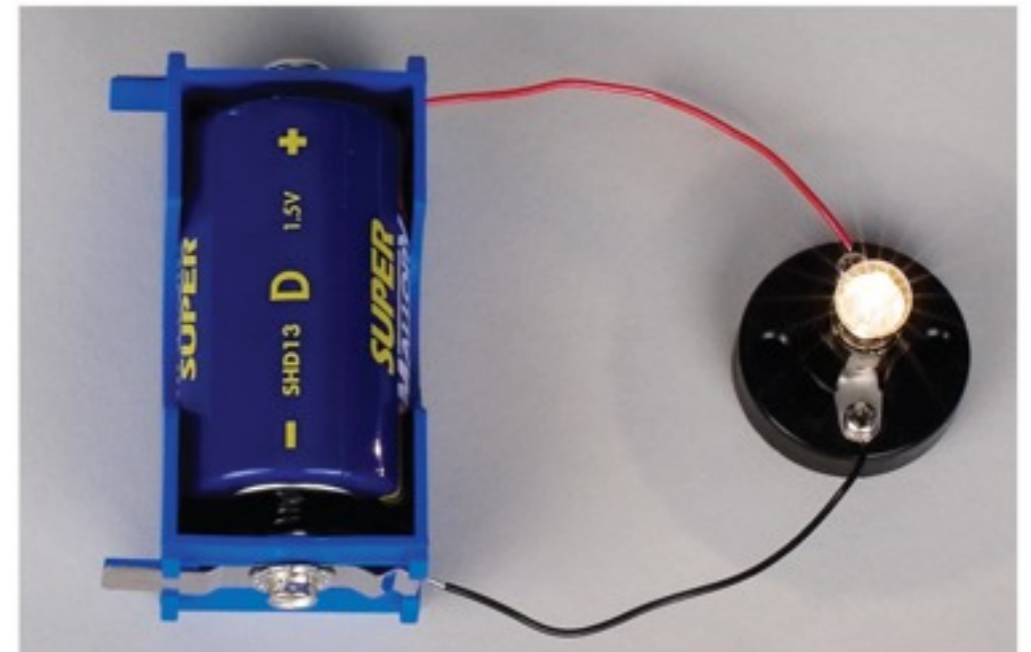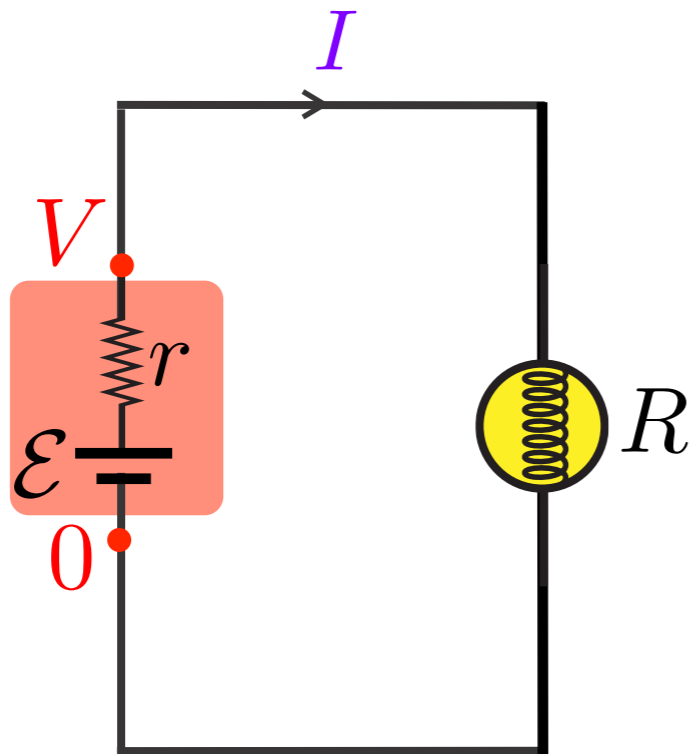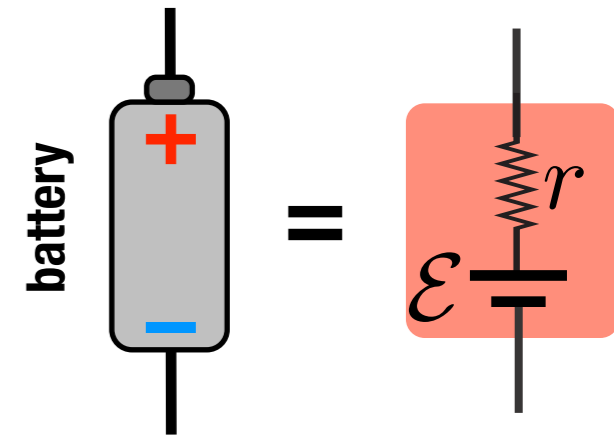As a flashlight battery ages its emf stays approximately constant, but its internal resistance increases. A fresh battery has an emf of 2.5 V and negligible internal resistance. When the battery needs replacing its emf is still 2.5 V but its internal resistance has increased to 1000 Ω . If this old battery is supplying 0.5 mA of current, what is its terminal voltage?



potential in a circuit - an analogy

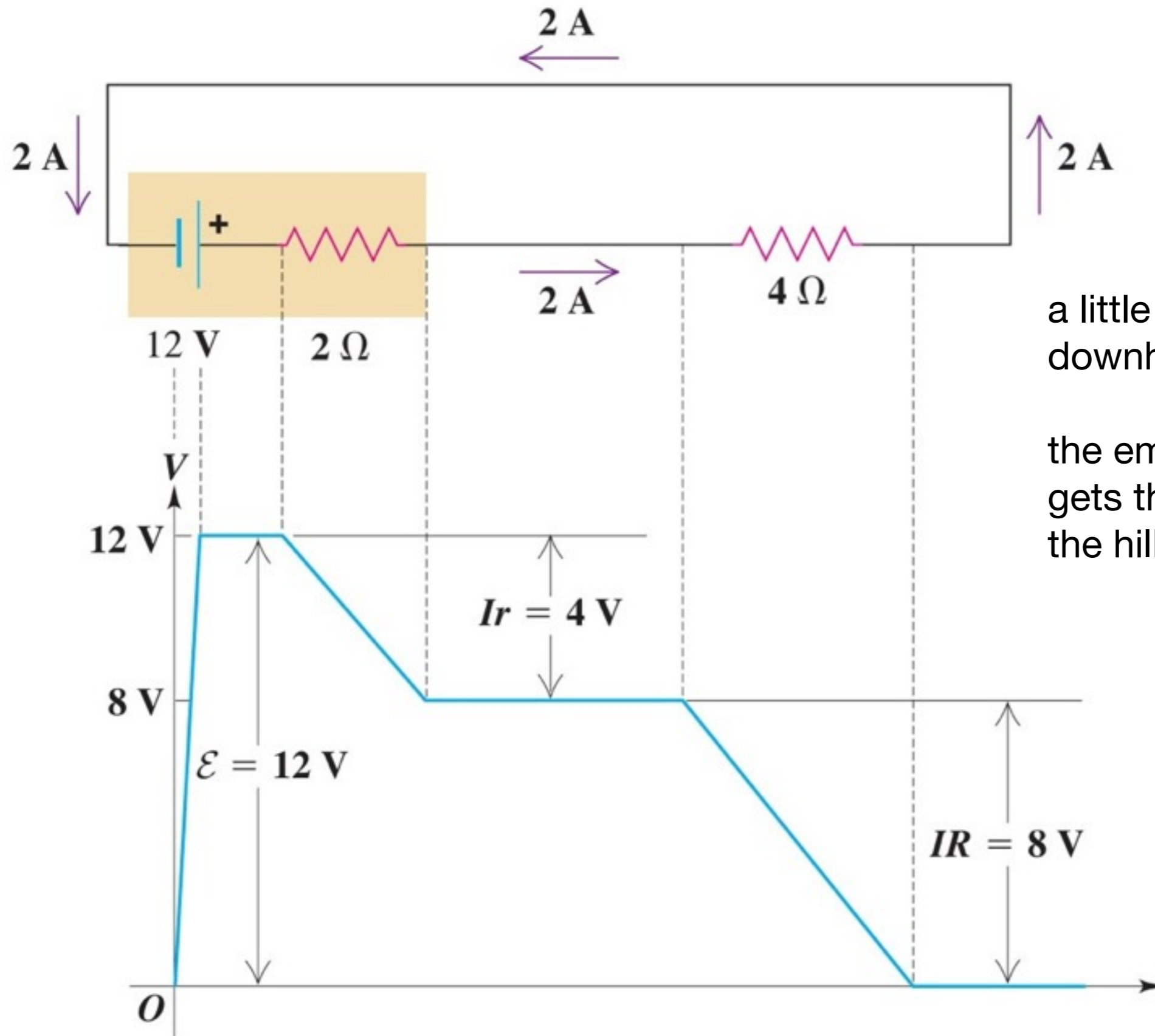


a little like water flowing downhill ?

the emf is like the pump that gets the water to the top of the hill


measurement, voltmeters and ammeters

it's handy to define idealised measurement tools

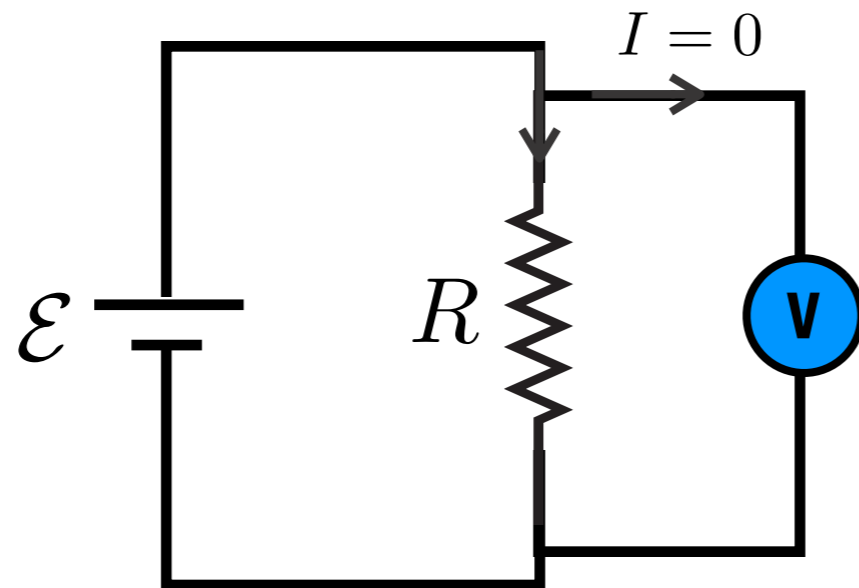→ ideal voltmeter draws no current (infinite resistance)



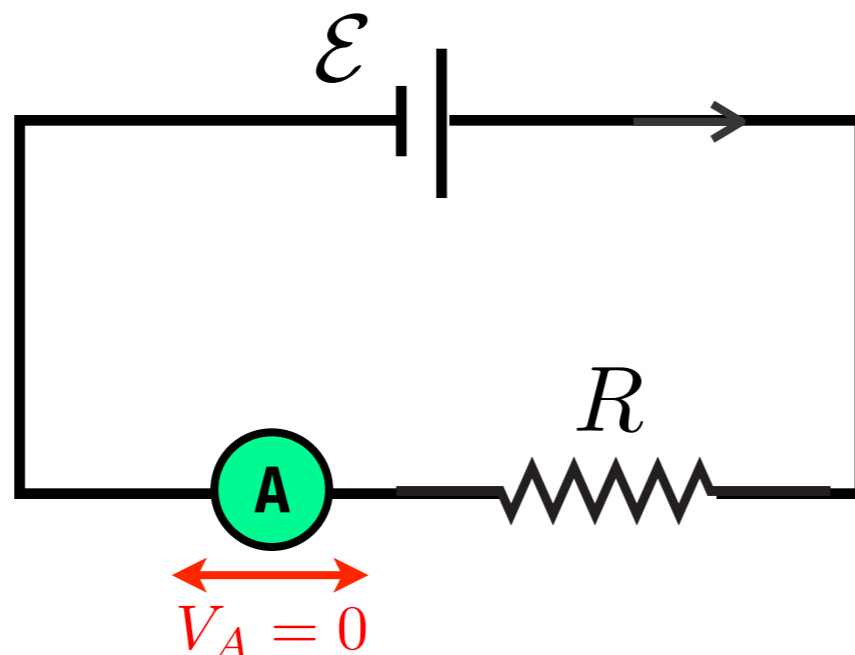→ ideal ammeter causes no change in potential (zero resistance)



power in electrical circuits

see the textbook for a derivation that shows the power transferred **into** a circuit element is

$$P = IV$$



$$V = V_a - V_b$$

suppose the circuit element is a resistor



then Ohm's law holds

$$V = IR$$

so then

$$P = I^2 R = \frac{V^2}{R}$$

is the power lost from the circuit (as heat)

power in electrical circuits


see the textbook for a derivation that shows the power transferred into a circuit element is

$$P = IV$$



$$V = V_a - V_b$$

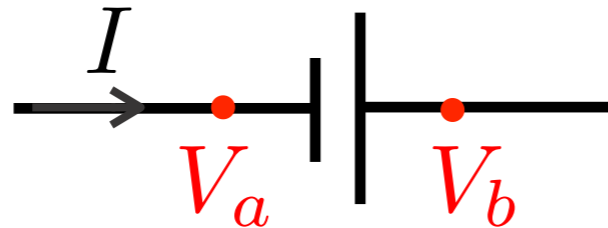suppose the circuit element is an ideal emf source



$$V_b = V_a + \mathcal{E}$$


$$V = -\mathcal{E}$$

$$P = -\mathcal{E}I$$

negative indicates that power is transferred **out** of the circuit element

resistors in series

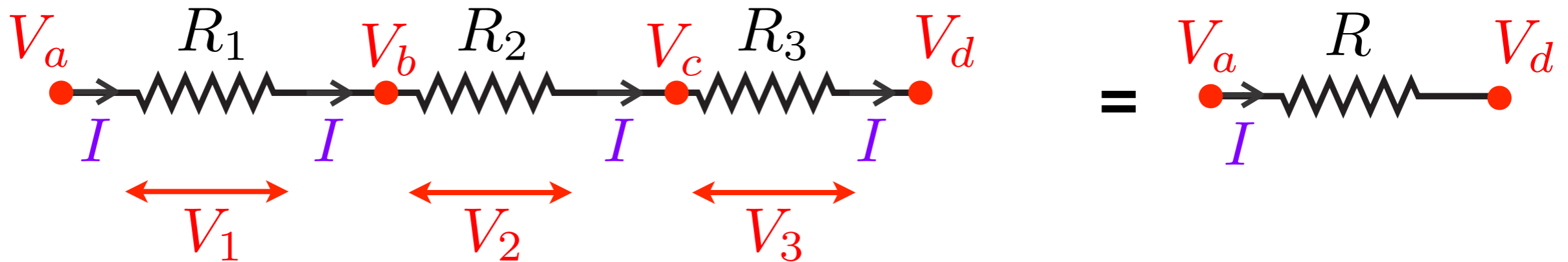Consider three resistors connected in series (part of a larger circuit)



$$V_a - V_d = IR$$


$$\left. \begin{array}{l} V_1 = IR_1 \\ V_2 = IR_2 \\ V_3 = IR_3 \end{array} \right\} \begin{array}{l} V_a - V_d = V_1 + V_2 + V_3 \\ = IR_1 + IR_2 + IR_3 \end{array}$$

$$IR = IR_1 + IR_2 + IR_3$$

$$R = R_1 + R_2 + R_3$$

resistors in parallel

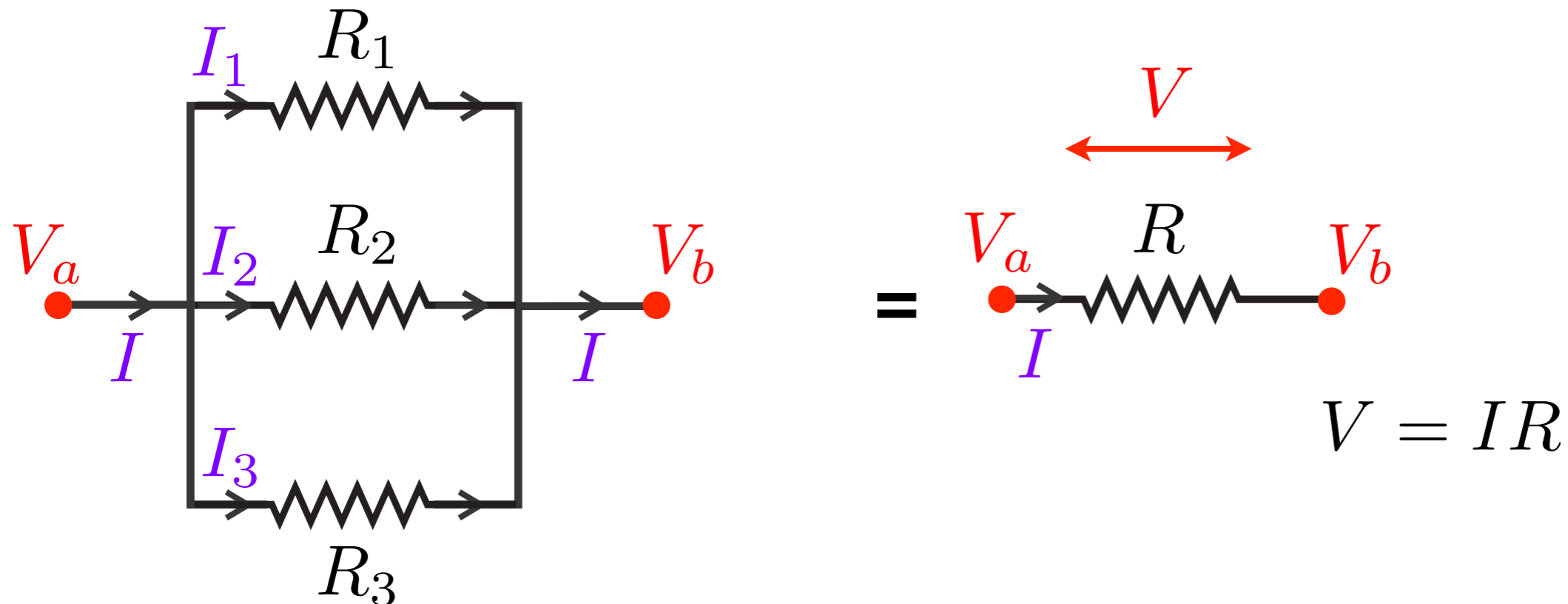Consider three resistors connected in parallel (part of a larger circuit)



$$V_a - V_b = I_1 R_1$$

$$V_a - V_b = I_2 R_2$$

$$V_a - V_b = I_3 R_3$$


$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\boxed{\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$


an example

find the current through each resistor

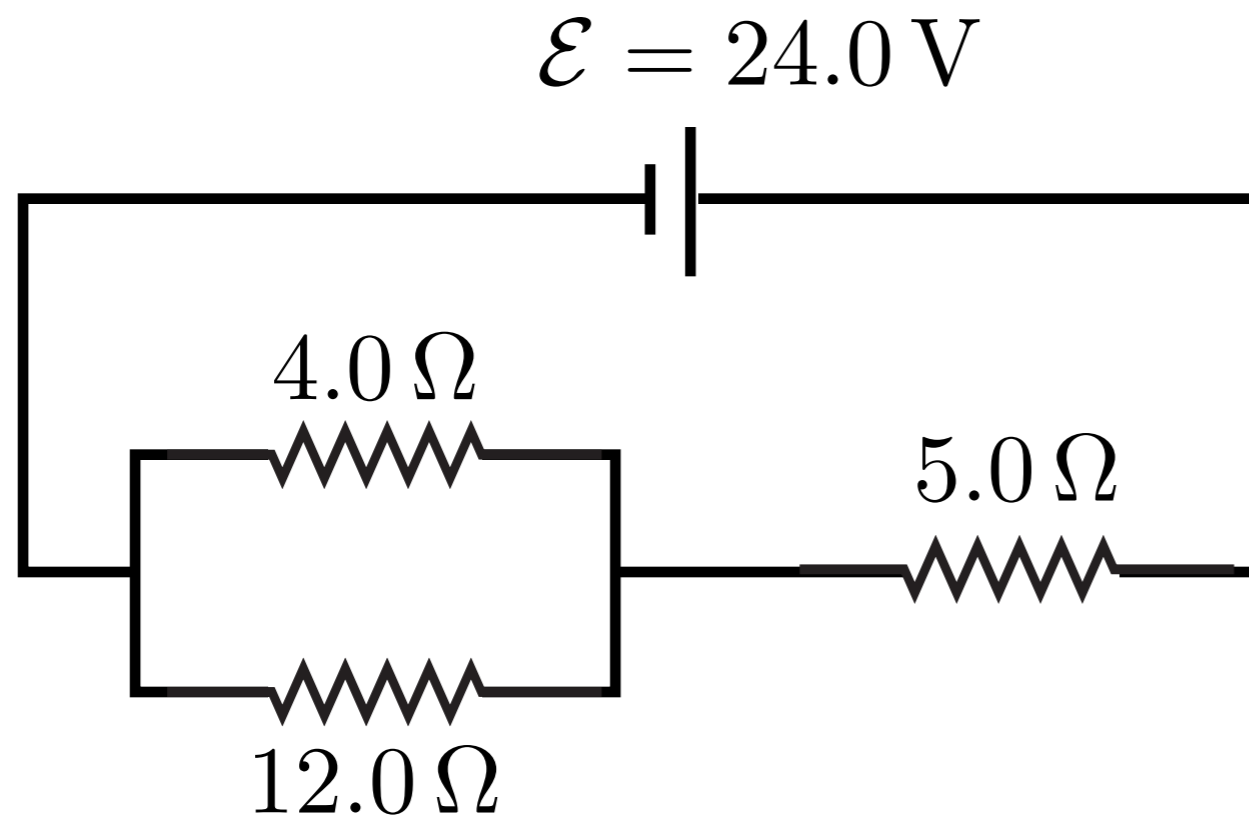

bulbs are resistors

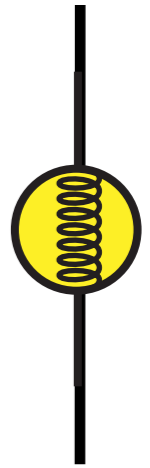
- bulbs act like resistors - power loss is through heat and light
- their brightness is proportional to the power loss in them, $I^2R = V^2/R$
- so the larger the current, the brighter the bulb
(or, the larger the potential drop, the brighter the bulb)




Kirchhoff's rules

- some circuits can't be expressed in terms of parallel and series set-ups
 - Kirchhoff's rules let us deal with these
 - just things we already know

→ junction rule

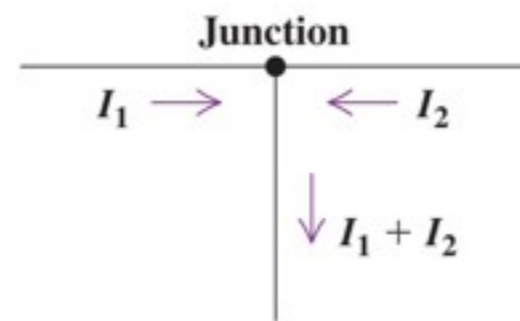

(a) Kirchhoff's junction rule

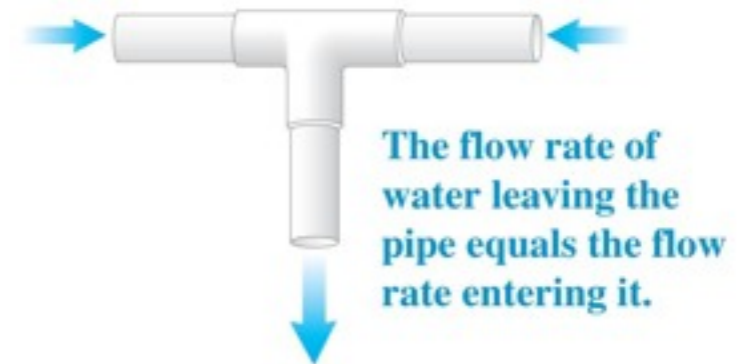

(b) Water-pipe analogy for Kirchhoff's junction rule

“current into a junction = current out of a junction”

“no current is lost in a junction”

the algebraic sum of the currents into a junction is zero $\sum I = 0$

Kirchhoff's rules


- some circuits can't be expressed in terms of parallel and series set-ups
 - Kirchhoff's rules let us deal with these
 - just things we already know

→ loop rule

the algebraic sum of the potential difference in any loop must equal zero

$$\sum_{\text{around loop}} V = 0$$


sign conventions

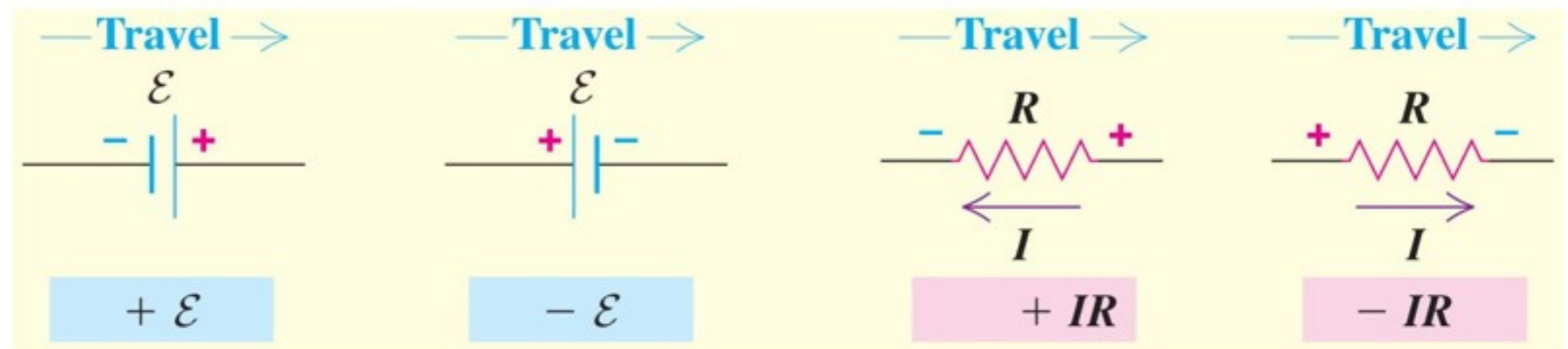

Kirchhoff's rules - example


→ just do a simple example to see how it works

→ find the current in the circuit

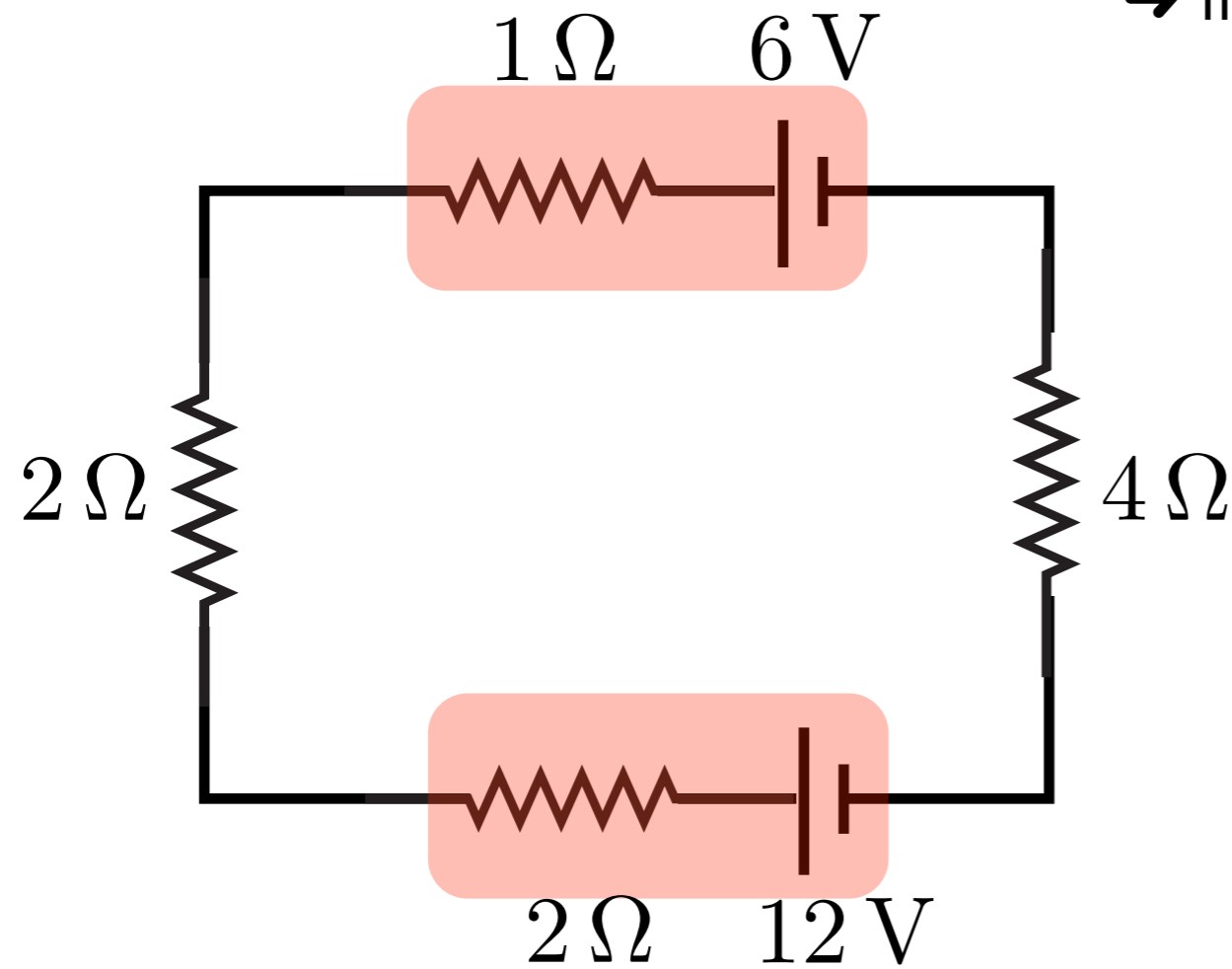

Kirchhoff's rules - example

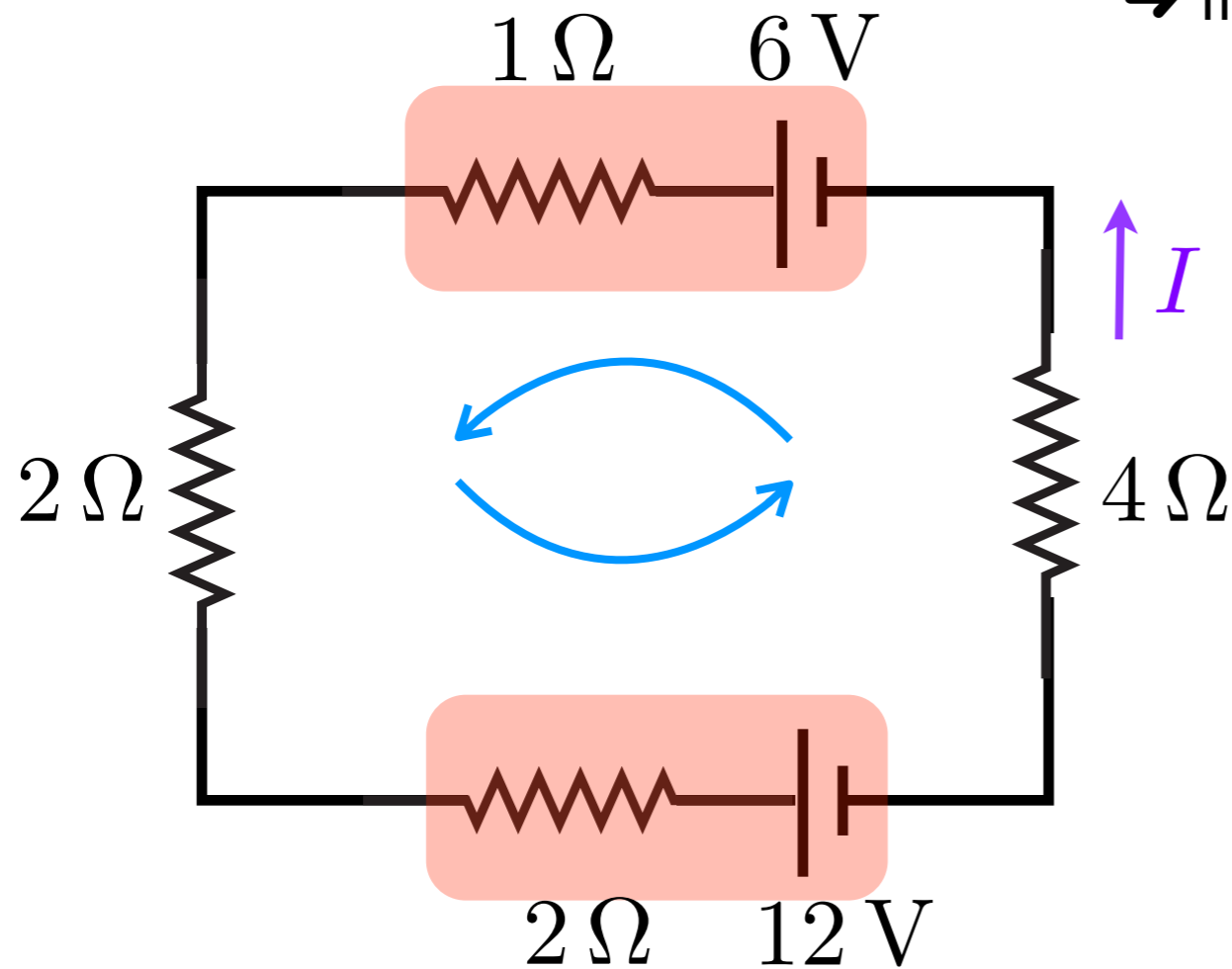→ just do a simple example to see how it works



→ find the current in the circuit


→ choose a direction for the current - doesn't matter if we're wrong, we'll just get a negative value for I

→ choose whether to go around the loop clockwise or counterclockwise - shouldn't change the result

Kirchhoff's rules - example

→ just do a simple example to see how it works


→ find the current in the circuit

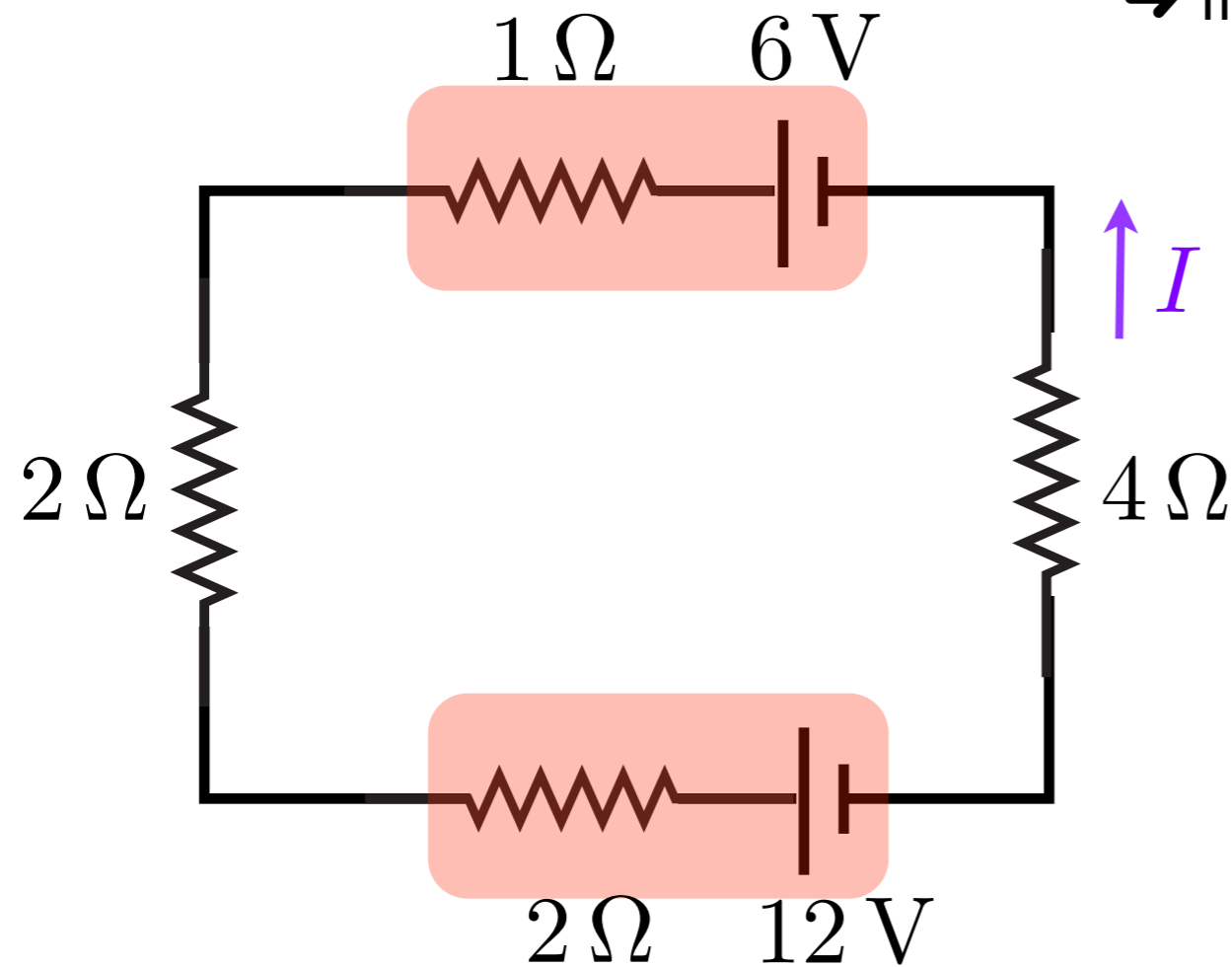

$$I = -\frac{2}{3} \text{ A}$$


so we guessed the current direction wrongly

Kirchhoff's rules - example

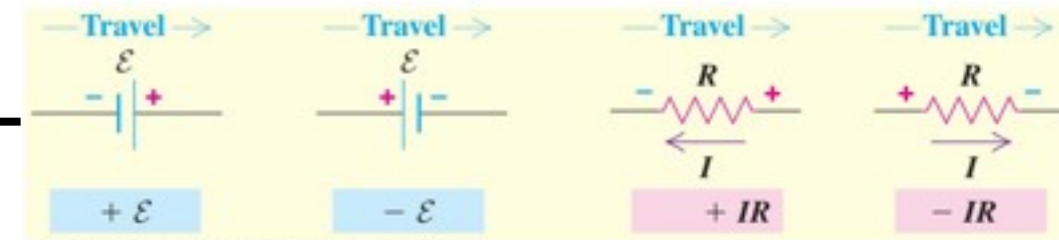

→ a more challenging example that uses both rules

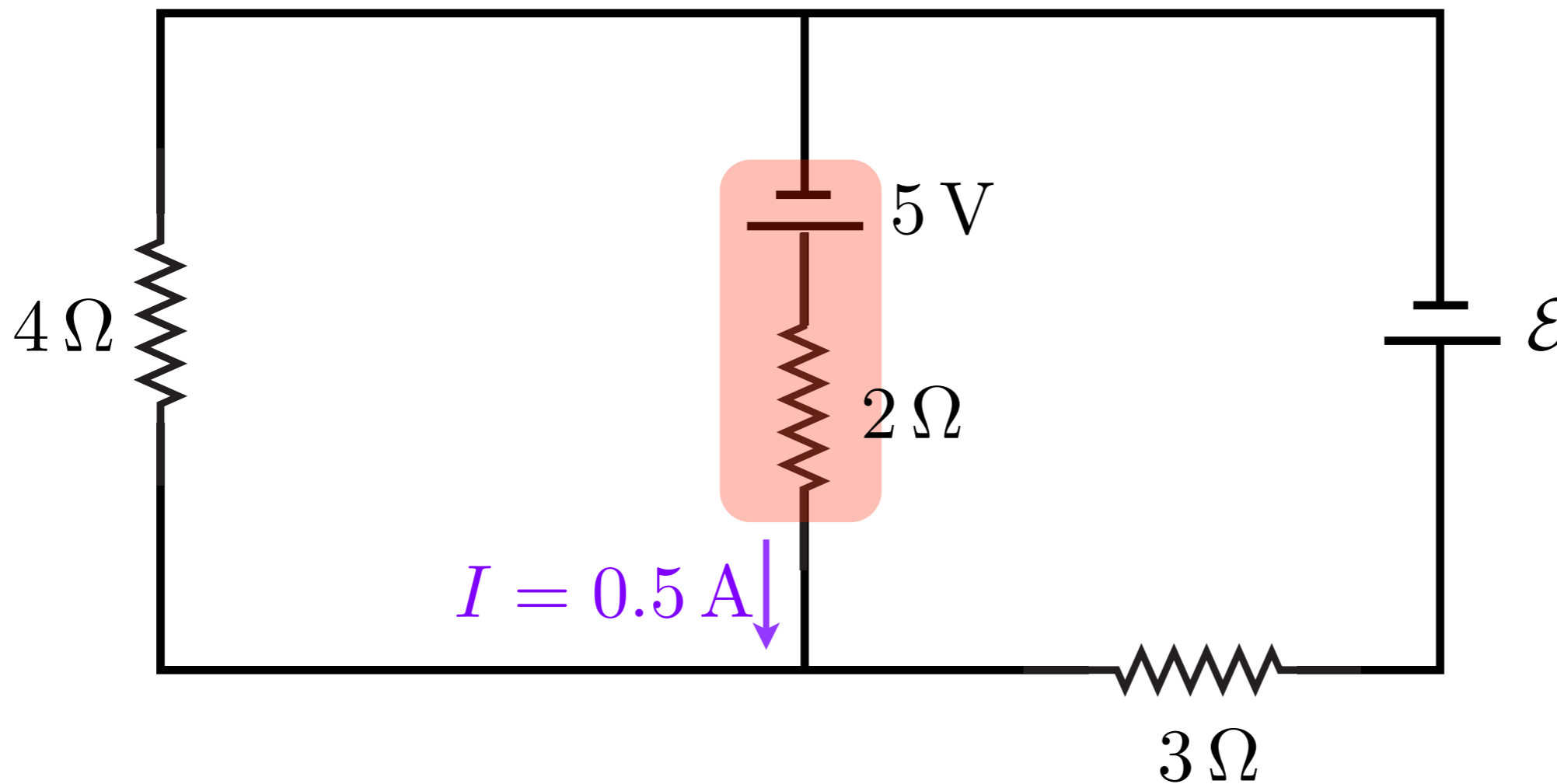
→ find the unknown emf, \mathcal{E} , and the current in the leftmost resistor



Kirchhoff's rules - example

→ a more challenging example that uses both rules

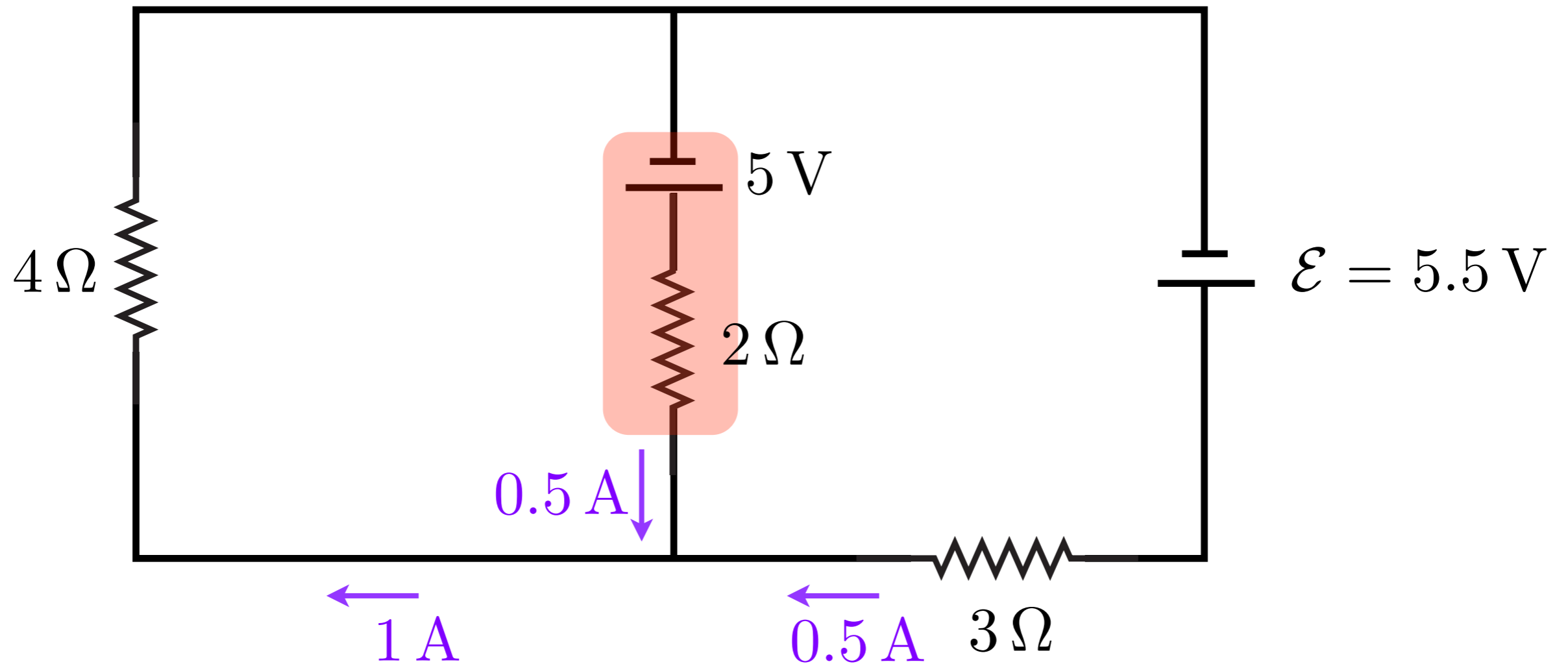→ find the unknown emf, \mathcal{E} , and the current in the leftmost resistor



SI units summary

charge in Coulombs, C

current in Amperes, A = C/s

* actually the 'base' unit (along with m, kg, s)

potential in Volts, V

energy in Joules, J = C V

power in Watts, W = J/s

resistance in Ohms, Ω = V/A