

# Lecture 10. Resistor Circuits, Batteries and EMF

## Outline:

- Connection of Resistors: In Parallel and In Series.
- Batteries.
- Non-ideal batteries: internal resistance.
- Potential distribution around a complete circuit



---

## **Lecture 9:**


DC current: flow of charge carriers, requires  $E \neq 0$  in a conductor. To keep current running, we need to maintain a non-zero potential difference across a conductor.

Microscopic picture: electron “mosquito cloud” slowly drifting in the field.

Linear regime: Ohm’s Law = drift velocity  $\propto E$

Resistance: the coefficient of proportionality between  $V$  and  $I$ , depends on materials parameters.


# Connections: In Series vs. In Parallel

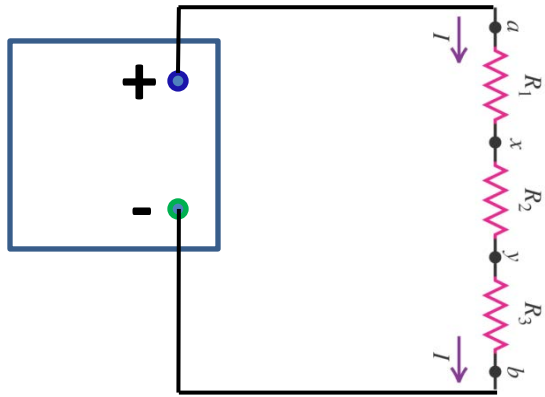

## ***In Series:***

current is the same through all elements

voltage across them can be different

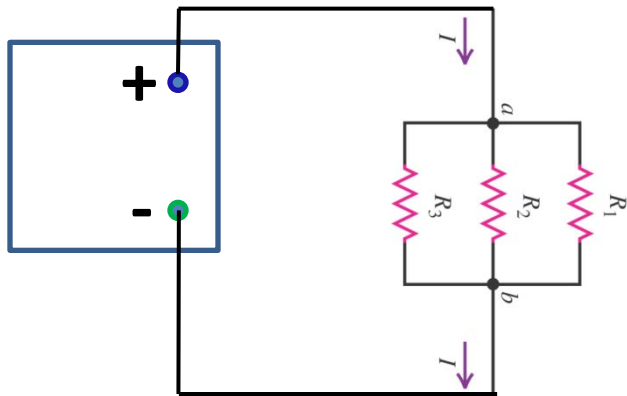


## ***In Parallel:***

voltage is the same across all elements

current through them can be different

(compare with capacitors: replace current with charge)
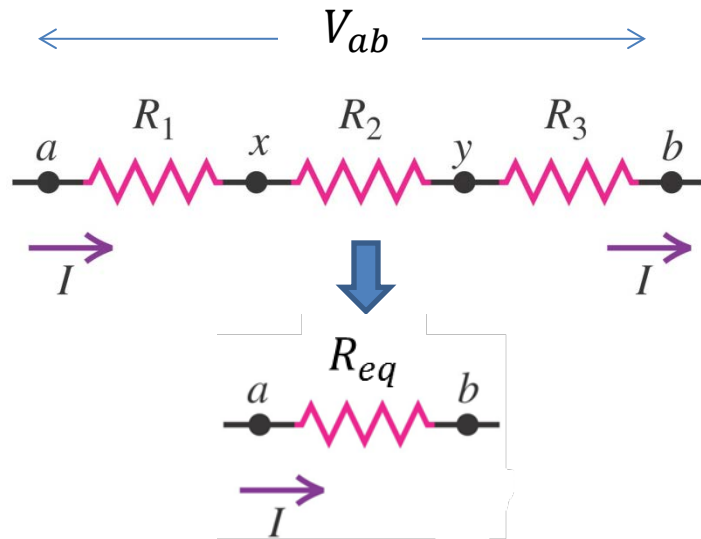
# Resistors: Connection in Series and in Parallel




## In Series

**Common quantity: current**

$$R_{eq} \equiv \frac{V_{ab}}{I} \quad \begin{array}{l} \text{- voltage difference across } R_1, R_2, R_3 \\ \text{- common current} \end{array}$$

$$V_{ab} = V_1 + V_2 + V_3 = I(R_1 + R_2 + R_3)$$

$$R_{eq} = \sum_i R_i$$

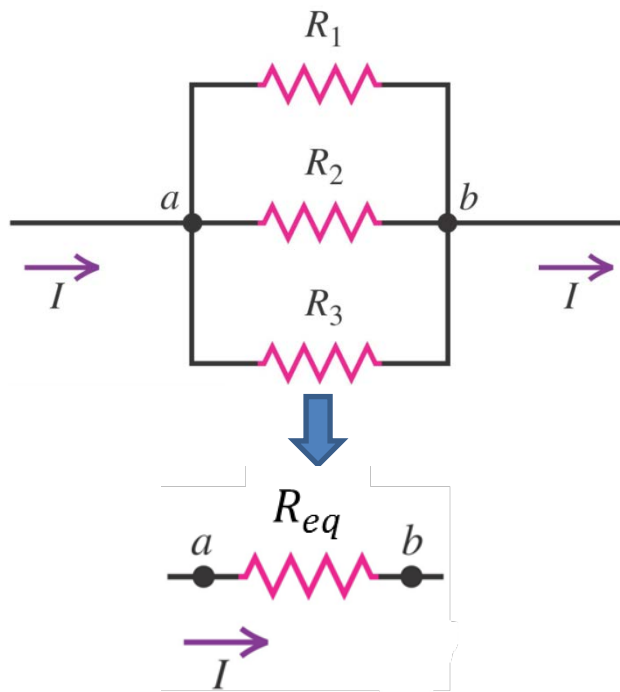

## In Parallel

**Common quantity: voltage difference**



$$R_{eq} \equiv \frac{V_{ab}}{I} \quad \begin{array}{l} \text{- common voltage difference} \\ \text{- total current } I \end{array}$$

$$I = I_1 + I_2 + I_3 = \frac{V_{ab}}{R_1} + \frac{V_{ab}}{R_2} + \frac{V_{ab}}{R_3}$$

$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} = \left( \sum_i \frac{1}{R_i} \right)^{-1}$$

$$R_1 \parallel R_2: \quad R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

# More Complex Circuits

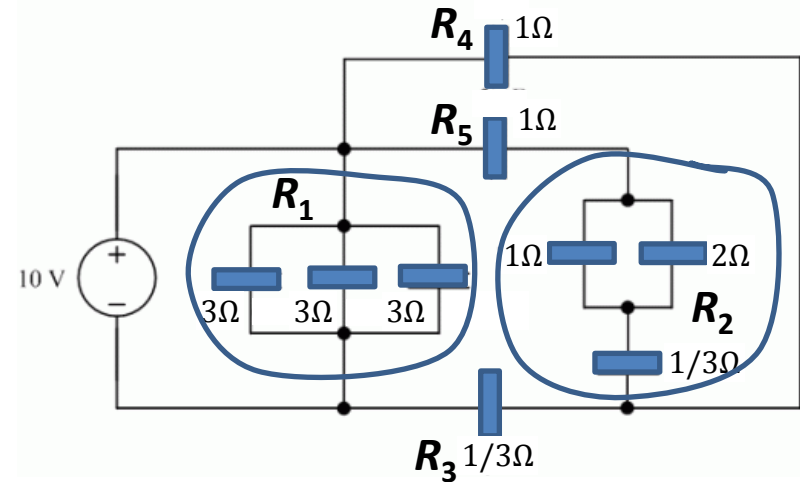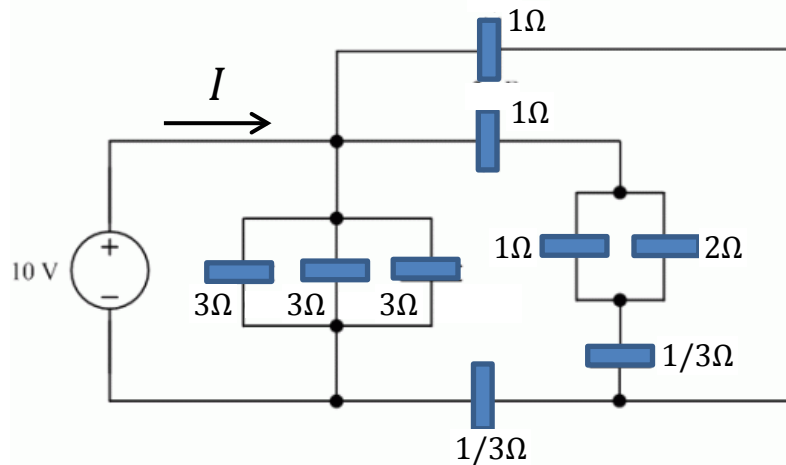

$$R_1 = \left( \frac{1}{3} + \frac{1}{3} + \frac{1}{3} \right)^{-1} = 1\Omega$$

$$R_2 = \frac{1 \cdot 2}{1 + 2} + \frac{1}{3} = 1\Omega$$

$$R_2 \dots R_5 = 1 + 1 = 2\Omega$$



$$R_4 \parallel (R_2 \dots R_5) = \frac{1 \cdot 2}{1 + 2} = \frac{2}{3}\Omega$$

$$R_3 \dots [R_4 \parallel (R_2 \dots R_5)] = \frac{2}{3} + \frac{1}{3} = 1\Omega$$

$$R_{eq} = R_1 \parallel \{ R_3 \dots [R_4 \parallel (R_2 \dots R_5)] \} = \frac{1 \cdot 1}{1 + 1} = 0.5\Omega$$



$$I = \frac{10V}{0.5\Omega} = 20A \quad P = IV = 200W$$
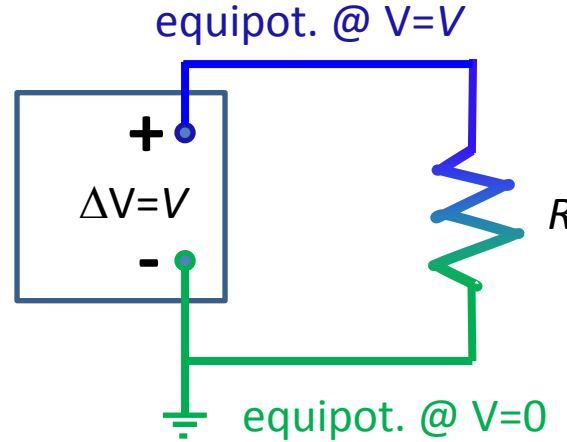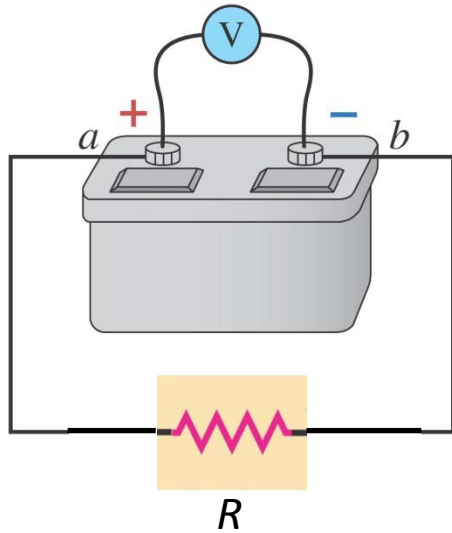
# Ideal Batteries (no energy dissipation inside battery)




We assume that the wires have resistance much smaller than the load  $R$  (all voltage difference provided by the battery is applied to the load  $R$ ).

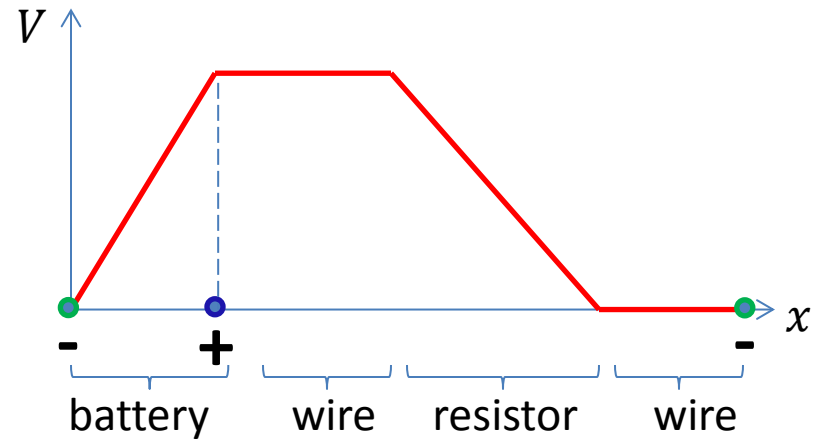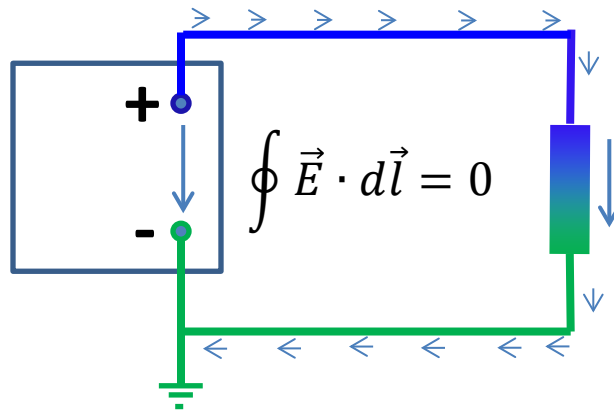Sketch of a (*conservative*) electric field




Conclusion: an “external agent” inside the battery (*not the electrostatic  $E$  !!*) forces the charge carriers to climb “the potential hill”.
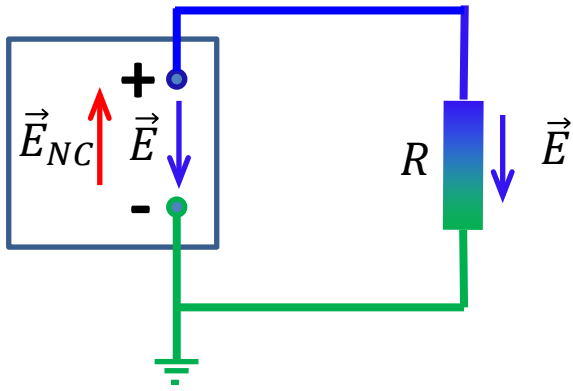
# External Forces (not Electrostatic Field) separate Charges



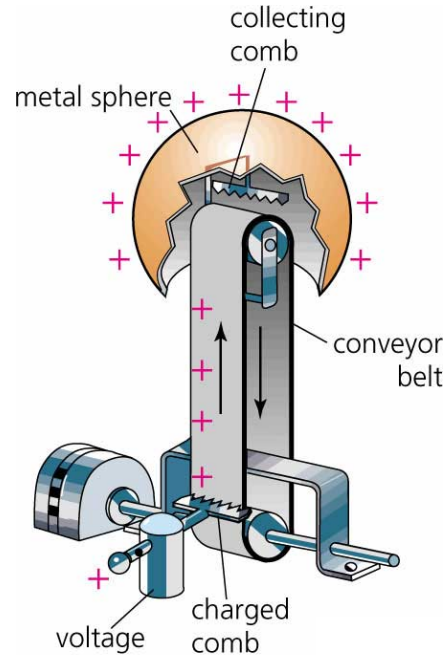
Demonstrations:  
“lemon” battery,  
dynamo



Mechanical analogy:  
van de Graaff  
generator


**Fictitious** field  $\vec{E}_{NC}$  inside the battery: a source of an additional force on charge carriers. This field is **non-conservative**:  $\oint \vec{E}_{NC} \cdot d\vec{l} \neq 0$  ( $\vec{E}_{NC}$  is zero outside the battery). Inside the battery, electrons are driven by the total electric field  $\vec{E}_{net} = \vec{E} + \vec{E}_{NC}$ .

# Electromotive Force (EMF)

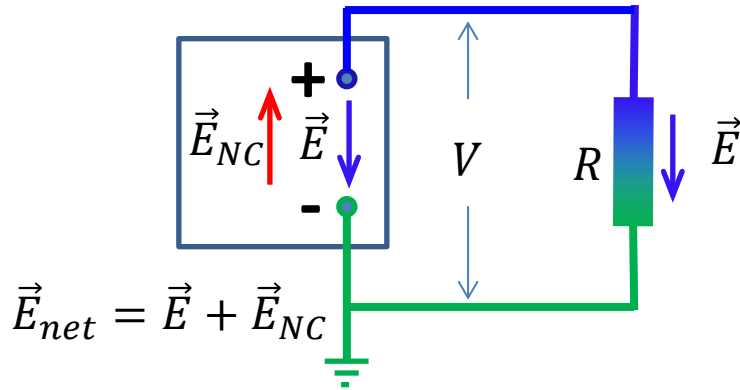

$$\mathcal{E} \equiv \int_{-}^{+} \vec{E}_{NC} \cdot d\vec{l} \quad - \text{ the electromotive force}$$

Units: volts

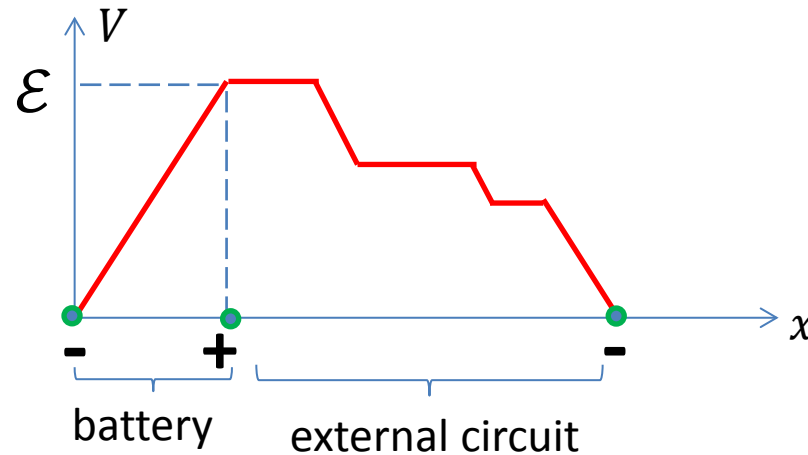


Ideal battery:

$$\mathcal{E} = V = IR$$

$V$  – voltage difference between the battery's electrodes

$R$  – net resistance of the external circuit

# Non-ideal Battery

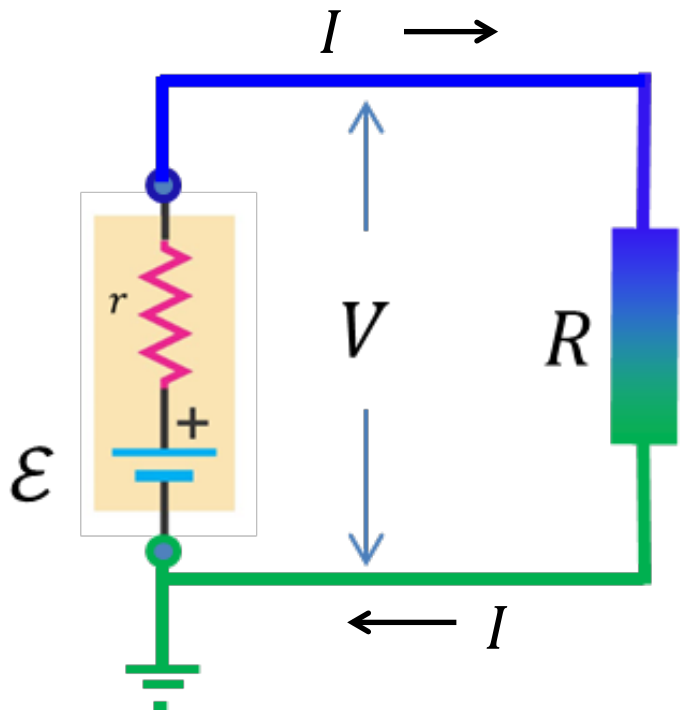

$r$  – the *internal resistance* of the battery

What is the output voltage?

$$R_{eq} = R + r$$

$$I = \frac{\mathcal{E}}{r + R}$$

$$V = \mathcal{E} - Ir = \mathcal{E} \frac{R}{r + R}$$

$$V = \mathcal{E} \frac{R}{r + R}$$



Demonstration of the internal resistance.


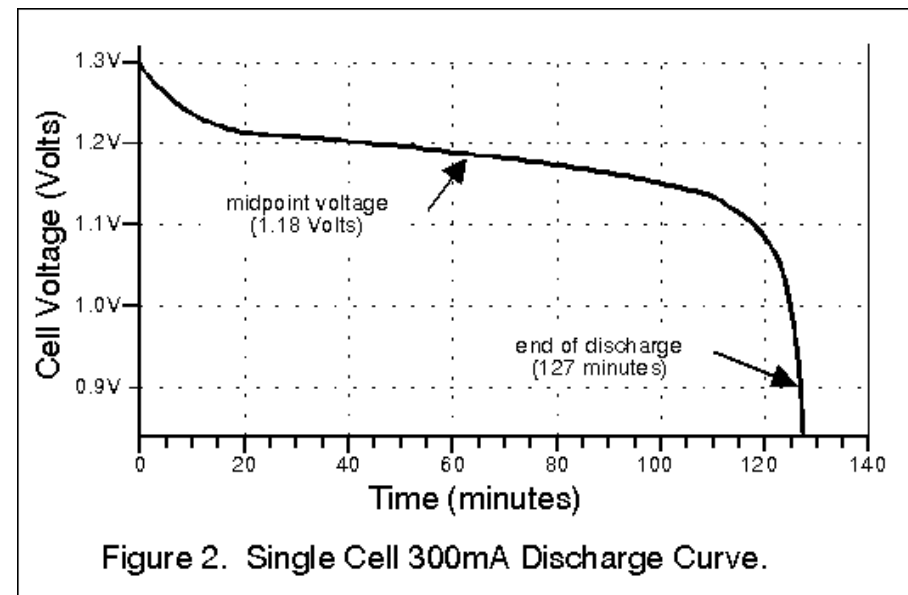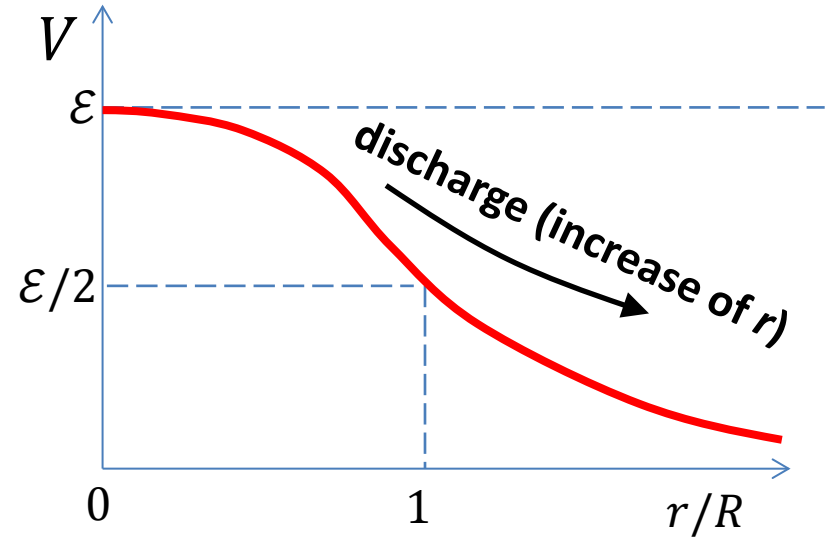
# Battery Discharge


The internal resistance of a battery increases in the process of work: it is small (*in comparison with a typical load resistor*) for a “fresh” battery, and becomes large for an “old” (discharged) one.

$$V = \mathcal{E} \frac{R}{r + R} = \mathcal{E} \frac{1}{r/R + 1}$$



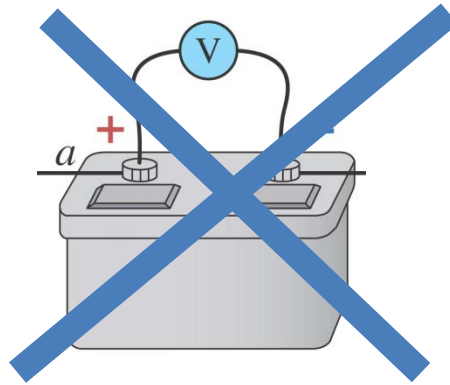
# Battery Tester


Can we use a voltmeter (very high  $r$ ) to test the “freshness” of a battery?



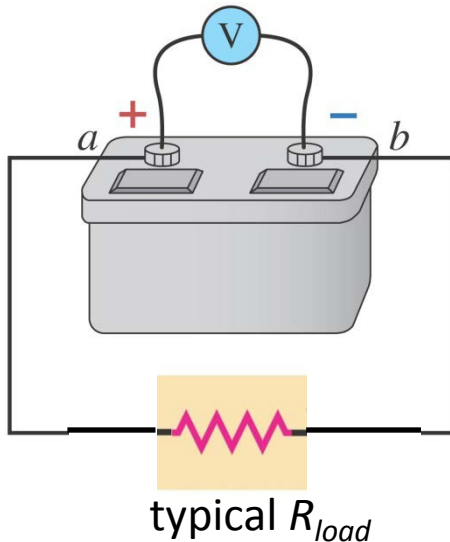The voltmeter will measure  $V \approx \mathcal{E}$  provided  $r \gg R_{in}$ . But  $R_s$  is usually as high as  $10^6 - 10^7 \Omega$ , and even if  $R_{in} \sim 10^3 - 10^4 \Omega$ , we won't notice the battery aging.



# Voltage Source

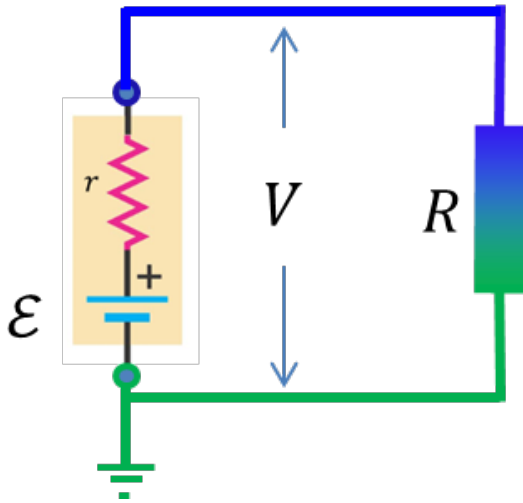


$$V = \varepsilon \frac{R}{r + R}$$

*The goal: to provide output voltage that is independent of the load resistance.*

*An ideal voltage source:*

- A. has “zero” internal resistance (“zero” means that  $r \ll$  all possible values of load  $R$ ).
- B. has “infinite” internal resistance (“infinite” means that  $r \gg$  all possible values of load  $R$ ).

# Voltage Source

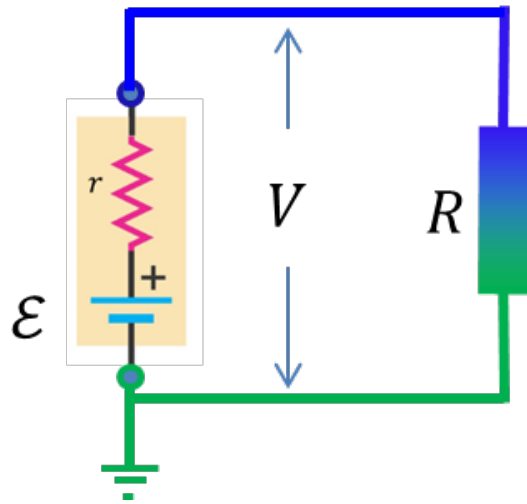


$$V = \epsilon \frac{R}{r + R}$$

*The goal: to provide output voltage that is independent of the load resistance.*

*An ideal voltage source:*

- A. has “zero” internal resistance (“zero” means that  $r \ll$  all possible values of load  $R$ ).
- B. has “infinite” internal resistance (“infinite” means that  $r \gg$  all possible values of load  $R$ ).

# Current Source

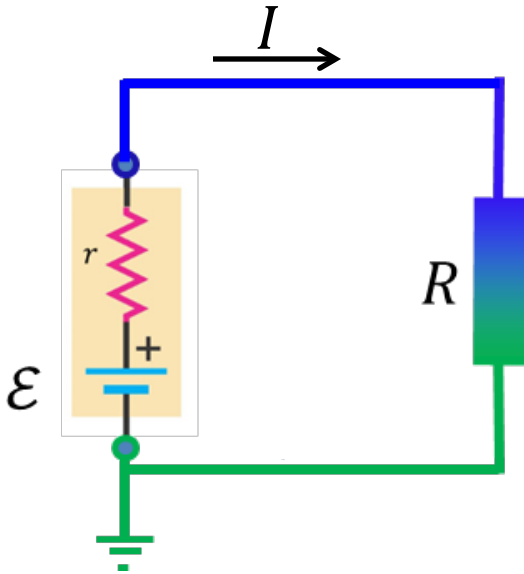


$$I = \frac{\epsilon}{r + R}$$

***The goal: to provide output current that is independent of the load resistance.***

***An ideal current source:***

- A. has “zero” internal resistance (“zero” means that  $r \ll$  all possible values of load  $R$ ).
- B. has “infinite” internal resistance (“infinite” means that  $r \gg$  all possible values of load  $R$ ).

# Current Source

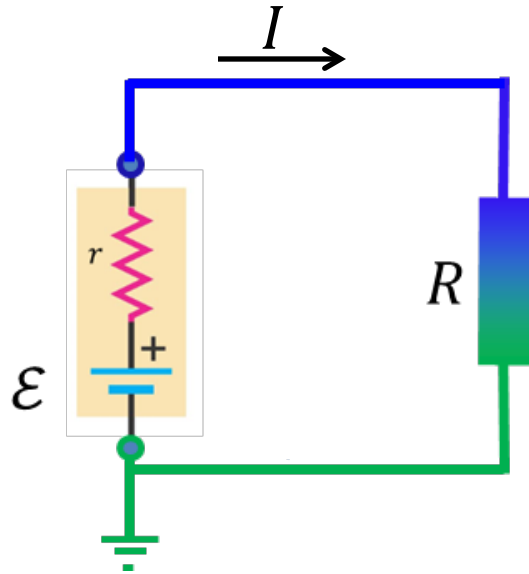

$$I = \frac{\epsilon}{r + R}$$

***The goal: to provide output current that is independent of the load resistance.***

***An ideal current source:***

- A. has “zero” internal resistance (“zero” means that  $r \ll$  all possible values of load  $R$ ).
- B. has “infinite” internal resistance (“infinite” means that  $r \gg$  all possible values of load  $R$ ).

# Conclusion

Batteries: the potential energy of charge carriers is increased by non-electrostatic (non-conservative) forces.


Non-ideal batteries: internal resistance.

Potential distribution around a complete circuit.

Energy and power in electric circuits.


Next time: Lecture 11: Connection of Resistors,  
Kirchhoff's Rules  
§§ 26.1 - 26.3
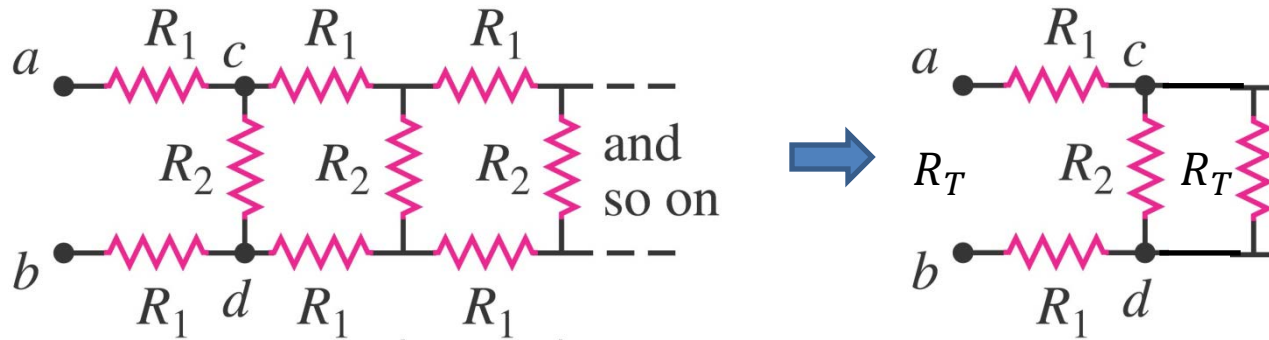
# Appendix 1: More Complicated Resistor Circuits





$$R_T = 2R_1 + \frac{R_2 R_T}{R_2 + R_T} \quad (R_T)^2 - 2R_1 R_T - 2R_1 R_2 = 0$$

All resistors are  $1 \Omega$

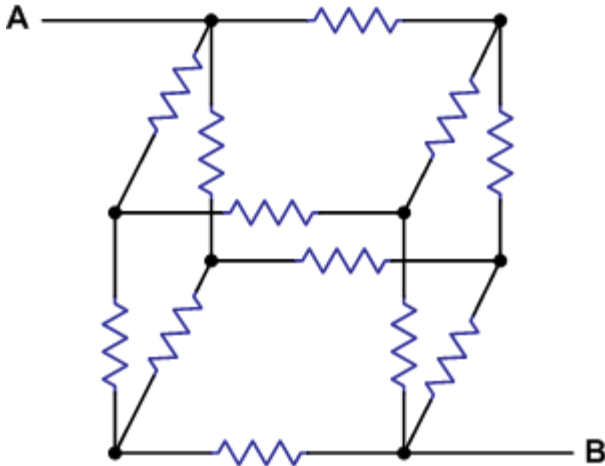

All resistors are  $1 \Omega$

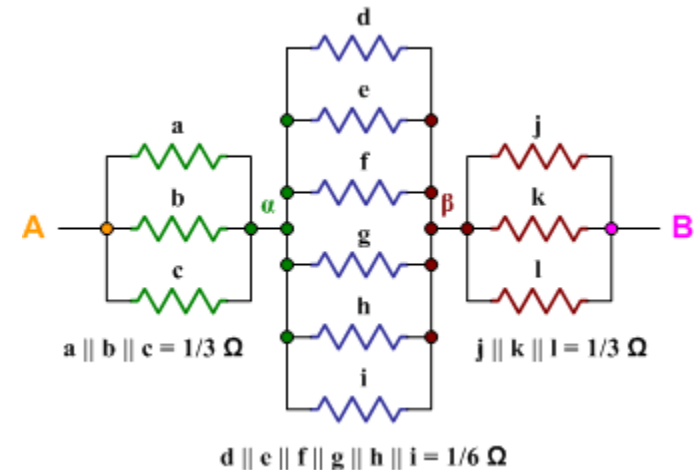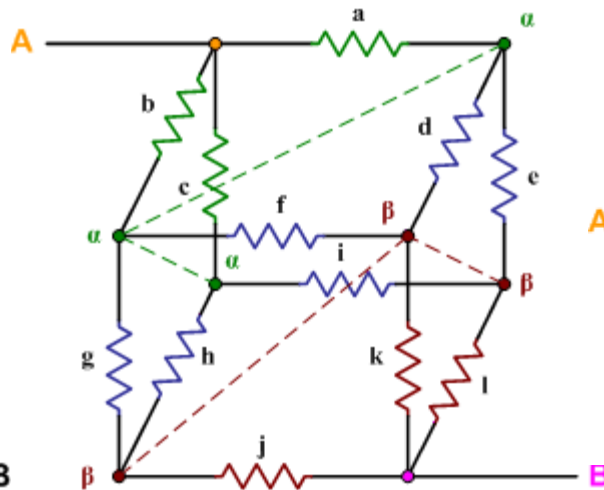

Symmetry helps! Equipotential points can be connected (all  $\alpha$ 's and  $\beta$ 's).