

A student in 1120 emailed me to ask how much extra he should expect to pay on his electric bill when he strings up a standard 1-strand box of icicle holiday lights outside his house. (total, cumulative cost)?

Try to make a real estimate, don't just guess!  
Energy in Colorado costs about 10¢/KW hr.

- A: Less than 1 cent
- B: Between 1 cent and 10 cents
- C: Between \$.10 and \$1.00
- D: Between \$1.00 and \$10.00
- E: More than \$10.00

50-100 Watts? (Like ONE bulb). 12 hrs/day? 30 days?  
~100 W \* 10 hrs/day \* 30 days = 30,000 W\*hrs = 30 kW hrs.  
⇒\$3

(for 100 million Joules! Energy is cheap...)

---

---

---

---

---

---

---

---

Welcome back!!

CAPA #13 is due Friday

[New online participation survey is up!](#)

Pretest tonight (and Tut hw for tomorrow)

Reading: catch up if you're behind! E.g. 35.6 (1st 2 pp)  
(We'll finish up Ch. 33 this week -all sections, including 33.6)

Last: Transformers and Induction

Today: Inductors in circuits

Next: AC circuits

---

---

---

---

---

---

---

---

### Inductor = (coil of wire)

Important fact: Magnetic Flux  $\Phi_B$  is proportional to the current making the  $\Phi_B$

All our equations for B-fields show that  $B \propto i$

$$d\vec{B} = \frac{\mu_0 i}{4\pi} \frac{d\vec{l} \times \hat{r}}{r^2}$$

Biot-Savart

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 i_{\text{thru}}$$

Ampere

---

---

---

---

---

---


---

---

Flux  $\Phi_B \propto B \propto i$

Flux  $\Phi_B \propto i$

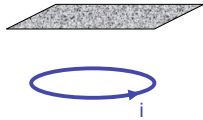Assumes leaving everything else the same.



If we double the current  $i$ , we will double the magnetic flux through any surface.

---

---

---

---

---

---

---

---

Self-Inductance (L) of a coil of wire

$$\Phi_B \equiv Li$$

This equation defines self-inductance.

$$L \equiv \frac{\Phi_B}{i}$$

Note that since  $\Phi_B \propto i$ , L must be independent of the current  $i$ .

L has units  $[L] = [\text{Tesla meter}^2]/[\text{Amperes}]$   
New unit for inductance = [Henry].



---

---

---

---


---

---

---

---

An inductor is just a coil of wire.

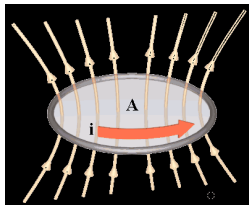

The Magnetic Flux created by the coil, through the coil itself:

$$\Phi_B = \oint \vec{B} \cdot d\vec{A}$$

This is quite hard to calculate for a single loop. Earlier we calculated B at the center, but it varies over the area.

---

---

---

---


---

---

---

---

Consider a simpler case of a solenoid

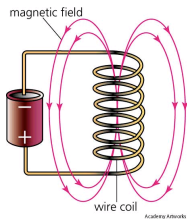

$$|\vec{B}_{inside}| = \mu_0 ni = \mu_0 \frac{N}{L'} i$$

Recall that the B-field inside a solenoid is uniform!

N = number of loops  
L' = length of solenoid  
\* Be careful with symbol L !

---

---

---


---

---

---

---

---

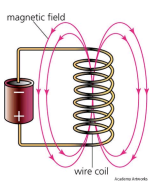

$$|\vec{B}_{inside}| = \mu_0 ni = \mu_0 \frac{N}{L'} i$$

$$\Phi_B = N \oint \vec{B} \cdot d\vec{A} = NBA = N(\mu_0 ni)A$$

$$L = \frac{\Phi_B}{i} = \mu_0 NnA = \mu_0 An^2 L'$$

Self-Inductance

Length

---

---

---

---

---

---

---

---

Inductor 1 consists of a single loop of wire. Inductor 2 is identical to 1 except it has two loops on top of each other. How do the self-inductances of the two loops compare?

A)  $L_2 = 2 L_1$

**B)  $L_2 > 2L_1$**

C)  $L_2 < 2L_1$



HINT 1: What is the B field at the center of coil 2, B2, compared to the field in the center of coil 1?  
HINT 2: inductance  $L = \Phi(\text{total})/i$

Answer:  $L_2 > 2L_1$ , in fact  $L_2$  is roughly 4  $L_1$ !  
Recall  $L = \Phi/i$ . When N doubles  $\Rightarrow$  B doubles.  
 $\Phi$ (each loop) doubles (because B is doubled)  
But  $\Phi(\text{tot}) = 2 \Phi(\text{each loop})$ , so double\*double = 4 times!

---

---

---

---

---

---


---

---

Clicker Question

Two long solenoids, each of inductance  $L$ , are connected together to form a single very long solenoid of inductance  $L_{\text{total}}$ . What is  $L_{\text{total}}$ ?

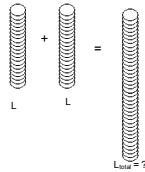- A)  $2L$
- B)  $4L$
- C)  $8L$
- D) none of these/don't know



Answer:  $2L$ . The inductance of a solenoid is  $L = \mu_0 n^2 L'$ , ( $n = N/L'$  and  $L'$  is the length.) In this case, we did not change  $n$ , but  $L'$  (length) doubled, so  $L$  doubles.

---

---

---

---

---

---

---

---

What does inductance tell us?

$$L = \frac{\Phi_B}{i}$$

$$\Phi_B = Li$$

$$\frac{d\Phi_B}{dt} = L \frac{di}{dt}$$

$L$  is independent of time.  
Depends only on geometry of inductor (like capacitance).

---

---

---

---

---

---

---

---

$$\frac{d\Phi_B}{dt} = L \frac{di}{dt}$$

Recall Faraday's Law

$$\mathcal{E} = -\frac{d\Phi_B}{dt}$$

$$-\mathcal{E} = L \frac{di}{dt}$$

$$\mathcal{E} = -L \frac{di}{dt}$$

Changing the current in an inductor creates an EMF which opposes the change in the current.  
Sometimes called "back EMF"

---

---

---

---

---

---

---

---

$$\varepsilon = -L \frac{di}{dt}$$

It is difficult (requires big external Voltage) to change quickly the current in an inductor.

The current in an inductor **cannot** change instantly.

If it did (or tried to), there would be an infinite back EMF. This infinite back EMF would be fighting the change!

---

---

---

---

---

---

---

---



---

---

---

---

---

---

---

---

What do these inductors do in circuits?

Just recall that the EMF or Voltage across an inductor is:

$$\varepsilon = -L \frac{di}{dt}$$

So, when we add them to circuits, we can apply the usual Kirchhoff's Voltage Law and include the inductors.

---

---

---

---


---

---

---

---

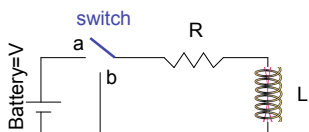Consider a circuit with a battery, resistor and inductor (RL circuit)



Suppose switch is in position (a) for a long time.

---

---

---

---


---

---

---

---

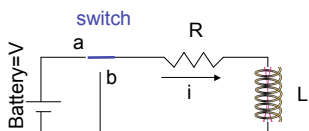Consider a circuit with a battery, resistor and inductor (RL circuit)



Suppose switch is in position (a) for a long time.

In steady state (after a long time), the current will no longer be changing and thus the inductor looks like a regular wire!

---

---

---


---

---

---

---

---

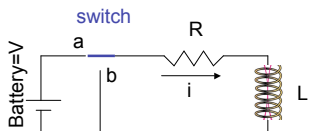

If after a long time the inductor acts like a wire:

$$\Delta V = V - iR = 0 \quad i = \frac{V}{R}$$

---

---

---


---

---

---

---

---

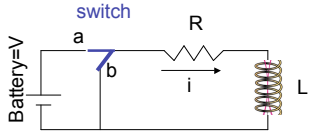

At  $t=0$ , move the switch to (b).

Normally one might expect there to immediately be zero current. However, inductors don't let the current change *instantly*.

---

---

---


---

---

---

---

---

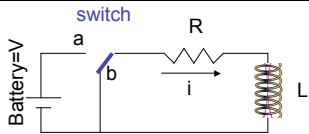

$$\Delta V = -iR - L \frac{di}{dt} = 0$$

$$\frac{di}{dt} = -\left(\frac{R}{L}\right)i$$

We need to solve this differential equation for  $i(t)$ .

---

---

---

---

---

---

---

---

$$\frac{di}{dt} = -\left(\frac{R}{L}\right)i$$

$$i(t) = i_0 e^{-\left(\frac{R}{L}\right)t} \quad \text{where} \quad i_0 = \frac{V}{R}$$

$$i(t) = i_0 e^{-t/\left(\frac{L}{R}\right)} \quad \text{Current exponentially decays with Time Constant } = \tau = L/R \text{ (units of seconds).}$$

---

---

---

---

---


---

---

---

Clicker Question

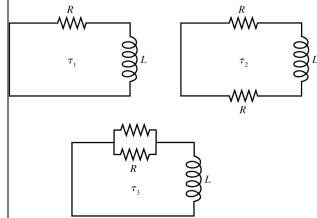Rank in order, from largest to smallest, the time constants  $\tau_1$ ,  $\tau_2$  and  $\tau_3$  in the three circuits.



- A.  $\tau_1 > \tau_2 > \tau_3$
- B.  $\tau_2 > \tau_1 > \tau_3$
- C.  $\tau_2 > \tau_3 > \tau_1$
- D.  $\tau_3 > \tau_1 > \tau_2$**
- E.  $\tau_3 > \tau_2 > \tau_1$

$$i(t) = i_0 e^{-t/\left(\frac{L}{R}\right)}$$

---

---

---

---

---


---

---

---

Clicker Question

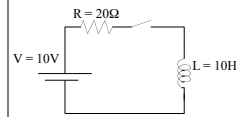The switch in the circuit below is closed at  $t=0$ .



What is the initial rate of change of current  $di/dt$  in the inductor, immediately after the switch is closed?

(Hint: what is the initial voltage across the inductor?)

- A) 0 A/s
- B) 0.5A/s
- C) 1A/s
- D) 10A/s
- E) None of these.

---

---

---

---

---

---

---

---