

## Lecture 10


### Simple FET Circuits and Small Signal Models

---


In this lecture you will learn:

- The operation of simple MOS FET circuits
- Small signal circuit models of the MOS FETs



### A NMOS Transistor in 3D

 

### A NMOS Transistor: A Review

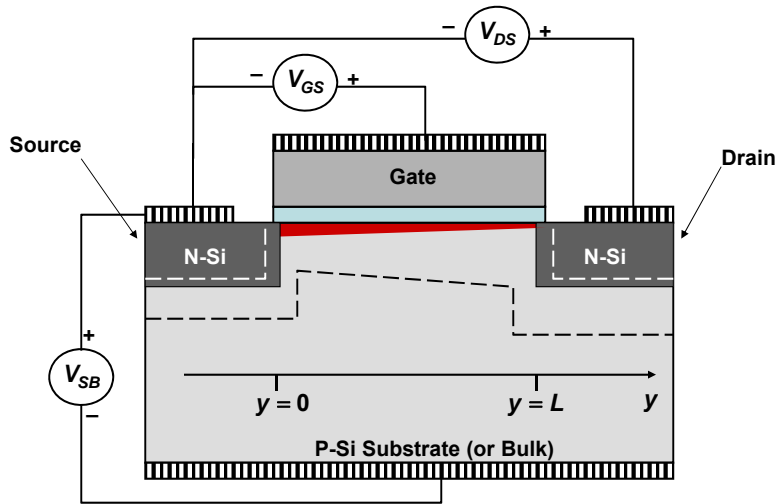

### NMOS Transistor: A Review

 
 


Simplified current model (good for hand calculations):

$$I_D = \begin{cases} 0 & \text{For } V_{GS} < V_{TN} & \text{Cut-off} \\ k_n \left[ V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right] V_{DS} & \text{For } 0 \leq V_{DS} \leq V_{GS} - V_{TN} & \text{Linear region} \\ \frac{k_n}{2} (V_{GS} - V_{TN})^2 & \text{For } 0 \leq V_{GS} - V_{TN} \leq V_{DS} & \text{Saturation region} \end{cases}$$

$$\left\{ k_n = \frac{W}{L} \mu_n C_{ox} \right.$$

### NMOS Transistor: A Review

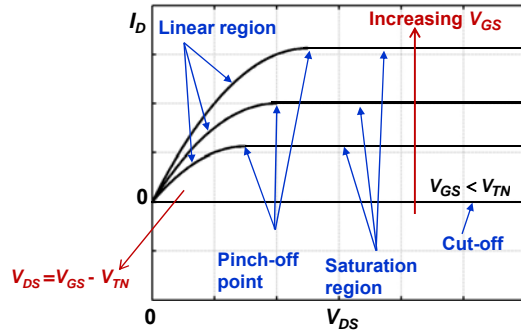 


Better current model:

$$I_D = \begin{cases} 0 & \text{For } V_{GS} < V_{TN} & \text{Cut-off} \\ k_n \left[ V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right] V_{DS} (1 + \lambda_n V_{DS}) & \text{For } 0 \leq V_{DS} \leq V_{GS} - V_{TN} & \text{Linear region} \\ \frac{k_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS}) & \text{For } 0 \leq V_{GS} - V_{TN} \leq V_{DS} & \text{Saturation region} \end{cases}$$

$$k_n = \frac{W}{L} \mu_n C_{ox}$$

### NFET Voltage Amplifier and Inverter

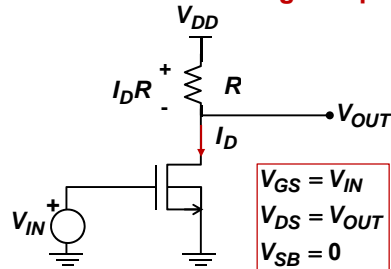

We need to find the relation between the output and the input voltage

1)  $V_{IN} < V_{TN}$



The FET is in cut-off regime and  $I_D = 0$  and consequently  $V_{OUT} = V_{DD}$

2)  $V_{IN} > V_{TN}$

The FET is turned on and  $I_D \neq 0$  and consequently  $V_{OUT} = V_{DD} - I_D R < V_{DD}$

$$\begin{array}{llll} V_{DS} > V_{GS} - V_{TN} & \text{(Saturation)} & \longrightarrow & V_{OUT} > V_{IN} - V_{TN} & \text{(Saturation)} \\ V_{DS} < V_{GS} - V_{TN} & \text{(Linear)} & \longrightarrow & V_{OUT} < V_{IN} - V_{TN} & \text{(Linear)} \end{array}$$
  
### NFET Voltage Amplifier and Inverter: A Graphical Solution






$$I_D = \frac{V_{DD} - V_{OUT}}{R}$$


$$I_D = \begin{cases} 0 & \text{For } V_{IN} < V_{TN} \\ k_n \left[ V_{IN} - V_{TN} - \frac{V_{OUT}}{2} \right] V_{OUT} & \text{For } 0 \leq V_{OUT} \leq V_{IN} - V_{TN} \\ \frac{k_n}{2} (V_{IN} - V_{TN})^2 & \text{For } 0 \leq V_{IN} - V_{TN} \leq V_{OUT} \end{cases}$$

$$k_n = \frac{W}{L} \mu_n C_{ox}$$
 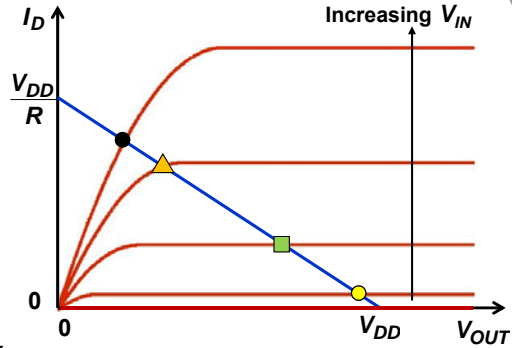 
### NFET Voltage Amplifier and Inverter: A Graphical Solution


 
### NFET Voltage Amplifier and Inverter: Transfer Curve



1) Assume the FET is in the saturation regime:


$$I_D = \frac{k_n}{2} (V_{IN} - V_{TN})^2$$

$$I_D = \frac{V_{DD} - V_{OUT}}{R}$$

Answer is:

$$V_{OUT} = V_{DD} - \frac{Rk_n}{2} (V_{IN} - V_{TN})^2$$
 
$$\Rightarrow \frac{dV_{OUT}}{dV_{IN}} = -Rk_n(V_{IN} - V_{TN})$$




But the assumption that the FET is in saturation is only valid provided that:

$$V_{DS} > V_{GS} - V_{TN}$$

$$\Rightarrow V_{OUT} > V_{IN} - V_{TN}$$
 
### NFET Voltage Amplifier and Inverter: Transfer Curve




2) Now assume the FET is in the linear regime:

$$I_D = k_n \left[ V_{IN} - V_{TN} - \frac{V_{OUT}}{2} \right] V_{OUT}$$

$$I_D = \frac{V_{DD} - V_{OUT}}{R}$$

 Answer can be found by solving the above two equations for  $V_{OUT}$  vs  $V_{IN}$




A high input voltage produces a low output voltage

A low input voltage produces a high output voltage

The device can therefore be used as a logical inverter!
 
### NFET Voltage Amplifier and Inverter: Transfer Curve




In the high gain region, the slope  $\left| \frac{dV_{OUT}}{dV_{IN}} \right|$  can be much larger than unity!

This means a small change in the input voltage will produce a large change in the output voltage

The circuit can therefore be used as a voltage amplifier!
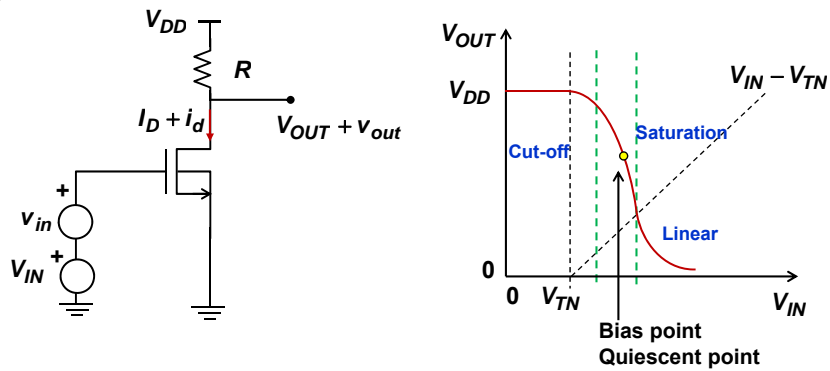
### NFET Common Source (CS) Voltage Amplifier



What is:  $\frac{v_{out}}{v_{in}} = ?$   $\longrightarrow$  Voltage gain


We need better techniques to calculate the voltage gain of such amplifier circuits

We need small signal models of the FETs!

 
### NFET Model with Channel Length Modulation Included

We will often use the following current model:


$$I_D = \begin{cases} 0 & \text{For } V_{GS} < V_{TN} \\ & \text{(Cut-off region)} \\ k_n \left[ V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right] V_{DS} (1 + \lambda_n V_{DS}) & \text{For } 0 \leq V_{DS} \leq V_{GS} - V_{TN} \\ & \text{(Linear region)} \\ \frac{k_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS}) & \text{For } 0 \leq V_{GS} - V_{TN} \leq V_{DS} \\ & \text{(Saturation region)} \end{cases}$$



### NFET Small Signal Model

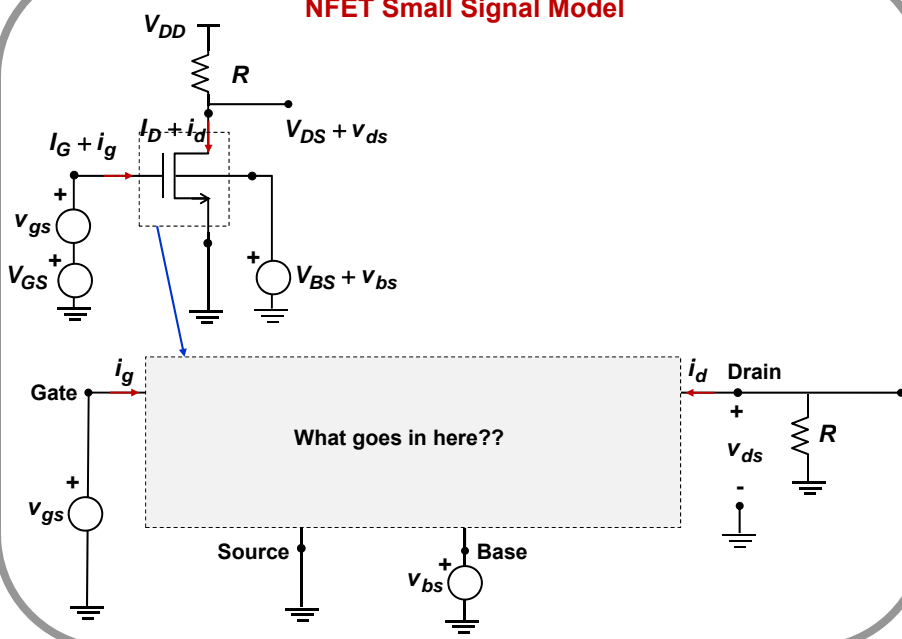


### NFET Small Signal Model – Part I

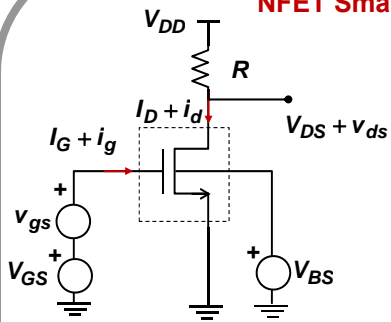

$$\begin{aligned}
 i_D &= I_D + i_d \\
 &= I_D(V_{GS} + v_{gs}) \quad \left\{ \text{IEEE notation!} \right. \\
 &= I_D + \frac{\partial I_D}{\partial V_{GS}} v_{gs} \\
 &= I_D + g_m v_{gs}
 \end{aligned}$$


$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

Transconductance

 


A voltage-controlled current source

### NFET Small Signal Model – Part II

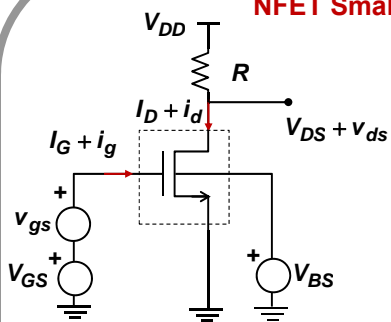


$$\begin{aligned}
 i_D &= I_D + i_d = I_D(V_{GS} + v_{gs}, V_{DS} + v_{ds}) \\
 &= I_D + \frac{\partial I_D}{\partial V_{GS}} v_{gs} + \frac{\partial I_D}{\partial V_{DS}} v_{ds} \\
 &= I_D + g_m v_{gs} + g_o v_{ds}
 \end{aligned}$$
 
$$\left. \begin{aligned}
 g_m &= \frac{\partial I_D}{\partial V_{GS}} & g_o &= \frac{\partial I_D}{\partial V_{DS}} \\
 \text{Transconductance} & & \text{Output conductance} &
 \end{aligned} \right\}$$





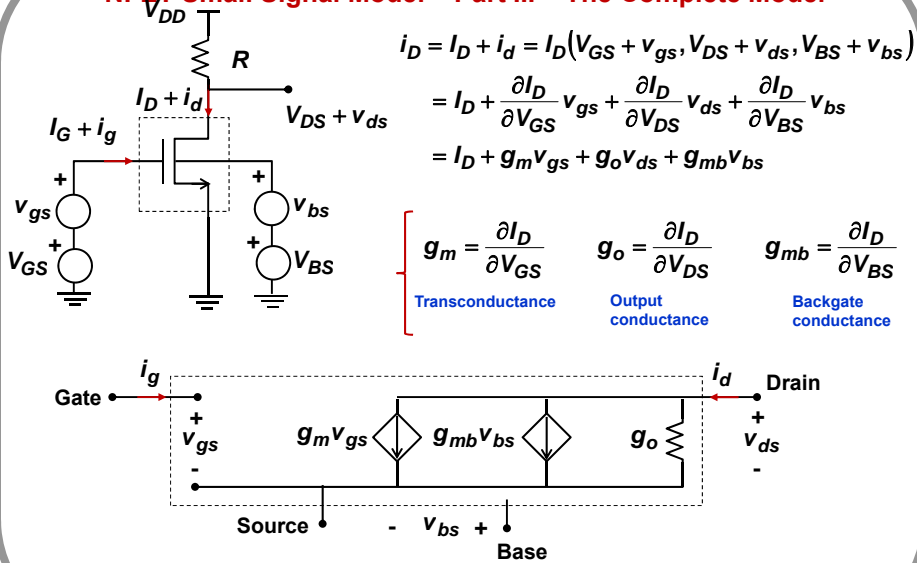
### NFET Small Signal Model – Part III – The Complete Model


 
### NFET Model

$$I_D = \begin{cases} 0 & \text{For } V_{GS} < V_{TN} \\ & \text{(Cut-off region)} \\ k_n \left[ V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right] V_{DS} (1 + \lambda_n V_{DS}) & \text{For } 0 \leq V_{DS} \leq V_{GS} - V_{TN} \\ & \text{(Linear region)} \\ \frac{k_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS}) & \text{For } 0 \leq V_{GS} - V_{TN} \leq V_{DS} \\ & \text{(Saturation region)} \end{cases}$$



$$g_m = \frac{\partial I_D}{\partial V_{GS}} \quad \text{Transconductance}$$

$$g_o = \frac{\partial I_D}{\partial V_{DS}} \quad \text{Output conductance}$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} \quad \text{Backgate conductance}$$


### NFET: Transconductance

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

Saturation:  $g_m = \frac{\partial I_D}{\partial V_{GS}} = k_n (V_{GS} - V_{TN})(1 + \lambda_n V_{DS}) = \sqrt{2k_n I_D (1 + \lambda_n V_{DS})}$

Linear:  $g_m = \frac{\partial I_D}{\partial V_{GS}} = k_n V_{DS} (1 + \lambda_n V_{DS})$

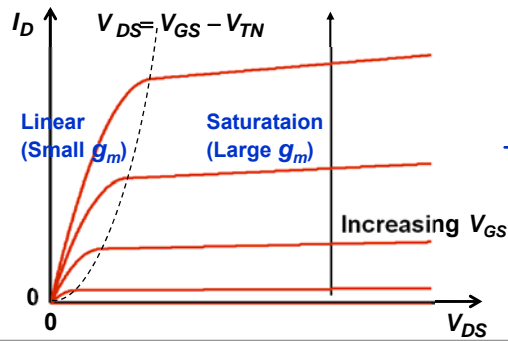Increases only as the square-root of the current



To achieve large  $g_m$  operate in the saturation region


### NFET: Transconductance

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

Saturation:  $g_m = \frac{\partial I_D}{\partial V_{GS}} = k_n (V_{GS} - V_{TN})(1 + \lambda_n V_{DS}) = \sqrt{2k_n I_D (1 + \lambda_n V_{DS})}$

Linear:  $g_m = \frac{\partial I_D}{\partial V_{GS}} = k_n V_{DS} (1 + \lambda_n V_{DS})$

 Increases only as the square-root of the current




### NFET: Output Conductance

$$g_o = \frac{\partial I_D}{\partial V_{DS}}$$

**Saturation:**  $g_o = \frac{\partial I_D}{\partial V_{DS}} = \frac{k_n}{2} (V_{GS} - V_{TN})^2 \lambda_n = \lambda_n I_D$

 **Linear:**  $g_o = \frac{\partial I_D}{\partial V_{DS}} = \lambda_n I_D + k_n (V_{GS} - V_{TN} - V_{DS})(1 + \lambda_n V_{DS})$




### NFET: Output Conductance

$$g_o = \frac{\partial I_D}{\partial V_{DS}}$$

**Saturation:**  $g_o = \frac{\partial I_D}{\partial V_{DS}} = \frac{k_n}{2} (V_{GS} - V_{TN})^2 \lambda_n = \lambda_n I_D$

 **Linear:**  $g_o = \frac{\partial I_D}{\partial V_{DS}} = \lambda_n I_D + k_n (V_{GS} - V_{TN} - V_{DS})(1 + \lambda_n V_{DS})$



### NFET: Backgate Conductance

Recall that the threshold voltage depends on the source-to-bulk voltage  $V_{SB}$ :

$$V_{TN} = V_{TN}(V_{SB} = 0) + \gamma_n (\sqrt{-2\phi_p + V_{SB}} - \sqrt{-2\phi_p})$$

$$\gamma_n = \frac{\sqrt{2 \epsilon_s q N_a}}{C_{ox}} = \text{Backgate effect (or the body effect) parameter}$$


$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = \frac{\partial I_D}{\partial V_{TN}} \frac{\partial V_{TN}}{\partial V_{BS}}$$

Saturation:  $g_{mb} = \frac{\partial I_D}{\partial V_{TN}} \frac{\partial V_{TN}}{\partial V_{BS}} = - \frac{\partial I_D}{\partial V_{GS}} \frac{\partial V_{TN}}{\partial V_{BS}} = g_m \frac{\gamma_n}{2\sqrt{-2\phi_p - V_{BS}}}$

Linear:  $g_{mb} = \frac{\partial I_D}{\partial V_{TN}} \frac{\partial V_{TN}}{\partial V_{BS}} = - \frac{\partial I_D}{\partial V_{GS}} \frac{\partial V_{TN}}{\partial V_{BS}} = g_m \frac{\gamma_n}{2\sqrt{-2\phi_p - V_{BS}}}$

### NFET Common Source (CS) Voltage Amplifier

$V_{BS} = 0$

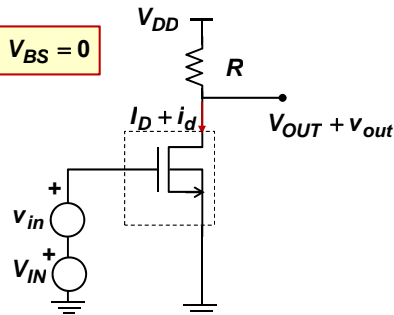


$$v_{gs} = v_{in}$$

$$i_d = g_m v_{gs} + \frac{v_{out}}{r_o} = - \frac{v_{out}}{R}$$


$$\Rightarrow v_{out} = -g_m (r_o \parallel R) v_{gs} = -g_m (r_o \parallel R) v_{in}$$

$$\Rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_m (r_o \parallel R)$$

Voltage gain

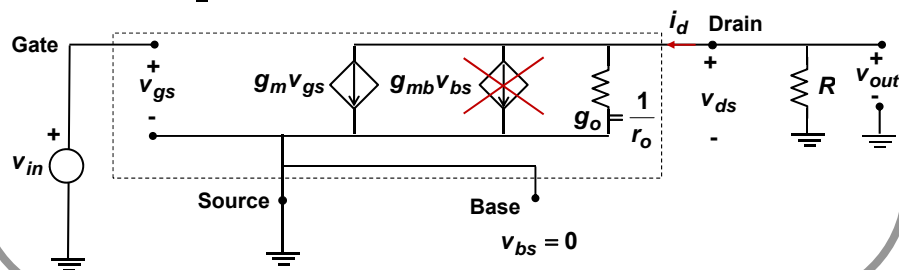
 
### NFET Common Source (CS) Voltage Amplifier



$V_{BS} = 0$

$$v_{gs} = v_{in}$$

$$i_d = g_m v_{gs} + \frac{v_{out}}{r_o} = -\frac{v_{out}}{R}$$

$$\Rightarrow v_{out} = -g_m (r_o \parallel R) v_{gs} = -g_m (r_o \parallel R) v_{in}$$

$$\Rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_m (r_o \parallel R)$$

↑  
Voltage gain

$$\frac{1}{r_o \parallel R} = \frac{1}{r_o} + \frac{1}{R}$$

$$\Rightarrow r_o \parallel R = \frac{R}{1 + g_o R}$$



$$\Rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_m (r_o \parallel R) = -g_m \frac{R}{1 + g_o R}$$

### A Note on Small Signal Modeling

When making a small signal model out of a complicated nonlinear signal remember that:

- 1) All DC voltage sources in the circuit become short circuits
- 2) All DC current sources in the circuit become open circuits
  
### NFET CS Amplifier: Limits of Output Voltage Swing





#### Minimum output voltage and maximum input voltage:

If the output voltage becomes too small (happens when the input voltage becomes too large), the FET will go into the **linear region** (in the linear region the gain is small)

#### Maximum output voltage and minimum input voltage:

If the input voltage becomes too small the FET will go into **cut-off**

### The Diode-Connected NFET

  


The gate and the drain of the FET are tied together

Since:

$$\begin{aligned} V_{DG} &= 0 \\ \Rightarrow V_{DS} &= V_{GS} \\ \Rightarrow V_{DS} &> V_{GS} - V_{TN} \end{aligned}$$

$\Rightarrow$  The FET is always operating in saturation when not in cut-off (i.e. provided  $V_{GS} > V_{TN}$ )

### The Diode-Connected NFET

 

Finding  $V_{OUT}$ :


$$I_D = \frac{k_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS})$$

$$\Rightarrow \frac{k_n}{2} (V_{OUT} - V_{TN})^2 (1 + \lambda_n V_{OUT}) = \frac{V_{DD} - V_{OUT}}{R}$$

$$\Rightarrow \frac{k_n}{2} (V_{OUT} - V_{TN})^2 \approx \frac{V_{DD} - V_{OUT}}{R}$$

The above equation can be solved for  $V_{OUT}$
 
### Including Parasitic and Overlap Capacitances




In Saturation:

$$C_{gs} = \frac{\partial Q_G}{\partial V_{GS}} \Big|_{V_{DS}, V_{SB}} = \frac{2}{3} W L C_{ox} + W C_{ov} + W C_p \neq \frac{2}{3} W L C_{ox}$$

$$C_{gd} = \frac{\partial Q_G}{\partial V_{GD}} \Big|_{V_{GS}, V_{SB}} = W C_{ov} + W C_p \neq 0$$

### PFET Voltage Amplifier and Inverter


 


We need to find the relation between the output and the input voltage

$I_D < 0$  and actual current is flowing out of the drain

- 1)  $V_{GS} = V_{IN} - V_{DD} > V_{TP}$   
The FET is in cut-off regime and  $I_D = 0$  and consequently  $V_{OUT} = 0$
- 2)  $V_{GS} = V_{IN} - V_{DD} < V_{TP}$   
The FET is turned on and  $I_D \neq 0$  and consequently  $V_{OUT} = -I_D R$
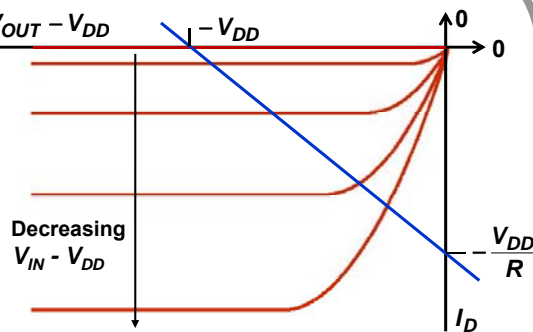 
### PFET Voltage Amplifier and Inverter: A Graphical Solution





$$I_D = -\frac{V_{OUT}}{R}$$

$$I_D = \begin{cases} 0 & \text{For } V_{IN} - V_{DD} > V_{TP} \\ -k_p \left[ V_{IN} - V_{DD} - V_{TP} - \frac{V_{OUT} - V_{DD}}{2} \right] (V_{OUT} - V_{DD}) & \text{For } 0 \geq V_{OUT} - V_{DD} \geq V_{IN} - V_{DD} - V_{TP} \\ -\frac{k_p}{2} (V_{IN} - V_{DD} - V_{TP})^2 & \text{For } 0 \geq V_{IN} - V_{DD} - V_{TP} \geq V_{OUT} - V_{DD} \end{cases}$$

$$k_p = \frac{W}{L} \mu_p C_{ox}$$


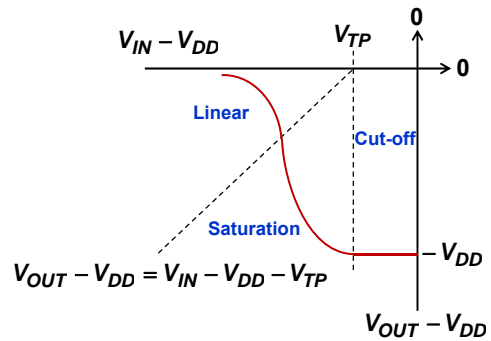 
### PFET Voltage Amplifier and Inverter: Transfer Curve





A high input voltage produces a low output voltage

A low input voltage produces a high output voltage

The device can therefore be used as a logical inverter!
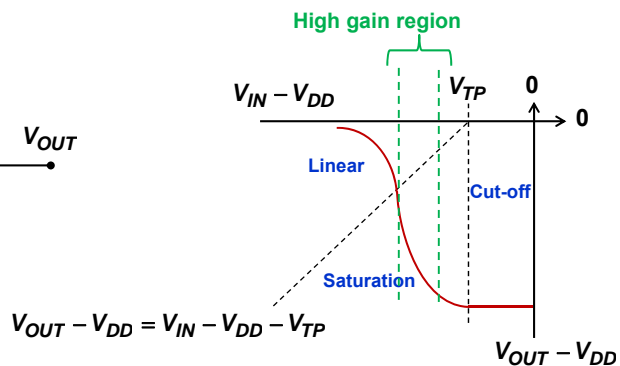 
### PFET Voltage Amplifier and Inverter: Transfer Curve




In the high gain region, the slope  $\left| \frac{dV_{OUT}}{dV_{IN}} \right|$  can be larger than unity!

This means a small change in the input voltage will produce a large change in the output voltage

The circuit can therefore be used as a voltage amplifier!
 
### PFET Common Source (CS) Voltage Amplifier



$$v_{gs} = v_{in}$$


$$i_d = g_m v_{gs} + \frac{v_{out}}{r_o} = -\frac{v_{out}}{R}$$

$$\Rightarrow v_{out} = -g_m (r_o \parallel R) v_{gs}$$

$$\Rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_m (r_o \parallel R)$$

Voltage gain

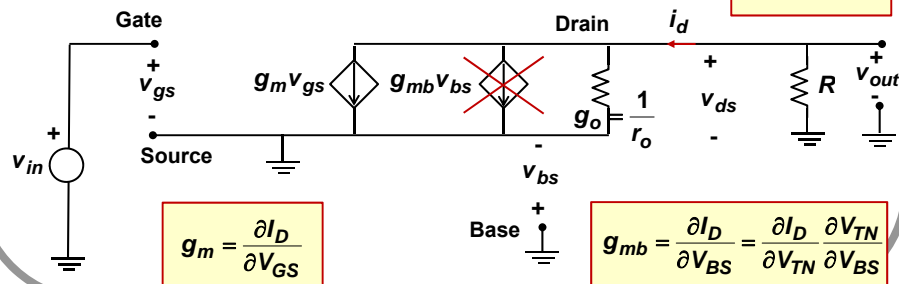
$$g_o = \frac{\partial I_D}{\partial V_{DS}}$$



$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = \frac{\partial I_D}{\partial V_{TN}} \frac{\partial V_{TN}}{\partial V_{BS}}$$

### The Standard CMOS Process

 

The NFETs and the PFETs can be realized on the same P-substrate by making a N-well inside the substrate for the PFETs

**The Double-Well CMOS Process**

