

## Lecture 13

### Biasing and Loading Single Stage FET Amplifiers

#### The Building Blocks of Analog Circuits - III


---

In this lecture you will learn:

- Current biasing of circuits
- Current sources and sinks for CS, CG, and CD circuits

 
#### A Poor Man's Current Source

What if one wanted to bias a device with a current source?



.....but one only had a voltage source?

 
**Solution:** Use a large voltage source with a large resistor in series!



Poor man's  
current source

$$I = \frac{V_{BIAS}}{R + R_D} \approx \frac{V_{BIAS}}{R}$$


### The Common Source Amplifier

 

Open circuit voltage gain:

$$A_v = \frac{v_{out}}{v_{in}} = -\frac{i_d R}{v_{in}} = -g_m (r_o \parallel R)$$
 
### The Common Source Amplifier: Problems



Open circuit voltage gain:

$$A_v = \frac{V_{out}}{v_{in}} = -g_m (r_o \parallel R)$$

In saturation:

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \sqrt{2k_n I_D (1 + \lambda_n V_{DS})}$$



To achieve large gain one needs:

- 1) A large DC current bias  $I_D$  in order to get a large  $g_m$
- 2) A large value of the resistor  $R$

Both the above requirements cannot be met easily simultaneously:

- Not easy to realize large resistors in micro-chips
- A large resistor  $R$  will limit the maximum value of the DC current bias  $I_D$  (because the potential drop  $I_D R$  can become large enough to put the FET in the linear region where  $g_m$  and the gain will be small)

### The Digital Logic Inverter: Problems

  


To achieve fast switching one needs:

- 1) A small resistor (because then the  $RC_L$  charging time will be smaller when the output switches from "0" to "1")

**But**

- A small resistor will require a very large current (to achieve a large potential drop across it) when the input is "1", and the NFET is turned on, and the output need to be low or "0" – and this means more power dissipation
- When the input is "1", and the NFET is turned on, there is constant static power dissipation
 
### The Common Source Amplifier with a Current Source



What is needed is an ideal current source in the drain that can supply a large DC current and at the same time has a large small signal resistance


The incremental (or differential or small signal) resistance looking into an ideal current source is infinite

$$A_v = \frac{v_{out}}{v_{in}} = -g_m r_o$$

An ideal current source, of course, does not exist

But one can certainly do much better than using a resistor in the drain
 
### The Common Source Amplifier with a Current Source: DC Biasing




$$I_D = I_{BIAS} = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS})$$

Suppose for  $V_{BIAS1}$  the output was  $V_{OUT1}$





Suppose  $V_{BIAS1}$  is changed to a smaller value  $V_{BIAS2}$

$$\Delta V_{BIAS} = V_{BIAS2} - V_{BIAS1} < 0$$


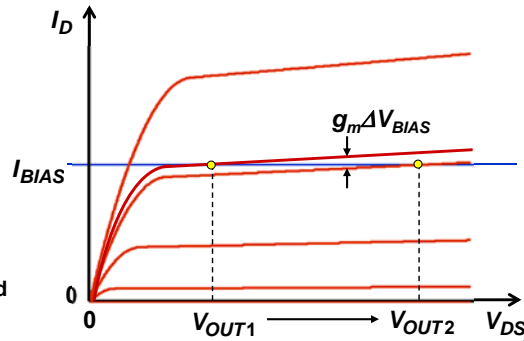
The output  $V_{OUT2}$  can be obtained graphically, as shown



    
### The Common Source Amplifier with a Current Source: DC Biasing



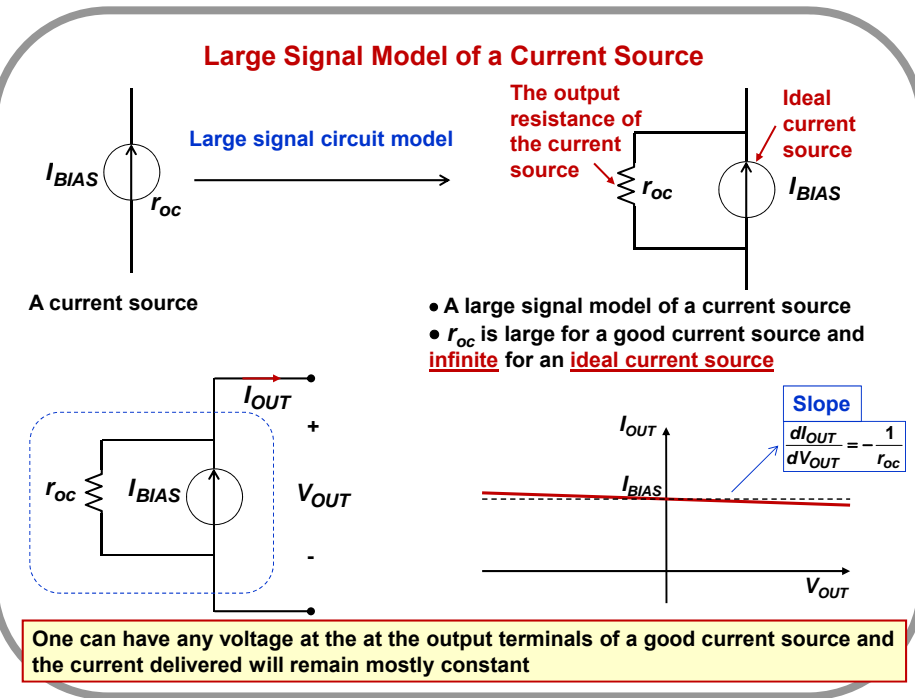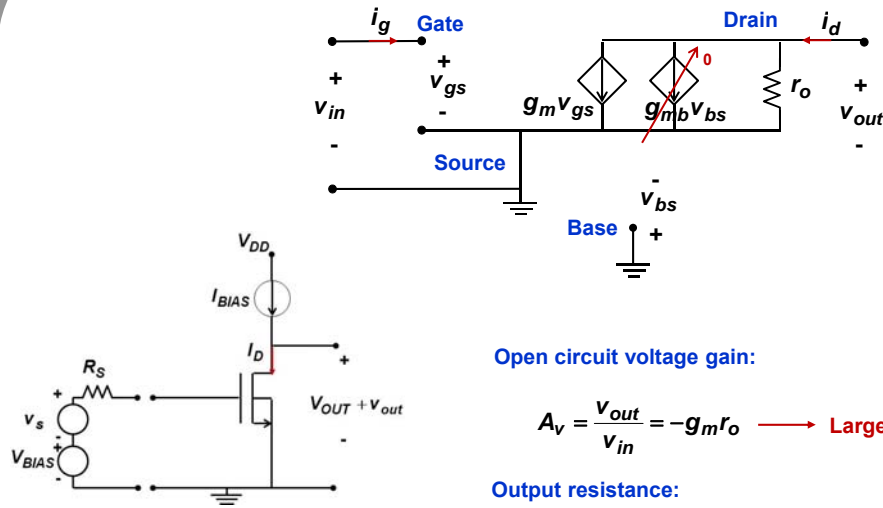
### The CS Amplifier with a Current Source: Small Signal Analysis



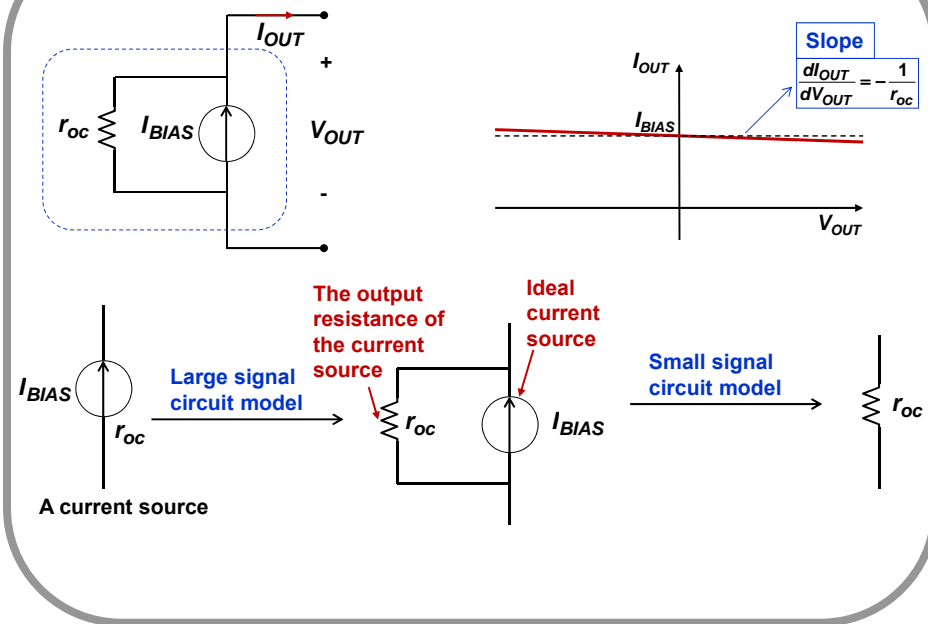
### Small Signal Model of a Current Source




### Large Signal Model of a Current Sink

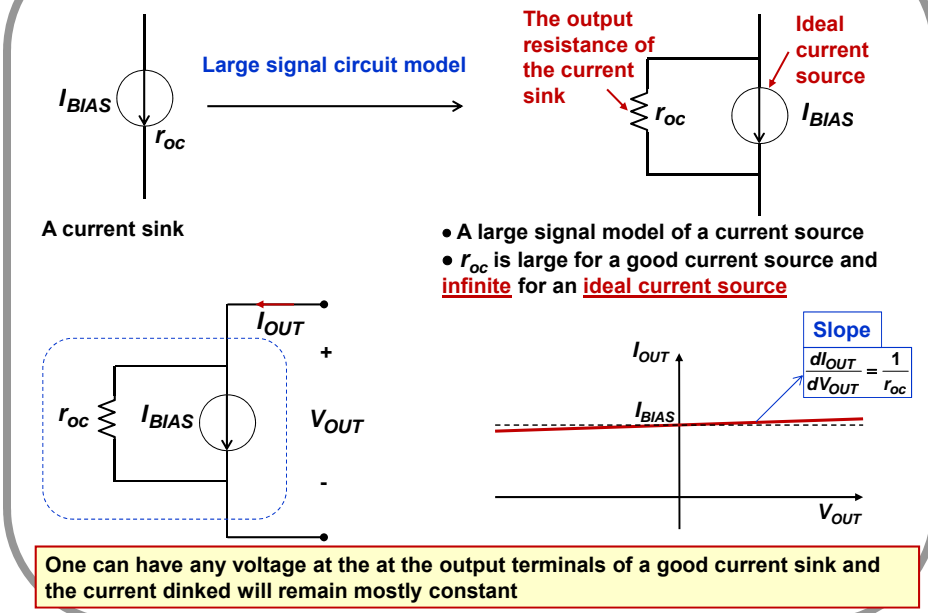

### Small Signal Model of a Current Sink

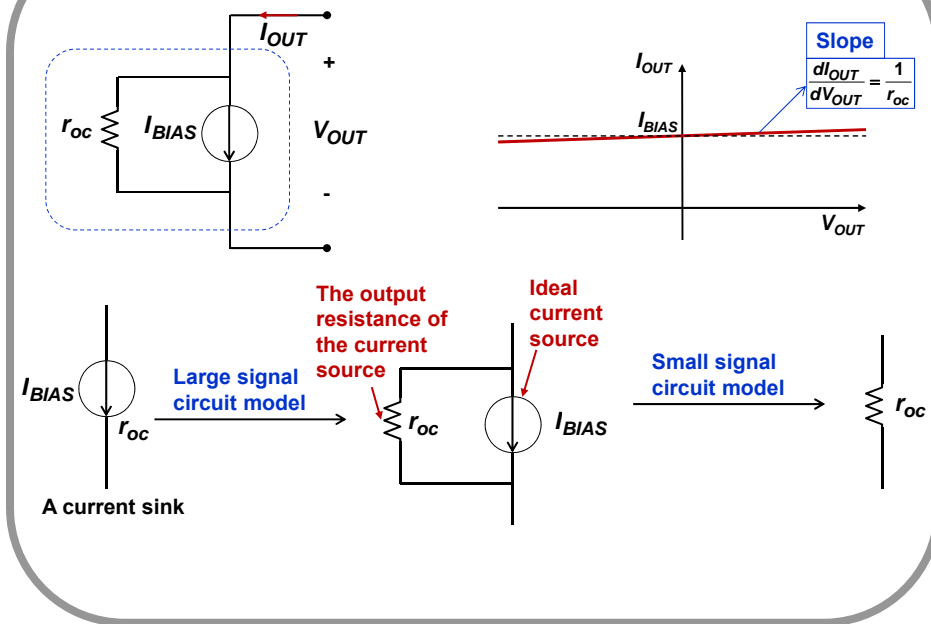

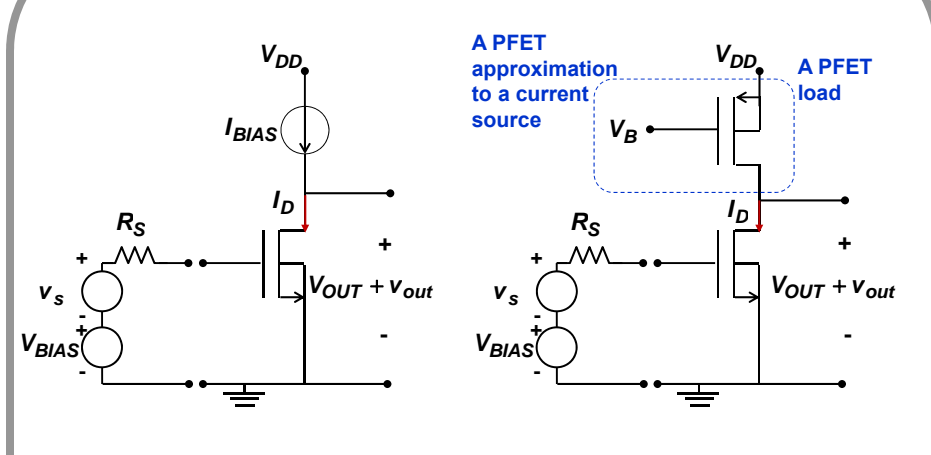
### PFET Loaded NFET Common Source Amplifier




An ideal current source, of course, does not exist  
 But one can certainly do much better than using a resistor in the drain  
**Use a PFET!**

## Current Sinks and NFET Transistors

**Current Sink:**

 

 
One can have any voltage at the at the output terminals of a good current sink and the current sinked will remain mostly constant




Characteristics in saturation resemble that of a non-ideal current source!

## Current Sources and PFET Transistors

**Current Sources:**

 

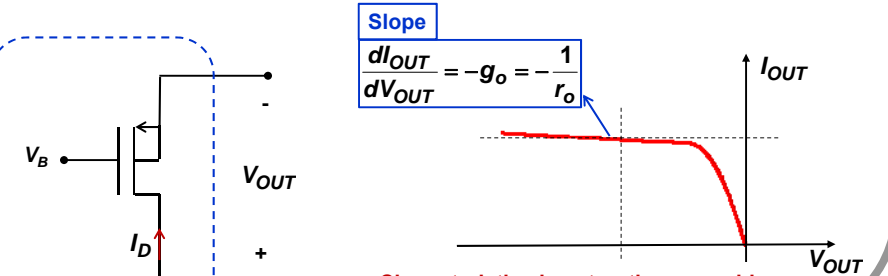
One can have any voltage at the at the output terminals of a good current source and the current delivered will remain mostly constant



Characteristics in saturation resemble that of a non-ideal current source!



 
### PFET Loaded NFET: Large Signal Analysis



$$V_{DS1} = V_{OUT}$$

$$V_{DS2} = V_{OUT} - V_{DD}$$


$$I_{D1} = I_D = -I_{D2}$$

 

Instead of the resistive load line, we now have the full  $I_D$  vs  $V_{DS}$  curves of the PFET

The biasing voltages need to be selected carefully, otherwise one of the transistors can go into the linear region!!

 
### PFET Loaded NFET: Large Signal Analysis



$$V_{DS1} = V_{OUT}$$

$$V_{DS2} = V_{OUT} - V_{DD}$$


$$I_{D1} = I_D = -I_{D2}$$

 

Instead of the resistive load line, we now have the full  $I_D$  vs  $V_{DS}$  curves of the PMOS

The biasing voltages need to be selected carefully, otherwise one of the transistors can go into the linear region!!
 
### PFET Loaded NFET: Large Signal Analysis



Assuming the biasing is correct, both the FETs are in saturation

Equate the drain current magnitudes of the two FETs

Then the only unknown will be  $V_{OUT}$ ; solve for it

Verify that the obtained value of  $V_{OUT}$  does indeed result in both the transistors being in saturation

**NFET**

$$I_{D1} = \frac{k_n}{2} (V_{GS1} - V_{TN})^2 (1 + \lambda_n V_{DS1}) = \frac{k_n}{2} (V_{BIAS} - V_{TN})^2 (1 + \lambda_n V_{OUT})$$

**PFET**


$$I_{D2} = -\frac{k_p}{2} (V_{GS2} - V_{TP})^2 (1 - \lambda_p V_{DS2}) = -\frac{k_p}{2} (V_B - V_{DD} - V_{TP})^2 (1 - \lambda_p (V_{OUT} - V_{DD}))$$

Equating:

$$I_{D1} = I_D = -I_{D2}$$

$$\Rightarrow \frac{k_n}{2} (V_{BIAS} - V_{TN})^2 (1 + \lambda_n V_{OUT}) = \frac{k_p}{2} (V_B - V_{DD} - V_{TP})^2 (1 + \lambda_p (V_{DD} - V_{OUT}))$$

### PFET Loaded NFET: Transfer Curve


 


**I:**  $V_{IN} < V_{TN}$   
M1 cut-off


**II:**  $V_{IN} > V_{TN}$  &  $V_{OUT} > V_{IN} - V_{TN}$  &  $V_{OUT} > V_B - V_{TP}$   
M1 saturation, M2 Linear

**III:**  $V_{IN} > V_{TN}$  &  $V_{OUT} > V_{IN} - V_{TN}$  &  $V_{OUT} < V_B - V_{TP}$   
M1 saturation, M2 saturation

  
**IV:**  $V_{IN} > V_{TN}$  &  $V_{OUT} < V_{IN} - V_{TN}$  &  $V_{OUT} < V_B - V_{TP}$   
M1 linear, M2 saturation



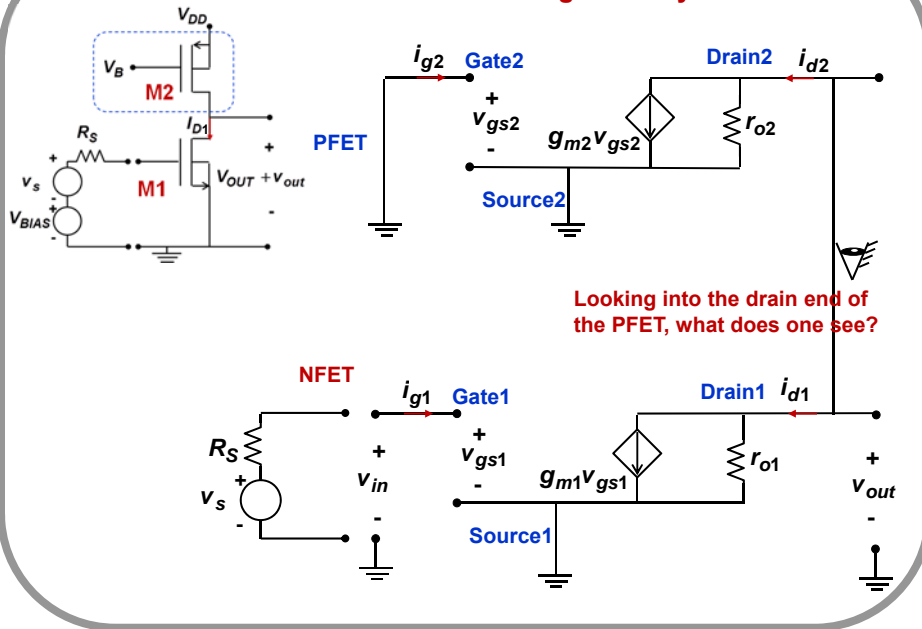
### PFET Loaded NFET: Small Signal Analysis


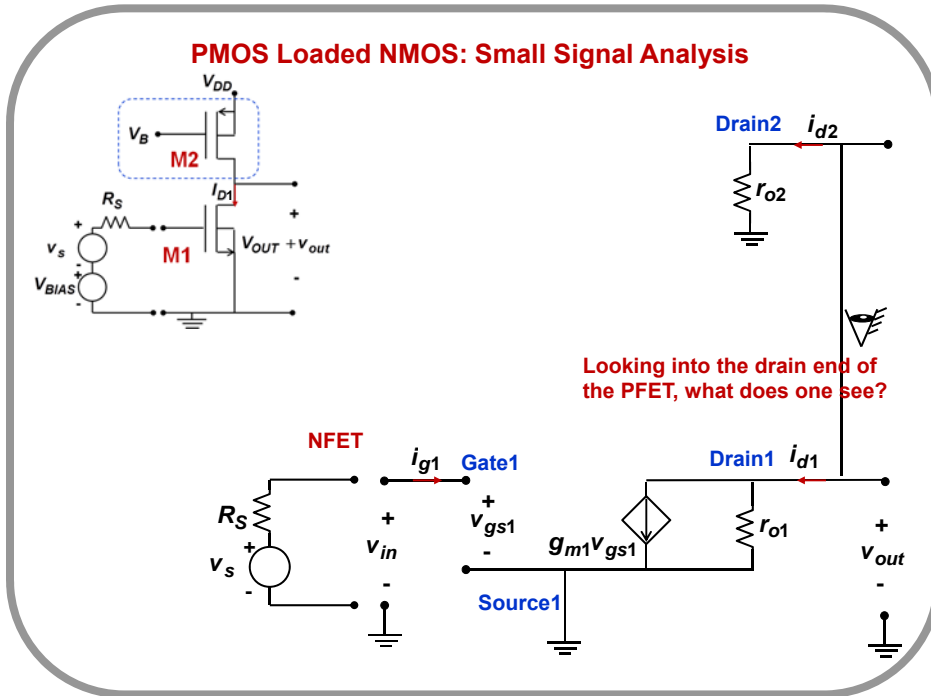
### PMOS Loaded NMOS: Small Signal Analysis


 
### PFET Loaded NFET: Small Signal Analysis




Open circuit voltage gain:

$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1}(r_{o1} \parallel r_{o2})$$

Output resistance:

$$R_{out} = r_{o1} \parallel r_{o2}$$

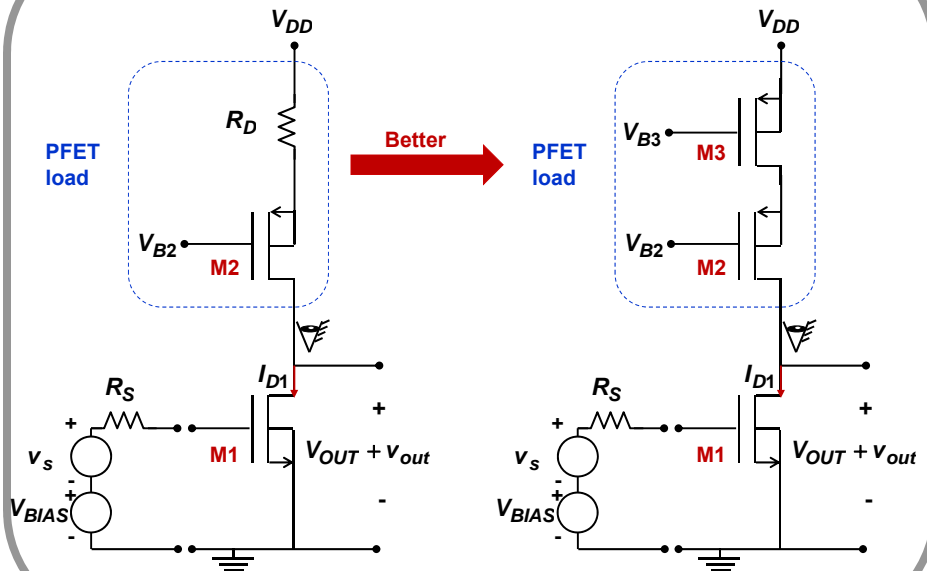
### PFET Loaded NFET: The Cascode PFET Load




This load has a larger resistance looking into it

This topology is called the "Cascode" current load

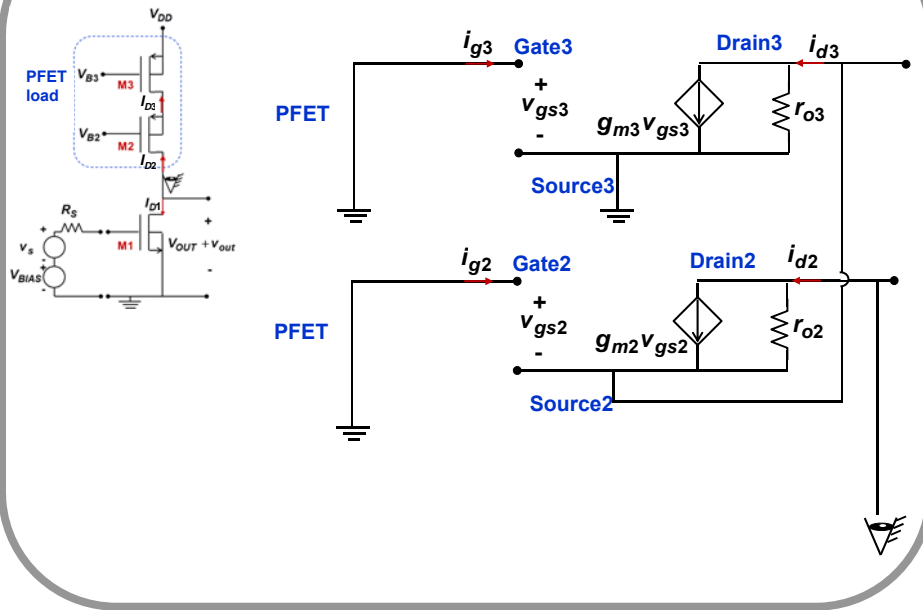
### Cascode PFET Load: Small Signal Analysis


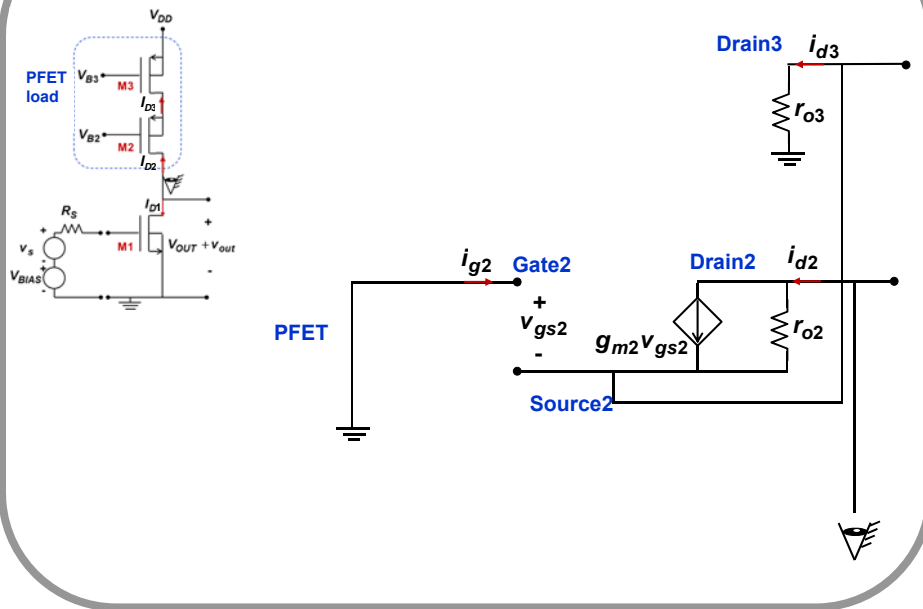
### Cascode PFET Load: Small Signal Analysis


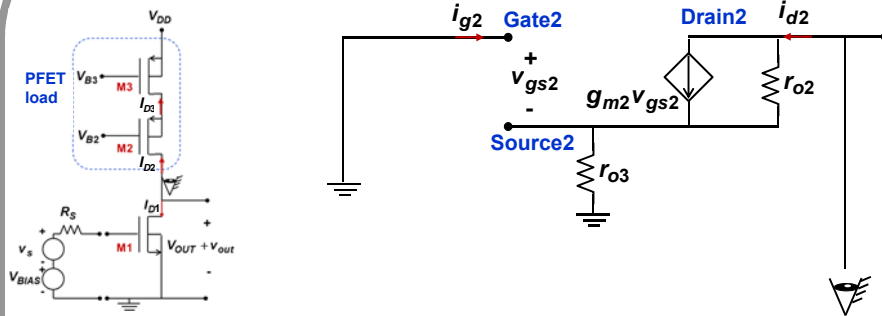
### Cascode PFET Load: Small Signal Analysis




Resistance looking into the current source is:

$$r_{o2} + r_{o3} + g_{m2}r_{o2}r_{o3} = r_{o2} + r_{o3}(1 + g_{m2}r_{o2}) \approx g_{m2}r_{o2}r_{o3}$$

Typically a good approximation
 
### Cascode PFET Load: Small Signal Analysis




Resistance looking into the current source is:

$$r_{o2} + r_{o3} + g_{m2}r_{o2}r_{o3} = r_{o2} + r_{o3}(1 + g_{m2}r_{o2}) \approx g_{m2}r_{o2}r_{o3}$$

Typically a good approximation
 
### Cascode PFET Load: Small Signal Analysis



Open circuit voltage gain:

$$A_v = \frac{V_{out}}{V_{in}} = -g_{m1}(r_{o1} \parallel (g_{m2}r_{o2}r_{o3})) \approx -g_{m1}r_{o1}$$


Typically a good approximation

Output resistance:

$$R_{out} = r_{o1} \parallel (g_{m2}r_{o2}r_{o3}) \approx r_{o1}$$

Typically a good approximation

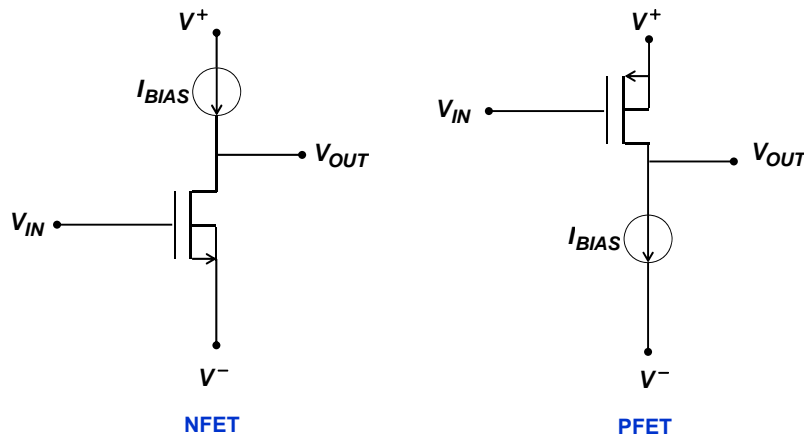
### The Common Source Amplifier: General Topology



$V^+$  is the most positive voltage in the circuit  
 $V^-$  is the most negative voltage in the circuit


- Large input resistance
- Large output resistance
- Large voltage gain
- Large current gain
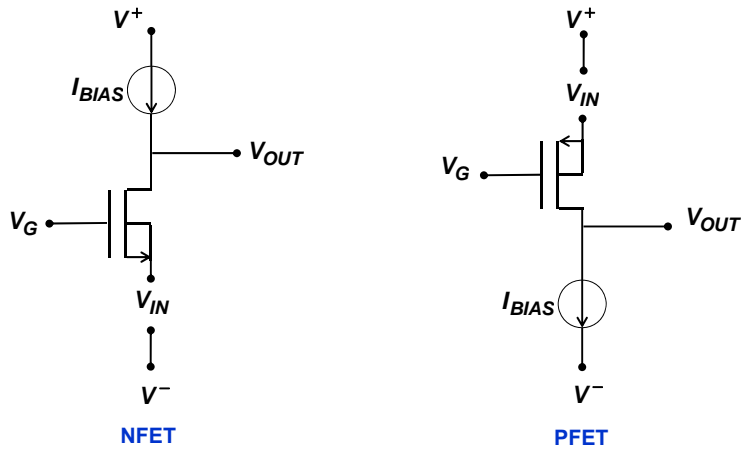
### The Common Gate Amplifier: General Topology



- Can have small input resistance
- Large output resistance
- Large voltage gain
- Small (unity) current gain
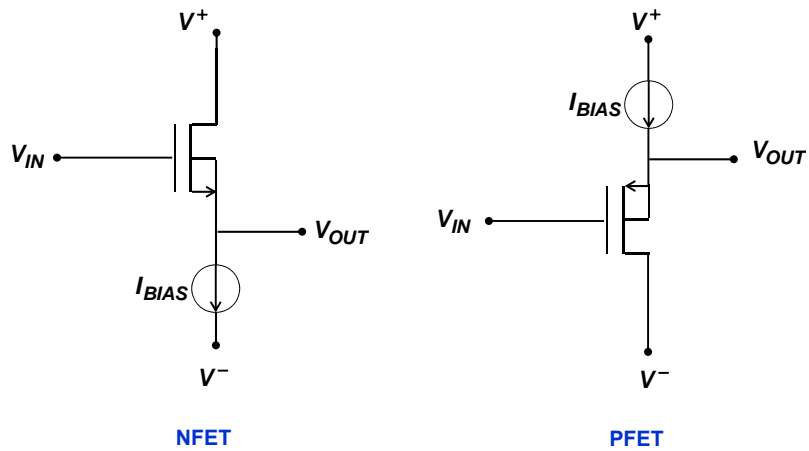
### The Common Drain Amplifier: General Topology



- Large input resistance
- Small output resistance
- Small (less than unity) voltage gain



## Chip-Based Current Sources and Voltage Sources

We have realized a decent load but .....

How does one generate voltage levels on a chip for biasing??

Current and voltage biasing of circuits require transistor based current and voltage sources on a chip!

What are the good figures of merit of chip-based voltage and current sources?

