

Lecture 17

Differential Amplifiers – II Current Mirror Load and Single-Ended Output

In this lecture you will learn:

- Differential Amplifiers
- Use of Current Mirrors in Differential Amplifiers
- Small Signal and Large Signal Models with Current Mirrors

Differential Amplifier: Review

Difference-Mode Gain:


$$A_{vd} = \frac{V_{od}}{V_{id}} = -g_{m1}(r_{o1} \parallel R)$$

Common-Mode Gain:


$$A_{vc} = \frac{V_{oc}}{V_{ic}} = -\frac{g_{m1}(r_{o1} \parallel R)}{1 + \frac{2r_{oc}}{r_{o1} + R} [1 + (g_{m1} + g_{mb1})r_{o1}]}$$

Common-Mode Rejection Ratio (CMRR):

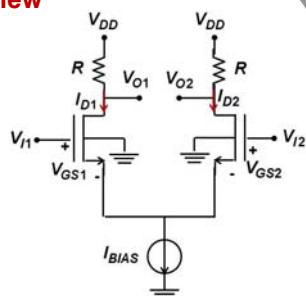
$$CMRR = \frac{A_{vd}}{A_{vc}} = 1 + \frac{2r_{oc}}{r_{o1} + R} [1 + (g_{m1} + g_{mb1})r_{o1}] \sim g_{m1} (2r_{oc}) \longrightarrow \text{Large if } r_{oc} \text{ is large}$$




Differential Amplifier: Review

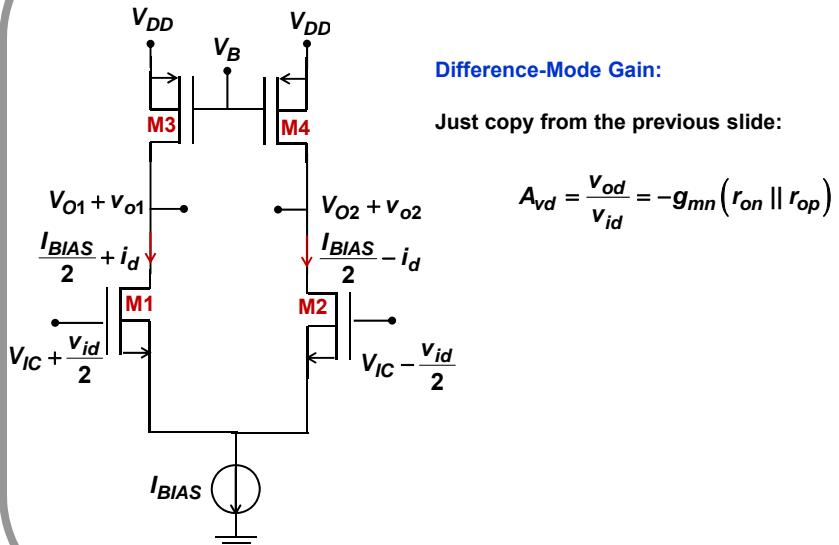

FET CS Amplifier Operation: Review

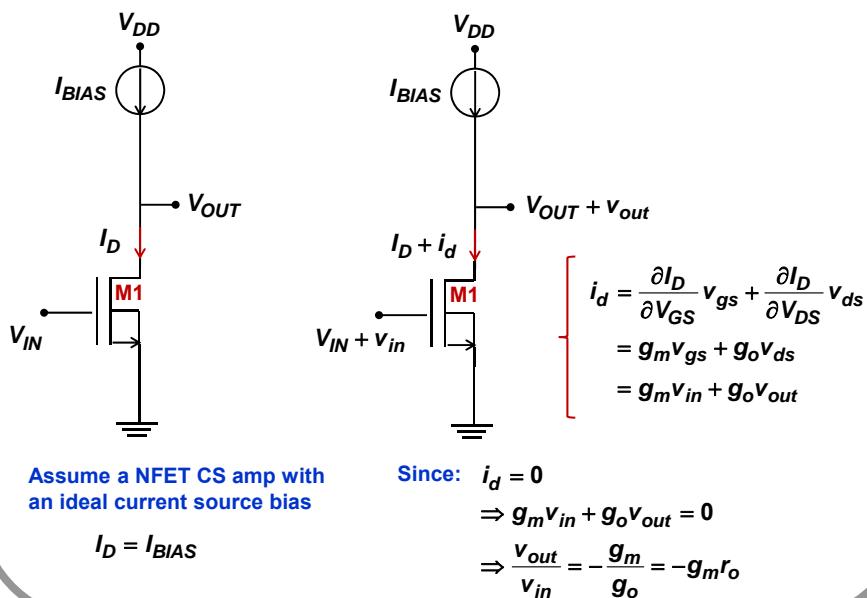


Differential Amplifier: Review

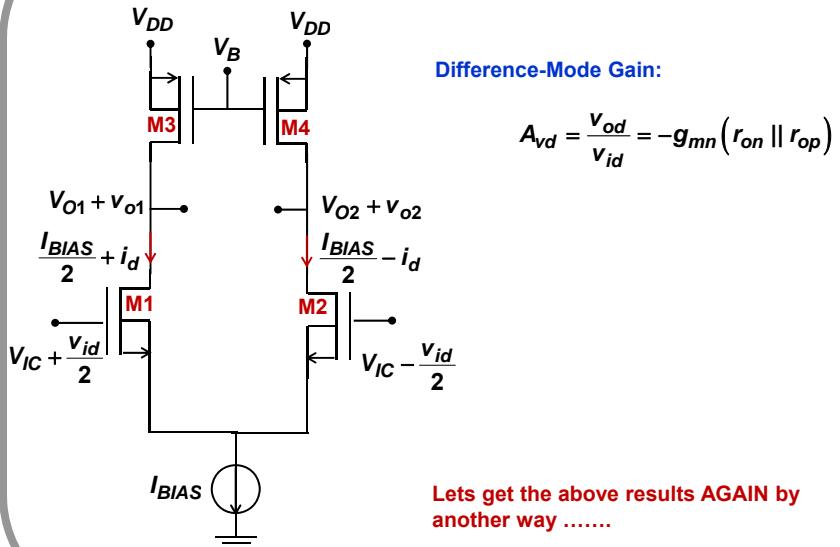

Difference-Mode Gain:

$$A_{vd} = \frac{V_{od}}{V_{id}} = -g_{mn} (r_{on} \parallel r_{op})$$

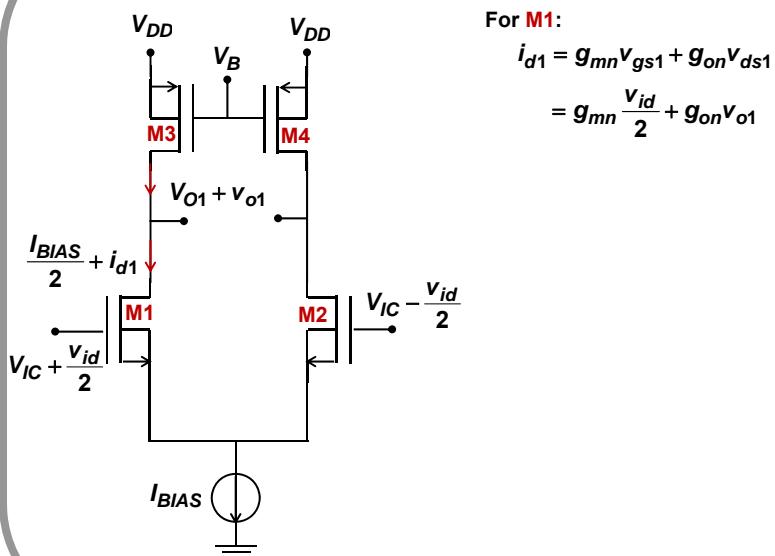Differential Amplifier: Double-Ended Output




For M1:

$$i_{d1} = g_{mn}v_{gs1} + g_{on}v_{ds1}$$

$$= g_{mn} \frac{v_{id}}{2} + g_{on}v_{o1}$$

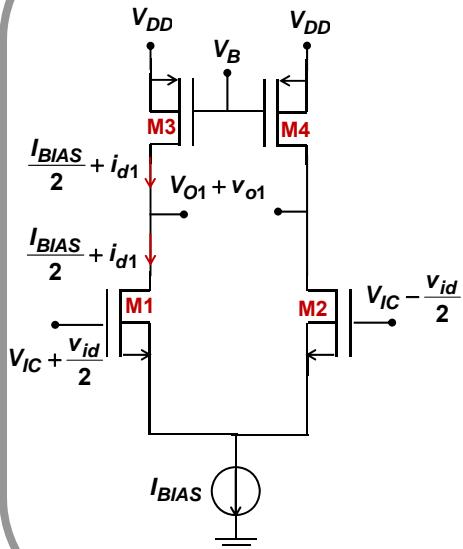Differential Amplifier: Double-Ended Output



For M1:

$$i_{d1} = g_{mn}v_{gs1} + g_{on}v_{ds1} \\ = g_{mn} \frac{v_{id}}{2} + g_{on}v_{o1}$$


For M3:

$$i_{d1} = -i_{d3} \\ = - (g_{mp}v_{gs3} + g_{op}v_{ds3}) \\ = - (g_{mp}0 + g_{op}v_{o1})$$

Equating:

$$\Rightarrow g_{mn} \frac{v_{id}}{2} + g_{on}v_{o1} = -g_{op}v_{o1} \\ \Rightarrow v_{o1} = -\left(\frac{v_{id}}{2}\right) \frac{g_{mn}}{g_{on} + g_{op}} \\ = -\left(\frac{v_{id}}{2}\right) g_{mn} (r_{on} \parallel r_{op})$$

Differential Amplifier: Review

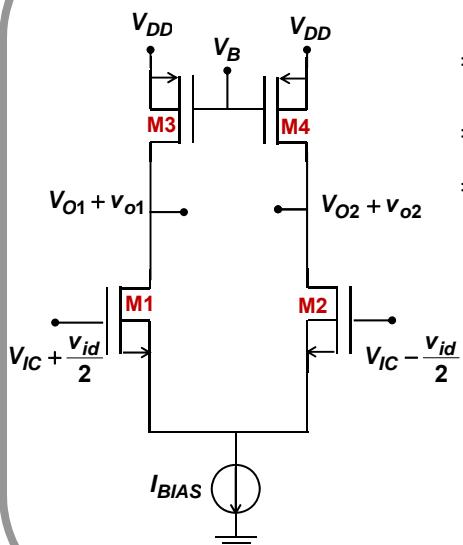

$$\Rightarrow v_{o1} = -\left(\frac{v_{id}}{2}\right) g_{mn} (r_{on} \parallel r_{op})$$


$$\Rightarrow v_{o2} = -v_{o1} = \left(\frac{v_{id}}{2}\right) g_{mn} (r_{on} \parallel r_{op})$$

$$\Rightarrow v_{od} = v_{o1} - v_{o2} \\ = -(v_{id}) g_{mn} (r_{on} \parallel r_{op})$$


Difference-Mode Gain:

$$A_{vd} = \frac{v_{od}}{v_{id}} = -g_{mn} (r_{on} \parallel r_{op})$$

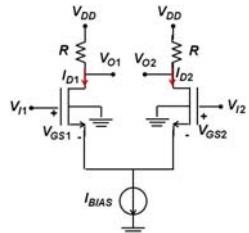Differential Amplifier: Double-Ended Output



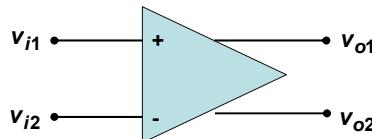The FET differential amplifiers considered had a double-ended output



$$v_{o1} = \frac{A_{vd}}{2} (v_{i1} - v_{i2}) + A_{vc} \left(\frac{v_{i1} + v_{i2}}{2} \right)$$

$$= A_{vd} \frac{v_{id}}{2} + A_{vc} v_{ic}$$

$$v_{o2} = -\frac{A_{vd}}{2} (v_{i1} - v_{i2}) + A_{vc} \left(\frac{v_{i1} + v_{i2}}{2} \right)$$

$$= -A_{vd} \frac{v_{id}}{2} + A_{vc} v_{ic}$$

Difference-Mode Output:


$$v_{od} = v_{o1} - v_{o2} = A_{vd} v_{id}$$

Common-Mode Output:

$$v_{oc} = \frac{v_{o1} + v_{o2}}{2} = A_{vc} v_{ic}$$

Differential Amplifier: Conversion to Single-Ended Output

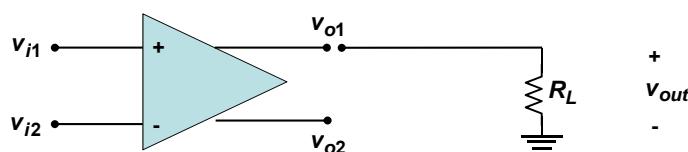
Suppose one tries to connect a load to one of the outputs:



$$v_{out} = v_{o1} = A_{vd} \frac{v_{id}}{2} + A_{vc} v_{ic} \approx A_{vd} \frac{v_{id}}{2} \longrightarrow \text{We have lost half of the voltage}$$

We can do better.....


Try another scheme:

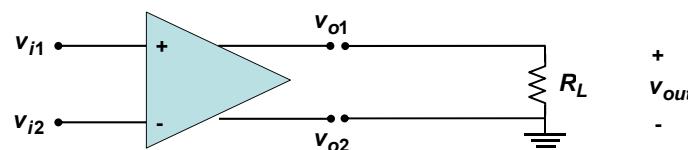


$$v_{out} = v_{od} = v_{o1} - v_{o2} = A_{vd} v_{id}$$

We have recovered the full signal but this scheme is not always practical


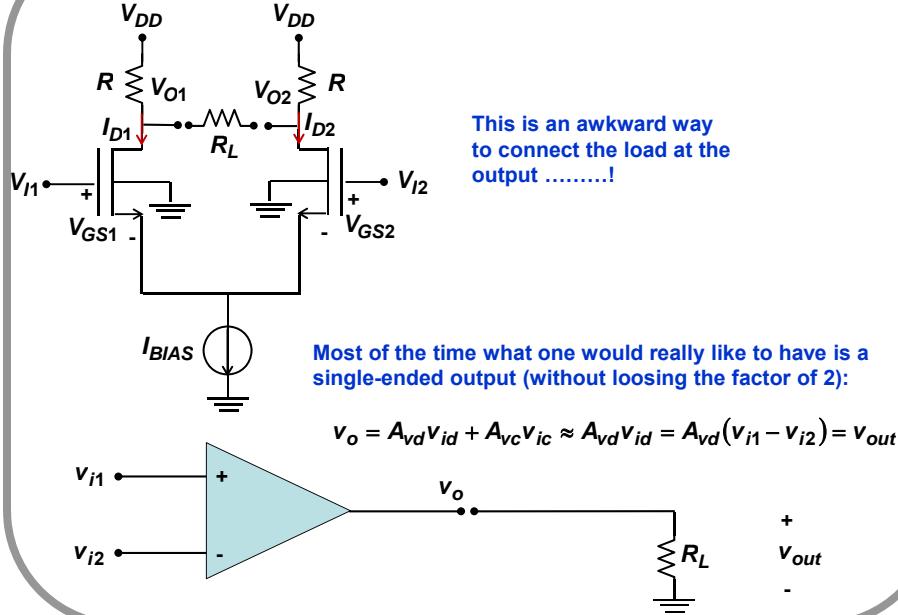
Differential Amplifier: Conversion to Single-Ended Output



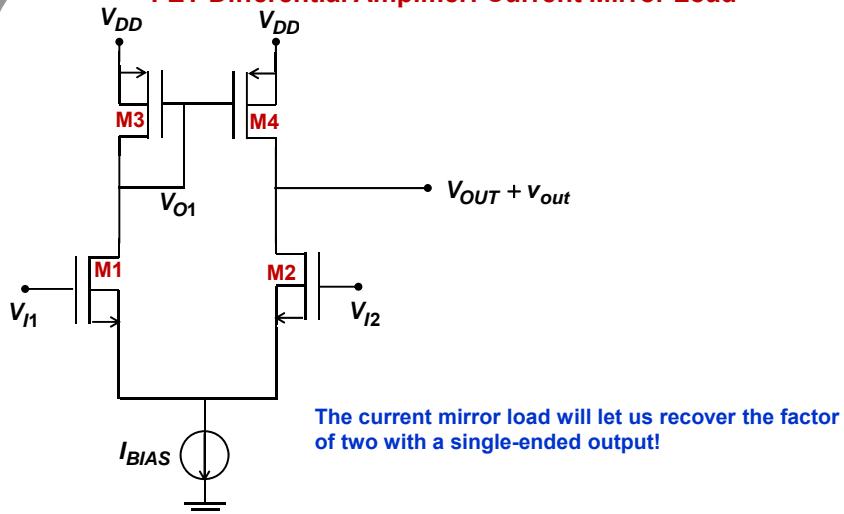
FET Differential Amplifier: Current Mirror Load



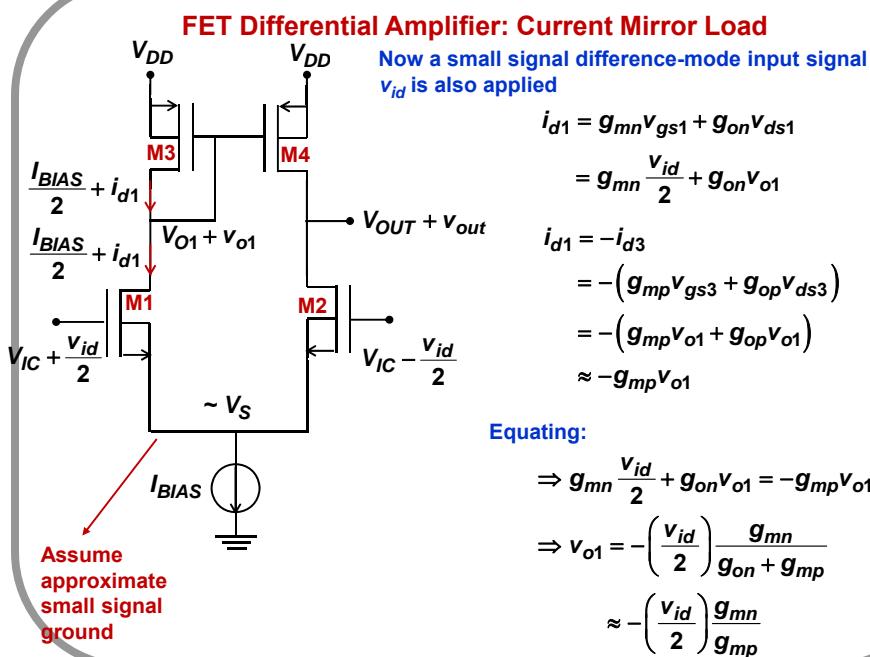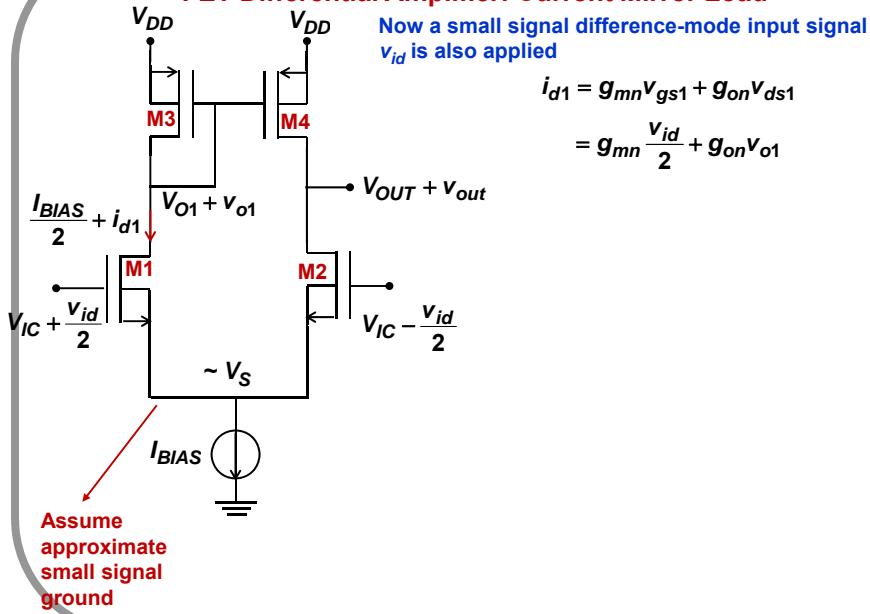FET Differential Amplifier: Current Mirror Load



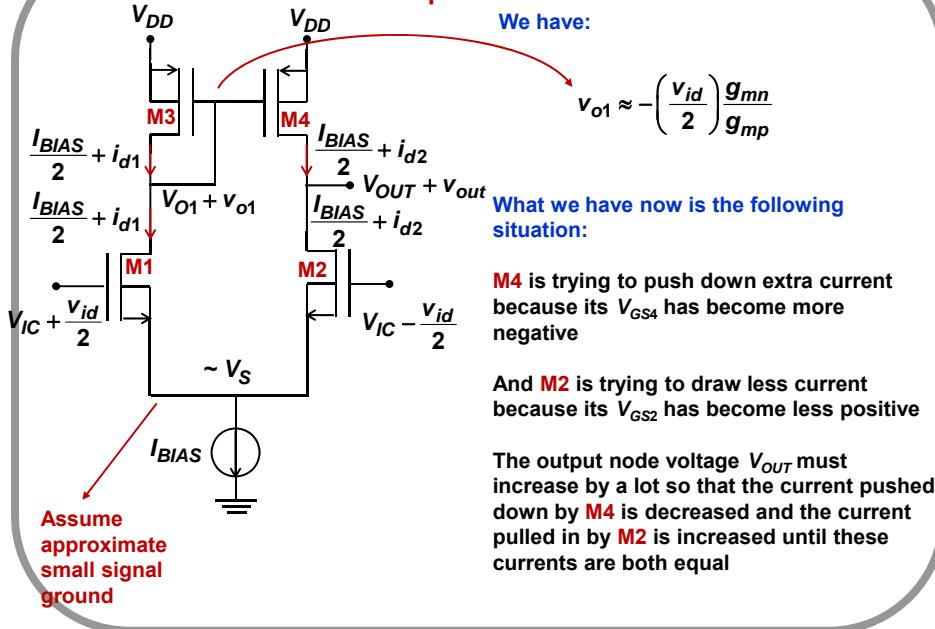FET Differential Amplifier: Current Mirror Load



FET Differential Amplifier: Current Mirror Load

So far we have:

$$v_{o1} \approx -\left(\frac{v_{id}}{2}\right) \frac{g_{mn}}{g_{mp}}$$

Let's look at the right arm now:

$$\begin{aligned} i_{d2} &= g_{mn}v_{gs2} + g_{on}v_{ds2} \\ &= -g_{mn}\frac{v_{id}}{2} + g_{on}v_{out} \end{aligned}$$

$$\begin{aligned} i_{d2} &= -i_{d4} \\ &= -(g_{mp}v_{gs4} + g_{op}v_{ds4}) \\ &= -(g_{mp}v_{o1} + g_{op}v_{out}) \end{aligned}$$

Equating:


$$-g_{mn}\frac{v_{id}}{2} + g_{on}v_{out} = -g_{mp}v_{o1} - g_{op}v_{out}$$

$$\Rightarrow -g_{mn}\frac{v_{id}}{2} + g_{on}v_{out} = g_{mn}\frac{v_{id}}{2} - g_{op}v_{out}$$


$$\Rightarrow A_{vd} = \frac{v_{out}}{v_{id}} = \frac{g_{mn}}{g_{on} + g_{op}} = g_{mn}(r_{on} \parallel r_{op})$$

Assume approximate small signal ground

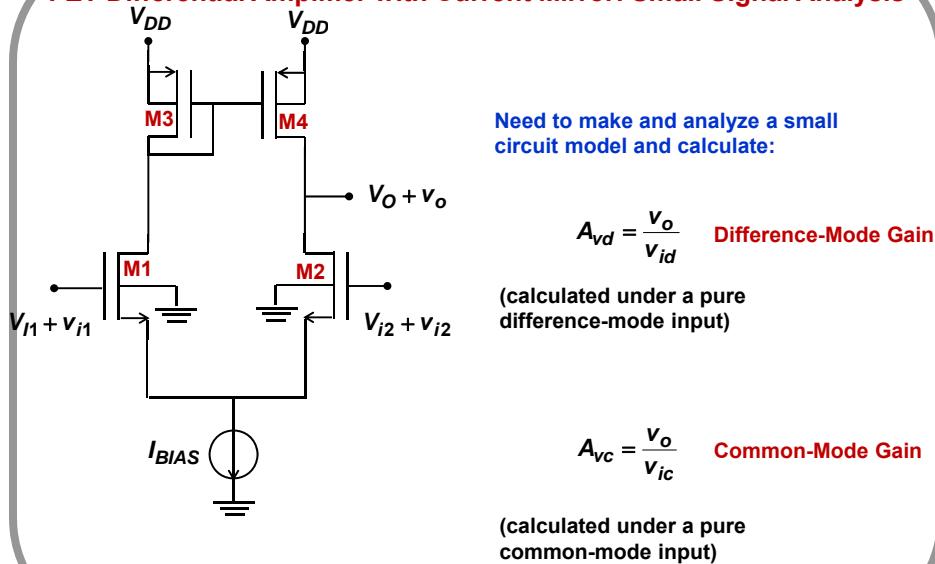
FET Differential Amplifier with Current Mirror: Small Signal Analysis



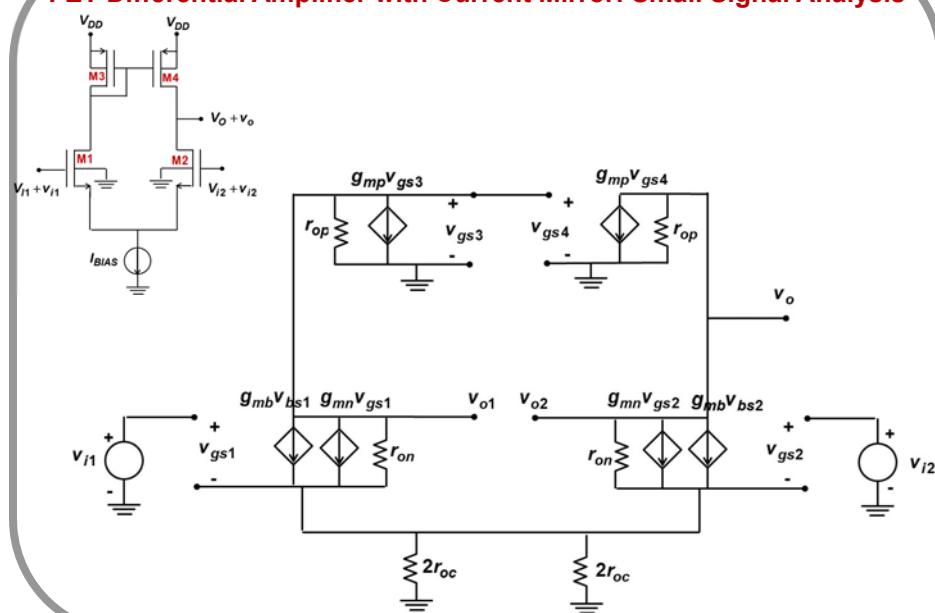
FET Differential Amplifier with Current Mirror: Small Signal Analysis



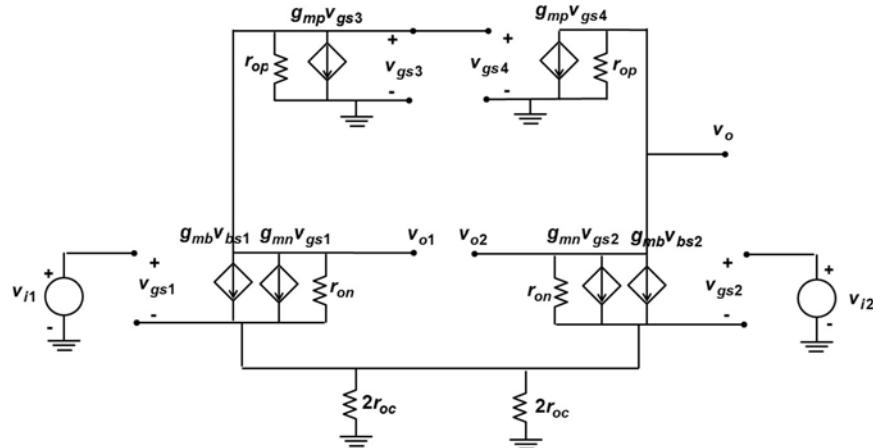FET Differential Amplifier with Current Mirror: Small Signal Analysis



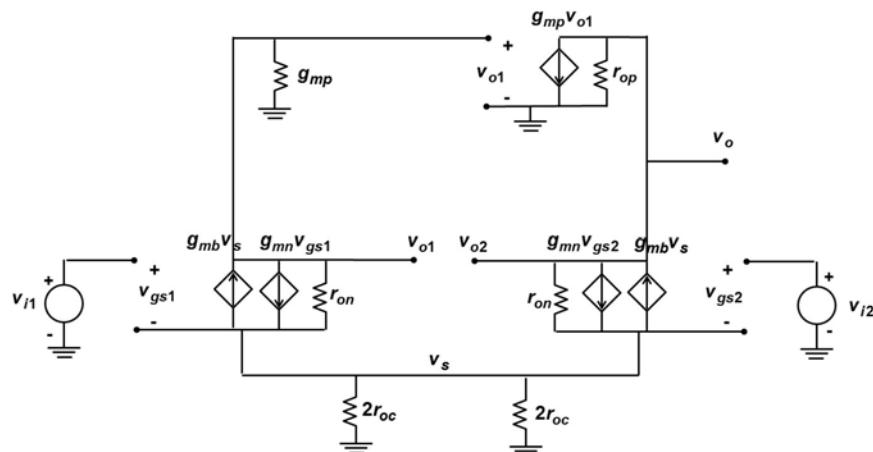
FET Differential Amplifier with Current Mirror: Small Signal Analysis



Small signal circuit model

Note the lack of symmetry!!

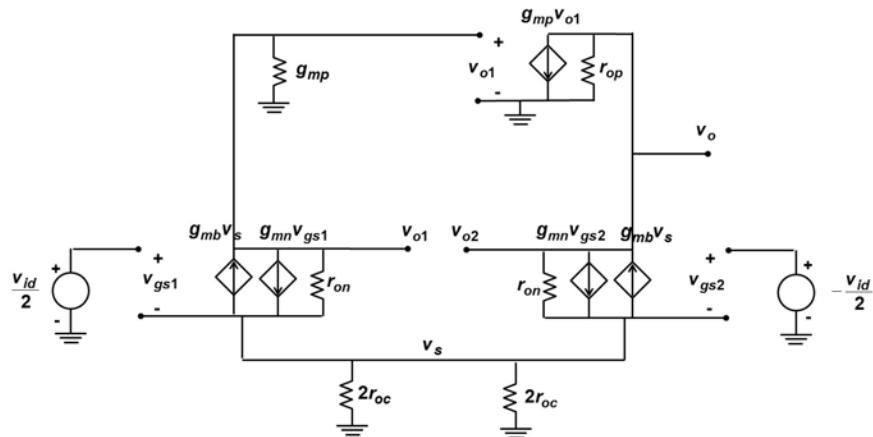Small Signal Analysis: Difference-Mode Input




There are three unknown internal voltage variables: v_{o1} v_{o2} v_s

We therefore need three equations


Try KCL at three different nodes.....

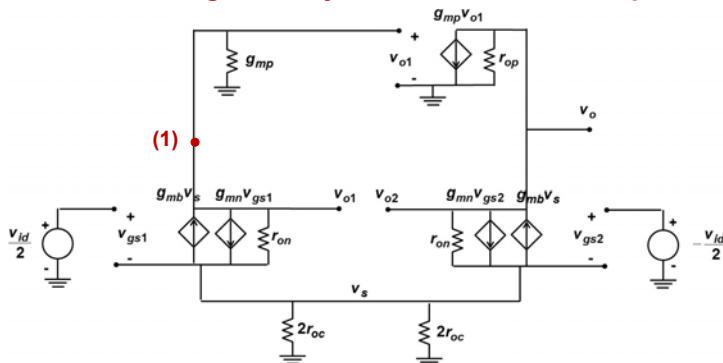Small Signal Analysis: Difference-Mode Input



$$\begin{aligned}
 (1) \quad & g_{mn} \left(\frac{v_{id}}{2} - v_s \right) + g_{on} (v_{o1} - v_s) - g_{mb} v_s + g_{mp} v_{o1} = 0 \\
 \Rightarrow & g_{mn} \left(\frac{v_{id}}{2} - v_s \right) - (g_{on} + g_{mb}) v_s + \cancel{(g_{on} + g_{mp})}^{\text{small}} v_{o1} = 0 \\
 \Rightarrow & g_{mn} \left(\frac{v_{id}}{2} - v_s \right) - (g_{on} + g_{mb}) v_s + g_{mp} v_{o1} = 0
 \end{aligned}$$

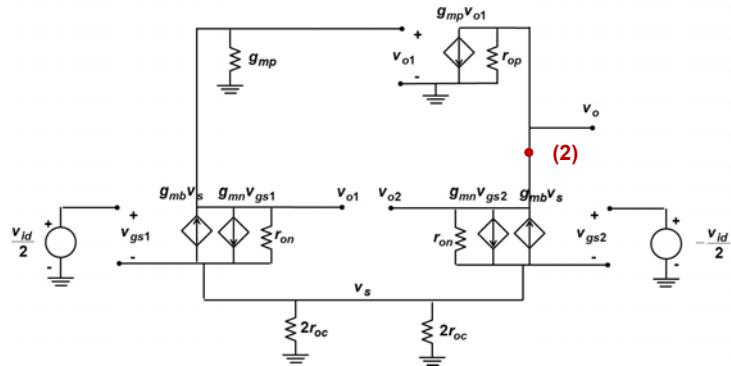
Small Signal Analysis: Difference-Mode Input



$$(2) \quad g_{mn} \left(-\frac{v_{id}}{2} - v_s \right) + g_{on} (v_{o2} - v_s) - g_{mb} v_s + g_{mp} v_{o1} + g_{op} v_{o2} = 0$$

$$\Rightarrow g_{mn} \left(-\frac{v_{id}}{2} - v_s \right) + (g_{on} + g_{op}) v_{o2} - (g_{on} + g_{mb}) v_s + g_{mp} v_{o1} = 0$$

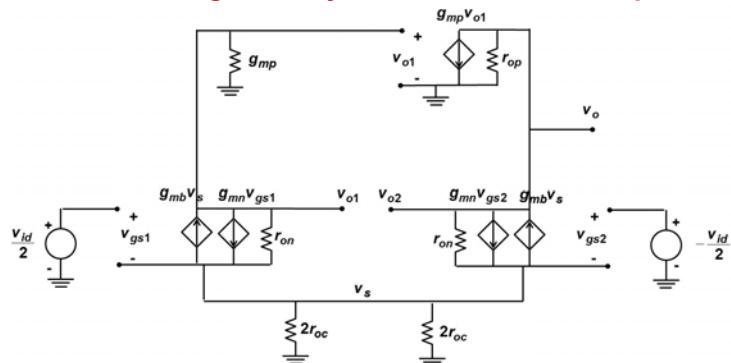Small Signal Analysis: Difference-Mode Input




Now subtract (2) from (1):

$$\Rightarrow g_{mn} v_{id} - (g_{on} + g_{op}) v_{o2} = 0$$

$$\Rightarrow v_o = v_{o2} = \frac{g_{mn}}{g_{on} + g_{op}} v_{id} = g_{mn} (r_{on} \parallel r_{op}) v_{id}$$

$$\Rightarrow A_{vd} = \frac{v_o}{v_{id}} \approx g_{mn} (r_{on} \parallel r_{op})$$

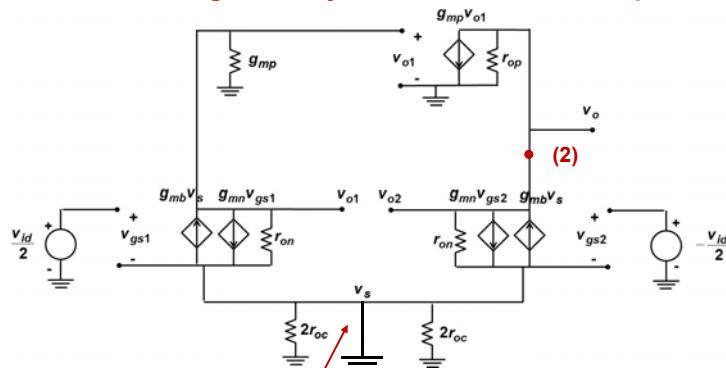Small Signal Analysis: Difference-Mode Input




One can also get the correct results by assuming a-priori that the in the difference-mode the voltage v_s is approximately zero (i.e. the node is a small signal ground)

If v_s is assumed to be approximately zero then:

$$v_{o1} \approx -\frac{g_{mn} v_{id}}{g_{mp}} \quad \rightarrow \quad v_o = v_{o2} \approx \frac{\left(-g_{mp} v_{o1} + g_{mn} \frac{v_{id}}{2} \right)}{(g_{on} + g_{op})} = \frac{g_{mn} v_{id}}{(g_{on} + g_{op})} = g_{mn} (r_{on} \parallel r_{op}) v_{id}$$


Small Signal Analysis: Common-Mode Input

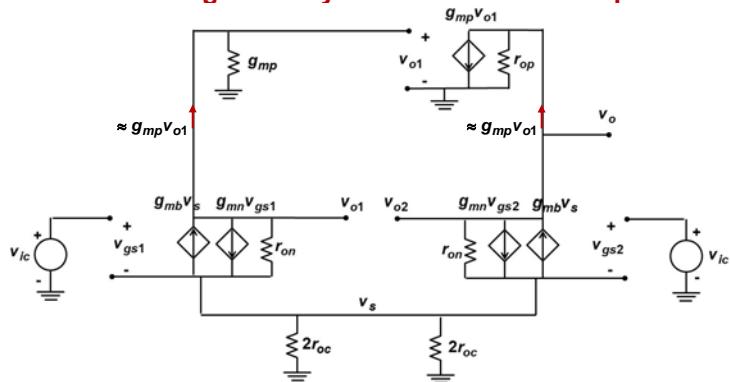

One good way to think about the amplifier in common-mode operation:

If the output resistance of M4 is assumed to be very large, then the current mirror, as the name suggests will ensure that the drain currents of M1 and M2 are identical (both equal to $-g_{mp} v_{o1}$) – as you can see above as well.

Small Signal Analysis: Common-Mode Input

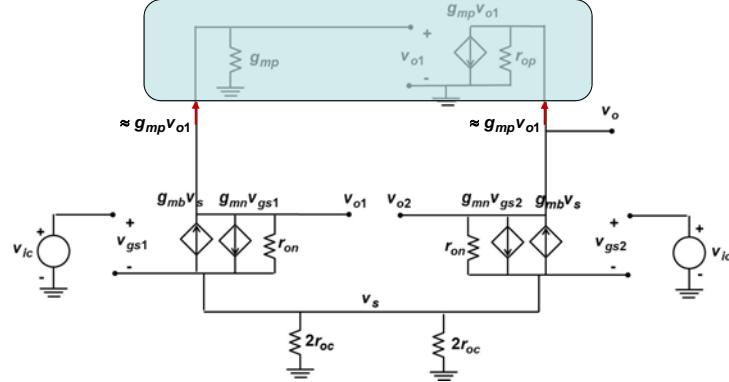


One good way to think about the amplifier in common-mode operation:

If the output resistance of M4 is assumed to be very large, then the current mirror, as the name suggests will ensure that the drain currents of M1 and M2 are identical (both equal to $-g_{mp}v_{o1}$) – as you can see above as well.


Since the input voltages, v_{ic} , on the two sides are also the same, the circuit (at least the bottom portion) has complete left-right symmetry in common-mode operation

Small Signal Analysis: Common-Mode Input

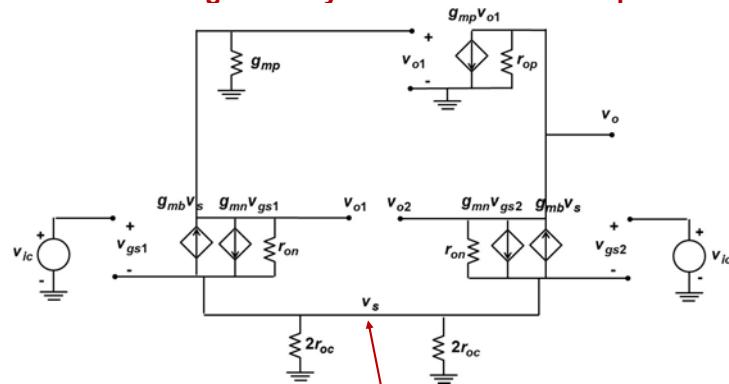

So one can assume that in the common-mode, even with the current mirror, no current flows in the bottom most horizontal wire (i.e. it is a small signal open)


Small Signal Analysis: Common-Mode Input

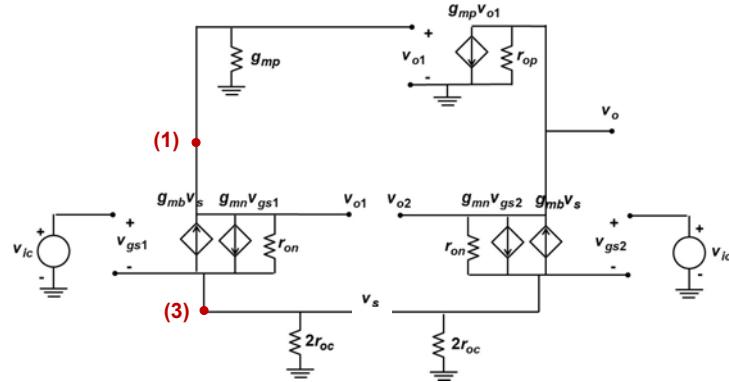

Doing KCL at (1) and (3) gives:

$$v_{o1} \approx -\frac{\frac{g_{mn} r_{on}}{g_{mp}}}{r_{on} + \frac{1}{g_{mp}} + 2r_{oc} + (g_{mn} + g_{mb})r_{on}(2r_{oc})} v_{ic}$$

Small Signal Analysis: Common-Mode Input

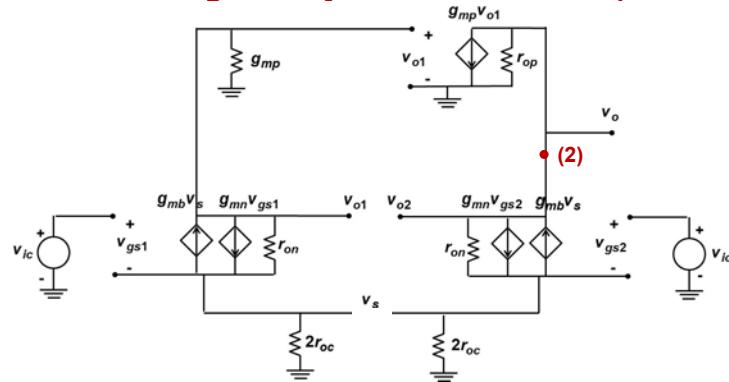


Using the left-right symmetry gives:

$$v_o = v_{o2} \approx v_{o1}$$

$$A_{vc} = \frac{v_o}{v_{ic}} \approx -\frac{\frac{g_{mn} r_{on}}{g_{mp}}}{r_{on} + \frac{1}{g_{mp}} + 2r_{oc} + (g_{mn} + g_{mb})r_{on}(2r_{oc})}$$



Small Signal Analysis: Output Resistance

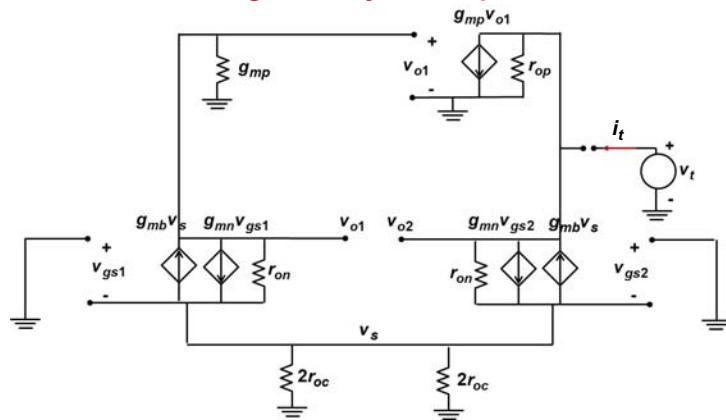


$$R_{out} \approx r_{on} \parallel r_{op}$$

Left for homework

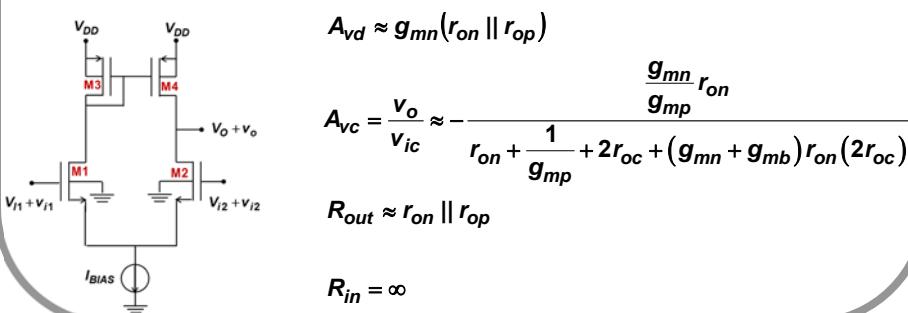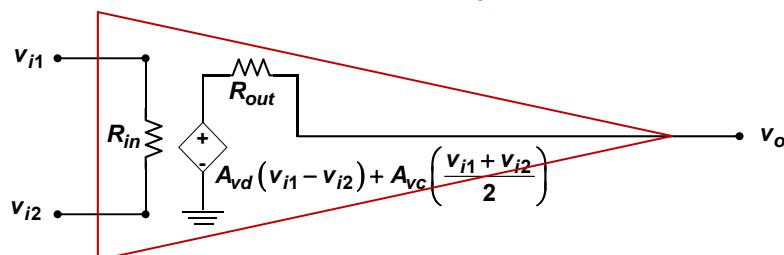Two-Port Model of a FET Differential Amplifier with Current Mirror



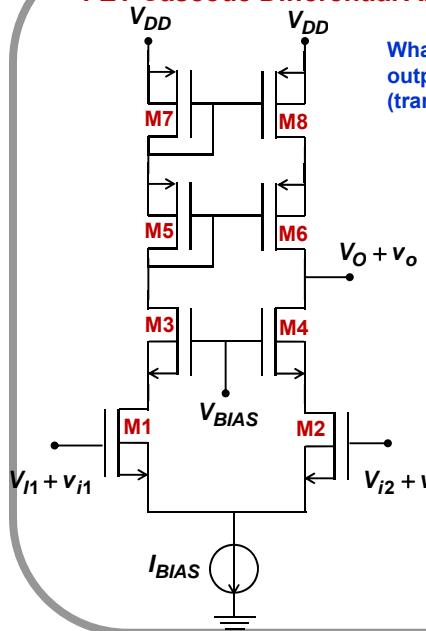FET Cascode Differential Amplifier with Cascode Current Mirror



What if one needs a large gain and a large output resistance from a differential (transconductance) amplifier?

$$R_{out} \approx (g_{mn}r_{on}r_{on}) \parallel (g_{mp}r_{op}r_{op})$$

$$A_{vd} \approx g_{mn} [(g_{mn}r_{on}r_{on}) \parallel (g_{mp}r_{op}r_{op})]$$