

## Lecture 19


### High Frequency Analysis of FET Circuits

---

In this lecture you will learn:

- High Frequency Analysis of FET Circuits
- Miller Effect and the Miller Capacitance

### Phasor Analysis: Complex Impedances

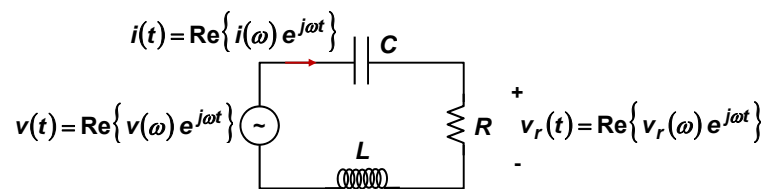


Capacitive Impedance/Admittance:

$$Z(\omega) = \frac{1}{Y(\omega)} = \frac{1}{j\omega C}$$

Inductance Impedance/Admittance:

$$Z(\omega) = \frac{1}{Y(\omega)} = j\omega L$$
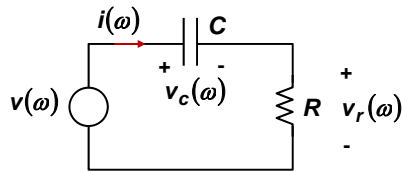
### Phasor Analysis: Calculations with Impedances




One can compute the voltage phasors using the impedances:

$$v_c(\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} v(\omega) = \frac{1}{1 + j\omega RC} v(\omega)$$


$$v_r(\omega) = \frac{R}{R + \frac{1}{j\omega C}} v(\omega) = \frac{j\omega RC}{1 + j\omega RC} v(\omega)$$

### Phasor Analysis: Bode Plots

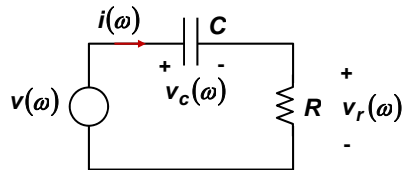


$$\frac{v_c(\omega)}{v(\omega)} = \frac{1}{1 + j\omega RC} = H(\omega)$$

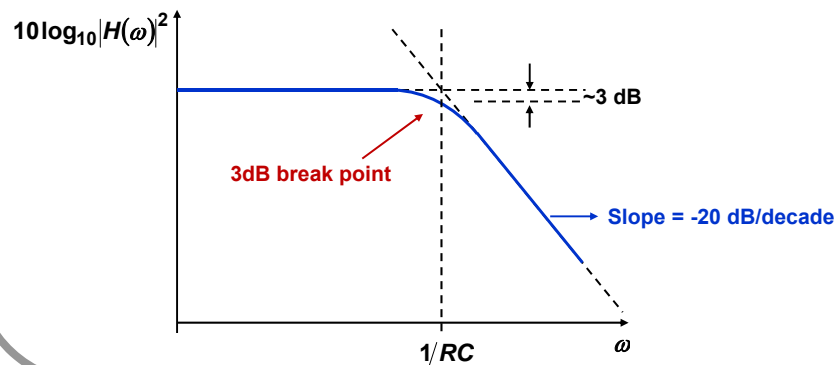A transfer function with a pole at frequency  $1/RC$


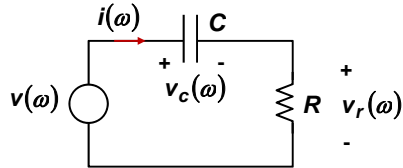
### Poles and Zeroes of Transfer Functions



$$\frac{v_c(\omega)}{v(\omega)} = \frac{1}{1 + j\omega RC} \longrightarrow \text{Pole at the complex frequency } \frac{j}{RC}$$


With a little abuse of language we will say a pole at the frequency  $\frac{1}{RC}$

$$\frac{v_r(\omega)}{v(\omega)} = \frac{j\omega RC}{1 + j\omega RC} \longrightarrow \text{Pole at the complex frequency } \frac{j}{RC}$$

Zero at the complex frequency 0

With a little abuse of language we will say pole at the frequency  $\frac{1}{RC}$  and a zero at 0 frequency
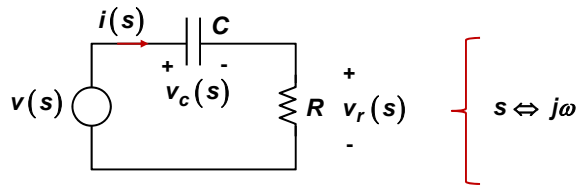
### Laplace Transform Calculations: Language Differences to Note




One can compute the voltages using Laplace transforms as well:

$$v_c(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} v(s) = \frac{1}{1 + sRC} v(s) \longrightarrow \text{Pole at } -\frac{1}{RC}$$


$$v_r(s) = \frac{R}{R + \frac{1}{sC}} v(s) = \frac{sRC}{1 + sRC} v(s) \longrightarrow \text{Pole at } -\frac{1}{RC}$$

Zero at 0

### Phasor Analysis: Bode Plots

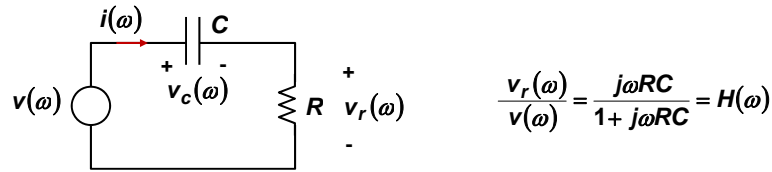

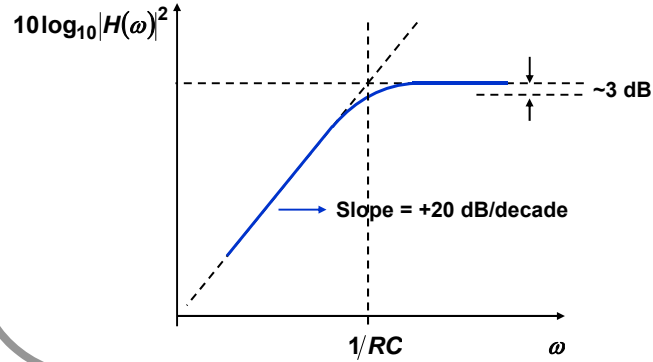
A transfer function with a zero at zero frequency and a pole at frequency  $1/RC$




### The Miller Effect and the Miller Capacitance

John A. Miller (1920)

Consider a voltage amplifier:

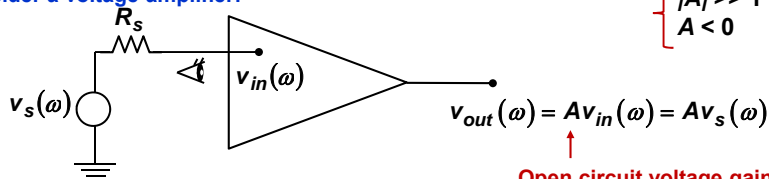


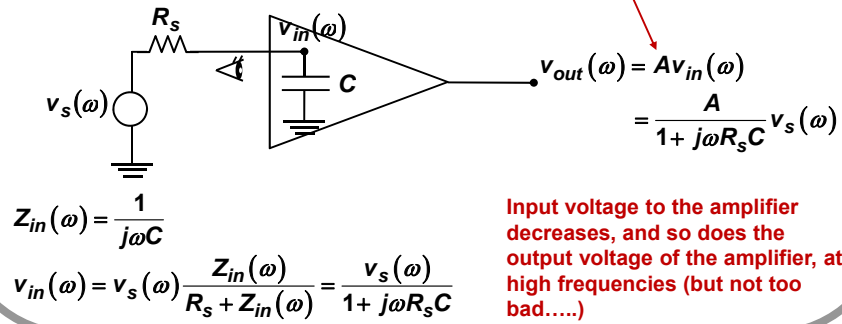Consider now a capacitor sitting at the input of an amplifier:


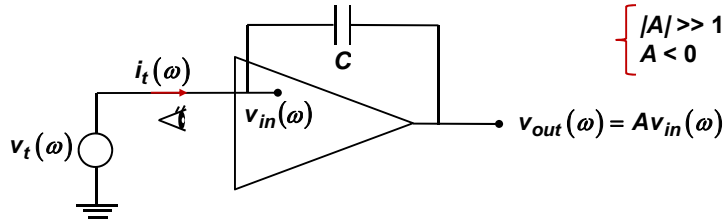
### The Miller Effect and the Miller Capacitance

Consider now a capacitor straddling the input and the output of an amplifier:




$$\begin{aligned}
 i_t(\omega) &= j\omega C [v_t(\omega) - v_{out}(\omega)] = j\omega C [v_t(\omega) - Av_t(\omega)] \\
 &= j\omega C(1-A)v_t(\omega) \\
 \Rightarrow Z_{in}(\omega) &= \frac{v_t(\omega)}{i_t(\omega)} = \frac{1}{j\omega C(1-A)}
 \end{aligned}$$

The capacitance, as seen from the input end, is effectively very large!
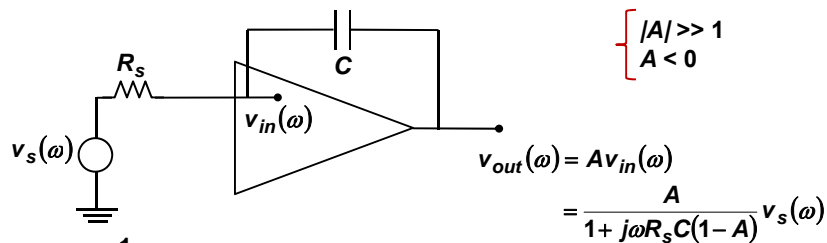
### The Miller Effect and the Miller Capacitance

Capacitor straddling the input and the output of an amplifier:



$$Z_{in}(\omega) = \frac{1}{j\omega C(1-A)}$$

$$v_{in}(\omega) = v_s(\omega) \frac{Z_{in}(\omega)}{R_s + Z_{in}(\omega)} = \frac{v_s(\omega)}{1 + j\omega R_s C(1-A)}$$


$$v_{out}(\omega) = Av_{in}(\omega) = \frac{A}{1 + j\omega R_s C(1-A)} v_s(\omega)$$

The pole has shifted to a much lower frequency!

The amplifier input voltage, and the output voltage, will now begin to drop-off at a much lower frequency!!

This is the Miller effect and the capacitance positioned this way is called the Miller capacitance
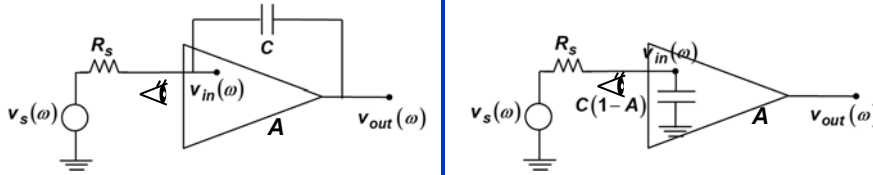
### The Miller Effect and the Miller Capacitance: Summary



In both cases:

$$Z_{in}(\omega) = \frac{1}{j\omega C(1-A)}$$

$$v_{in}(\omega) = v_s(\omega) \frac{Z_{in}(\omega)}{R_s + Z_{in}(\omega)}$$

$$v_{out}(\omega) = Av_{in}(\omega)$$


$$= \frac{A}{1 + j\omega R_s C(1-A)} v_s(\omega)$$

**Lesson:**

A capacitor  $C$  straddling the input-output terminals of an amplifier of gain  $A = -|A|$  behaves like a very large capacitor  $C(1-A)$  sitting between the input and the ground terminals.


This capacitor reduces the gain bandwidth of the circuit

### NFET: Capacitances

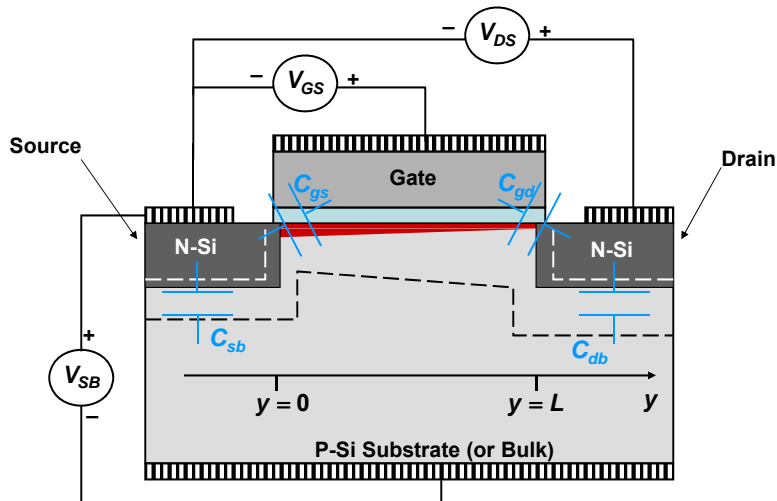


### NFET: High Frequency Small Signal Model

FET high frequency model:

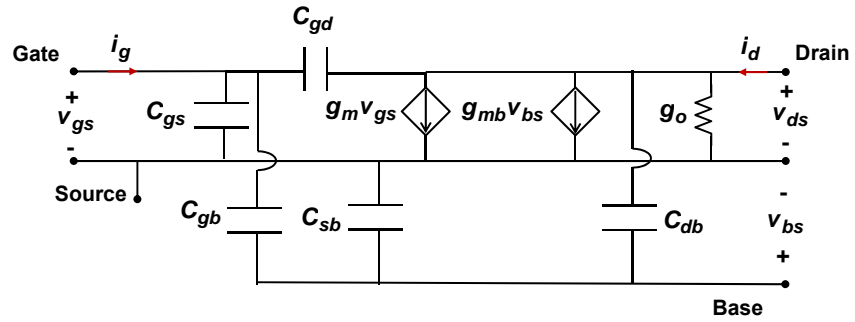

### NFET: High Frequency Small Signal Model

Our simplified high frequency model:

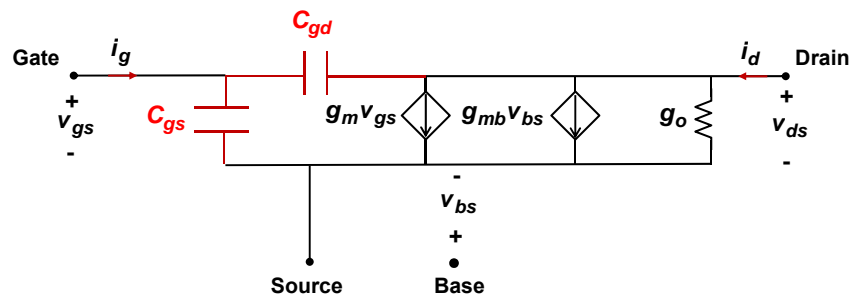

### NFET Gate Charge

The total gate charge  $Q_{TG}$  (units: Coulombs) consists of the image charge due to:

- 1) The total inversion layer charge  $Q_{TN}$
- 2) The total depletion layer charge  $Q_{TB}$


$$Q_{TG} = -(Q_{TN} + Q_{TB})$$

The inversion layer charge  $Q_N$  (units: Coulombs/unit area) is a function of position “ $y$ ” in the device:

$$Q_N(y) = -C_{ox}(V_{GS} - V_{TN} - V_{CS}(y))$$

The total inversion layer charge  $Q_{TN}$  (units: Coulombs) can be found by integration over the entire area of the FET:
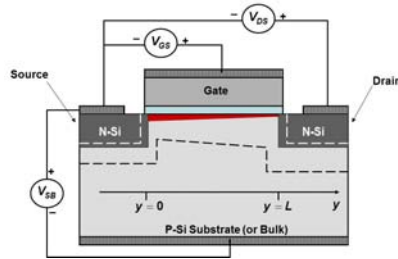
$$\begin{aligned} Q_{TN} &= W \int_0^L Q_N(y) dy \\ &= -WC_{ox} \int_0^L (V_{GS} - V_{TN} - V_{CS}(y)) dy \end{aligned}$$




### NFET Gate Charge

$$\begin{aligned} Q_{TN} &= -WC_{ox} \int_0^L (V_{GS} - V_{TN} - V_{CS}(y)) dy \\ &= -WC_{ox} \int_0^{V_{DS}} (V_{GS} - V_{TN} - V_{CS}) \frac{dy}{dV_{CS}} dV_{CS} \end{aligned}$$

Recall that (Lecture 10):

$$\begin{aligned} I_D &= WQ_N(y) \mu_n E_y(y) \\ &= W \mu_n C_{ox} (V_{GS} - V_{TN} - V_{CS}(y)) \frac{dV_{CS}(y)}{dy} \\ \Rightarrow \frac{dy}{dV_{CS}} &= \frac{W \mu_n C_{ox} (V_{GS} - V_{TN} - V_{CS}(y))}{I_D} \end{aligned}$$
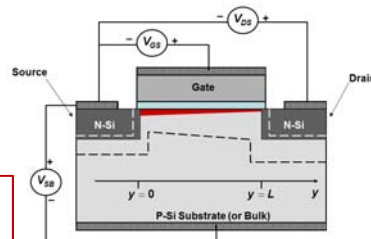
$$\begin{aligned} Q_{TN} &= -\frac{\mu_n}{I_D} (WC_{ox})^2 \int_0^{V_{DS}} (V_{GS} - V_{TN} - V_{CS})^2 dV_{CS} \\ &= \frac{\mu_n}{3I_D} (WC_{ox})^2 \left[ (V_{GS} - V_{TN} - V_{DS})^3 - (V_{GS} - V_{TN})^3 \right] \end{aligned}$$






### NFET: Inversion Layer Charge in Linear and Saturation

For  $V_{DS} \leq V_{GS} - V_{TN}$  : Linear Region:


Channel potential:  $V_{CS}(y) = V_{DS}$

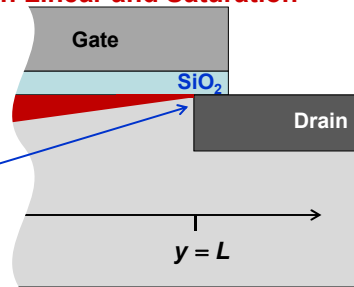

For  $V_{DS} \geq V_{GS} - V_{TN}$  : Saturation Region:

Channel potential:  $V_{CS}(y) = V_{GS} - V_{TN}$

Channel potential:  $V_{CS}(y) = V_{DS}$

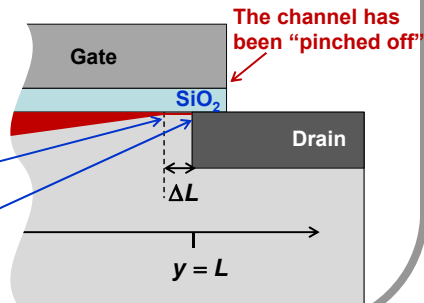

### NFET Gate Charge

Inversion layer charge  $Q_N$ :

$$Q_{TN} = \frac{\mu_n}{3I_D} (WC_{ox})^2 \left[ (V_{GS} - V_{TN} - V_{DS})^3 - (V_{GS} - V_{TN})^3 \right] \quad \left\{ \begin{array}{l} \text{Expression only} \\ \text{works in the} \\ \text{linear region} \end{array} \right.$$


In **saturation** ( $V_{DS} > V_{GS} - V_{TN}$ ) but the inversion charge remains fixed at the value when  $V_{DS} = V_{GS} - V_{TN}$  because of pinch-off:

$$Q_{TN} = -\frac{2}{3} WLC_{ox} (V_{GS} - V_{TN})$$

Therefore, in **saturation** (since the depletion region thickness and charge do not change with the gate voltage), we get:


$$Q_{TG} = -(Q_{TN} + Q_{TB})$$

$$C_{gs} = \left. \frac{\partial Q_{TG}}{\partial V_{GS}} \right|_{V_{GD}, V_{GB}} = -\left. \frac{\partial Q_{TN}}{\partial V_{GS}} \right|_{V_{GD}, V_{GB}} = \frac{2}{3} WLC_{ox}$$

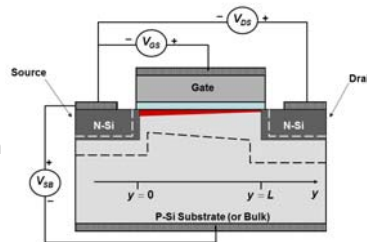

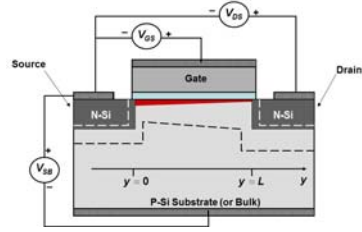
## NFET Capacitances in Saturation: A Simple Model

In **saturation**, because of pinch off, the inversion layer charge  $Q_{TN}$  is not affected by the drain voltage:



$$C_{gd} = \frac{\partial Q_{TG}}{\partial V_{GD}} \Big|_{V_{GS}, V_{GB}} = - \frac{\partial Q_{TG}}{\partial V_{DS}} \Big|_{V_{GS}, V_{GB}} = \frac{\partial Q_{TN}}{\partial V_{DS}} \Big|_{V_{GS}, V_{GB}} = 0$$

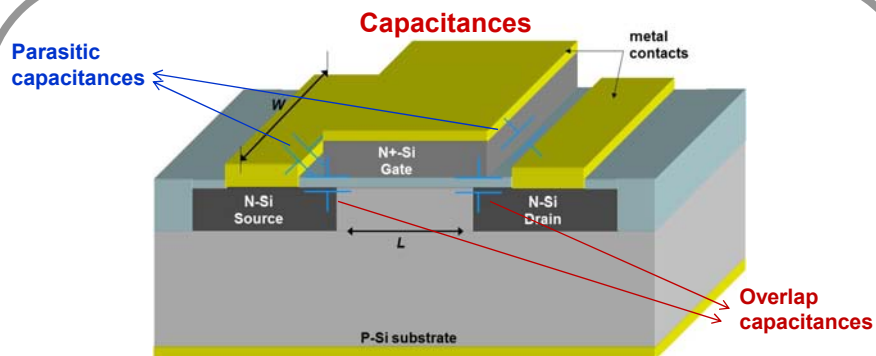


In Saturation:

$$C_{gs} = \frac{\partial Q_G}{\partial V_{GS}} \Big|_{V_{GS}, V_{SB}} = \frac{2}{3} WLC_{ox} + WC_{ov} + WC_p > \frac{2}{3} WLC_{ox}$$

$$C_{gd} = \frac{\partial Q_G}{\partial V_{GD}} \Big|_{V_{GS}, V_{SB}} = 0 + WC_{ov} + WC_p > 0$$

## NFET: High Frequency Small Signal Model for Saturation Region


Our simplified high frequency model:

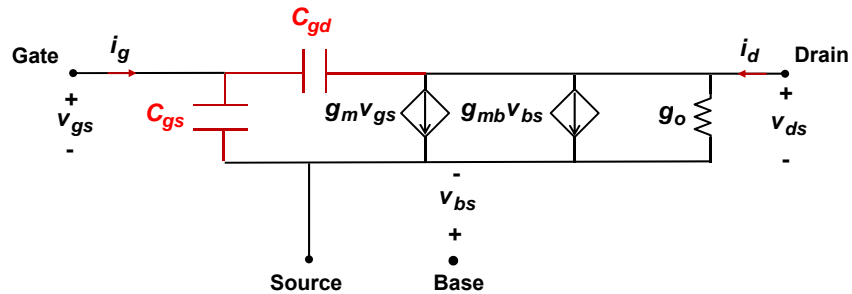

$$C_{gs} = \frac{2}{3} WLC_{ox} + WC_{ov} + WC_p$$


$$C_{gd} = WC_{ov} + WC_p$$

## The Common Source Amplifier

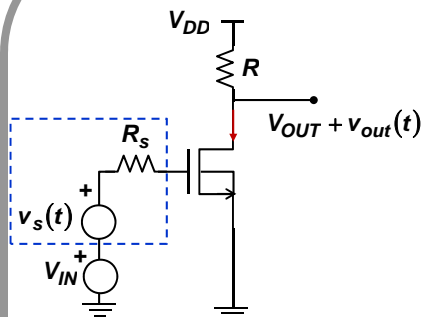


$$v_s(t) = \text{Re}\{v_s(\omega)e^{j\omega t}\}$$

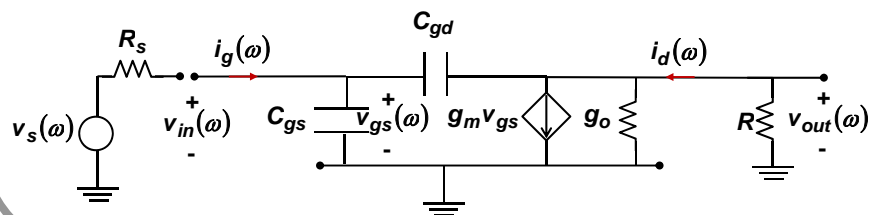A high frequency small signal model can be built as follows:


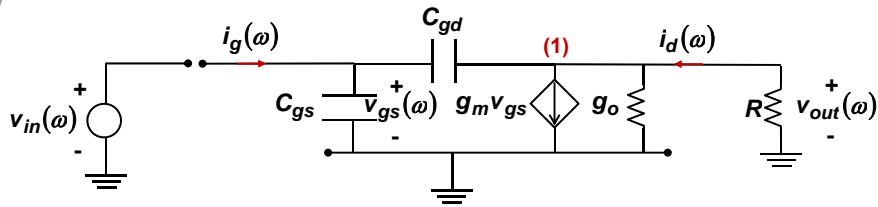
### The Common Source Amplifier: Open Circuit Voltage Gain



Need to find:

$$A_v(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} \quad \text{and} \quad H(\omega) = \frac{v_{out}(\omega)}{v_s(\omega)}$$

KCL at (1) gives:

$$i_d(\omega) = g_o v_{out}(\omega) + g_m v_{in}(\omega) + [v_{out}(\omega) - v_{in}(\omega)] j\omega C_{gd}$$

Also:


$$v_{out}(\omega) = -i_d(\omega)R$$

The above two give:

$$A_v(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = -\frac{g_m R - j\omega R C_{gd}}{1 + g_o R + j\omega R C_{gd}}$$
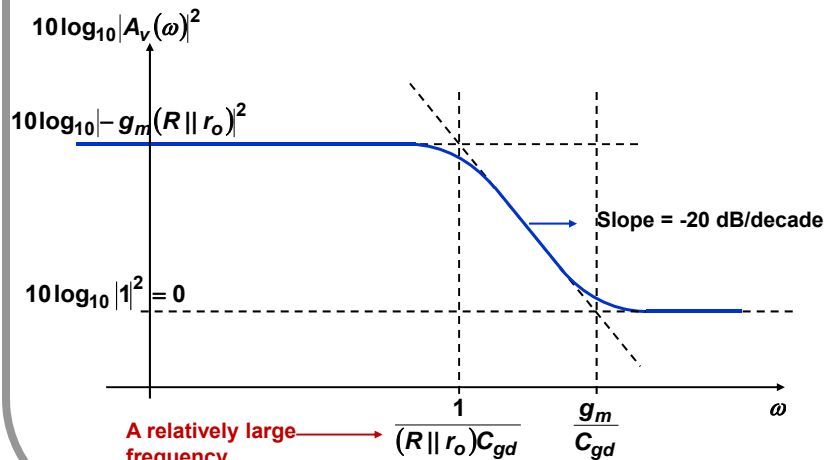
### The Common Source Amplifier: Open Circuit Voltage Gain


$$A_v(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = -\frac{g_m R - j\omega R C_{gd}}{1 + g_o R + j\omega R C_{gd}} = -g_m (R \parallel r_o) \frac{1 - j\omega \frac{C_{gd}}{g_m}}{1 + j\omega C_{gd} (R \parallel r_o)}$$




A relatively large frequency  $\rightarrow \frac{1}{(R \parallel r_o) C_{gd}}$   $\frac{g_m}{C_{gd}}$   
 These poles might not limit the frequency performance.....PTO
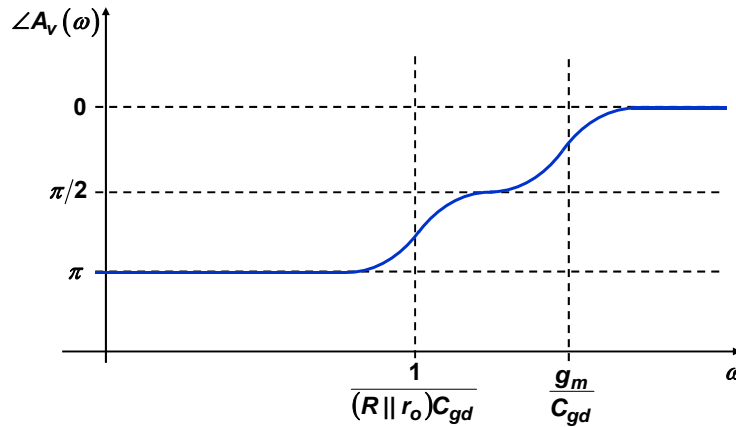
### The Common Source Amplifier: Open Circuit Voltage Gain

$$A_V(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = -\frac{g_m R - j\omega R C_{gd}}{1 + g_o R + j\omega R C_{gd}} = -g_m (R \parallel r_o) \frac{1 - j\omega \frac{C_{gd}}{g_m}}{1 + j\omega C_{gd} (R \parallel r_o)}$$


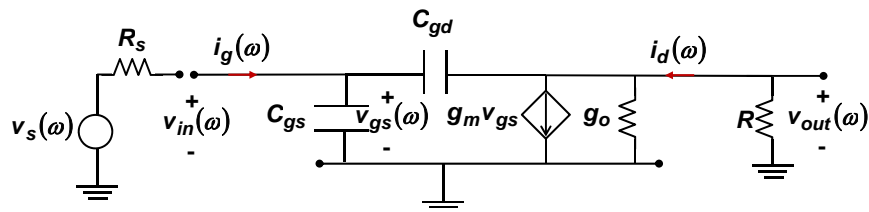
### The Common Source Amplifier: Input-Output Response




So far we have found the open circuit voltage gain:

$$A_V(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = -\frac{g_m R - j\omega R C_{gd}}{1 + g_o R + j\omega R C_{gd}} = -g_m (R \parallel r_o) \frac{1 - j\omega \frac{C_{gd}}{g_m}}{1 + j\omega C_{gd} (R \parallel r_o)}$$

What about:

$$\frac{v_{out}(\omega)}{v_s(\omega)} = ??$$
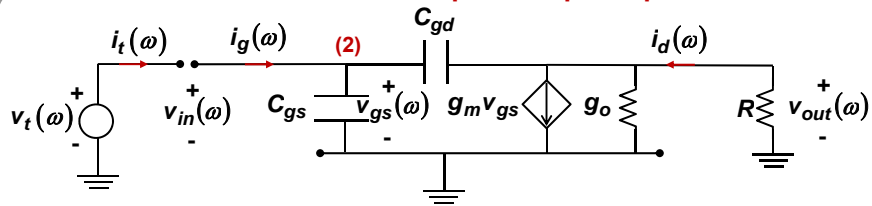
### The Common Source Amplifier: Input Impedance



KCL at (2) gives:

$$i_t(\omega) = j\omega C_{gs}v_t(\omega) + j\omega C_{gd}[v_t(\omega) - v_{out}(\omega)]$$

$$= (j\omega C_{gs} + j\omega C_{gd}[1 - A_v(\omega)])v_t(\omega)$$


$$\frac{v_t(\omega)}{i_t(\omega)} = Z_{in}(\omega) = \frac{1}{j\omega C_{gs} + j\omega C_{gd}[1 - A_v(\omega)]}$$

$$\left\{ \frac{v_{out}(\omega)}{v_{in}(\omega)} = A_v(\omega) \right.$$

The input impedance is:

$$Z_{in}(\omega) \approx \frac{1}{j\omega[C_{gs} + C_{gd}(1 - A_v(\omega))]}$$

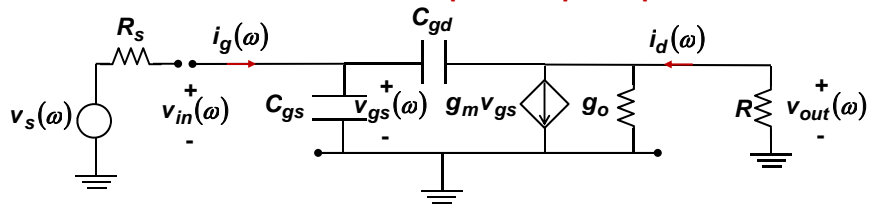
### The Common Source Amplifier: Input Impedance



$$\frac{v_{in}(\omega)}{v_s(\omega)} \approx \underbrace{\frac{Z_{in}(\omega)}{R_s + Z_{in}(\omega)}}_{\text{Input voltage divider}} = \frac{1}{1 + j\omega \underbrace{[C_{gs} + C_{gd}(1 - A_v(\omega))]R_s}_{\text{Miller Effect!!}}}$$

Looking in from the input terminal the capacitance  $C_{gd}$  seems to be magnified by a factor proportional to the open circuit voltage gain of the amplifier!!
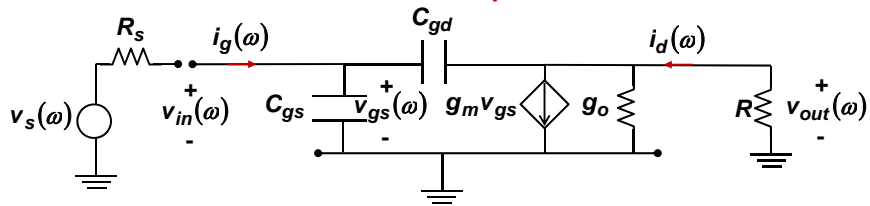
### The Common Source Amplifier: Total Gain



Finally:

$$H(\omega) = \frac{v_{out}(\omega)}{v_s(\omega)} = \frac{v_{out}(\omega)}{v_{in}(\omega)} \frac{v_{in}(\omega)}{v_s(\omega)} = A_V(\omega) \frac{Z_{in}(\omega)}{R_s + Z_{in}(\omega)}$$

$$= \frac{A_V(\omega)}{1 + j\omega [C_{gs} + C_{gd}(1 - A_V(\omega))] R_s}$$

Where:

$$A_V(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = -g_m (R \parallel r_o) \left[ \frac{1 - j\omega \frac{C_{gd}}{g_m}}{1 + j\omega C_{gd} (R \parallel r_o)} \right]$$

### The Common Source Amplifier: Poles and Zeros of the Total Gain

$$H(\omega) = \frac{A_V(\omega)}{1 + j\omega [C_{gs} + C_{gd}(1 - A_V(\omega))] R_s} = \frac{H(0)(1 - j\omega\tau_3)}{(1 + j\omega\tau_1)(1 + j\omega\tau_2)} \quad \left[ H(0) \approx -g_m (R \parallel r_o) \right]$$

A little tedious algebra can show that the transfer function above has two poles and a zero

$$\frac{1}{\tau_3} = \frac{g_m}{C_{gd}}$$

1) Assuming  $g_m R_s \gg 1$ , these poles are:

$$\frac{1}{\tau_1} \approx \frac{g_m}{C_{gs}} + \frac{1}{C_{gd}(R \parallel r_o)} \quad \frac{1}{\tau_2} \approx \frac{1}{[C_{gs} + C_{gd}(g_m(R \parallel r_o))] R_s}$$

This pole will likely determine the smallest frequency at which the total gain rolls over

2) Assuming  $g_m R_s \ll 1$ , these poles are:

$$\frac{1}{\tau_1} \approx \frac{1}{R_s C_{gs}} \quad \frac{1}{\tau_2} \approx \frac{1}{C_{gd}(R \parallel r_o)}$$

This pole will likely determine the smallest frequency at which the total gain rolls over

### The Common Source Amplifier: The Miller Approximation

$$H(\omega) = \frac{v_{out}(\omega)}{v_s(\omega)} = \frac{A_v(\omega)}{1 + j\omega [C_{gs} + C_{gd}(1 - A_v(\omega))] R_s}$$

If the poles in  $A_v(\omega)$  are at high enough frequencies such that the lowest poles of the full transfer function are determined by other poles (which would be the case if  $g_m R_s \gg 1$ ) then one may approximate the open circuit gain  $A_v(\omega)$  by its low frequency value:

$$A_v(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = -\frac{g_m R - j\omega R C_{gd}}{1 + g_o R + j\omega R C_{gd}} \approx A_v(\omega = 0) = -g_m (R \parallel r_o) \quad \left\{ \begin{array}{l} \text{Miller} \\ \text{approximation} \end{array} \right.$$


And then:

$$H(\omega) = \frac{v_{out}(\omega)}{v_s(\omega)} = \frac{A_v(\omega)}{1 + j\omega [C_{gs} + C_{gd}(1 - A_v(\omega))] R_s} \approx \frac{-g_m (R \parallel r_o)}{1 + j\omega [C_{gs} + C_{gd}(1 + g_m (R \parallel r_o))] R_s}$$


Looking in from the input terminal the capacitance  $C_{gd}$  seems to be magnified by a factor proportional to the low frequency open circuit voltage gain of the amplifier!!

And now the single pole is at:  $\frac{1}{\tau} \approx \frac{1}{[C_{gs} + C_{gd}(1 + g_m (R \parallel r_o))] R_s}$
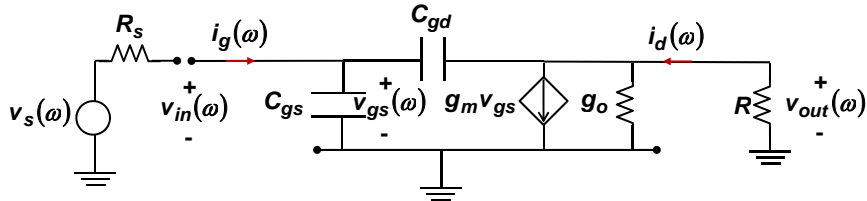
### The Common Source Amplifier: Total Gain Under the Miller Approx



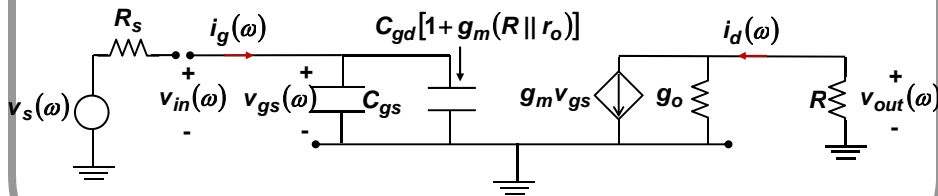
Miller approximation is equivalent to saying that the following circuit will describe the input-output response at not too high frequencies.....




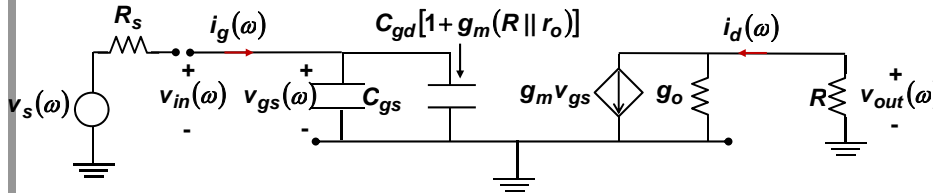
### The Common Source Amplifier: Input Impedance



Miller approximation is equivalent to saying that the following circuit will describe the input-output response at not too high frequencies.....




Looking in from the input terminal the capacitance  $C_{gd}$  seems to be magnified by a factor proportional to the low frequency open circuit voltage gain of the amplifier!!

$$Z_{in}(\omega) \approx \frac{1}{j\omega [C_{gs} + \underbrace{C_{gd}(1 + g_m(R \parallel r_o))}_{\text{Miller Magnification}}]}$$
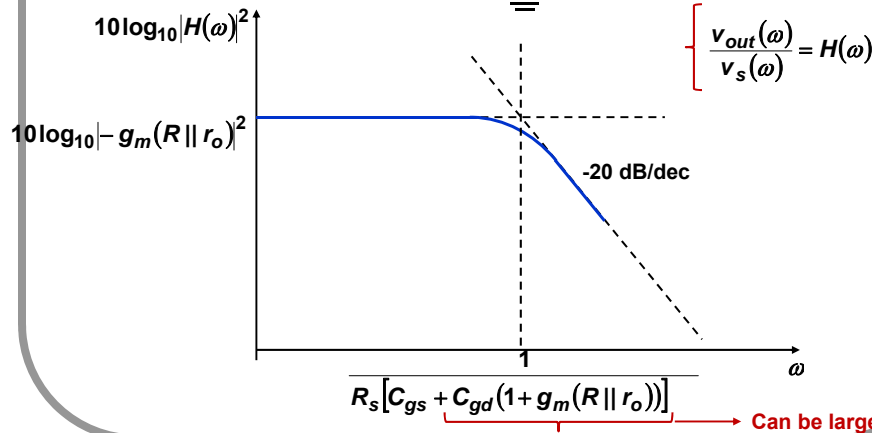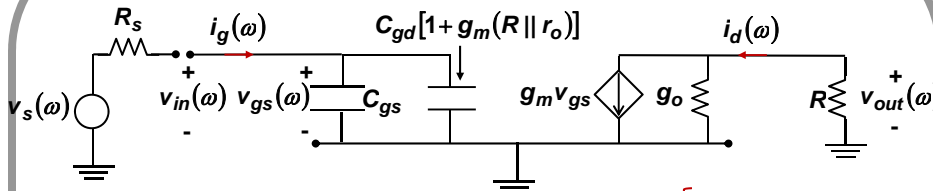
### The Common Source Amplifier: Total Gain Under the Miller Approx


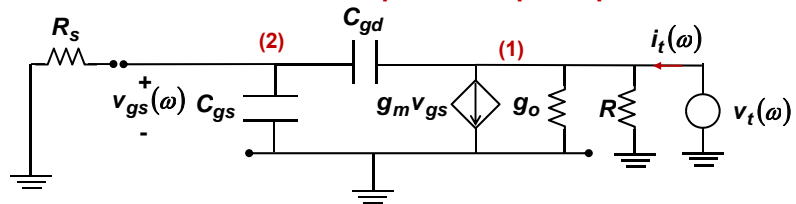
### The Common Source Amplifier: Output Impedance



Need to find:

$$Z_{out}(\omega)$$


KCL at (2) gives:

$$[v_t(\omega) - v_{gs}(\omega)]j\omega C_{gd} = j\omega C_{gs}v_{gs} + \frac{v_{gs}}{R_s}$$

This gives:

$$v_{gs}(\omega) = \frac{j\omega C_{gd}R_s}{j\omega(C_{gs} + C_{gd})R_s + 1} v_t(\omega)$$
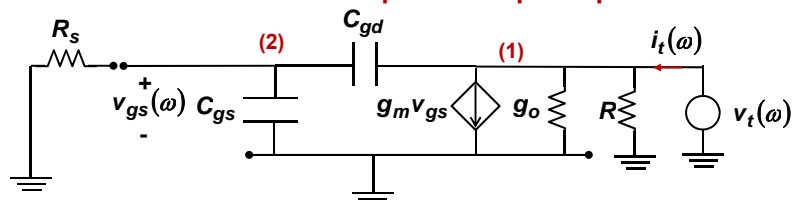
### The Common Source Amplifier: Output Impedance



$$v_{gs}(\omega) = \frac{j\omega C_{gd}R_s}{j\omega(C_{gs} + C_{gd})R_s + 1} v_t(\omega)$$


KCL at (1) gives:

$$i_t(\omega) = \frac{v_t(\omega)}{R \parallel r_o} + g_m v_{gs}(\omega) + [v_t(\omega) - v_{gs}(\omega)]j\omega C_{gd}$$

$$\Rightarrow \frac{1}{Z_{out}(\omega)} = \frac{1}{R \parallel r_o} + \frac{(g_m + j\omega C_{gs})j\omega C_{gd}R_s}{j\omega(C_{gs} + C_{gd})R_s + 1}$$

↑  
Not a bad approximation  
even at moderately high  
frequencies
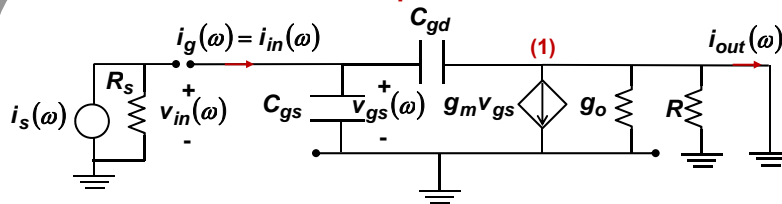
### The Common Source Amplifier: Short Circuit Current Gain



Need to find:

$$\frac{i_{out}(\omega)}{i_{in}(\omega)} \quad \left[ \quad Z_{in}(\omega) \approx \frac{1}{j\omega[C_{gs} + C_{gd}]} \right]$$

Start from KCL at (1):

$$(0 - v_{in}(\omega))j\omega C_{gd} + g_m v_{in}(\omega) + i_{out}(\omega) = 0$$

$$\Rightarrow \frac{i_{out}(\omega)}{v_{in}(\omega)} = -(g_m - j\omega C_{gd})$$


$$\begin{aligned} \Rightarrow \frac{i_{out}(\omega)}{i_{in}(\omega)} &= \frac{i_{out}(\omega)}{v_{in}(\omega)} \frac{v_{in}(\omega)}{i_{in}(\omega)} = -(g_m - j\omega C_{gd}) Z_{in}(\omega) \approx -g_m Z_{in}(\omega) \\ &= -\frac{g_m}{j\omega(C_{gs} + C_{gd})} \end{aligned}$$

### Short Circuit Current Gain and the Transition Frequency ( $f_T$ or $\omega_T$ )

For most transistors, the short circuit current gain falls off with frequency with a -20 dB/dec slope (at high enough frequencies)


The frequency at which the short circuit current gain equals unity is called the transition frequency ( $f_T$  or  $\omega_T$ )

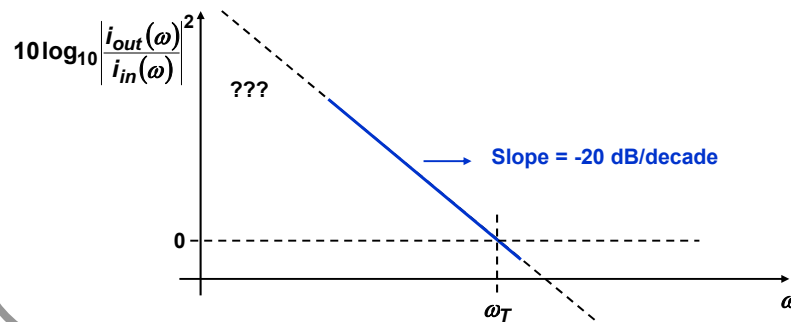The transition frequency expresses the maximum useful frequency of operation of the transistor


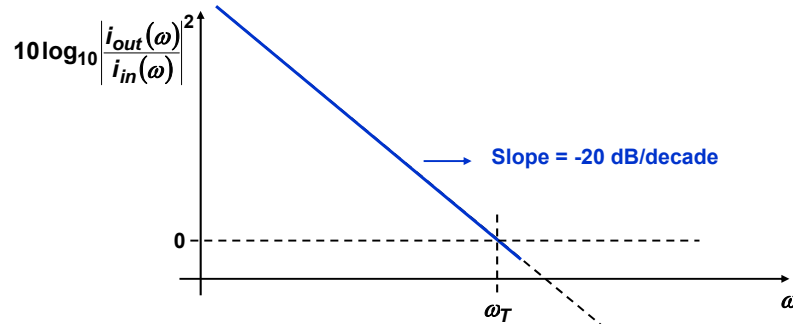
### The Common Source Amplifier: The Transition Frequency

$$\frac{i_{out}(\omega)}{i_{in}(\omega)} = -\frac{g_m}{j\omega(C_{gs} + C_{gd})}$$



The transition frequency is:

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}} \approx \frac{g_m}{C_{gs}}$$

### The Common Source Amplifier: The Transition Frequency

The FET transition frequency is:


$$\omega_T \approx \frac{g_m}{C_{gs}}$$

This is the highest frequency at which the transistor is still useful

Q: What is its physical significance?

$$g_m = \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TN})$$

$$C_{gs} = \frac{2}{3} W L C_{ox}$$

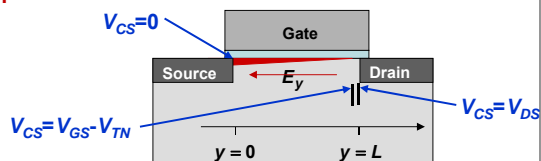

Therefore the transition frequency is:

$$\omega_T = \frac{g_m}{C_{gs}} = \frac{3}{2} \mu_n \frac{(V_{GS} - V_{TN})}{L^2}$$

$$\omega_T \propto \mu_n \frac{(V_{GS} - V_{TN})}{L^2} = \frac{\mu_n (V_{GS} - V_{TN})}{L} = \frac{\mu_n |E_y|}{L} = \frac{v_n}{L} = \frac{1}{\tau_t}$$

Electron transit time through the FET

Therefore, the electron transit time sets the maximum frequency of operation of the FET!!

