


Lecture 24

CMOS Logic Gates and Digital VLSI – II

In this lecture you will learn:


- Static CMOS Logic Gates
- FET Scaling
- CMOS Memory, SRAM and DRAM
- CMOS Latches, and Registers (Flip-Flops)
- Clocked CMOS
- CCDs

CMOS Logic: General Architecture

 

Pull-up network:

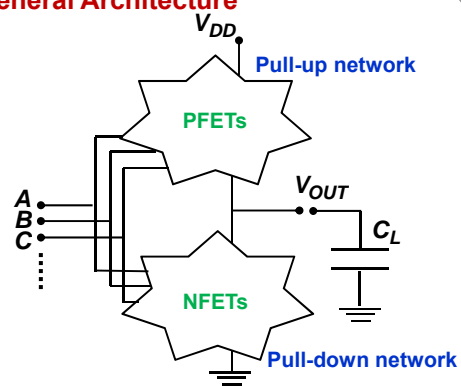
Consists of only **PFETs**
Charges the output to HIGH



Pull-down network:


Consists of only **NFETs**
Discharges the output to LOW

CMOS NAND Gate

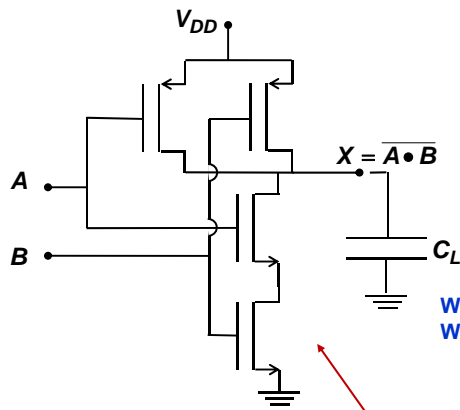


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

 When both A and B are HIGH, output is LOW
 When either A or B is LOW, output is HIGH




In designing the pull-down network, see when the output ought to be LOW and then arrange the NFETs accordingly.
 The pull-up network will have the complimentary topology.

CMOS NOR Gate

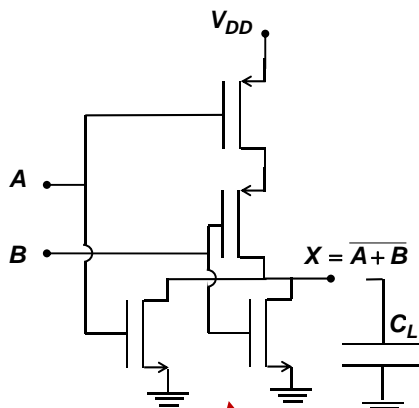

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

 
When both A and B are LOW, output is HIGH
 When either A or B is HIGH, output is LOW



In designing the pull-down network, see when the output ought to be LOW and then arrange the NFETs accordingly.


The pull-up network will have the complimentary topology.

CMOS Gates: Pull Down Network Design

 

If A and B are both HIGH, output will be LOW

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

 


If either A or B is HIGH, output will be LOW

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0


CMOS Gates: Pull Up Network Design

 In designing the pull-up network, see when the output ought to be HIGH and then arrange the PFETs accordingly. The pull-down network will have the complimentary topology.



If either A or B is LOW, output will be HIGH

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

 


If A and B are both LOW, output will be HIGH

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

$A \bullet B = \bar{A} + \bar{B}$ ← De Morgan's Law → $A + B = \overline{\bar{A} \bullet \bar{B}}$

 CMOS Gates: Pull Up and Pull Down Network Design



Pull up and pull down networks are “complimentary” of each other.

Hence the name “Complimentary MOS” or CMOS!


CMOS Gates: More Complex Logic Gates

Suppose we need to design a logic gate for:


$$X = \overline{(A + B)} \bullet C$$

If ((A or B) and C) are HIGH, the output will be LOW

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

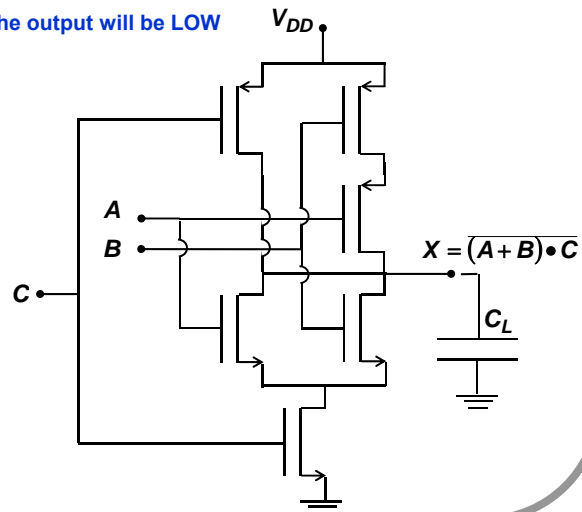

FET Scaling – Inverter

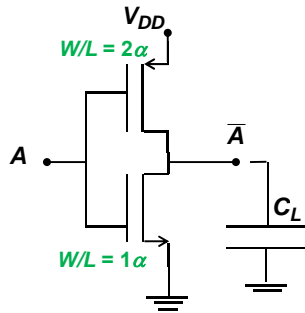

The mobility of electrons in NFETs is generally almost twice that of the holes in PFETs


One would want the current drives for charging and discharging the output and, consequently, the rise and fall times for the output to be identical (i.e. one would want the NFETs and the PFETs to have the same current drives)

$$t_r \approx \frac{2C_L}{k_p(V_{DD} + V_{TP})} \left\{ \frac{-V_{TP}}{V_{DD} + V_{TP}} - \frac{1}{2} \ln \left[\frac{0.1V_{DD}}{2(V_{DD} + V_{TP}) - 0.1V_{DD}} \right] \right\}$$


$$t_f \approx \frac{2C_L}{k_n(V_{DD} - V_{TN})} \left\{ \frac{V_{TN}}{V_{DD} - V_{TN}} - \frac{1}{2} \ln \left[\frac{0.1V_{DD}}{2(V_{DD} - V_{TN}) - 0.1V_{DD}} \right] \right\}$$

Need $k_n = k_p$

 Therefore the W/L ratio of the PFET is chosen to be twice that of the NFET in an inverter




 Fabricated FET Inverter: Dual Well CMOS Technology



Lundstrom EE-612 F08

FET Scaling – NAND Gate

 


As in the inverter case, one scales the PFETs by 2α

A HIGH output has to be discharged through the two NFETs in series

Two FETs in series, with the same gate voltage, are like one FET that is twice as long

Therefore, in order to keep the same current drive in discharging a HIGH output in the NAND gate as in the simple inverter, one needs to scale the NFETs by 2α each

FET Scaling – NOR Gate

 


As in the inverter case, one scales the NFETs by 1α

A LOW output has to be charged through the two PFETs in series


Two FETs in series, with the same gate voltage, are like one FET that is twice as long

Therefore, in order to keep the same current drive in charging a LOW output in the NOR gate as in the simple inverter, one needs to scale the PFETs by 4α each

FET Scaling – A More Complex Example

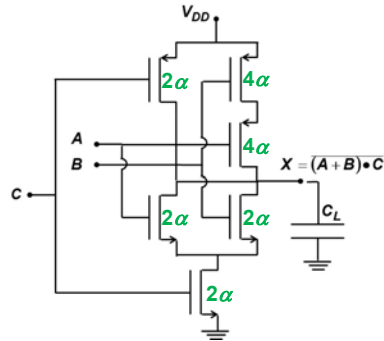


The Transmission Gate

 

A transmission gate allows the logical value to pass from the input to the output only if the gate is OPEN (i.e. the control signal B is HIGH and the switch above is closed)


If the gate is closed (i.e. the control signal B is LOW and the switch above is open) the input and the output are disconnected from each other

The Transmission Gate

 


A transmission gate allows the logical value to pass from the input to the output only if the gate is OPEN (meaning the control signal B is HIGH)

 If the gate is closed (meaning the control signal B is LOW) the input and the output are disconnected from each other



The Transmission Gate

 
Case I: Input is sitting at HIGH, the output is sitting at LOW, and the gate opens



Although both the NFET and the PFET will pass the current, the NFET will cut-off when the output node is still V_{TN} below logical HIGH value ($\sim V_{DD}$)

So the PFET is required to charge the output to the HIGH value ($\sim V_{DD}$)

 Case II: Input is sitting at LOW, the output is sitting at HIGH, and the gate opens




Although both the NFET and the PFET will pass the current, the PFET will cut-off when the output node is still $-V_{TP}$ above the logical LOW value (~ 0)

So the NFET is required to discharge the output to the LOW value (~ 0)

CMOS Memory Element


Two inverters can be used to realize a bistable memory element

 Both of the following states are allowed:




CMOS Memory Element

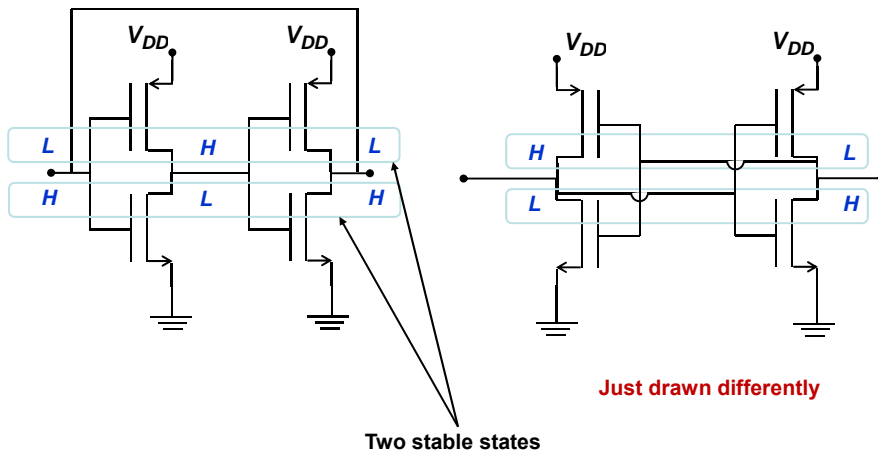Two inverters can be used to realize a bistable memory element



Static Random Access Memory (SRAM)

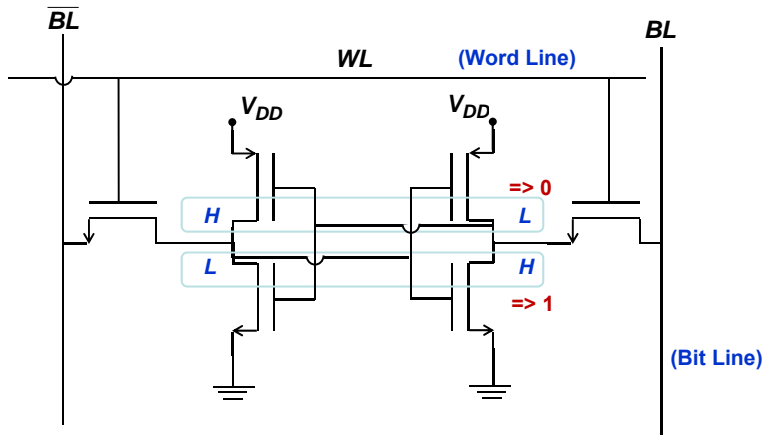
Two inverters can be used together with NFET gates to realize a 6 FET SRAM cell



SRAM is fast


Used for implementing fast caches in microprocessors or fast memories in electronic instruments

Static Random Access Memory (SRAM)

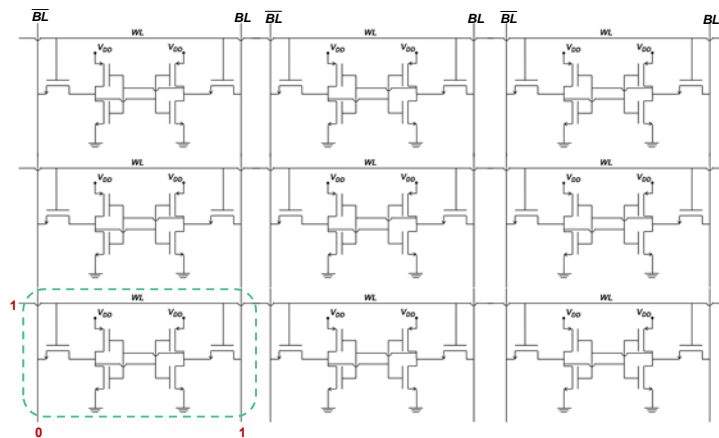


The indicated values show the voltages when a logical 1 is being written in the cell shown

 Intel Core-i7 (4 Core) with 8MB L3 Cache (SRAM)



 
Intel Core-i7 (6 Core) with 12MB L3 Cache (SRAM)



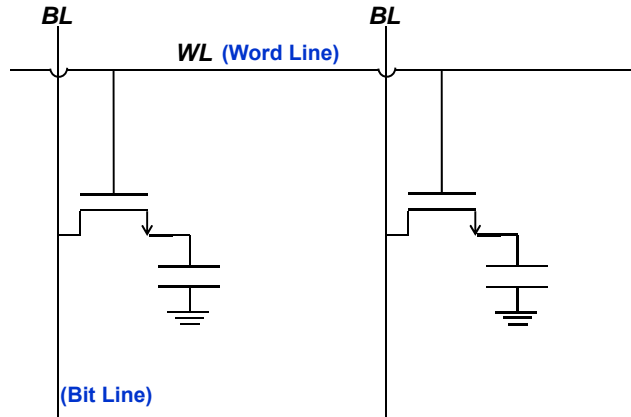1.17 Billion FETs

Dynamic Random Access Memory (DRAM)





A DRAM cell can be implemented using just one FET and one capacitor



DRAM is much slower than SRAM
 Capacitor can discharge via leakage currents (needs periodic refresh)
 Reading a stored bit destroys the stored bit – every read must be followed by a write
 Used for implementing large memory in computers

Dynamic Random Access Memory (DRAM)



Types of DRAM Capacitors

    

The DRAM cell ($0.5 \mu\text{m}^2$) uses stacked cylindrical capacitors with hemispherical silicon grains (HSG) in a capacitor (SAMSUNG)


CMOS Latch

  - Data passes through from the input (D) to the output (Q) when the CLK is HIGH (i.e. the latch is transparent)
- Data at the output (Q) is latched (and held in place) when the CLK is LOW




CMOS Latch

 
- Data passes through from the input (D) to the output (Q) when the CLK is HIGH (i.e. the latch is transparent)
- Data at the output (Q) is latched (and held in place) when the CLK is LOW




CLK = HIGH

 

CLK = LOW

 


CMOS Latch: One Example

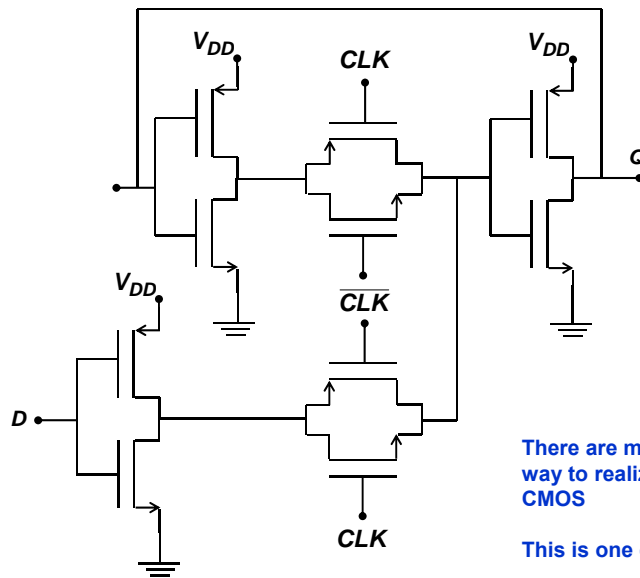



There are many different way to realize a latch in CMOS
This is one example...



CMOS Latch: Operation

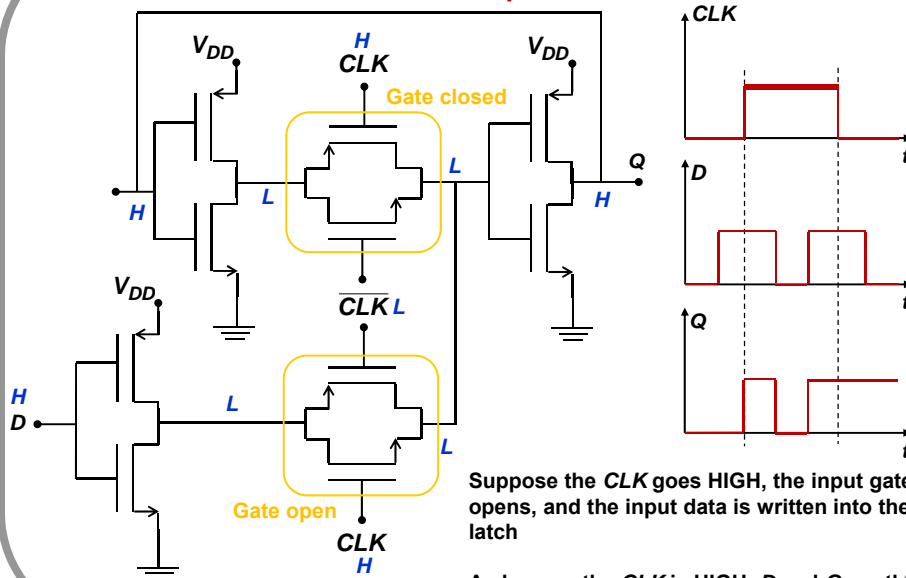


Suppose the CLK goes HIGH, the input gate opens, and the input data is written into the latch

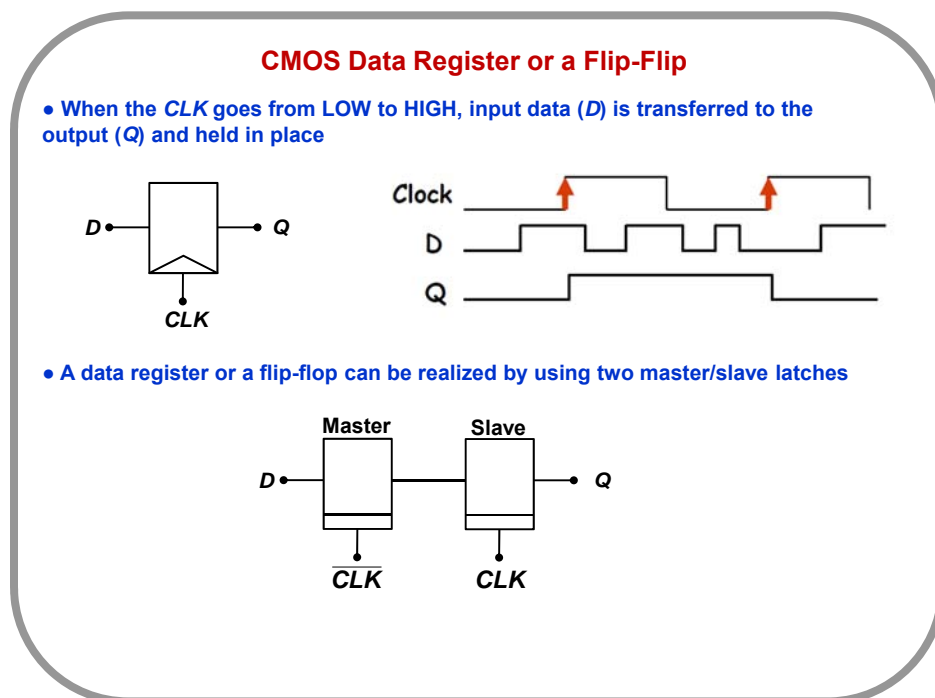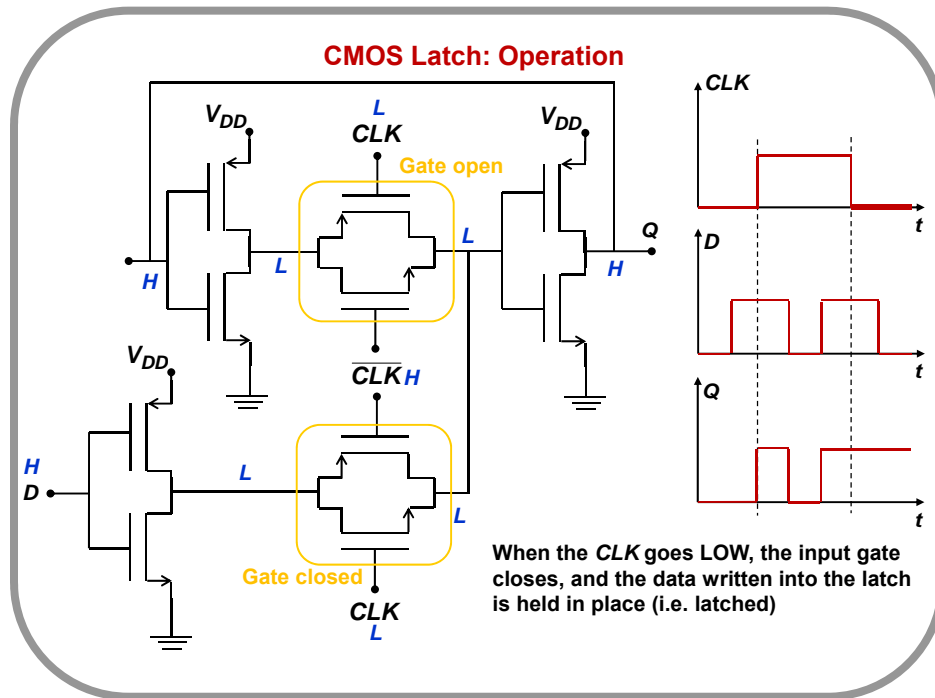As long as the CLK is HIGH, D and Q are the same (i.e. the latch is transparent)



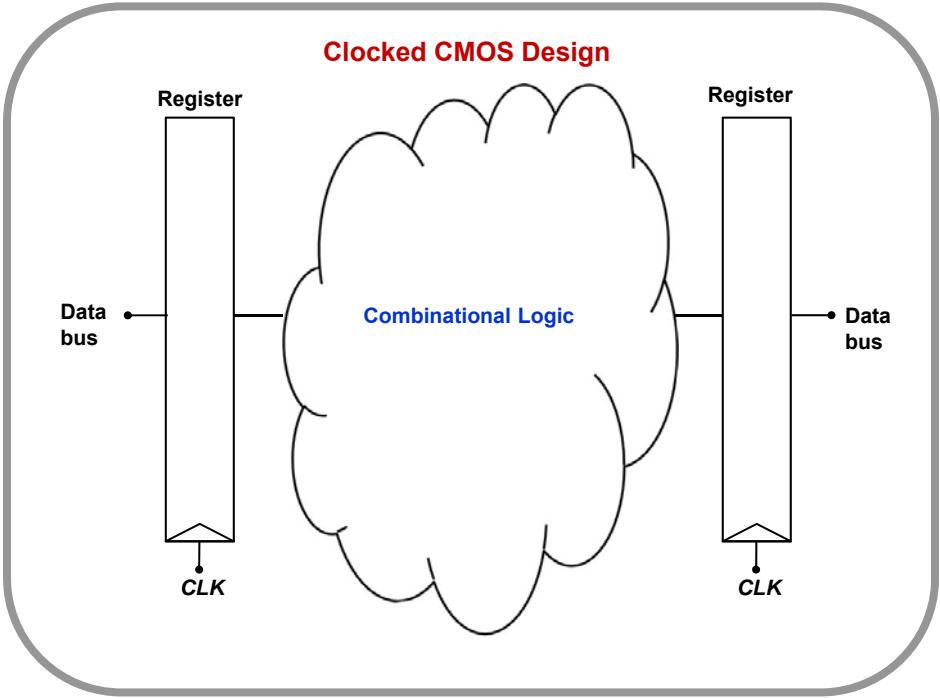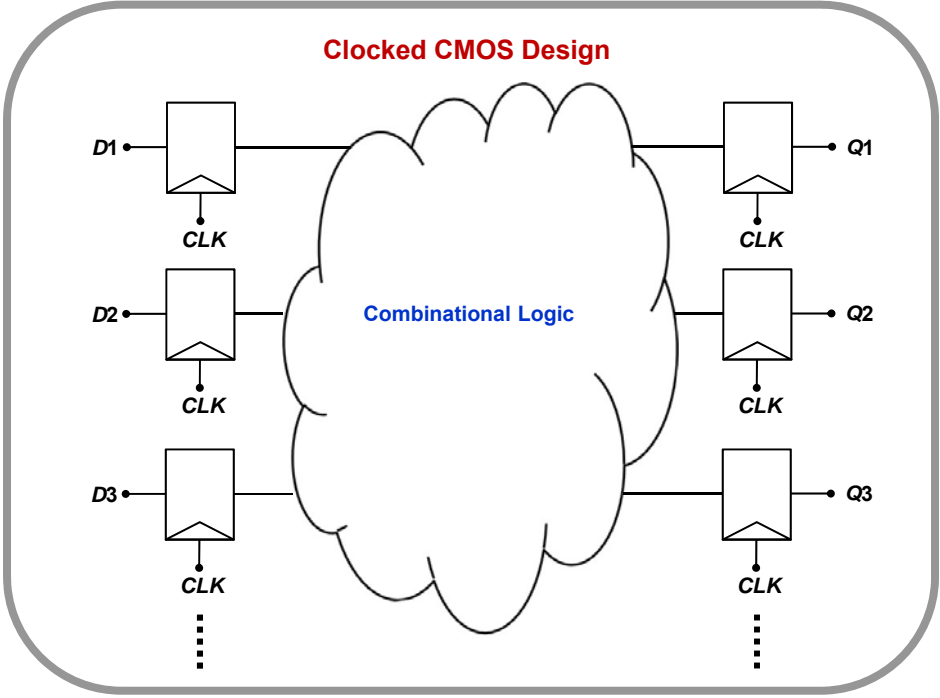


Pipelined CMOS Digital Design

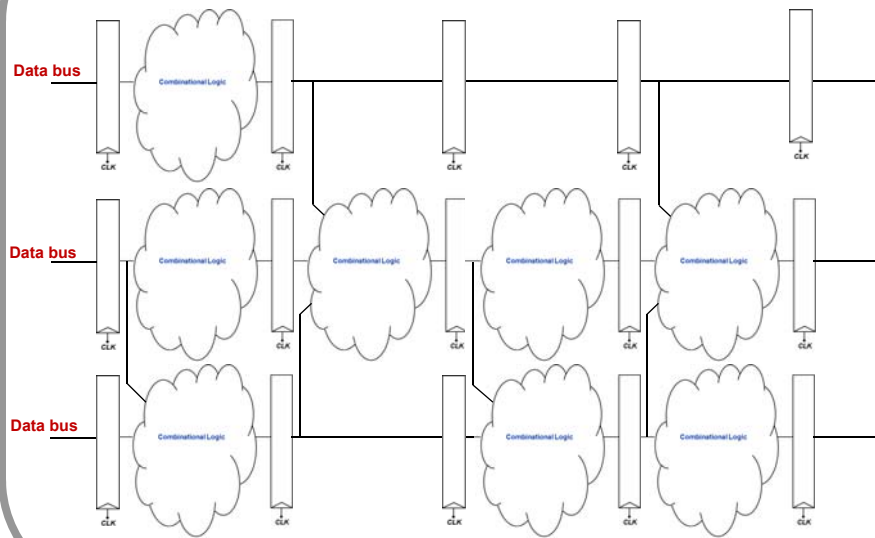


FETs and Charge-Coupled Devices (CCDs)

A 24-MP CCD imaging chip

 


Willard S. Boyle and George E. Smith
(Bell Labs)
(2009 Nobel Prize in Physics)

 MOS Structures and Charge-Coupled Devices (CCDs)




FETs and Charge-Coupled Devices (CCDs)

 

Challenge:

How to get photo-generated charge out of each individual pixel in a simple cost-effective way??

FETs and Charge-Coupled Devices (CCDs)

 

Solution:

Charge-coupled MOS structures can be used as shift-registers to move charge!