
 
 
 
 
 
 
 
 
 
 
 
 
 


CMOS Logic Families

- Many "families" of logic exist beyond Static CMOS


- Comparison of logic families for a 2-input multiplexer

 - Briefly overview
 - pseudo-nMOS
 - differential (CVSL)
 - dynamic/domino
 - complementary pass-gate



nMOS Inverter


- Logic Inverter
- nMOS Inverter

 

x	y = \bar{x}
0	1
1	0

- assume a resistive load to VDD
- nMOS switches pull output low based on inputs


nMOS Inverter

 

 - (a) nMOS is **off**,
- (b) nMOS is **on**

Active loads

- use pMOS transistor in place of resistor
- resistance varies with Gate connection




- Ground \rightarrow always on
- Drain=Output \rightarrow turns off when $V_{out} > V_{DD} - V_{tp}$
 - $V_{SG} = V_{SD}$ so always in saturation
- Vbias \rightarrow can turn Vbias for needed switching characteristics




Pseudo-nMOS


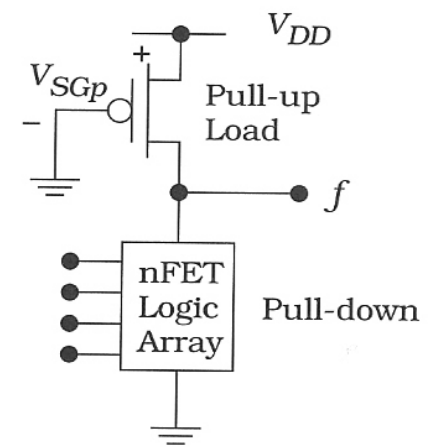
- full nMOS logic array
- replace pMOS array with single pull up transistor
- Ratioed Logic
 - requires proper tx size ratios
- Advantages
 - less load capacitance on input signals
 - faster switching
 - fewer transistors
 - higher circuit density
- Disadvantage
 - pull up is always on
 - significant static power dissipation
 - $V_{OL} > 0$



generic pseudo-nMOS logic gate

 

pseudo-nMOS inverter

 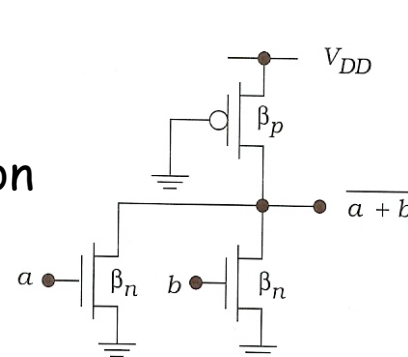

pseudo-nMOS NAND and NOR



Pseudo nMOS DC Operation

- Output High Voltage, V_{OH} (Maximum output)

- occurs when input is low ($V_{in} = 0V$), nMOS is OFF
- pMOS has very small $V_{SD} \rightarrow$ triode operation

$$I_{D2} \cong \mu_p C_{ox} \left(\frac{W}{L}\right)_2 V_{eff-2} V_{SD-2}$$

- pMOS pulls V_{out} to VDD

- $V_{OH} = VDD$

- Output Low Voltage, V_{OL} (Minimum output)



- occurs when input is high ($V_{in} = VDD$)
- both nMOS and pMOS are ON
 - nMOS is "on stronger"; pulls V_{out} low
- as V_{out} goes low, nMOS enters triode
 - continues to sink current from pMOS load

$$V_{OL} = I_{D-2} r_{ds-1} = \frac{1}{2} \frac{\mu_p (V_{DD}/2 + V_{tp})^2 (W/L)_2}{\mu_n (V_{DD} - V_{tn}) (W/L)_1}$$

- $V_{OL} > 0V$ (active load always pulling)

- Logic Swing (max output swing)



- $V_L = V_{OH} - V_{OL} < VDD$

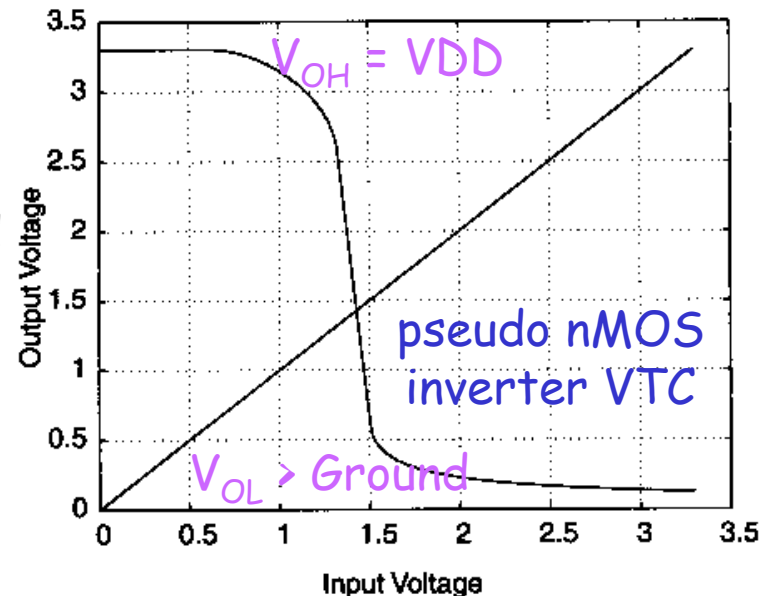 

Pseudo nMOS Transient Analysis

- Rise and Fall Times
 - harder to analyze for pseudo nMOS
 - due to "always on" active load
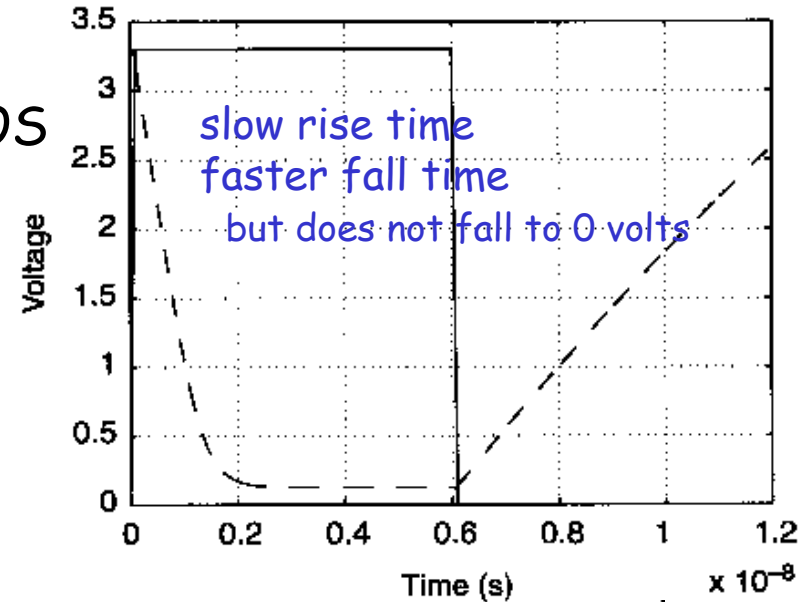 
$$t_{+70\%} = \frac{C_L \Delta V_{out}}{I_{D-2}} = \frac{2C_L 2.3}{\mu_p C_{ox} (W/L)_2 [(V_{DD}/2) + V_{tp}]^2}$$



$$I_{D-1} = \frac{\mu_n C_{ox} (W/L)_1}{2} (V_{DD} - V_{tn})^2$$

$$R_{TR} = \frac{1}{\mu_n C_{ox} (W/L)_1 (V_{DD} - V_{tn})}$$


$$R_{eq} = \frac{V_{DD} - V_{tn}}{\frac{\mu_n C_{ox} (W/L)_1 (V_{DD} - V_{tn})^2}{2}} = \frac{2}{\mu_n C_{ox} (W/L)_1 (V_{DD} - V_{tn})}$$

$$R_{eq} = \frac{2.5}{\mu_n C_{ox} (W/L)_1 (V_{DD} - V_{tn})}$$




Differential Logic

- Cascode Voltage Switch Logic (CVSL)
 - aka, Differential Logic
- Performance advantage of ratioed circuits without the extra power
- Requires complementary inputs
 - produces complementary outputs
- Operation
 - two nMOS arrays
 - one for f , one for \bar{f}
 - cross-coupled load pMOS
 - one path is always active
 - since either f or \bar{f} is always true
 - other path is turned off
 - no static power

 

generic differential logic gate

 


differential AND/NAND gate



Differential Logic


- Advantages of CVSL
 - low load capacitance on inputs
 - no static power consumption
 - automatic complementary functions
- Disadvantages
 - requires complementary inputs
 - more transistors
 - for single function
- Very useful in some circuit blocks where complementary signals are generally needed
 - interesting implementation in adders

 

differential 4-input XOR/XNOR

Dynamic Logic

 - Advantages of ratioed logic without power consumption of pseudo-nMOS or excess tx of differential
- Dynamic operation: output not always valid
- Precharge stage
 - clock-gated pull-up precharges output high
 - logic array disabled
- Evaluation stage
 - precharge pull-up disabled
 - logic array enabled & if true, discharges output



generic dynamic logic gate


 
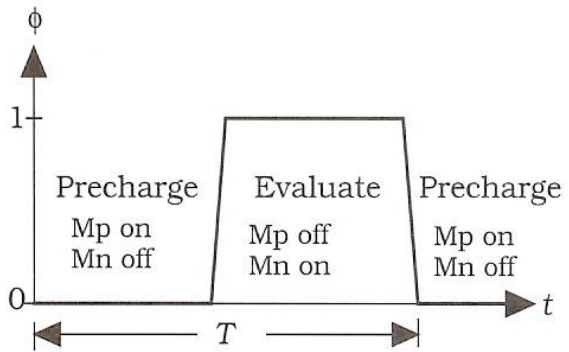
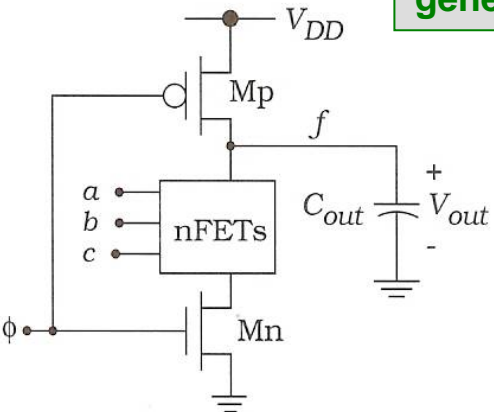
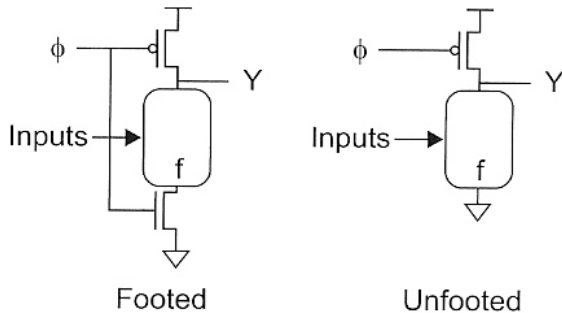
 


FIG 6.21 Comparison of (a) static CMOS, (b) pseudo-nMOS, and (c) dynamic inverters

Dynamic Logic


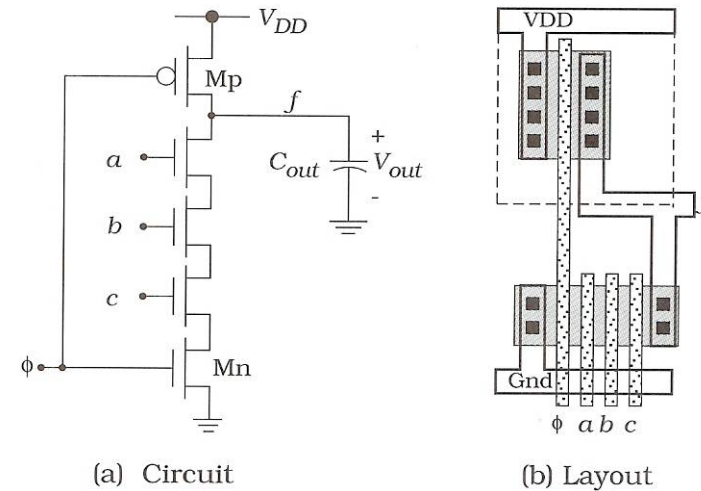
- Example: Footed dynamic NAND3
- Footed vs. Unfooted
 - foot tx ensures nMOS array disabled during precharge





unfooted

footed



Inverter

  

NAND2

  


NOR2

  

Charge Redistribution in Dynamic Logic

- Major potential problem

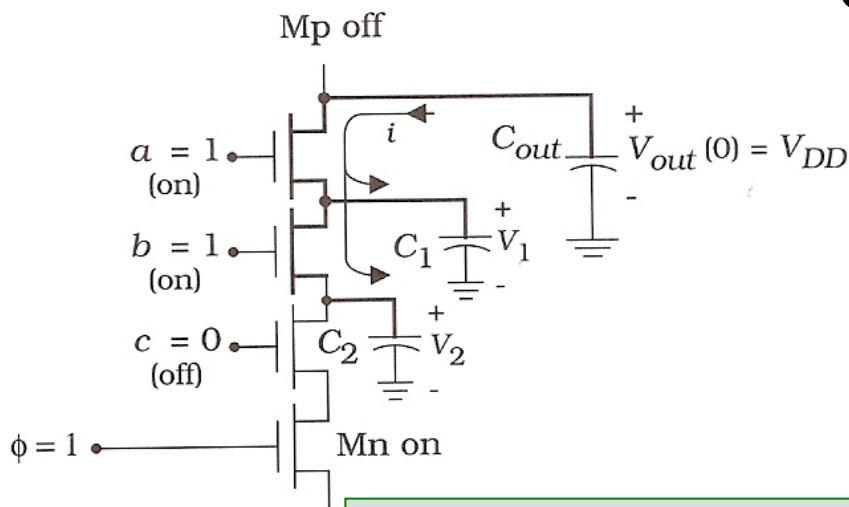
- during evaluation, precharge charge is distributed over parasitic capacitances within the nMOS array
 - causes output to decrease (same charge over larger $C \rightarrow$ less V)
- if the function is not true, output should be HIGH but could be much less than V_{DD}



charge distribution over nMOS parasitics during evaluation

- One possible solution

 
- "keeper" transistor
 - injects charge during evaluation if output should be HIGH
 - keeps output at V_{DD}
- keeper controlled by output_bar
 - on when output is high




Domino Logic

- Dynamic logic can only *drive* an output LOW
 - output HIGH is precharged only with limited drive
- Domino logic adds an inverter buffer at output

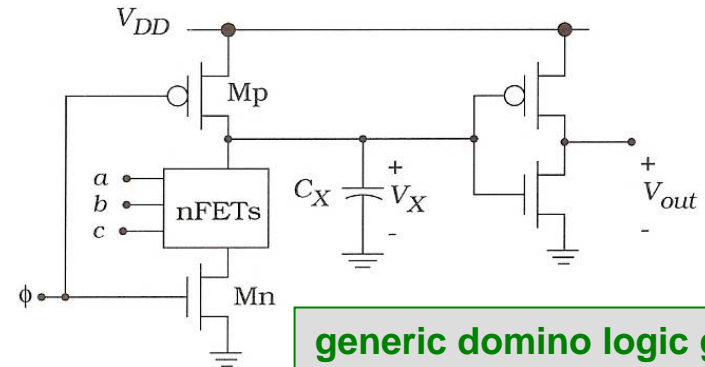
- Cascading domino logic
 - must alter precharge/eval cycles
 - clock each stage on opposite clock phase



generic domino logic gate

 



NP dynamic logic

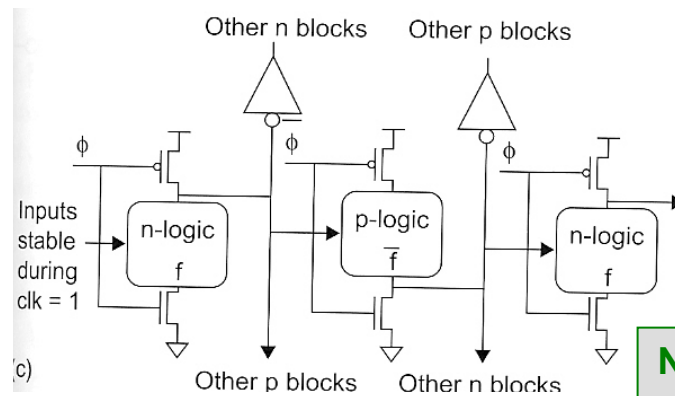

NO RAcE (NORA) domino logic





Pass Transistor (PT) Logic

  

- ❑ Gate is static – a low-impedance path exists to both supply rails under all circumstances
- ❑ N transistors instead of $2N$
- ❑ No static power consumption
- ❑ Ratioless
- ❑ Bidirectional (versus unidirectional)




VTC of PT AND Gate

  

- Pure PT logic is not **regenerative** - the signal gradually degrades after passing through a number of PTs (can fix with static CMOS inverter insertion)





nMOS Only PT Driving an Inverter

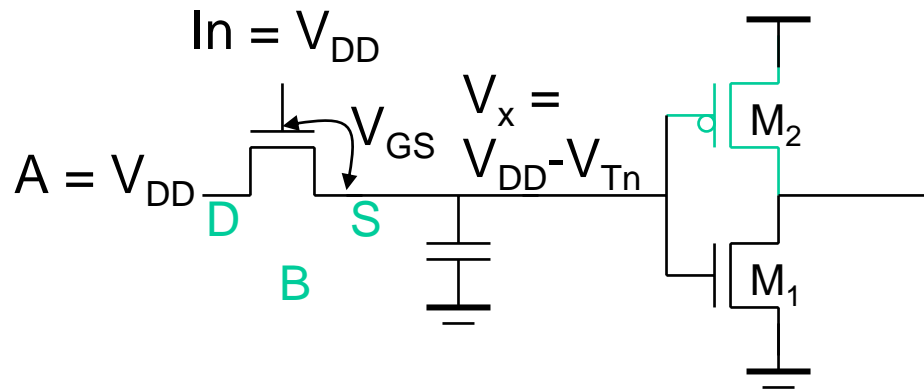

- V_x does not pull up to V_{DD} , but $V_{DD} - V_{Tn}$
- Threshold voltage drop causes static power consumption (M_2 may be weakly conducting forming a path from V_{DD} to GND)
- Notice V_{Tn} increases of pass transistor due to **body effect** (V_{SB})



Voltage Swing of PT Driving an Inverter

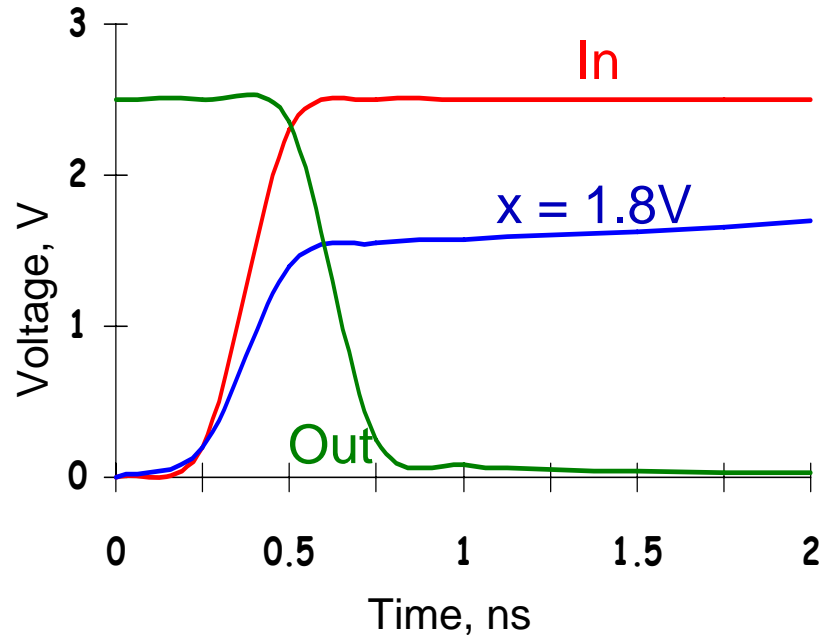 


- **Body effect** - large V_{SB} at x - when pulling high (B is tied to GND and S charged up close to V_{DD})
- So the voltage drop is even worse

$$V_x = V_{DD} - (V_{Tn0} + \gamma(\sqrt{(|2\phi_f| + V_x)} - \sqrt{|2\phi_f|}))$$



TG Full Adder

 

16 Transistors; full swing - transmission gates




Basic CMOS Isolation Structures

- LOCOS -Local Oxidation of Silicon
- STI -Shallow Trench Isolation
- LDD -Lightly-Doped Drain
 - Used to reduce the lateral electric field in the channel
- SOI -Silicon on Insulator
- BiCMOS -Bipolar and CMOS on same chip




LOCOS

 - Isolation between transistor
 - Field Oxide (FOX)
- FOX formed by
 - masking active regions
 - thermal oxidation of non-masked areas
- Self-aligned gate
 - S/D formed after poly gate
 - S/D automatically aligned to gate




Cross section view

 

Layout view


 
Problems with LOCOS

- Device “packing” density limited by “bird’s beak effect of FOX isolation layer.
 - effects the width (W) of the transistor
- Can improve density with Shallow Trench Isolation (STI)




Shallow Trench Isolation (STI)

  - Form Gate and S/D first
- Then isolate devices by
 - etching trench ($\sim 0.4\mu\text{m}$) in substrate between devices
 - filling trench with deposited oxide
- Eliminates the area lost to bird's beak effect of LOCOS
- Well doping and channel implants done later in process via high energy ion implantation





Lightly-Doped Drain (LDD)

 - Create lightly doped regions in S/D near the channel
- Necessary for submicron fabrication
 - reduces the electric field across the channel
 - reduces the velocity of electrons in the channel (hot carrier effect)
 - reduces performance, but allows higher density
- Can be used with any isolation process




Silicon On Insulator (SOI)

  - Buried SiO_2 layer beneath surface of active single-crystal Si substrate
- More expensive, but excellent isolation
 - no leakage current to substrate
 - no latchup
 - high transconductance
 - good subthreshold performance
 - reduced short channel effects
 - radiation immunity



BiCMOS

 


- Advantage
 - both Bipolar and CMOS transistor
- Disadvantage
 - Increased process complexity
 - Reduced density (just no way to make small BJTs)



Scaling Options

 - Constant Voltage (CV)
 - voltage remains constant as feature size is reduced
 - causes electric field in channel to increase
 - decreases performance
 - but, device will fail if electric field gets too large
- Constant Electric Field (CE)
 - scale down voltage with feature size
 - keeps electric field constant
 - maintain good performance
 - but, limit to how low voltage can go



Low Voltage Issues


- Reasons modern/future circuits have lower voltage
 - lower voltage = lower dynamic power: $P_{\text{dyn}} = \alpha C_L V_{\text{DD}}^2 f_{\text{CLK}}$
 - lower voltage required for smaller feature size
 - feature sizes reduced to improve performance/speed
 - smaller features = shorter distances across the channel
 - stronger electric fields in channel
 - poorer performance or device failure
 - » unless voltage is reduced also
- Side effects of reducing voltage
 - reduces current (speed) and increases noise problems
 - as supply voltage decreases, must also reduce threshold voltage
 - otherwise, circuits will not switch correctly
 - reduced threshold voltage = increased subthreshold current
 - increased leakage currents
 - increased static power consumption



Short Channels


- Effective channel length
 - must account for depletion region spreading into the channel
 - more important as channel length gets shorter
 
$$L_{eff} = L(\text{drawn}) - 2L_D - X_d \quad X_d = \sqrt{\left(\frac{2\epsilon_s(V_D - (V_G - V_t))}{qN_A}\right)}$$



- For short channels, roughly measured by $L < 1\mu\text{m}$
 - Source-Substrate and Drain-Substrate junction depletion layer extend noticeably into the channel
 - will reduce the amount of bulk charge, Q_B , in the channel
 - thus reduce the threshold voltage as channel length decreases
 - called the short channel effect

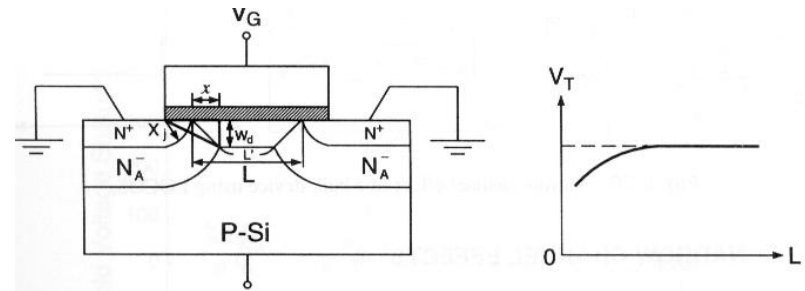- need a new way to calculate Q_B
 - some bulk charge lost to depletion layers



(from Kuo and Lou, p. 43)



Short Channel Effects

- Short channel lengths introduce effects which must be considered
 - in selecting process technologies for a given application
 - in design of circuits
- Short Channel Effects
 - mobility degradation
 - threshold voltage degradation
 - velocity saturation
 - hot carrier effects
- Other effects made worse by short channels
 - leakage currents
 - latch-up
 - subthreshold operation




Velocity Saturation

- Charge Velocity
 - $v_n = \mu E$, μ is mobility and E is electric field
 - valid for small E , as assumed in previous I-V equations
- Velocity Saturation
 - if $E > E_c$ (critical field level), velocity will reach a maximum
 - v_{sat} = saturation velocity, velocity at $E > E_c$
- Short Channel Devices
 - lateral field near drain is very high \rightarrow charge can experience velocity saturation
 - even at V_{DS} voltages before pinchoff occurs
 - here
$$I_D = \frac{\mu_n C_{OX}}{2} \frac{W}{L} \left[2(V_{GS} - V_t) V'_{DSAT} - V_{DSAT}^2 \right]$$
 - where V'_{DSAT} is the drain-source voltage which generates the critical electric field, E_c
 - valid when $V'_{DSAT} < V_{GS} - V_t$ (when velocity saturation occurs before channel pinchoff)
- Velocity Overshoot
 - with very short channels, carriers can travel faster than saturation velocity
 - occurs in **deep submicron devices** with channel lengths less than $0.1\mu\text{m}$
 - the velocity saturation equation above becomes inaccurate for very small channel lengths and more detailed models are required.



Hot Carrier Effects

- High E-field in channel will accelerate charge carriers
- Accelerated carriers can start colliding with the substrate atoms
 - generates electron-hole pairs during the collision
 - these will be accelerated, collide with substrate atoms and form even more electron-hole pairs: called **impact ionization**
- Impact ionization can lead to
 - avalanche breakdown within the device
 - large substrate currents
 - degradation of the oxide
 - high energy electrons collide with gate oxide and become imbedded
 - causes a shift in threshold voltage
 - considered catastrophic effect
 - leads to unstable performance

 

Hot Carrier Effects II

- Supply voltages dropping slower than channel length
 - as a result electric fields in channel continue to increase.
- Hot carrier effect must be considered for submicron devices
 - may potentially be a limiting factor in how far devices can be scaled down
 - unless we can reduce electric fields in channel
- To reduce hot carrier effects, increase channel length
- pMOS devices may be better overall for deep submicron circuits
 - hole mobility is closer to electron mobility under high electric fields which occur in submicron devices
 - hot carrier effects are worse in nMOS devices than pMOS






Leakage Currents

- All p-n junctions in the MOSFET structure will have a reverse bias leakage current
- Leakage Current, I_{lk}
 - where
$$I_{lk} = \frac{qA_j n_i}{2\tau_0} x_d$$
 - A_j is the junction area
 - n_i is the intrinsic carrier concentration
 - τ_0 is the effective minority carrier lifetime
 - x_d is the depletion layer thickness, $x_d = f(V_R)$
- Undesired effects of leakage currents
 - add to unwanted static power consumption
 - limit the charge storage time of dynamic circuits
- Factors in leakage
 - n_i is a strong function of temperature (doubles every 11°C)
 - significant in high power density circuit that generate heat



Latch-Up


- Latch-up is a very real, very important factor in circuit design that must be accounted for
- Due to (relatively) large current in substrate or n-well
 - create voltage drops across the resistive substrate/well
 - most common during large power/ground current spikes
 - turns on parasitic BJT devices, **effectively shorting power & ground**
 - often results in device failure with fused-open wire bonds or interconnects
 - **hot carrier effects** can also result in latch-up
 - latch-up very important for short channel devices
- **Avoid latch-up** by
 - including as many substrate/well contacts as possible
 - limiting the maximum supply current on the chip

  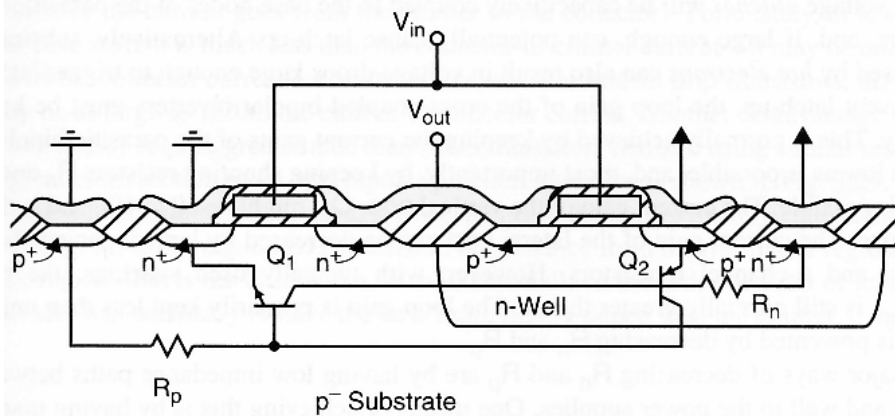

Subthreshold Operation

- **Weak inversion**, when $V_G > 0$ but $< V_t$
 - some channel charge and the drain current is small but not zero.
 - referred to as the *subthreshold region*
- Subthreshold operation
 - the drain current is an exponential function of the gate voltage
 - the current increases sharply with V_{GS} until the device turns on
 
$$I_D = I_{D0} \frac{W}{L} e^{(qV_{GS} / nkT)}$$



- where
 - I_{D0} is a process dependent constant, typically $\sim 20\text{nA}$
 - n is a process dependent constant, typically $n=1.5$
 - $kT/q = 26\text{mV}$ at room temperature
- Channel Length
 - subthreshold currents are much larger in short channel devices
 - due to high e-fields at the drain reducing effective channel length
 - effect can be reduced by using **lightly-doped drain** regions under the gate



Subthreshold Operation

- Analog Circuits
 - subthreshold operation is exploited for low power operation in low frequency applications
- Digital Circuits
 - subthreshold current serves as undesired leakage current
 - want to quickly transition in/out of subthreshold
- How can we decrease subthreshold currents and speed transition?
 - thinner gate oxide = faster transition
 - same as current technology trend
 - lighter substrate doping = faster transition
 - opposite of current technology trend
 - higher doping needed for better short channel performance
 - faster transition = less subthreshold leakage current = lower power
 - process must be chosen to match the speed, power, and performance spec's for each circuit
 - what is best for DRAM is not best for microprocessors, etc.

$$I_D = I_{D0} \frac{W}{L} e^{(qV_{GS} / nkT)}$$

