
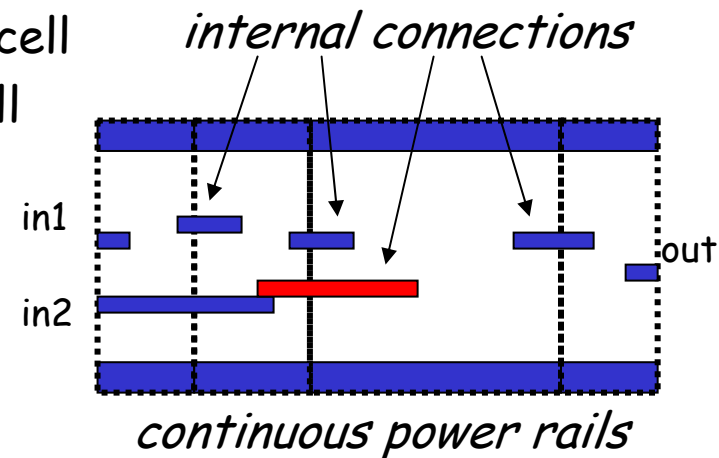

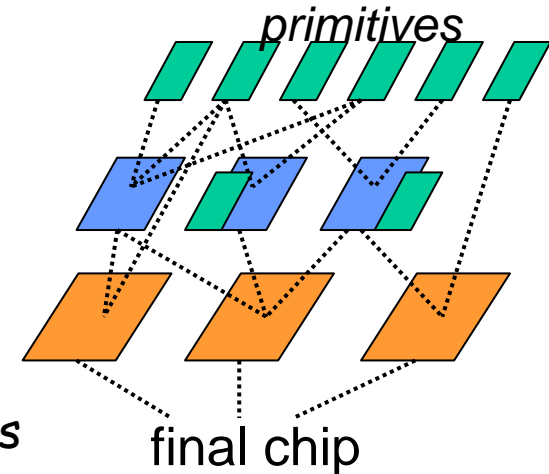
# Layout of Multiple Cells

- Beyond the primitive tier
  - add instances of primitives
  - add additional transistors if necessary
    - add substrate/well contacts (plugs)
  - add additional polygons where needed
    - add metal-1 to make VDD/GND rail continuous
    - add n-well to avoid breaks in n-wells that violate rules
    - add interconnects and contacts to make signal interconnections
  - connect signals within cell boundary
    - if possible, keep internal signal within cell
    - ensure cell I/Os accessible outside cell
  - minimize layout area
    - avoid unnecessary gaps between cells
  - pass design rule check
    - ALWAYS, at every cell level



# Multi-Instance Cells

- Cell Placement




- pack cells side-by-side
  - abut cells and align power rails
- avoid gaps between cells
  - unless needed for signal connections

- Signal Routing

- make internal connections using poly and metal-1, if possible
- use jumpers outside rails only when necessary
  - jump up/down using poly (short trace) or metal-2 (if long trace)
    - poly for traces close to cell
    - metal-2 for traces far from cell
  - leave room for widened power rails

- Power Routing

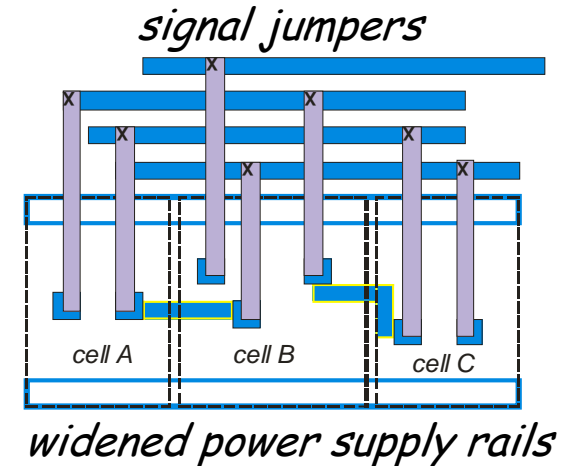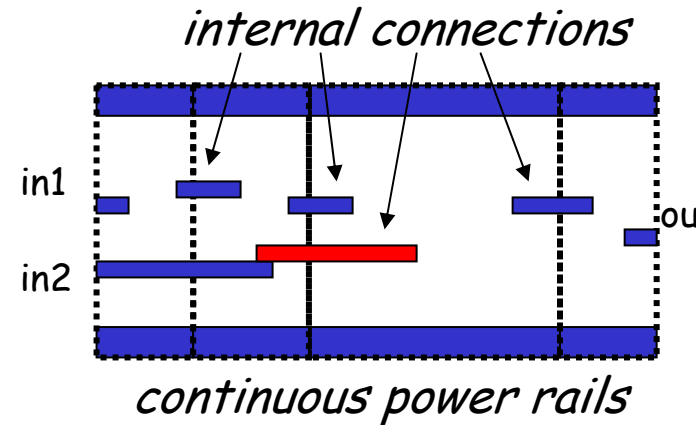 
- more cells mean more supply current
- widen power supply rail for long cascades of cells


 
# High-Level Layout

- Cell Placement

- cascade cells with same pitch
- stack cascaded cells





- Cell Orientation

- maintain orientation when stacking
  - signal jumpers between stacks


or

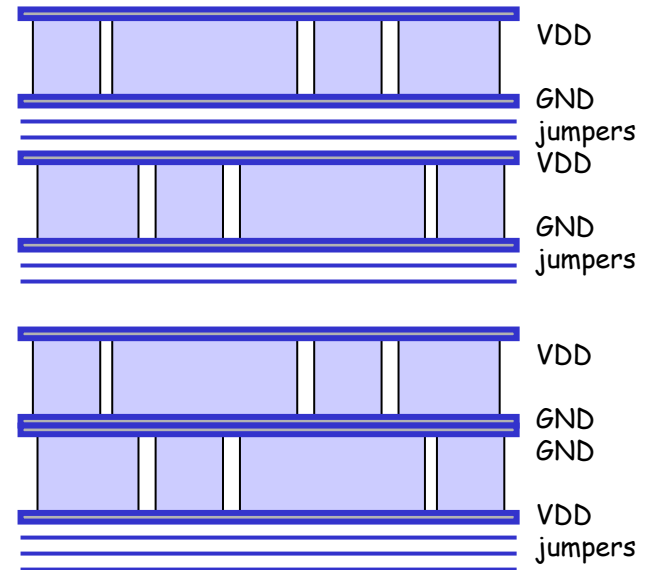 - alternate orientation
  - signal jumpers on top and/or bottom



- Power Routing

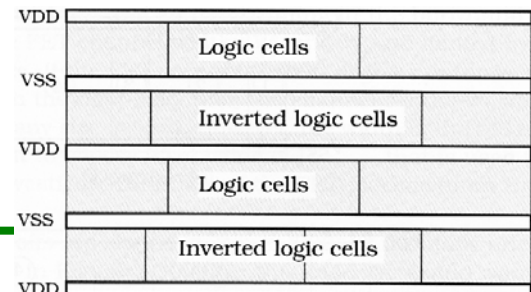- widen supply rails for long cascades
- connect rails outside cell cascades
  - example follows



# Metal Routing Strategy

- General Rules
  - use lowest level interconnects possible
    - if process has less than ~3 metal layers
      - try to route a cell cascade using only poly and metal-1
    - if process has more than ~3 metals
      - route cell cascade using metal-1 and metal-2, avoid using poly
  - alternate directions for each interconnect
    - e.g., metal1 horizontally, metal2 vertically, metal 3 horizontally, etc.

## • Example

### poly


- within primitives
- local interconnects
  - only if <3 metal layers

### metal1

- within primitives
- power rails
- horizontal jumpers
 
### metal2

- vertical traces between stacked cascades





- Note: new process technologies have specially defined metal layers
  - e.g. metal\_5 might be dedicated to VDD routing


  
# Power Routing


- Power Rails for Combined Cells

- join adjacent cells with continuous power rails
- keep power rails wide enough for long power traces
  - more cells  $\rightarrow$  more current  $\rightarrow$  need traces with lower resistance
- power tree concept
  - power enters chip on one pin
  - must "branch" across chip
  - traces should be thicker near pin and narrow into smaller cells




*branching of power traces across a chip, from thick lines (chip) to thin lines (cell)*

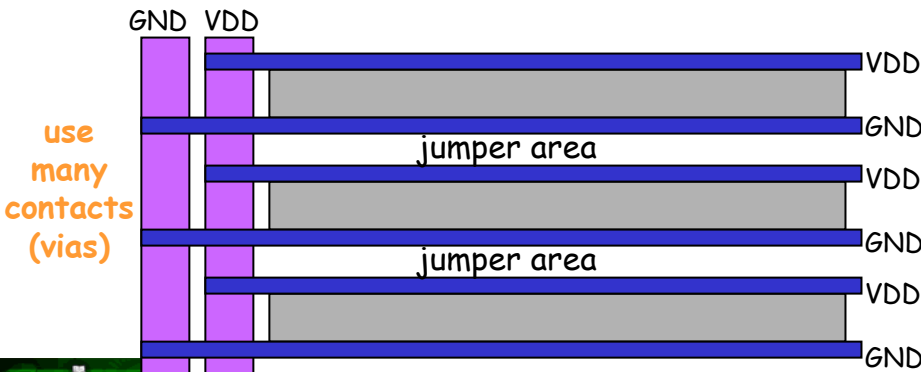- Connecting rails in stacked cell cascades



zooming out...

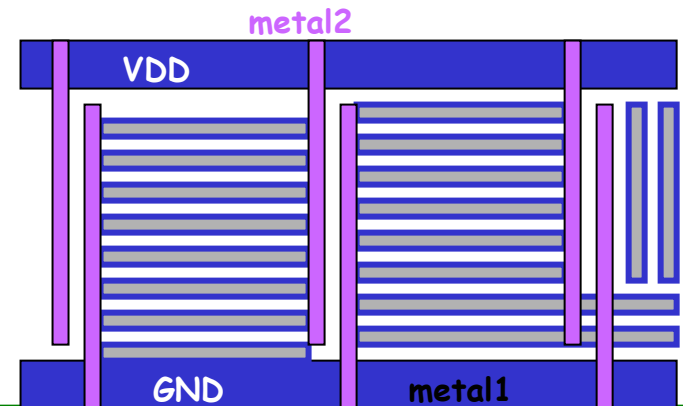


# Signal Buffers

- Loading and Fan-Out

- gate input capacitance
  - $C_G = 2C_{ox}WL$  (1 for pMOS 1 for nMOS)
- load capacitance
  - standard gate designed to drive a load of 3 gates  $\rightarrow C_L = 3C_G$
- output drive capability
  - $I \propto W$ , increase  $W$  for more output signal drive
  - increasing  $W$  increase  $C_G$

- Buffers


 
- single stage inverter buffers
  - isolate internal signals from output load
- scaled inverter buffers
  - add drive strength to a signal
  - inverters with larger than minimum tx
    - typically increase by 3x at with each stage




# Transmission Gate Multiplexers

- Logical Function of a Multiplexor
  - select one output from multiple inputs
  - 2:1 MUX logic


$$f = p_0 \cdot \bar{s} + p_1 \cdot s$$

  

 - CMOS Multiplexors
  - generally formed using switch logic rather than static
- 2:1 MUX using Transmission Gates




- 4:1 MUX using 2:1 MUXs

 

# Pass-gate Multiplexors

- 2:1 MUX using pass-gates

- nMOS switch circuit

 



- 4:1 MUX using pass-gates

- Pass-gate MUX with rail-to-rail output

- add full pMOS network
  - see Figure 11.7 in textbook

- Multi-bit MUXs

- use parallel single-bit MUXs

 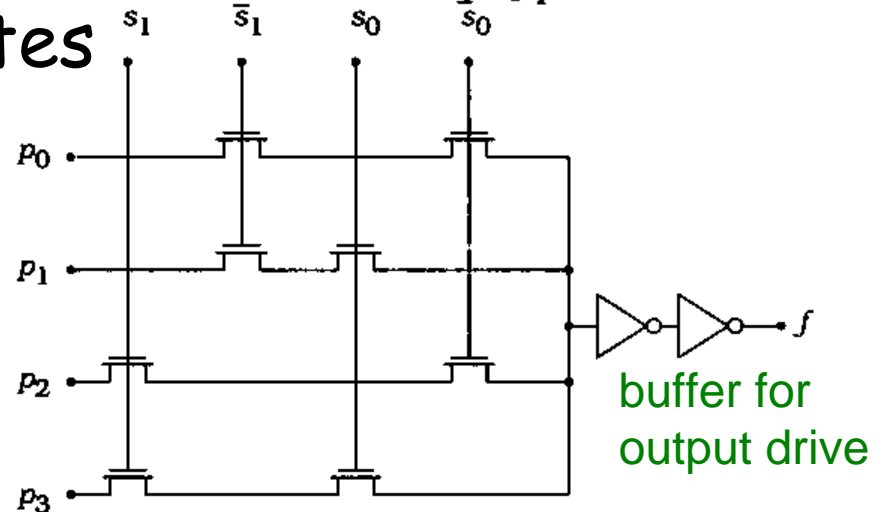



# Binary Decoders

- Decoder Basic Function

- $n$  bits can be decoded into  $m$  values
  - max  $m$  is  $2^n$
- decoded values are active only one at a time
  - active high: only selected value is logic 1
  - active low: only selected value is logic 0

$n$  select bits decode into  $2^n$  outputs values

- Example: 2/4 (2-to-4) Decoder

- 2 control bits decoded into 4 values
  - truth table
  - equations

$$d_0 = \overline{s_1} \cdot \overline{s_0} = \overline{s_1 + s_0} \qquad d_2 = s_1 \cdot \overline{s_0} = \overline{\overline{s_1 + s_0}}$$

$$d_1 = \overline{s_1} \cdot s_0 = \overline{\overline{s_1 + s_0}} \qquad d_3 = s_1 \cdot s_0 = \overline{\overline{\overline{s_1 + s_0}}}$$

- active high decoder equations require NOR operation

control inputs      active high decoded outputs

$s_1$	$s_0$	$d_0$	$d_1$	$d_2$	$d_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

control inputs select one active output




# CMOS Decoder Circuits


- 2/4 Active High Decoder

$s_1$	$s_0$	$d_0$	$d_1$	$d_2$	$d_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Truth Table

 

Symbol

 


NOR2 Circuit  
active high  
2/4 decoder

- 2/4 Active Low Decoder


- implemented with NAND gates

$s_1$	$s_0$	$d_0$	$d_1$	$d_2$	$d_3$
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

Truth Table

 

Symbol

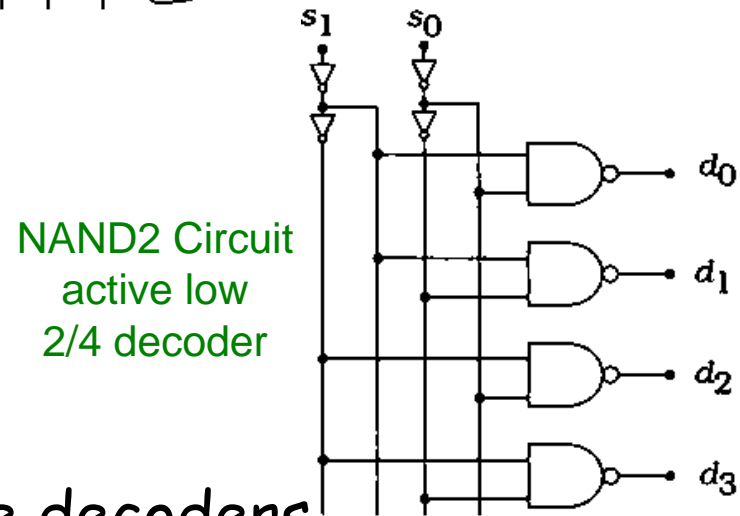

NAND2 Circuit  
active low  
2/4 decoder

- Similar approach for higher-value decoders

3/8 decoder requires 3-input gates, higher values get complex




# Transmission Gate Decoders

- EXAMPLE: 3/8 Active-High Decoder
  - each output connected to VDD through 3 transmission gates
  - TG selects set to turn on only one of the 8 possible combinations of the 3-bit select


s2	s1	s0	d7	d6	d5	d4	d3	d2	d1	d0
0	0	0								1
0	0	1							1	
0	1	0						1		
0	1	1					1			
1	0	0				1				
1	0	1			1					
1	1	0		1						
1	1	1	1							

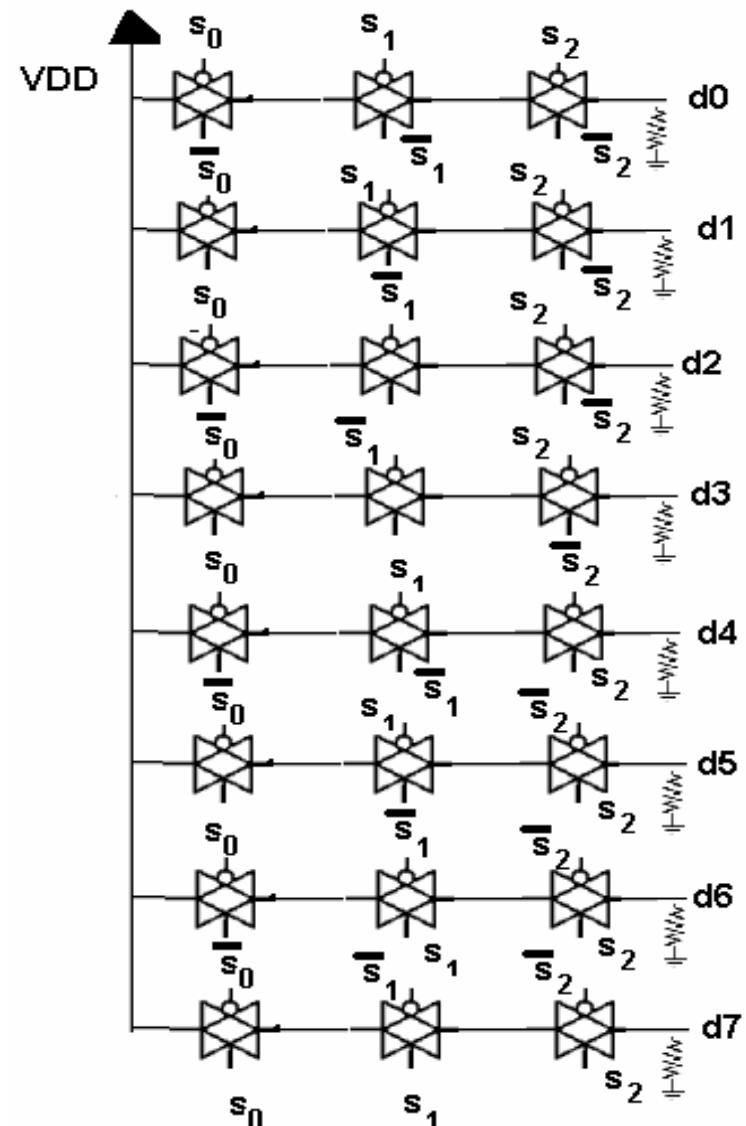- What do the resistors at output do?
- What is the signal value at the unselected outputs?



 
# Magnitude Comparators

- Often need to compare the value of 2 n-bit numbers
  - EQUAL if values are the same
  - GREATER THAN if a is greater than b
  - LESS THAN if b is greater than a
- Equality:  $a\_EQ\_b$ , can be generated by XNOR operation
  - $a = b$  iff  $a \text{ XNOR } b = 1$  for each binary digit
    - example: 4b equality comparator using XNOR
  - also,  $a=b$  if  $a > b = 0$  and  $a < b = 0$  for each binary digit
- Greater/Less Than, by bit-by-bit comparison



4b Equality Circuit

 

4b GT, LT Logic


Condition	GT	LT
$a > b$	1	0
$a < b$	0	1
$a = b$	0	0

note: can get Equal from GT, LT circuit


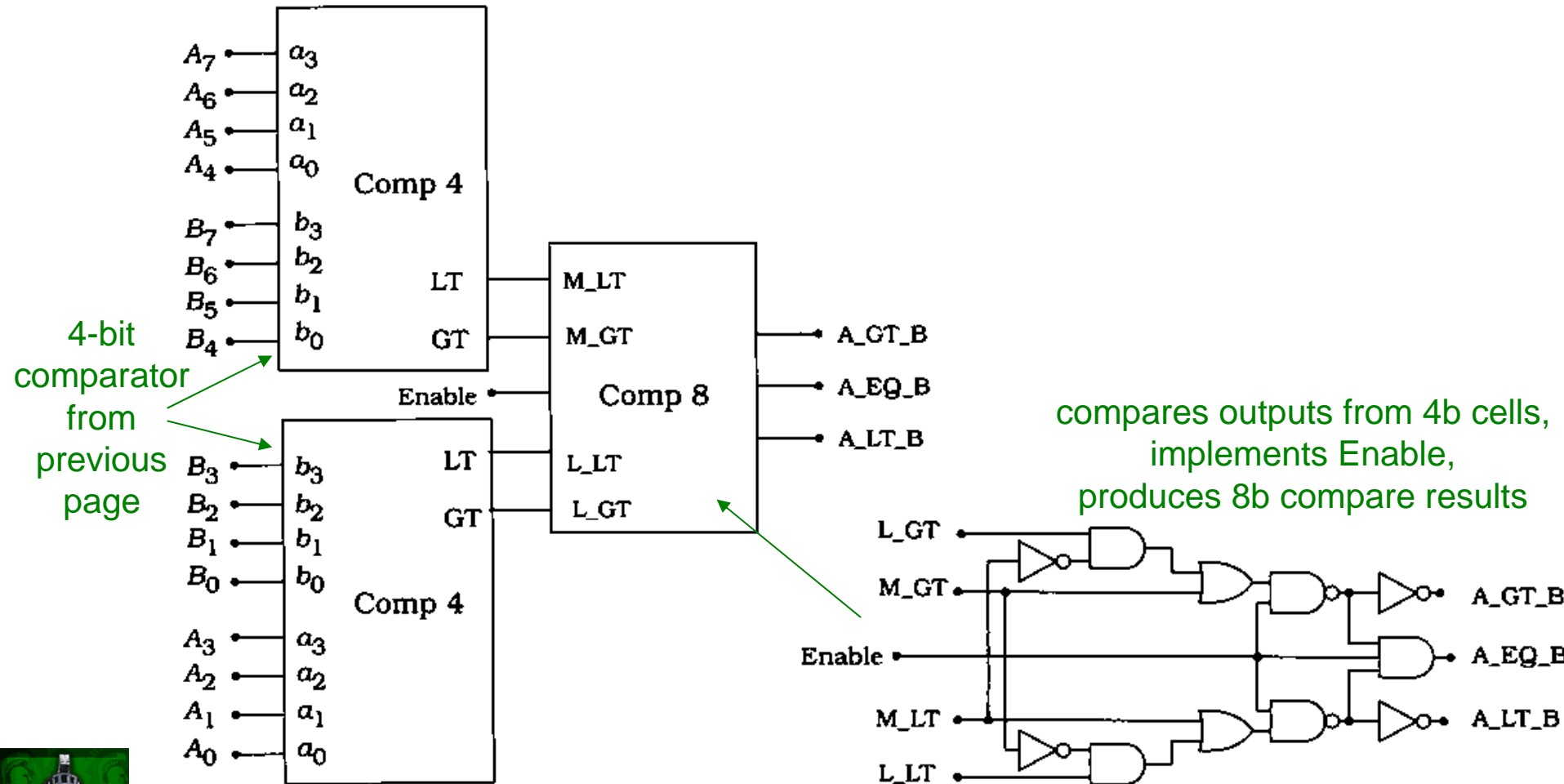
# Combined Comparator Circuits

- 8b Magnitude Comparator with Output Enable
  - generates, EQ (equal), GT (greater than), LT (less than)



# Priority Encoders

- Priority Encoders generates an encoded result showing
  - IF a binary number has a logic 1 in any bit
  - WHERE the most significant logic 1 occurs
- Output is an encoded value of the location of the most significant '1'
- Example: 8b priority encoder

$d_7$	$d_6$	$d_5$	$d_4$	$d_3$	$d_2$	$d_1$	$d_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	0	0	1	1	0	0	0
0	0	0	0	0	0	1	-	1	0	0	1
0	0	0	0	0	1	-	-	1	0	1	0
0	0	0	0	1	-	-	-	1	0	1	1
0	0	0	1	-	-	-	-	1	1	0	0
0	0	1	-	-	-	-	-	1	1	0	1
0	1	-	-	-	-	-	-	1	1	1	0
1	-	-	-	-	-	-	-	1	1	1	1
0	0	0	0	0	0	0	0	0	0	0	0

assign  $d_7$  highest priority,  
 $d_0$  lowest  
 $Q_2$ - $Q_0$  encode the value of  
 the highest priority 1  
 $Q_3$  is high if any bit in  $d$  is logic 1

- Outputs can be constructed from the truth table
  - see textbook for illustrations of CMOS logic



# Data Latches

- Latch Function



- store a data value
  - non-volatile; will not lose value over time
- often incorporated in static memory
- building block for a master-slave flip flop

Latches also improve signal noise immunity; feedback forces signal to hold value and filters noise

- Static CMOS Digital Latch


- most common structure
  - cross-coupled inverters, in positive feedback arrangement
- circuit forces itself to maintain data value
  - inverter *a* outputs a 1 causing inverter *b* to output a 0
  - or, inverter *a* outputs a 0 causing inverter *b* to output a 1

Bistable circuit

  

 
# D-Latch Logic Circuit


- Accessing Latch to Set Value
  - apply input D to set latched value
- NOR D-Latch
  - uses NOR cells to create latch function




**Transistor-Level Circuit**

 

 - D-Latch with Enable
  - En selects if output
    - set by input, D
    - or from internal feedback



(a) Symbol

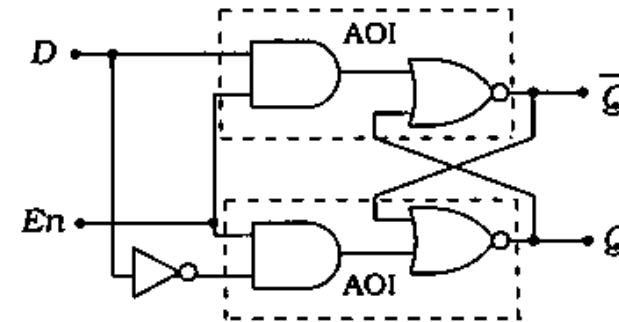

(b) Logic diagram

- Different structures used in VLSI





 
# CMOS VLSI Clocked Latches


- Clocked (enable) Latch using TGs

- can use TGs to determine
  - if latch sees D
    - $C = 1 \Rightarrow Q' = D'$ , set data mode
  - or if positive feedback is applied
    - $C = 0 \Rightarrow Q' = Q'$ , hold data mode





- Reducing Transistor Count

 - Single TG D-Latch
  - input must overdrive feedback signal
    - must use weak feedback inverter
  - useful when chip area is critical
    - but input signal must be strong




- Pass-gate D-Latch

  - replace TG with nMOS Pass-gate
- very common VLSI latch circuit


 
# Flip Flop Basics

- storage element for **synchronous** circuits
  - save logic state at each clock cycle
- 1 or 2 signal inputs and a **clock**
- differential outputs, Q and Q'
  - output changes on rising (or falling) clock edge
  - output held until next rising (or falling) clock edge
- optional **asynchronous set** and/or **reset**
  - regardless of clock state, output set (1) or reset (0)
- typically **master-slave** circuit using 2 cascaded latches
- types include
  - JK
  - T (toggle)
  - SR (set-reset)
  - D -most common for ICs




Flip-flop symbol (SR) for rising and falling edge clocks



# Types of Flip Flops

- D-type (DFF)

D	$Q_{n+1}$
0	0
1	1

 


NOTE: Circuit based on standard logic gates is typically much larger than possible with a reduced CMOS circuit

- SR-type


same as D if  $S=D$  and  $R=D'$

S	R	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	Indeterminate

 


- JK-type

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\bar{Q}_n$

 
 
# JK and T Flip Flops from DFF

- D-Flip Flop can be used to create most other FF types
- Can construct a JK FF from a DFF



J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\bar{Q}_n$

- T-type (toggle) FF can be constructed from a JK FF
  - $T=1$ 
    - output changes state on each clock cycle
  - $T=0$ 
    - hold output to previous value
  - form from JK by connecting J and K inputs together as T



T	$Q_{n+1}$
0	$Q_n$
1	$\bar{Q}_n$

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\bar{Q}_n$


 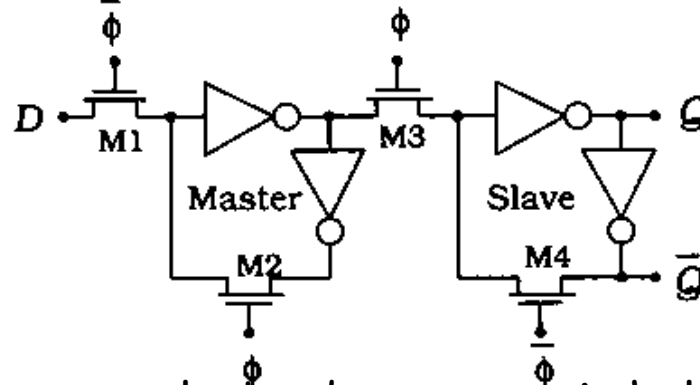
# Master-Slave D Flip Flop

- D-type master-slave flip flop is the most common in VLSI
- Master-Slave Concept
  - cascade 2 latches clocked on opposite clock phases
    - $\phi = 1, \bar{\phi} = 0$ : D passes to master, slave holds previous value
    - $\phi = 0, \bar{\phi} = 1$ : D is blocked from master, master holds value and passes value to slave



- Triggering
  - Output only changes on clock edge; output is held when clock is at a level value (0 or 1)
  - Positive Edge
    - output changes only on rising edge of clock
  - Negative Edge
    - output changes only on falling edge of clock






# Set/Reset Flip Flops

- Asynchronous Set and Reset
  - Asynchronous = not based/linked to clock signal
  - Typically negative logic (0=active, 1=inactive)
  - **Set**: forces Q to logic 1
  - **Reset**: forces Q to logic 0

- Logic Diagrams

- DFFR
  - with Reset (clear)
- DFFRS
  - with Reset (clear) and Set


Alternate logic structure

 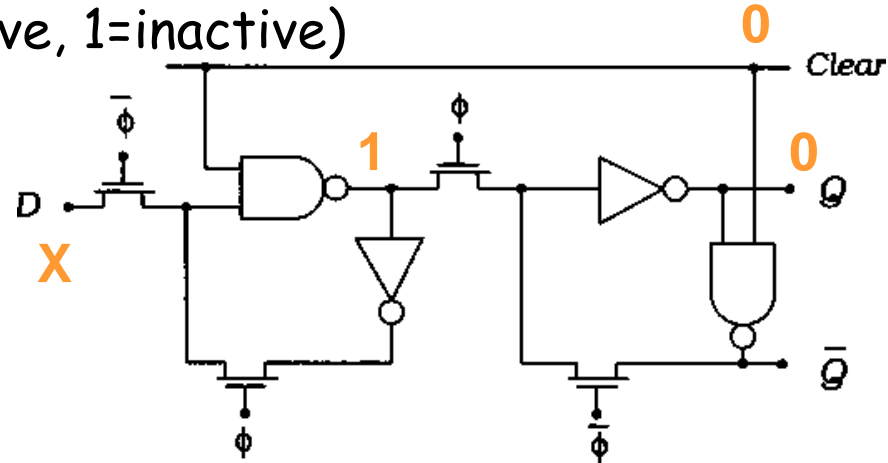 
 
# Buffering in Flip Flops

- What is a buffer?


- inverter buffers
  - isolate output load from internal signals
- scaled inverter buffers
  - add drive strength to a signal
  - inverters with larger than minimum tx
    - typically increase by 3x at with each stage



- Inter-cell Buffering


- Clock
  - so each flip flop provide only  $1 C_G$  load on input CLK
- Output
  - so load at output won't affect internal operation of the cell
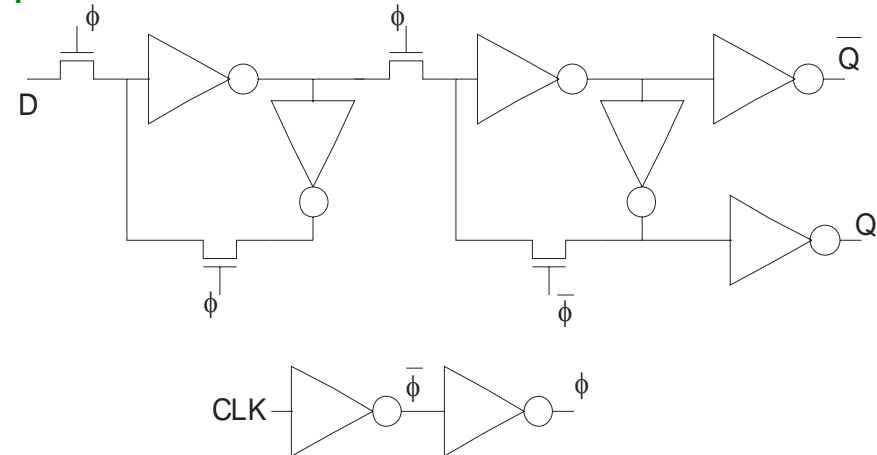
## Example: Buffers in the Lab 7 DFF cell


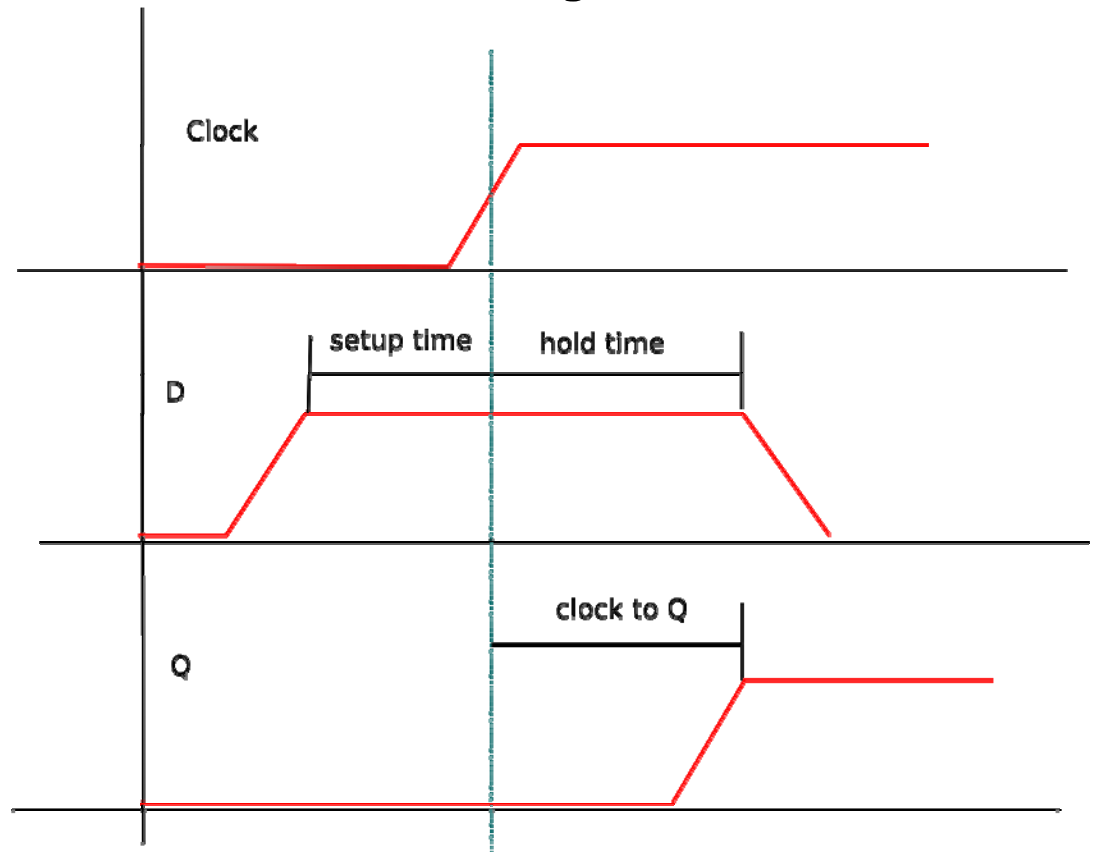
# Characterizing Flip Flop Timing


- **Setup Time:**  $t_{su}$  - Time D must remain stable before the clock changes
- **Hold Time:**  $t_h$  - Time D must remain stable after the clock changes
- **Clock to Q Time:**  $t_{c2q}$  - Time from the clock edge until the correct value appears at Q




 
# Analyzing DFF Timing

- Setup
  - When  $\phi$  is low D must propagate through both master inverters, if clock changes before then the master may switch
  - $t_{su} = t_{M1} + t_{I1} + t_{I2}$
- Hold
  - As soon as  $\phi$  is goes high, D is cutoff
  - $t_h = 0$
- Clock to Q
  - For both outputs to be valid must wait for both slave inverters to change.
  - $t_{c2Q} = t_{M3} + t_{I2} + t_{I3}$




**Different types of flip flops exhibit different timing characteristics**


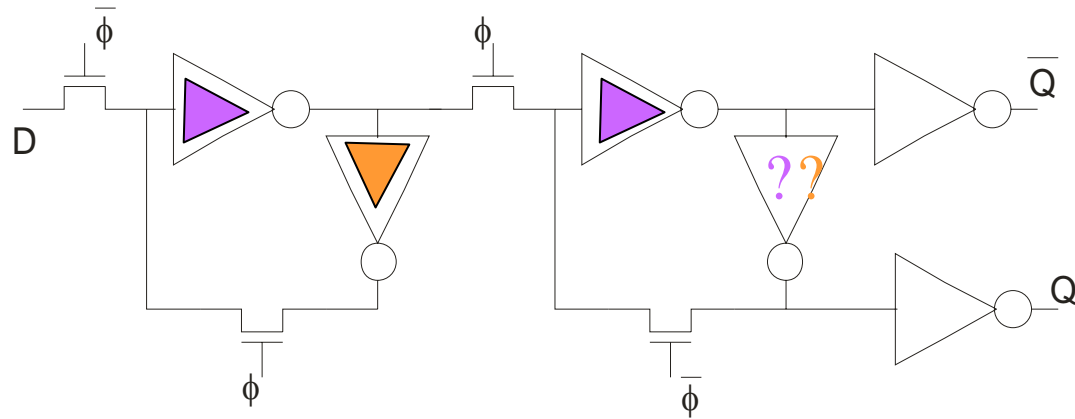
# Transistor Sizing in Flip Flops

- All Minimum-Size Tx Flip Flops
  - will not be optimized for speed
  - might have some output glitches
  - but much more simple to lay out



- Size Considerations
  - varies widely with chosen FF design
  - feedback INV can be weak
  - tx in direct path to signal output should be larger
  - switches -typically minimum sized to reduce noise



# Load Control in Flip Flops





- To mask (block) clocking (loading) of the FF, a load control can be added

- load control allows new data to be loaded or blocks the clock thereby stopping new data from loading


- Load Controlled FF

- Load = 1, data passed
- Load = 0, data blocked

- Alternative Design

   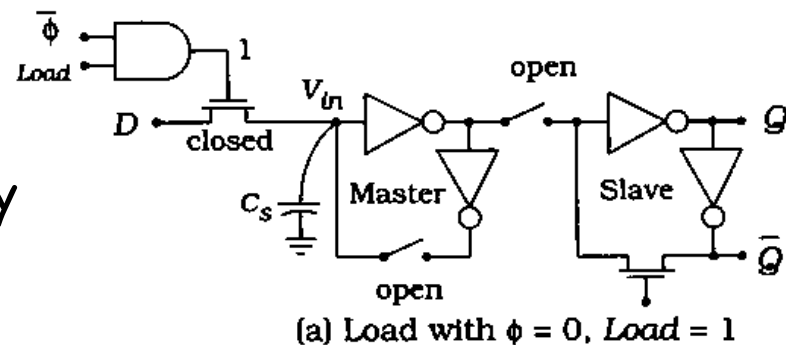

(a) Wiring diagram

 


(b) Symbol



 
# Tri-State Circuits

- covered in Section 9.3 in textbook
- Tri-State = circuit with 3 output states
  - high, low, high impedance (Z)
- High Impedance State
  - output disconnected from power or ground
  - open circuit, with impedance of a MOSFET in OFF state
- Tri-State Inverter
  - Enable signal, enable/disables output drive



En	f
0	Z
1	$\overline{\text{Data}}$


- CMOS implementation

 
 
# Advanced Latches and Flip Flops


- $C^2MOS$  Inverter

- $C^2MOS$  = clocked CMOS
- inverter where input can be enabled
  - $\Phi = 0$ , out =  $D'$
  - $\Phi = 1$ , out = floating




- $C^2MOS$  Static Latch

 - merge TGs into latch design
- $C^2MOS$  inverter input stage
  - passes inverted input when  $\Phi = 0$
  - static inverter sets  $Q = D$
- $C^2MOS$  inverter feedback
  - provides feedback when  $\Phi = 1$
- Either input of feedback is active
  - not both at the same time



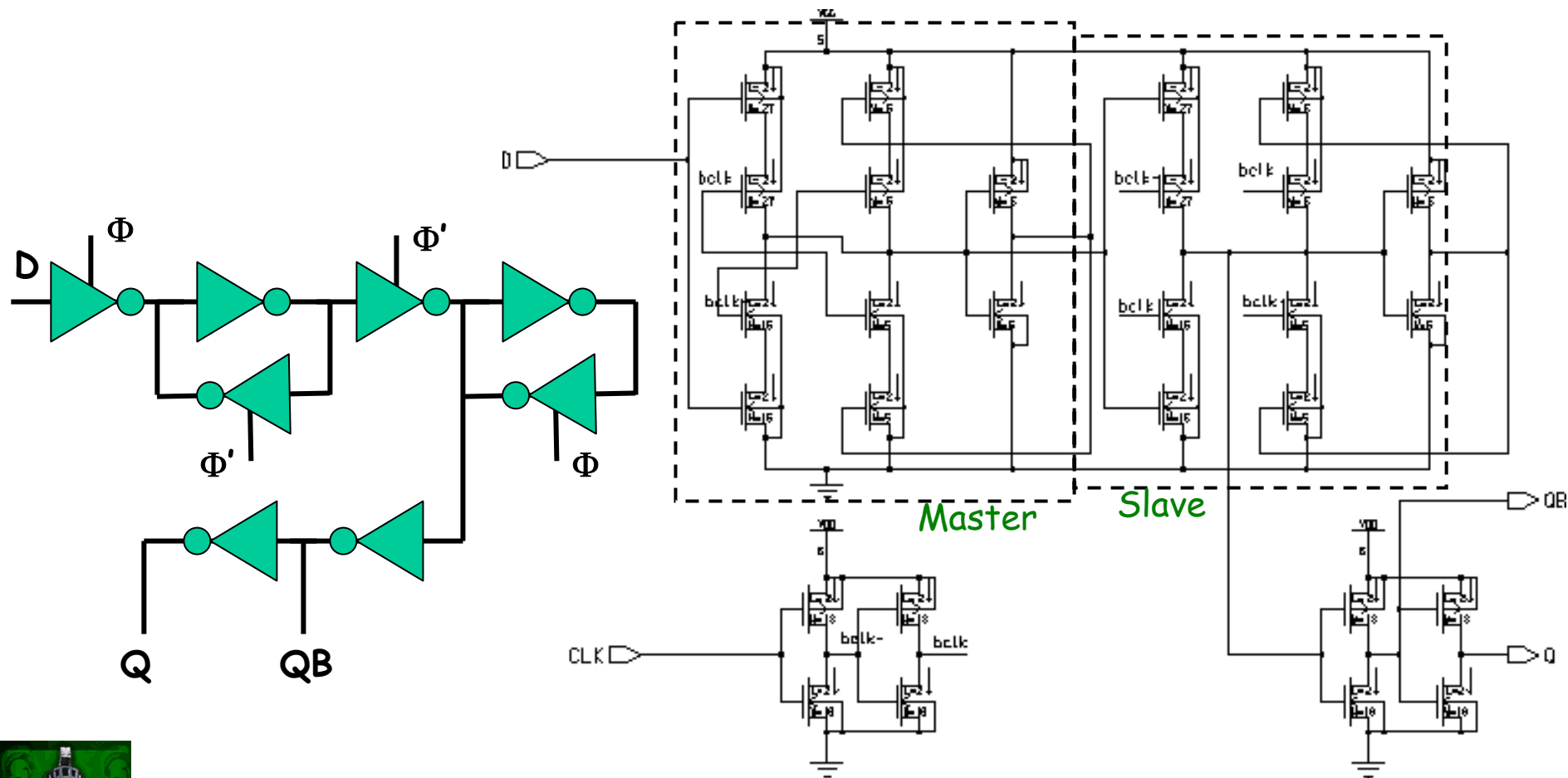
# C<sup>2</sup>MOS D Flip Flop

- Cascade 2 C<sup>2</sup>MOS Latches
  - switch clock phases of master and slave blocks



 
# Discussion of DFF Timing

- Why is output propagation delay different for  $D=1$  and  $D=0$ ?
  - propagation delay in DFF = time between clock edge and Q change
  - delay set by transitions in the slave (second) stage
    - master stage can be ignored when output changes
  - output changes when  $\Phi$  goes high






positive-edge triggered master-slave DFF using bistable circuits with pass gates

 - $D=1 \rightarrow x=0$ 
  - $V_{GS} = VDD$ , tx is ON with strong  $V_{GS}$ ,  $V_{GS}$  constant as output changes
  - $V_{DS}$ :  $VDD \Rightarrow 0$ , tx in Saturation then in Triode



- $D=0 \rightarrow x=1$ 
  - $V_{GS} = VDD \Rightarrow V_{tn}$ , tx is ON, but  $V_{GS}$  decreases as output changes
  - $V_{DS}$ :  $VDD \Rightarrow V_{tn}$ , tx in Saturation then in Triode

   
Output change is slower for  $D=0$  since pass-gate has weak current



# Flip Flop Layout

- A DFFR (with reset) cell with

- all tx. min. size
- no buffers

 

- Good features

- compact layout, small area demand
- very 'regular' physical structure
  - due to all minimum-sized transistors
- pitch matched to other primitive cells

- Bad features


- - several S/D junctions larger than necessary
- - several long poly traces, might affect speed
- - access to inputs/outputs must be in metal2




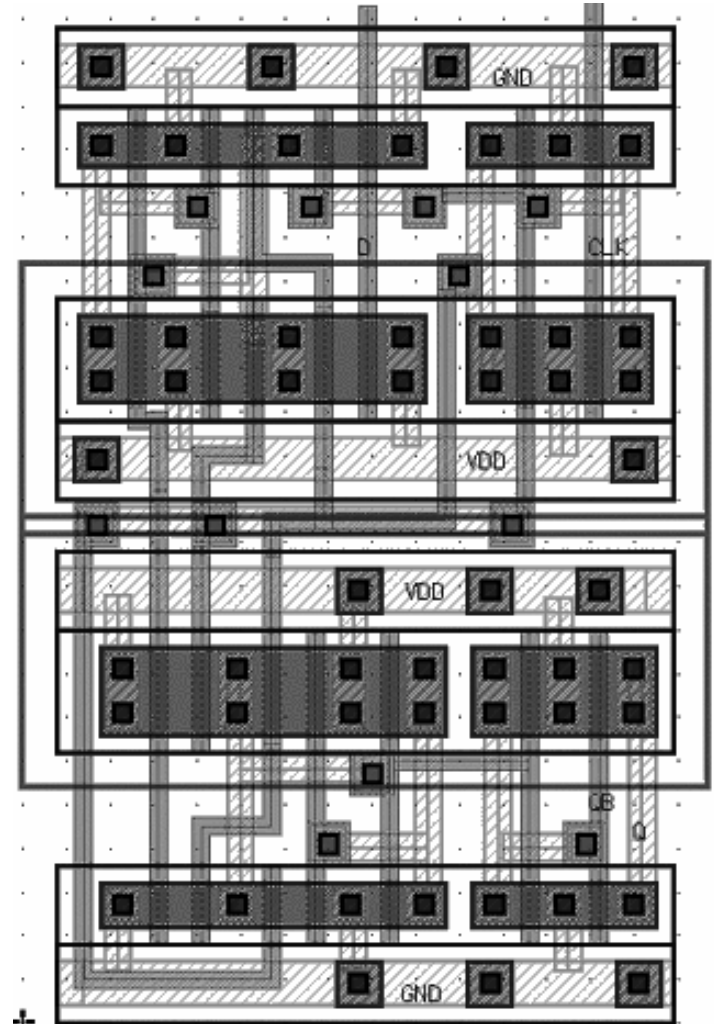
# Flip Flop Layout II

- Physical Design of  $C^2$ MOS Flip Flop
  - double-wide FF
    - pitch is 2x pitch of basic gates
- Using tall cells with standard height cells
  - match power rails




# Registers

- Basic Register Function

- store a byte of data
- implement data movement functions such as
  - shift
  - rotate
- basis for other functions
  - counter/timer

- Basic Register Circuit

 - cascade of DFF cells
- additional logic to multiplex multiple inputs/outputs
- typical I/O options
  - parallel load
  - load from left/right cell (shift)
  - parallel output




# Shift and Rotate Operations

- Rotate
  - move each bit of data to an adjacent bit
  - roll end bit to other end
- Shift
  - move each bit of data to an adjacent bit
  - load '0' into the open end bit

 - Examples: 4b operations on data  $a_3a_2a_1a_0$

- Rotate Left: output =  $a_2a_1a_0a_3$
- Rotate Right: output =  $a_0a_3a_2a_1$
- Shift Left: output =  $a_2a_1a_00$
- Shift Right: output =  $0a_3a_2a_1$




# Shift Register

- Example: 4-bit register capable of

- shift left/right
- rotate left/right
- parallel load
- reset (all bits go to 0)
- set (load all bits with 1)

s2	s1	s0	function
0	0	x	parallel load
0	1	0	shift right
0	1	1	rotate right
1	0	0	shift left
1	0	1	rotate left
1	1	x	load '1'

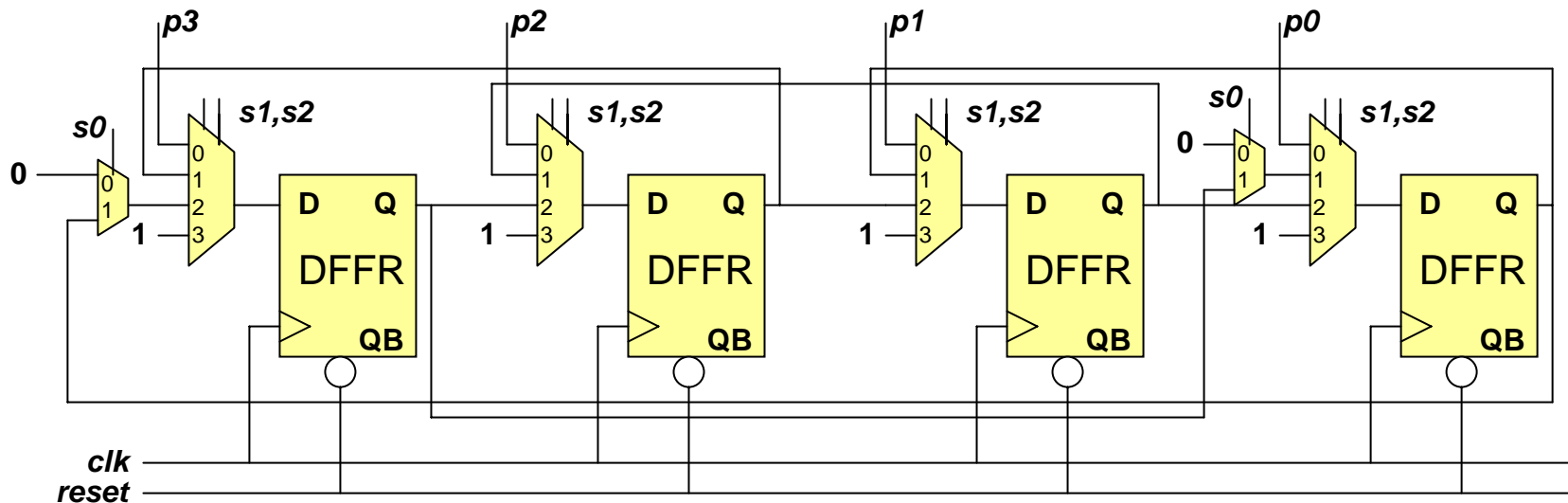


could add an Enable at the clock input to select between multiple bytes


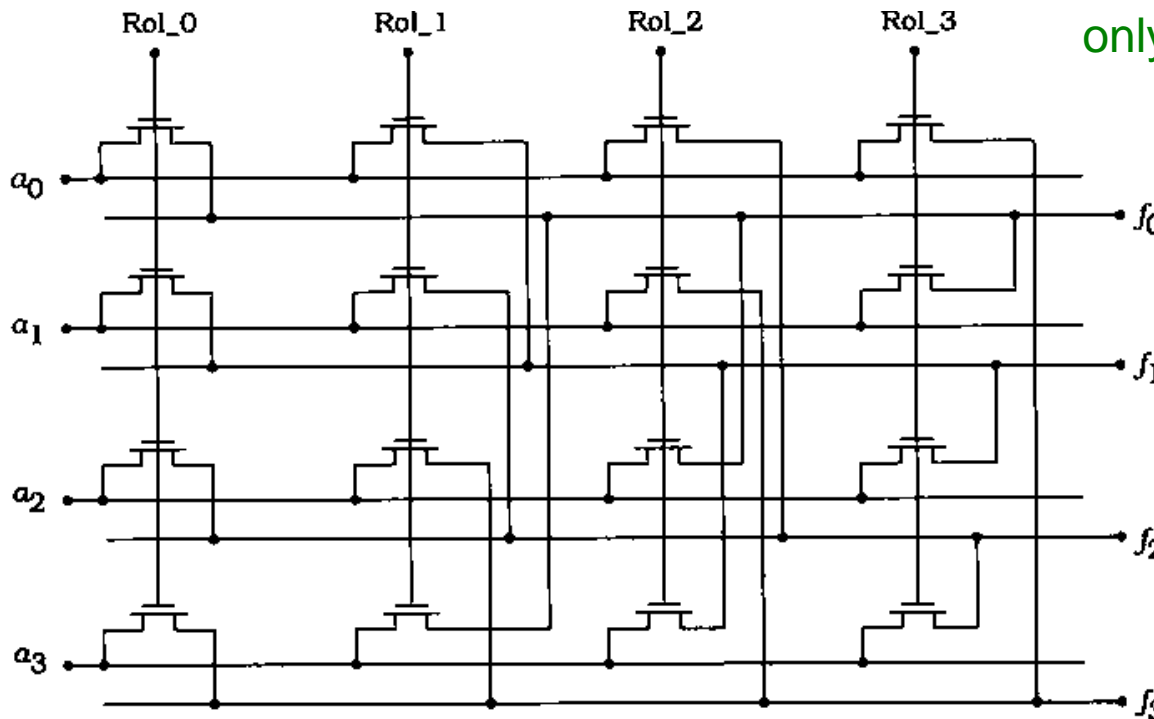
# Switch Shift/Rotate Circuits

- Can use switch circuits to implement fast multi-shift/rotate functions
  - will not store/hold data since no FF is used & is not synchronous
  - Example: 4-bit Left Rotate Switching Array

Rotate Left, moves lower bits to higher bits



only one select (Rol\_x) is active at a time


	Rol0	Rol1	Rol2	Rol3
a <sub>0</sub>	a <sub>0</sub>	a <sub>3</sub>	a <sub>2</sub>	a <sub>1</sub>
a <sub>1</sub>	a <sub>1</sub>	a <sub>0</sub>	a <sub>3</sub>	a <sub>2</sub>
a <sub>2</sub>	a <sub>2</sub>	a <sub>1</sub>	a <sub>0</sub>	a <sub>3</sub>
a <sub>3</sub>	a <sub>3</sub>	a <sub>2</sub>	a <sub>1</sub>	a <sub>0</sub>



# Barrel Shifter

- Shifts  $m$  inputs into  $n$  outputs
  - typically  $n = m$  or  $n = m/2$
- Example 8x4 barrel shifter
  - outputs 1 of 4 combinations of 4-adjacent-bits

shift	$b_0b_1b_2b_3$
0	$a_0a_1a_2a_3$
1	$a_1a_2a_3a_4$
2	$a_2a_3a_4a_5$
3	$a_3a_4a_5a_6$
4	$a_4a_5a_6a_7$

 


8x4 nMOS switch barrel shifter


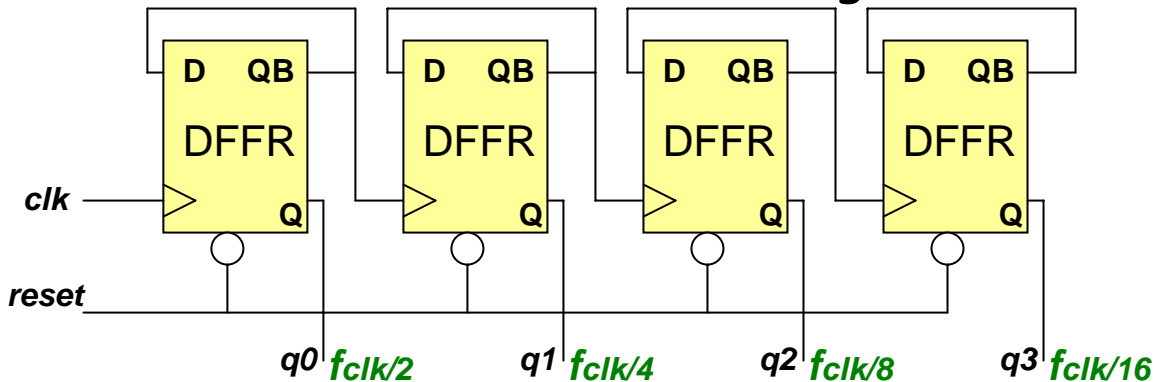
# Asynchronous Counter

- Counts the number of input clock edges (+ive or -ive)
- Output is a binary code of the number of clocks counted
- Example: 4-bit counter
  - output\_bar of each bit provides clock to next bit
  - output is also fed back to input
  - frequency of each output is 1/2 the previous bit frequency
    - clock divider: divide by 2, by 4, by 8, by 16, etc.
  - reset used to start counting from Zero




#clks	q3	q2	q1	q0
0	0	0	0	0
1	0	0	0	1
3	0	0	1	0
5	0	0	1	1
7	0	1	0	0
9	0	1	0	1
11	0	1	1	0
13	0	1	1	1
15	1	0	0	0
*				
31	1	1	1	1

can you design a counter that can count up and down and can parallel load a starting value?


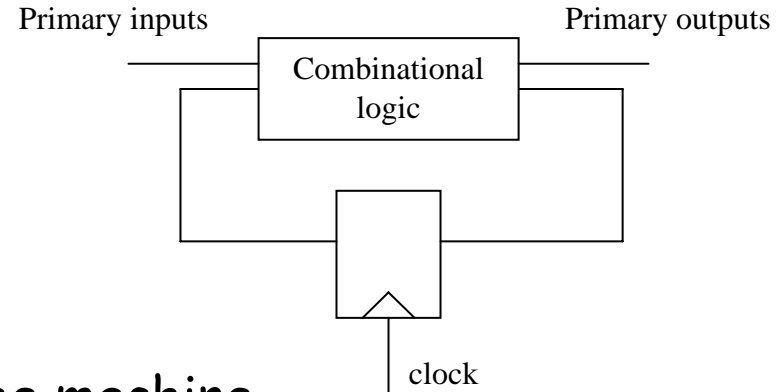
# Sequential Circuits

- A sequential circuit
  - outputs depend on current inputs
  - AND on pervious inputs (history)
- Finite State Machine
  - generic sequential circuit
  - a D-Flip-Flop holds the state of the machine
  - combinational logic generates the next state and output(s)
  - state machine inputs/outputs are called primary inputs/outputs
    - **Mealy machine:** primary outputs are a function of
      - current state
      - primary inputs
    - **Moore machine:** primary outputs depend only on
      - current state
- Sequential machines occur in nearly every chip design.






# State Machine Example

- 2-bit synchronous counter
  - example of a sequential state machine
- 2-bit synchronous counter function
  - increments output from 0 to 3 at each clock
  - and then start from 0 again
  - counter has no inputs, only states (Moore machine)

## • Design Steps
 
### 1. Specify the state transition graph.

- Four states in the 2-bit counter: 0, 1, 2, 3.
- State transition graph for 2-bit counter machine changes to the next state on each clock



### 2. Determine number of DFF in the state machine.

- Number of FF needed for a state machine is given by  $2^n = N$   
N is the number of states and n is the number of flip flops
- 2-bit counter has 4 states 00, 01, 10, and 11
- → need 2 DFFs



# State Machine Example Continued

- Design Steps continued
3. Draw the state transition table for the state transition graph.

Present State		Next State	
<i>DFF_1</i>	<i>DFF_0</i>	<i>DFF_1</i>	<i>DFF_0</i>
0	0	0	1
<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>
1	0	1	1
1	1	0	0

Example: at present state 1 (binary “01”), next state will be 2 (binary “10”).

4. Design the logic to compute the next state.
- One K-map is used for each DFF
  - Example: *DFF\_0* has the following K-map

	$DFF_{0\_old} = 0$	$DFF_{0\_old} = 1$
$DFF_{1\_old} = 0$	1	0
$DFF_{1\_old} = 1$	1	0

table shows  
next state value




Thus,  $DFF_{0\_next} = \overline{DFF_{0\_old}}$

Similar approach to find  $DFF_{1\_next}$


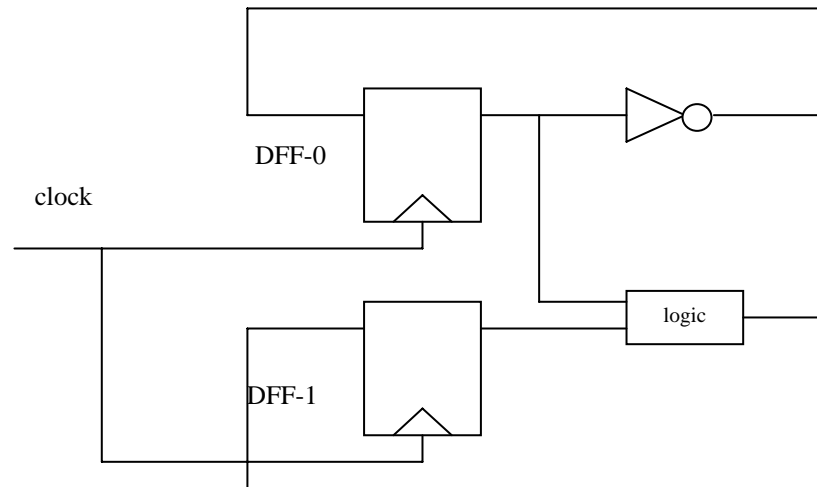
# Synchronous Counter

- Design Steps continued
5. Connect combinational logic & the DFFs to construct 2-bit counter



- A 2-bit, synchronous, 4-state counter

