

Binary Adder

- Binary Addition

- single bit addition

$$\begin{array}{r} x \quad y \quad x + y \text{ (binary sum)} \\ \hline \end{array}$$

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10 \text{ (binary, i.e. 2 in base-10)}$$

- sum of 2 binary numbers can be larger than either number
- need a "carry-out" to store the overflow


- Half-Adder

- 2 inputs (x and y) and 2 outputs (sum and carry)

x	y	s	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = x \oplus y \quad \text{XOR}$$

$$C = x \cdot y \quad \text{AND}$$

 


half-adder symbol



Half-Adder Circuits

- Simple Logic
 - using XOR gate

 


x	y	s	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


$$s = x \oplus y$$

$$c = x \cdot y$$

 - Most Basic Logic
 - NAND and NOR only circuits



(a) NAND2 logic

 

(b) NOR-based network

Take-home Questions:

Which of these 3 half-adders will be fastest? slowest? why??

Which has fewest transistors? Which transition has the critical delay?



Full-Adder

- When adding more than one bit, must consider the carry of the previous bit
 - full-adder has a "carry-in" input
- Full-Adder Equation

$$\begin{array}{r}
 c_i \\
 a_i \\
 + b_i \\
 \hline
 c_{i+1} \quad s_i
 \end{array}
 \begin{array}{l}
 \text{for every } i\text{-th bit} \\
 \text{carry-in} \\
 + a \\
 + b \\
 = \text{carry-out, sum}
 \end{array}$$


- Full-Adder Truth Table

a_i	b_i	c_i	s	c_{i+1}
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

$$\begin{aligned}
 s_i &= a_i \oplus b_i \oplus c_i \\
 c_{i+1} &= a_i \cdot b_i + c_i \cdot (a_i \oplus b_i)
 \end{aligned}$$

if not trying to 'reuse' the $a_i \oplus b_i$ term from sum, can write
 
$$c_{i+1} = a_i \cdot b_i + c_i \cdot (a_i + b_i)$$




full-adder symbol




Full-Adder Circuits

Full-Adder Equations: $s_i = a_i \oplus b_i \oplus c_i$ and $c_{i+1} = a_i \cdot b_i + c_i \cdot (a_i \oplus b_i)$

- XOR-based FA

 

- HA-based FA

 

- Other FA Circuits

- a few others options are covered in the textbook




Full Adder Circuits

- AOI Structure FA
 - implements following SOP equations


$$c_{i+1} = a_i \cdot b_i + c_i \cdot (a_i + b_i)$$

$$\bar{s}_i = (a_i + b_i + c_i) \cdot c_{i+1} + (a_i \cdot b_i \cdot c_i)$$

- sum delayed from carry

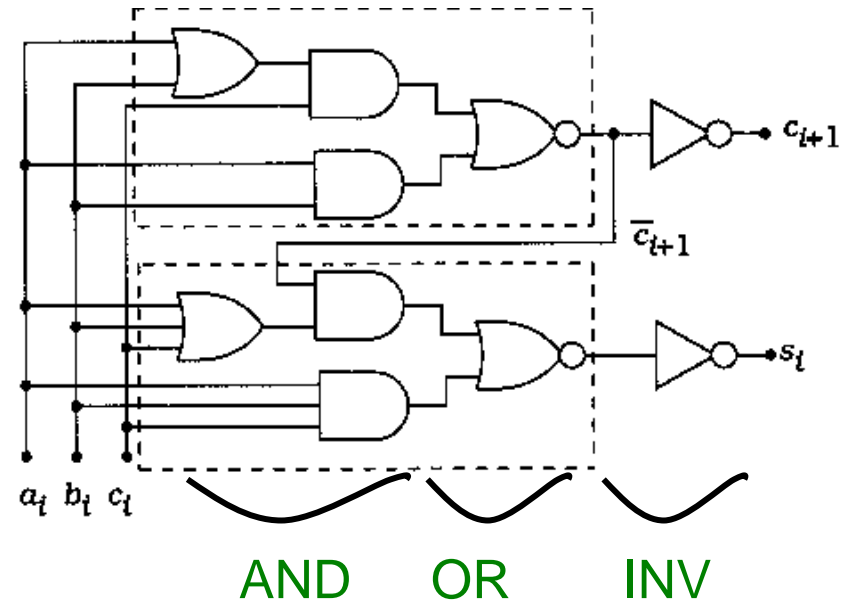

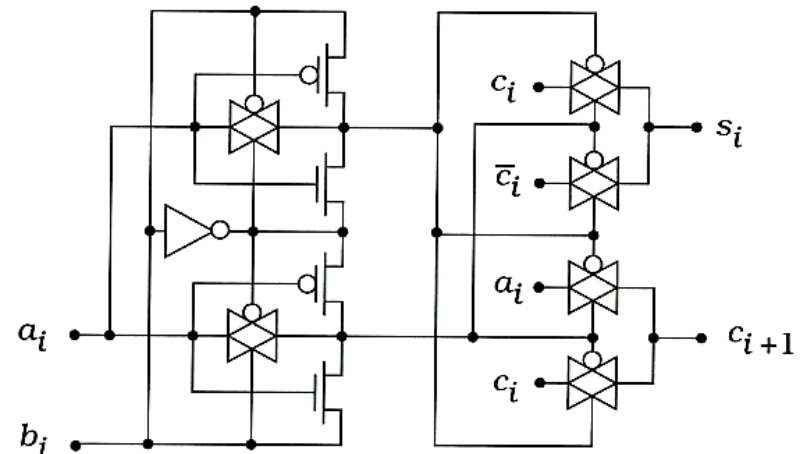- Transmission Gate FA
 - sum and carry have about the same delay




Full Adder in CMOS

- Consider nMOS logic for c_out

$$c_{i+1} = a_i \cdot b_i + c_i \cdot (a_i + b_i)$$



- two "paths" to ground

 

(a) Standard nFET logic

- Mirror CMOS Full Adder

- carry out circuit

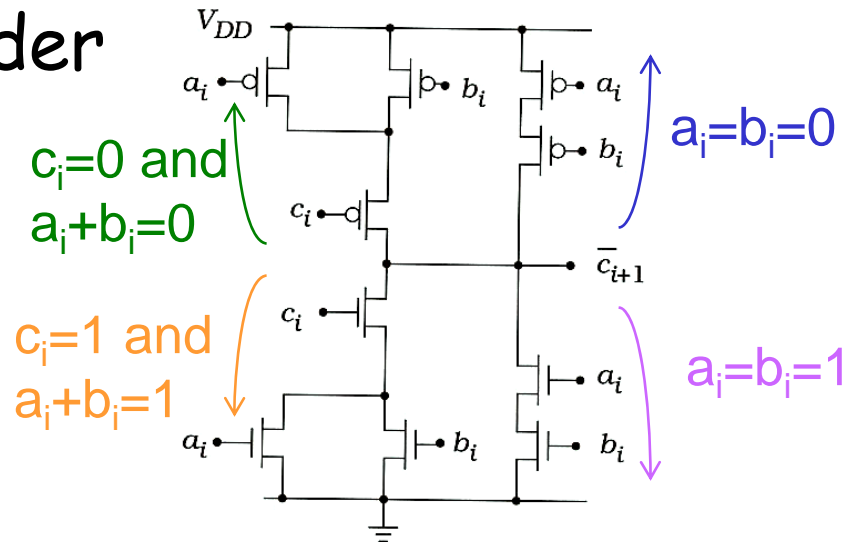 

(b) Mirror circuit

- complete circuit


FA Using 2:1 MUX

- If we re-arrange the FA truth table
 - can simplify the output (sum, carry) expressions

a_i	b_i	c_i	$a \oplus b$	s	c_{i+1}
0	0	0	0	0	0
1	1	0	0	0	1
0	0	1	0	1	0
1	1	1	0	1	1
0	1	0	1	1	0
1	0	0	1	1	0
0	1	1	1	0	1
1	0	1	1	0	1

If $(A \oplus B = 0)$, $SUM=Cin$;
 Else, $SUM=Cin_bar$;

$Cout=A$;
 $Cout=Cin$;

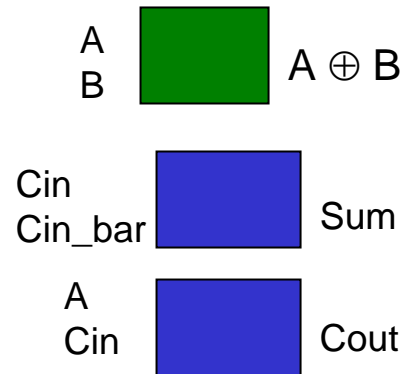

Partial Schematic
 can you figure out
 the details?

Implementation

- use an XOR to make the decision ($a \oplus b = 0$?)
- use a 2:1 MUX to select which equation/value of sum and carry to pass to the output



Binary Word Adders

- Adding 2 binary (multi-bit) words

- adding 2 n-bit word produces an n-bit **sum** and a **carry**

- **example:** 4b addition

$$\begin{array}{r}
 a_3 \ a_2 \ a_1 \ a_0 \quad \text{4b input a} \\
 + \ b_3 \ b_2 \ b_1 \ b_0 \quad \text{+ 4b input b} \\
 \hline
 C_4 \ S_3 \ S_2 \ S_1 \ S_0 \quad \text{= carry-out, 4b sum}
 \end{array}$$

- Carry Bits


- binary adding of n-bits will produce an n+1 carry

- can be used as carry-in for next stage or as an overflow flag

- Cascading Multi-bit Adders

- carry-out from a binary word adder can be passed to next cell to add larger words


 
- **example:** 3 cascaded 4b binary adders for 12b addition



Ripple Carry Adder

- To use single bit full-adders to add multi-bit words
 - must apply carry-out from each bit addition to next bit addition
 - essentially like adding 3 multi-bit words
 - each c_i is generated from the $i-1$ addition
 - c_0 will be 0 for addition
 - kept in equation for generality
- symbol for an n-bit adder
  
$$\begin{array}{r}
 C_3 \ C_2 \ C_1 \ C_0 \quad \text{carry-in bits} \\
 a_3 \ a_2 \ a_1 \ a_0 \quad \text{4b input a} \\
 + \ b_3 \ b_2 \ b_1 \ b_0 \quad \text{+ 4b input b} \\
 \hline
 C_4 \ S_3 \ S_2 \ S_1 \ S_0 \quad = \text{carry-out, 4b sum}
 \end{array}$$



4b ripple-carry adder using 4 FAs


Ripple-Carry Adder

- passes carry-out of each bit to carry-in of next bit
- for n -bit addition, requires n Full-Adders



Adder/Subtractor using R-C Adders

 - Subtraction using 2's complements
 - 2's complement of X: $X_{2s} = \overline{X} + 1$
 - invert and add 1
 - Subtraction via addition: $Y - X = Y + X_{2s}$
- R-C Adder/Subtractor Cell
 - control line, add_sub: 0 = add, 1 = subtract
 - XOR used to pass (add_sub=1) or invert (add_sub=0)
 - set first carry-in, c_0 , to 1 will add 1 for 2's complement





a = add		sub
a	b	$a \oplus b$
0	0	0 <i>b</i>
0	1	1
1	0	1 \overline{b}
1	1	0 \overline{b}



Ripple-Carry Adders in CMOS

- Simple to implement and connect for multi-bit addition
 - but, they are very slow
- Worse-case delays in R-C Adders
 - each bit in the cascade requires carry-out from the previous bit
 - major speed limitation of R-C Adders
 - delay depends somewhat on the type of FA implemented
 - general assumptions
 - worst delay in an FA is the sum
 - but carry is more important due to cascade structure
 - total delay is sum of delays to pass carry to final stage
 - total delay for n-input R-C adder

 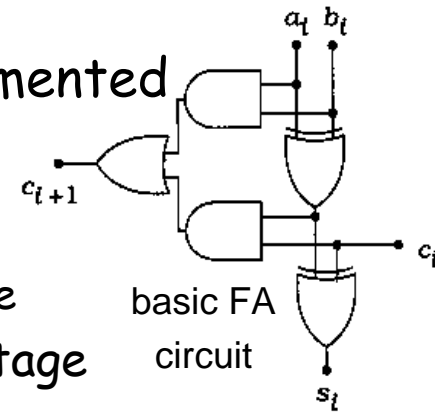

Carry Look-Ahead Adder

- CLA designed to overcome delay issue in R-C Adders
 - eliminates the ripple (cascading) effect of the carry bits
- Algorithm based calculating all *carry* terms at once
- Introduces **generate** and **propagate** signals
 - rewrite $c_{i+1} = a_i \cdot b_i + c_i \cdot (a_i \oplus b_i) \rightarrow c_{i+1} = g_i + c_i \cdot p_i$
 - **generate** term, $g_i = a_i \cdot b_i$
 - **propagate** term, $p_i = a_i \oplus b_i$
 - approach: evaluate all g_i and p_i terms and use them to calculate all carry terms without waiting for a carry-out ripple
- All *sum* terms evaluated at once
 - the sum of each bit is: $s_i = p_i \oplus c_i$
- Pros and Cons
 - no cascade delays; outputs expressed in terms of inputs only
 - requires complex circuits for higher bit-order adders (next slide)



Logic Circuits for a 4b CLA Adder

- Carry-out expressions for 4b CLA

- $c_1 = g_0 + c_0 \cdot p_0$, $c_2 = g_1 + c_1 \cdot p_1$, $c_3 = g_2 + c_2 \cdot p_2$, $c_4 = g_3 + c_3 \cdot p_3$

- Expressed only in terms of known inputs

- $c_2 = g_1 + p_1 \cdot (g_0 + c_0 \cdot p_0)$

- $c_3 = g_2 + p_2 \cdot [g_1 + p_1 \cdot (g_0 + c_0 \cdot p_0)]$

- $c_4 = g_3 + p_3 \cdot \{g_2 + p_2 \cdot [g_1 + p_1 \cdot (g_0 + c_0 \cdot p_0)]\}$



- nested Sum-of-Products expressions

- gets more complex for higher bit adders

- Sums obtained by an XOR with carries


$$g_i = a_i \cdot b_i$$

$$p_i = a_i \oplus b_i$$

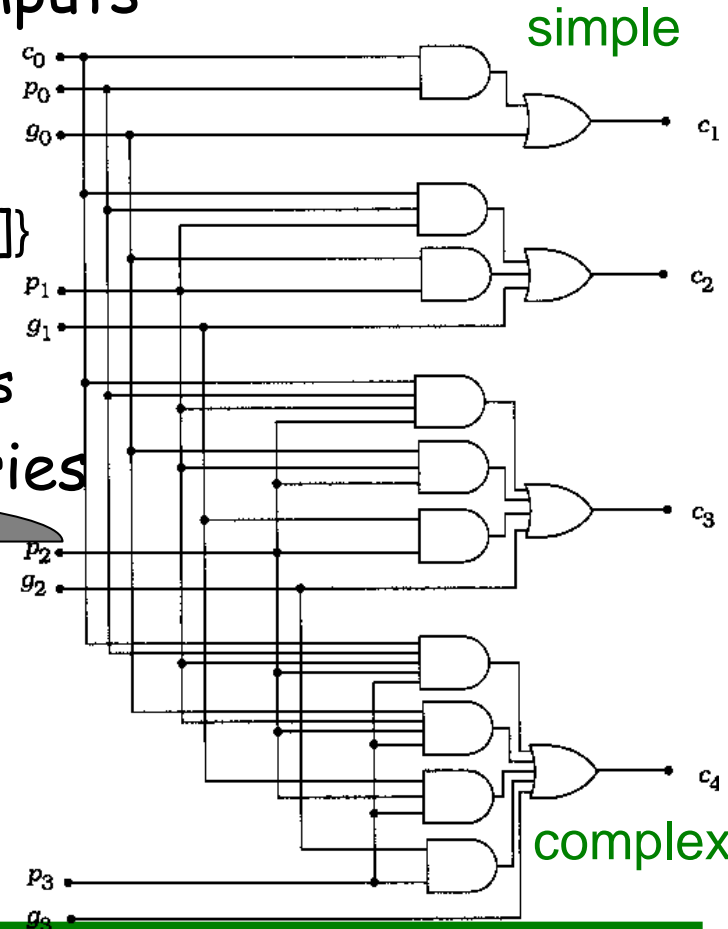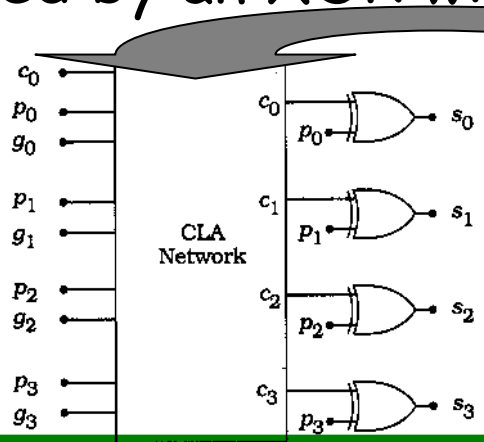


CLA Carry Generation in Reduced CMOS


- Reduce logic by constructing a CMOS push-pull network for each carry term
 - expanded carry terms
 - $c_1 = g_0 + c_0 \cdot p_0$
 - $c_2 = g_1 + g_0 \cdot p_1 + c_0 \cdot p_0 \cdot p_1$
 - $c_3 = g_2 + g_1 \cdot p_2 + g_0 \cdot p_1 \cdot p_2 + c_0 \cdot p_0 \cdot p_1 \cdot p_2$
 - $c_4 = g_3 + g_2 \cdot p_3 + g_1 \cdot p_2 \cdot p_3 + g_0 \cdot p_1 \cdot p_2 \cdot p_3 + c_0 \cdot p_0 \cdot p_1 \cdot p_2 \cdot p_3$
- nFETs network for each carry term
 - pFET pull-up not shown
 - notice nested structure

 


(a) c_1 logic

 

(b) c_2 logic

 

(c) c_3 logic

 


(d) c_4 logic



CLA in Advanced Logic Structures



- CLA algorithm better implemented in **dynamic logic**
- Dynamic Logic (*jump to next slide*)
- Dynamic Logic CLA Implementation
 - multiple output domino logic (MODL)

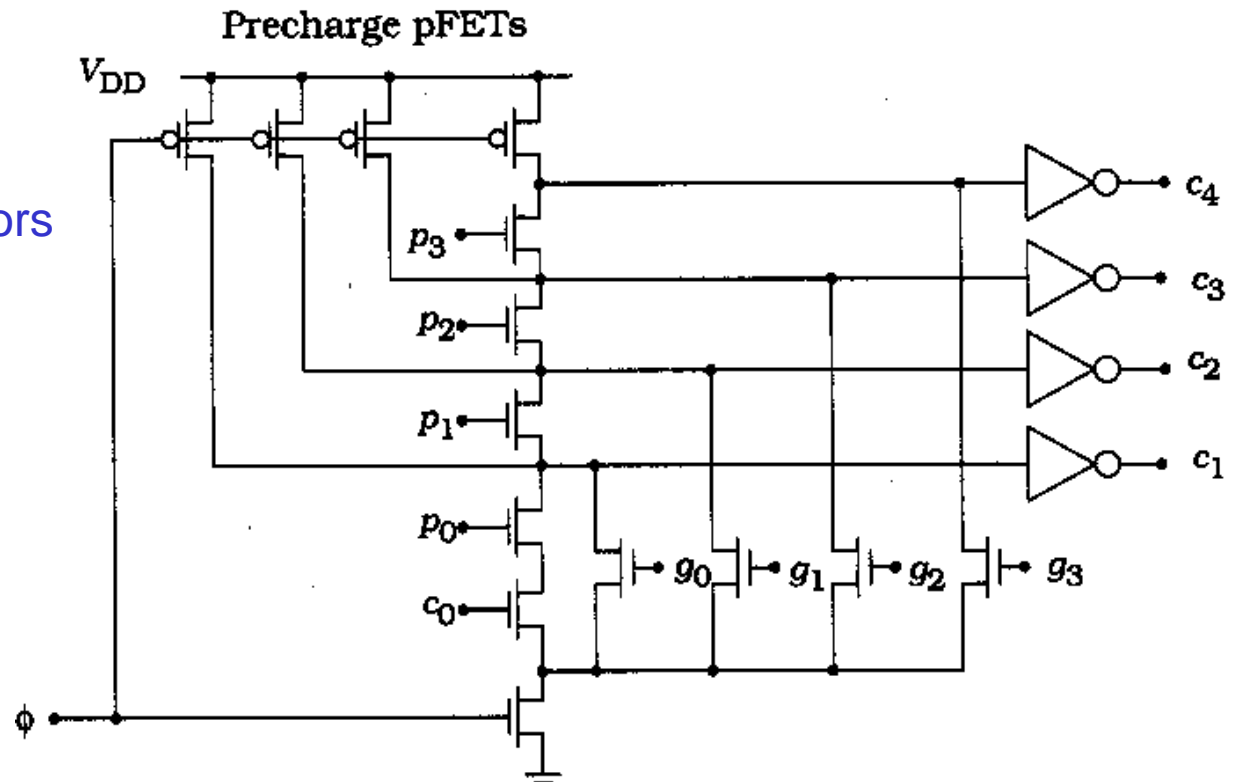- significantly fewer transistors
- faster
- less chip area
- output only valid during evaluate period



Dynamic Logic - Quick Look

- Advantages: fewer transistors & less power consumption
- General dynamic logic gate
 - nFET logic evaluation network
 - clocked "precharge" pull up pFET
 - clocked disabling nFET
- Precharge stage
 - clock-gated pull-up precharges output high
 - logic array disabled
- Evaluation stage
 - precharge pull-up disabled
 - logic array enabled & if true, discharges output
- Dynamic operation: output not always valid

 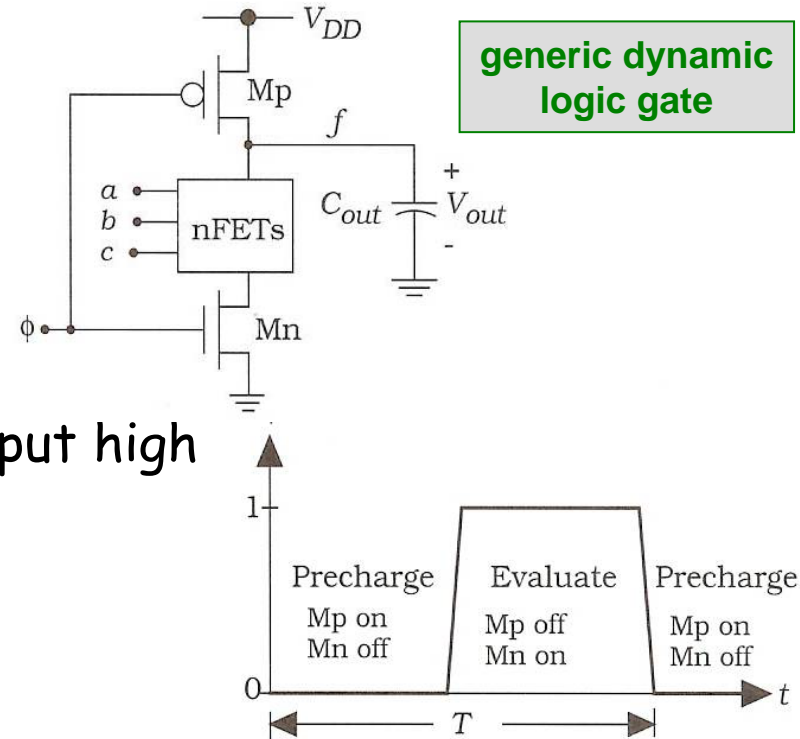

Manchester Carry Generation Concept

- Alternative structure for *carry* evaluation
 - define *carry* in terms of control signals such that
 - only one control is active at a given time
 - implement in **switch-logic**

- Consider single bit FA truth table

- *p* OR *g* is high in 6 of 8 logic states
 - *p* and *g* are not high at the same time
- introduce **carry-kill**, *k*
 - on/high when neither *p* or *g* is high
 - carry_out always 0 when *k*=1

a_i	b_i	c_i	c_{i+1}	p_i	g_i	k_i
0	0	0	0	0	0	1
0	1	0	0	1	0	0
1	0	0	0	1	0	0
1	1	0	1	0	1	0
0	0	1	0	0	0	1
0	1	1	1	1	0	0
1	0	1	1	1	0	0
1	1	1	1	0	1	0

generate	$g_i = a_i \cdot b_i$
propagate	$p_i = a_i \oplus b_i$
carry-kill	$k_i = \overline{a_i + b_i}$



Manchester Carry Generation Concept

- Switch-logic implementation of truth table

- 3 independent control signals g, p, k
- express carry_out in terms of g, p, k

generate	$g_i = a_i \cdot b_i$
propagate	$p_i = a_i \oplus b_i$
carry-kill	$k_i = \overline{a_i + b_i}$


if $g = 1 \rightarrow c_{i+1} = 1$

if $p = 1 \rightarrow c_{i+1} = c_i$

if $k = 1 \rightarrow c_{i+1} = 0$

- implement in **switch-logic**

- only one switch ON at any time

 

a_i	b_i	c_i	c_{i+1}	p_i	g_i	k_i
0	0	0	0	0	0	1
0	1	0	0	1	0	0
1	0	0	0	1	0	0
1	1	0	1	0	1	0
0	0	1	0	0	0	1
0	1	1	1	1	0	0
1	0	1	1	1	0	0
1	1	1	1	0	1	0



Static CMOS Manchester Implementation

- Manchester carry generation circuit

- Static CMOS

- modify for inverting logic
 - input $\rightarrow c_i_bar$ & output $\rightarrow c_{i+1_bar}$

- New truth table

- Possible implementation

- $\overline{c_{i+1}} = 1$ if $g_i=0$
- $\overline{c_{i+1}} = 0$ if $g_i=1$ AND $p_i=0$
- $\overline{c_{i+1}} = \overline{c_i}$ if $p_i=1$
 - but $g_i=0$ here. problem?
- carry-kill is not needed

a_i	b_i	$\overline{c_i}$	$\overline{c_{i+1}}$	p_i	g_i
0	0	1	1	0	0
0	1	1	1	1	0
1	0	1	1	1	0
1	1	1	0	0	1
0	0	0	1	0	0
0	1	0	0	1	0
1	0	0	0	1	0
1	1	0	0	0	1



Static CMOS Manchester Implementation

Textbook Circuit Implementation


- $\overline{c_{i+1}} = 1$ if $g_i=0$
- $\overline{c_{i+1}} = 0$ if $g_i=1$ AND $p_i=0$
- $\overline{c_{i+1}} = \overline{c_i}$ if $p_i=1$

- error

- when $g_i=0, p_i=1, \overline{c_i}=0, \overline{c_{i+1}} \rightarrow 0$
- pulled low through M1
- but M4 pulls it high


a_i	b_i	$\overline{c_i}$	$\overline{c_{i+1}}$	p_i	g_i
0	0	1	1	0	0
0	1	1	1	1	0
1	0	1	1	1	0
1	1	1	0	0	1
0	0	0	1	0	0
0	1	0	0	1	0
1	0	0	0	1	0
1	1	0	0	0	1

static
CMOS
from textbook

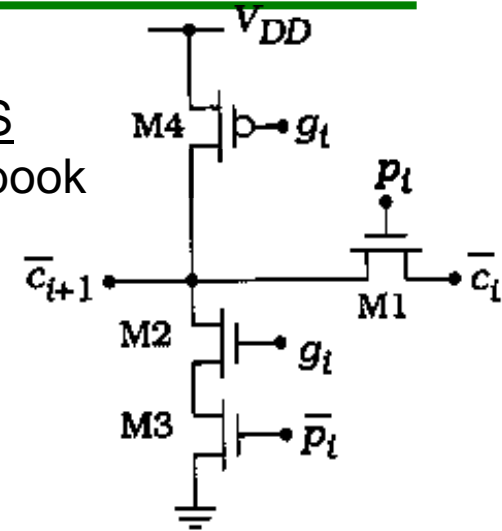

Possible Correction?

 - insert switch in pull-up path to disable when $\overline{c_i}=0$
- solves error when $g_i=0, p_i=1, \overline{c_i}=0 \rightarrow \overline{c_{i+1}}=0$
- but introduces error when $g_i=0, p_i=1, \overline{c_i}=0 \rightarrow \overline{c_{i+1}}=1$
 - M4 can not pull high since new nMOS cuts off path



Manchester Implementation

Corrected Manchester Carry Generation Circuit

- truth table organized by p_i

• if $p_i = 0$

- $\overline{c_{i+1}} = g_i$ (NOT g_i)
- block c_i , pass VDD or GND

• if $p_i = 1$

- $\overline{c_{i+1}} = \overline{c_i}$
- pass c_i , block VDD & GND


a_i	b_i	$\overline{c_i}$	$\overline{c_{i+1}}$	p_i	g_i	VDD	GND	C_i
0	0	1	1	0	0	act	x	x
0	0	0	1	0	0	act	x	x
1	1	1	0	0	1	x	act	x
1	1	0	0	0	1	x	act	x
0	1	1	1	1	0	x	x	act
1	0	1	1	1	0	x	x	act
0	1	0	0	1	0	x	x	act
1	0	0	0	1	0	x	x	act

act = active
x = disabled

a_i	b_i	$\overline{c_i}$	$\overline{c_{i+1}}$	p_i	g_i
0	0	1	1	0	0
0	1	1	1	1	0
1	0	1	1	1	0
1	1	1	0	0	1
0	0	0	1	0	0
0	1	0	0	1	0
1	0	0	0	1	0
1	1	0	0	0	1

alternative design:

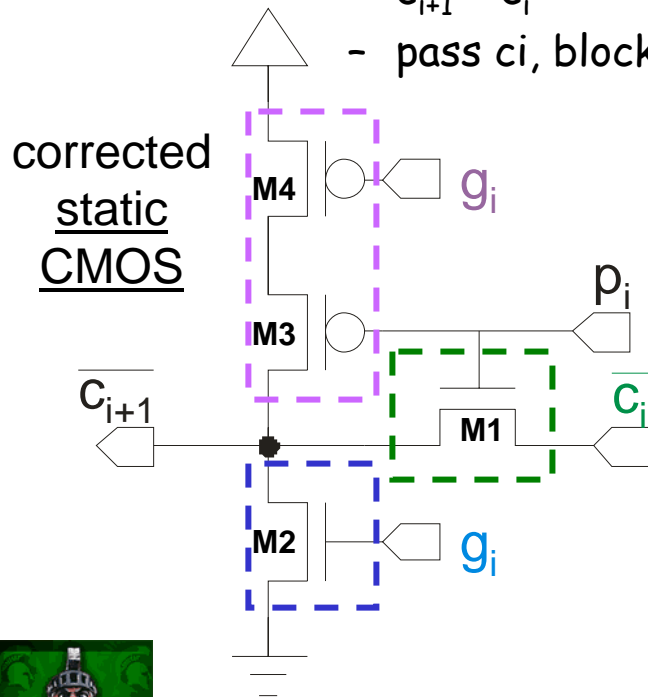- do not add pMOS M3
- make W of M1 significantly larger than W of M4
- C_i will override VDD




Manchester Implementation

- Dynamic Logic Circuit


- evaluate when $\phi = 1$
- c_{i+1} stays high unless
 - $g_i = 1$ ($c_{i+1} \rightarrow 0$) or $p_i = 1$ ($c_{i+1} \rightarrow c_i$)

 single bit carry generation in dynamic logic



- 4b Dynamic Manchester Carry Generation

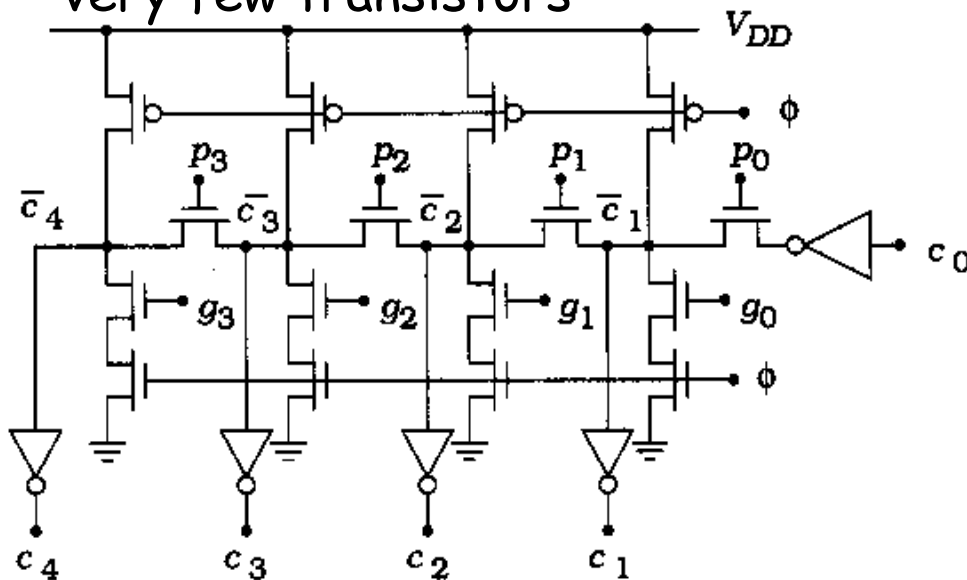- minor ripple delay
- threshold drop on propagate
- very few transistors



internal output, c_{i+1}
dynamically pulled high

propagate


pulled low (generate)

a_i	b_i	\bar{c}_i	\bar{c}_{i+1}	p_i	g_i
0	0	1	1	0	0
0	1	1	1	1	0
1	0	1	1	1	0
1	1	1	0	0	1
0	0	0	1	0	0
0	1	0	0	1	0
1	0	0	0	1	0
1	1	0	0	0	1




CLA for Wide Words

- number of terms in the carry equation increases with the width of the binary word to be added
 - gets overwhelming (and slow) with large binary words
- one method is to break wide adders into smaller blocks
 - e.g., use 4b blocks (4b is common, but could be any number)
 - must create **block generate** and **propagate** signals to carry information to the next block
 - $g_{[i,i+3]} = g_{i+3} + g_{i+2} \cdot p_{i+3} + g_{i+1} \cdot p_{i+2} \cdot p_{i+3} + g_i \cdot p_{i+1} \cdot p_{i+2} \cdot p_{i+3}$
 - $p_{[i,i+3]} = p_i \cdot p_{i+1} \cdot p_{i+2} \cdot p_{i+3}$
 - for block i thru i+3 of an n-sized adder

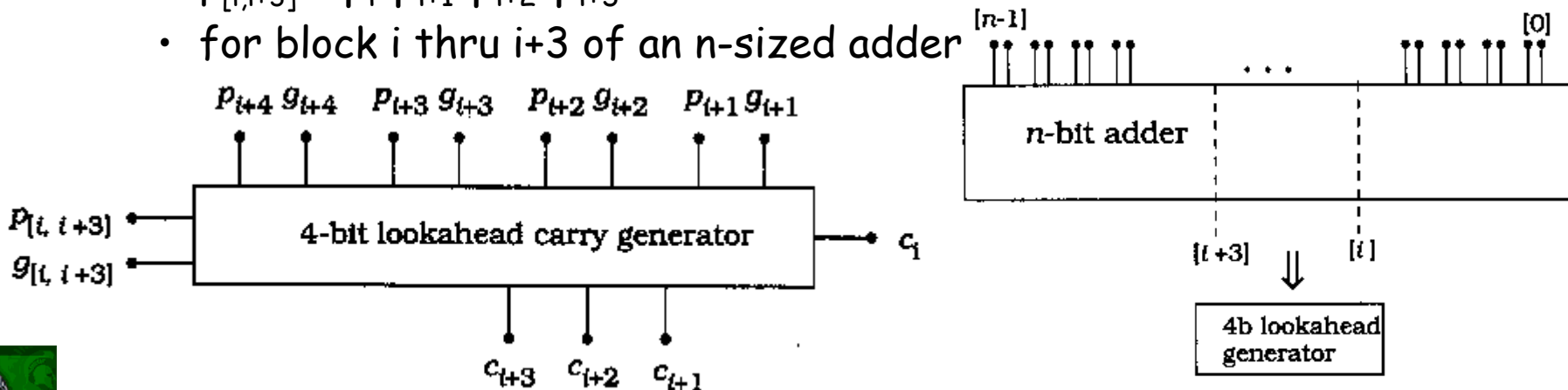

16b Adder Using 4b CLA Blocks

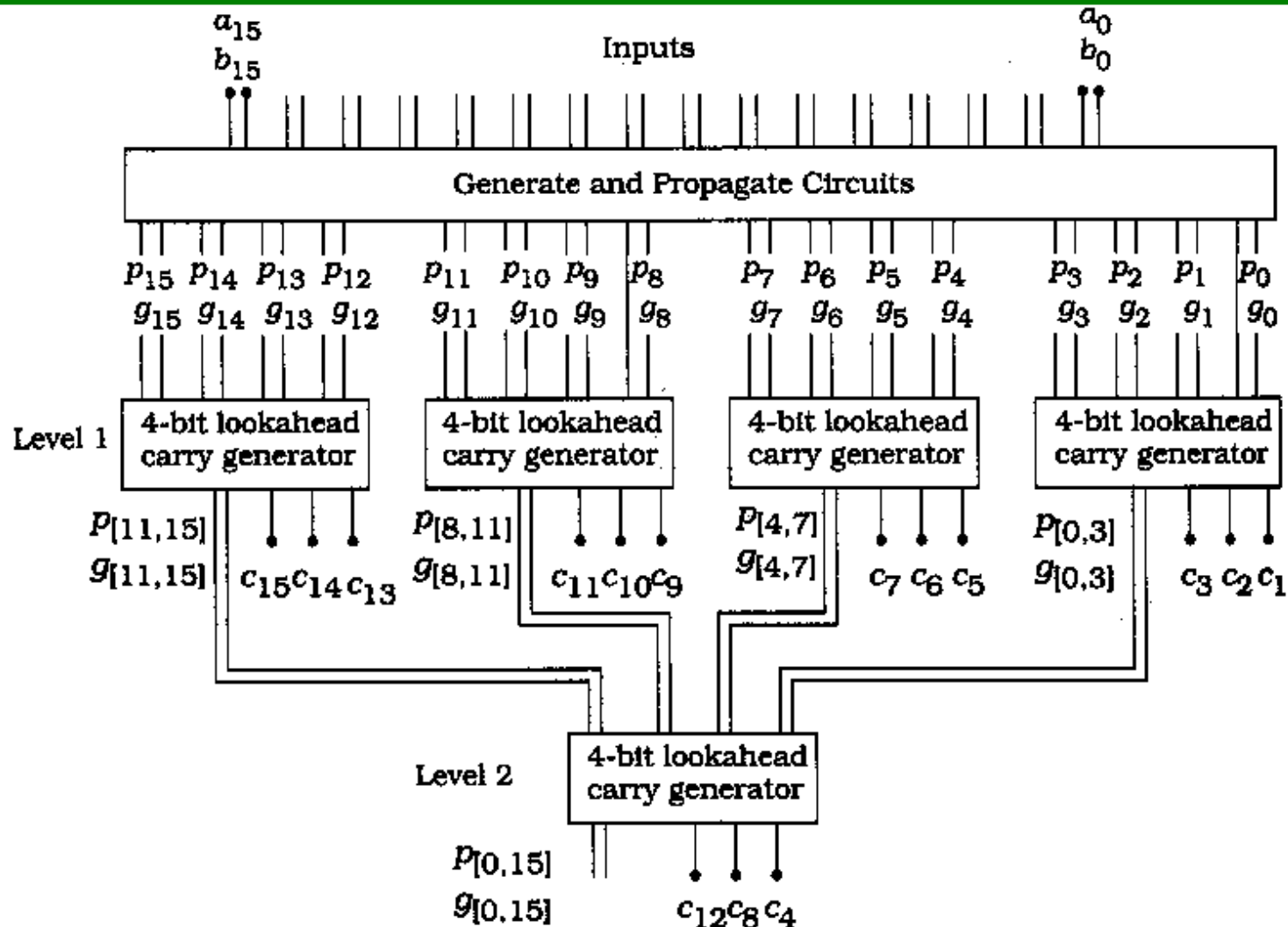

- Create SUMs from outputs of this circuit




Other Adder Implementations

- Alternative implementations for high-speed adders
- **Carry-Skip Adder**
 - quickly generate a carry under certain conditions and skip the carry-generation block
 - recall $c_{i+1} = g_i + c_i \cdot p_i$, $g_i = a_i \cdot b_i$, $p_i = a_i \oplus b_i$
 - note generation of p_i is more complex (XOR) than g_i (AND)
 - so, generate p_i and check $c_i p_i$ case, skip g_i generation if $c_i p_i = 1$
- **Carry-Select Adder**
 - uses multiple adder blocks to increase speed
 - take a lot of chip area
- **Carry-Save Adder**
 - parallel FA, 3 inputs and 2 outputs
 - does not add carry-out to next bit (thus no ripple)
 - carry is saved for use by other blocks
 - useful for adding more than 2 numbers




Fully Differential Full Adder

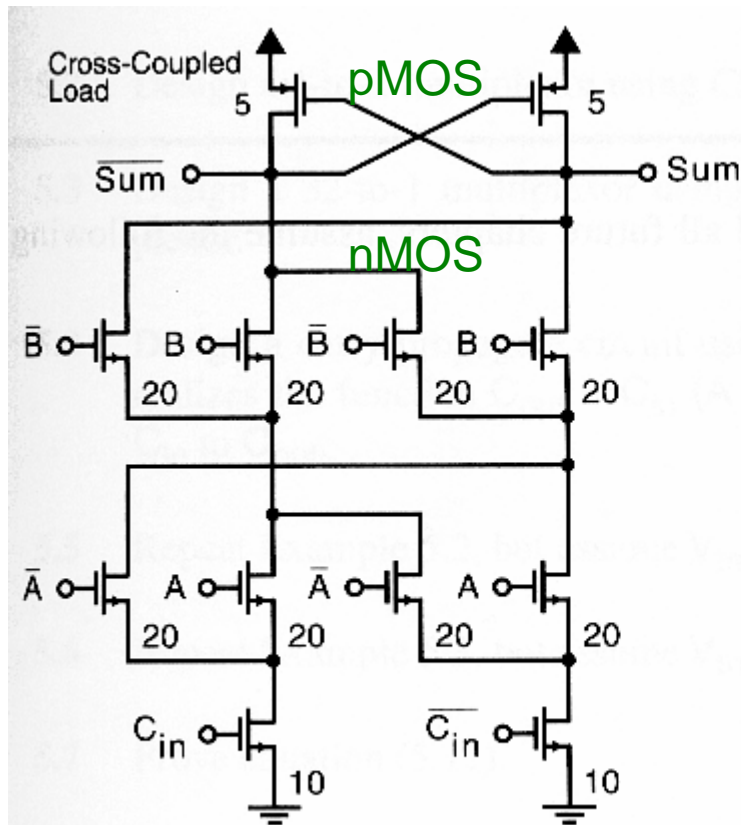- (a) sum-generate circuit
- (b) carry generate circuit



(a)

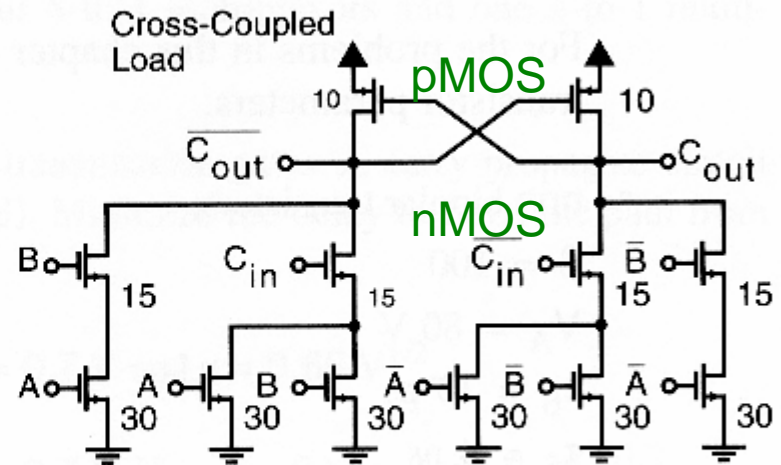

(b)



Multiplier Basics

- Single-Bit Binary Multiplication
 - $0 \times 0 = 0$, $0 \times 1 = 0$, $1 \times 0 = 0$, $1 \times 1 = 1$
 - same result as logic AND operation (1b output, no carry!)
- Multiple-Bit Multiplication
 - n-bit word TIMES an n-bit word give 2n-bit product
 - 4b example
 - 16 single-bit multiplies
 - multiply each bit of a by each bit of b
 - shift products for summing


note: can multiply by 2 by shifting the word to the left by one, multiply by 4 by left-shift twice, 8 three times, etc.

		a_3	a_2	a_1	a_0	multiplicand		
	\times	b_3	b_2	b_1	b_0	multiplier		
		$a_3 b_0$	$a_2 b_0$	$a_1 b_0$	$a_0 b_0$			
	+	$a_3 b_1$	$a_2 b_1$	$a_1 b_1$	$a_0 b_1$			
	+	$a_3 b_2$	$a_2 b_2$	$a_1 b_2$	$a_0 b_2$			
	+	$a_3 b_3$	$a_2 b_3$	$a_1 b_3$	$a_0 b_3$			
p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	product




Implementing Multiplier Circuits

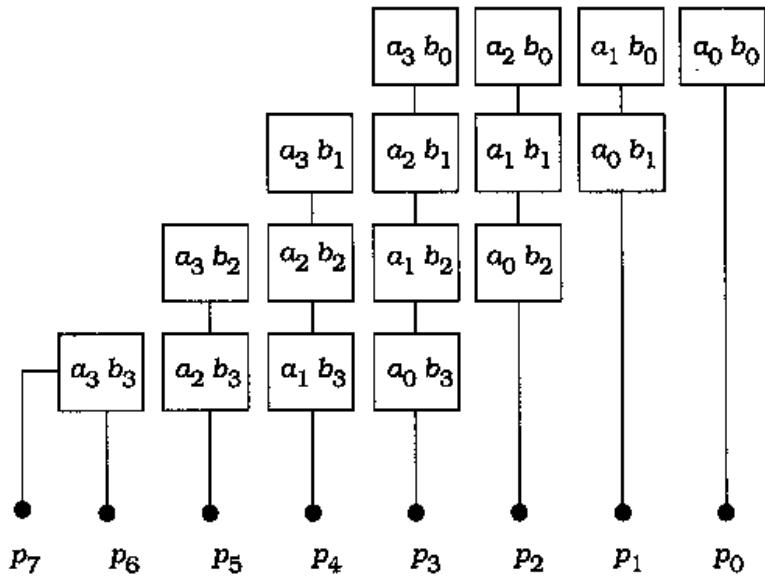- Multiplication Sequence
 - organization of ANDs and ADDs



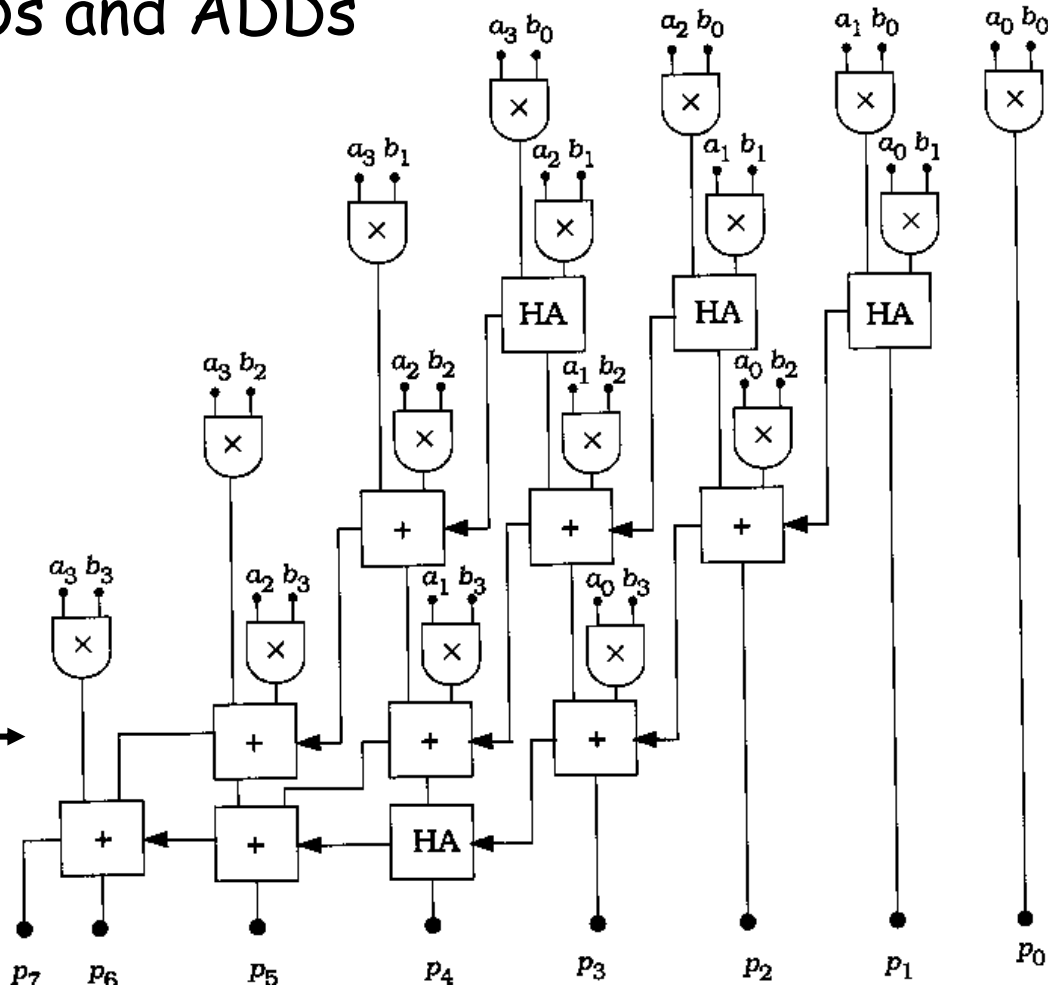- 4x4 Array Multiplier Circuit
 - 8b output



Signed Multiplication: Booth Encoding

- Signed Numbers

- 2's complement

$$+m = m$$

$$-m = 2 - m$$

Ex: 3-bit signed numbers

$$3 = 0\ 1\ 1$$


$$2+3 = 5 = 2 - (-3)$$

$$\Rightarrow 1\ 0\ 1 = -3$$

- Booth Encoding

- evaluate number 2-bits at a time

 - generate 'action' based on 2-bit sequence



-1: a sequence of “1 0”

0: no change in sequence

1: a sequence of “0 1”

$$0\ 1\ 1\ 0\ 1 = (13)_{10} = [1*2^4 + 0*2^3 - 1*2^2 + 1*2^1 - 1*2^0]$$

Benefit: Number of shift-add reduces if long seq. of “1” or “0”



4b x 4b Booth Multiplication

Multiply $m \times r$:

$$A = m_3 m_2 m_1 m_0 \times r_3 r_2 r_1 r_0$$

$$\text{Ex : } 0101 \times 1011 \quad (5^* -5 = -25)$$

Rules:

Start with product $A = 0$

Examine r_n, r_{n-1}

00 : shift R right

01 : add M ($A+M$)
shift A right

10 : sub M ($A-M$)
shift A right

11 : shift A right

n	r_n	r_{n-1}	Action	$A = 0000$
0	1	0	Sub M ($A-M$)	1011
			Shift Rt	11011
1	1	1	Shift Rt	111011
2	0	1	Add M ($A+M$)	001111 ←
			Shift Rt	0001111
3	1	0	Sub M ($A-M$)	1100111 = -25 ←

111011

0101

001111

0001111

1011

1100111



Arithmetic/Logic Unit Structure

- ALU performs basic arithmetic and logic functions in a single block
 - core unit in a microprocessor


- Basic n-bit ALU

- Inputs

- 2 n-bit inputs
 - carry in
 - function selects


- Outputs

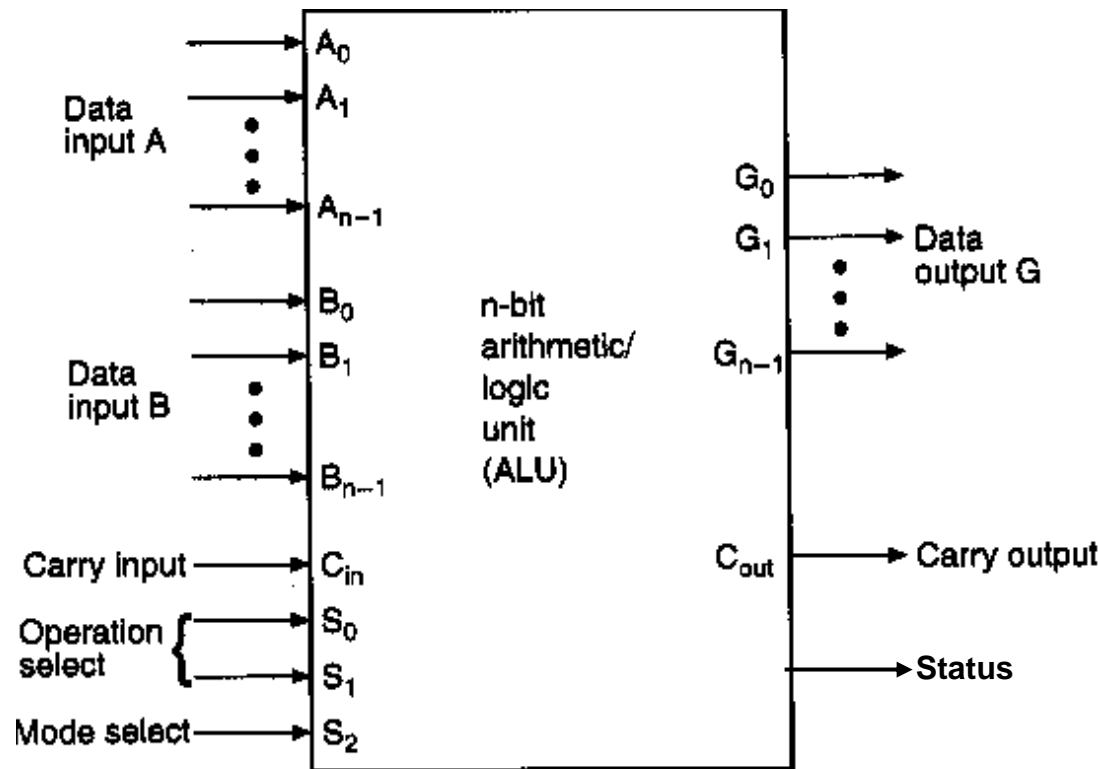- 1 n-bit result
 - carry out
 - status outputs
 - minus, zero, etc.



ALU Arithmetic Components

 - ALU Components
 - Arithmetic Block
 - Logic Block
 - Data Movement
 - sometimes done in register file
- Arithmetic Block
 - implements arithmetic functions
 - add
 - subtract
 - increment/decrement
 - sometimes
 - multiply
 - divide




 Example 4b Arithmetic Block



ALU Logic Components

- Logic Block
 - implements logic functions
 - NOT
 - AND
 - OR
 - XOR
- Data Movement
 - somewhere in the ALU
 - or in the register file
 - shift
 - rotate




S_1	S_0	Output	Operation
0	0	$G = A \wedge B$	AND
0	1	$G = A \vee B$	OR
1	0	$G = A \oplus B$	XOR
1	1	$G = \bar{A}$	NOT

Example 1-bit Logic Block



Example ALU Organization & Function

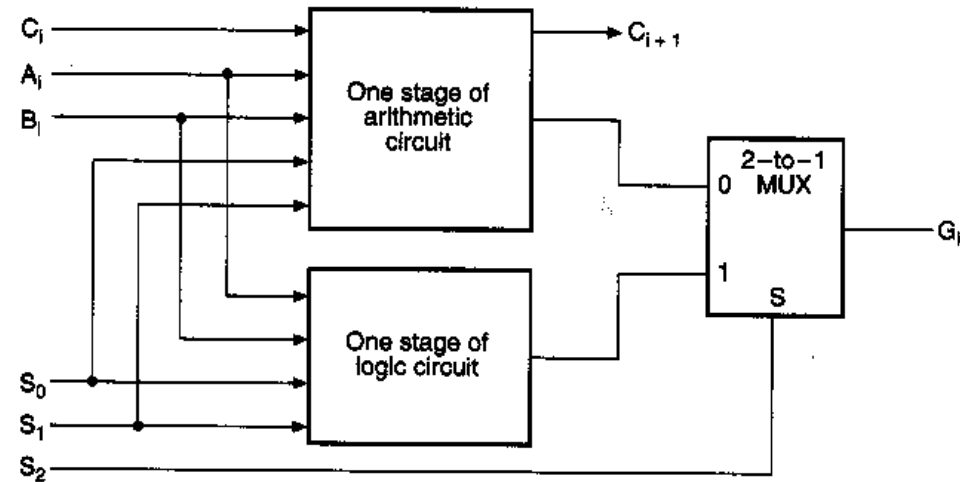- Example ALU Bit Slice
 - implementation of one bit



- Example Function Table

Operation Select				Operation	Function
S ₂	S ₁	S ₀	C _{in}		
0	0	0	0	$G = A$	Transfer A
0	0	0	1	$G = A + 1$	Increment A
0	0	1	0	$G = A + B$	Addition
0	0	1	1	$G = A + B + 1$	Add with carry input of 1
0	1	0	0	$G = A + \overline{B}$	A plus 1's complement of B
0	1	0	1	$G = A + \overline{B} + 1$	Subtraction
0	1	1	0	$G = A - 1$	Decrement A
0	1	1	1	$G = A$	Transfer A
1	0	0	X	$G = A \wedge B$	AND
1	0	1	X	$G = A \vee B$	OR
1	1	0	X	$G = A \oplus B$	XOR
1	1	1	X	$G = \overline{A}$	NOT (1's complement)

function set for a simple ALU

function determined by select inputs

