


Memory Basics

- **RAM: Random Access Memory**
 - historically defined as memory array with individual bit access
 - refers to memory with **both Read and Write capabilities**
- **ROM: Read Only Memory**
 - no capabilities for "online" memory Write operations
 - Write typically requires high voltages or erasing by UV light
- **Volatility of Memory**
 - volatile memory loses data over time or when power is removed
 - RAM is volatile
 - non-volatile memory stores data even when power is removed
 - ROM is non-volatile
- **Static vs. Dynamic Memory**
 - Static: holds data as long as power is applied (SRAM)
 - Dynamic: must be refreshed periodically (DRAM)




SRAM Basics

- SRAM = Static Random Access Memory
 - Static: holds data as long as power is applied
 - Volatile: can not hold data if power is removed
- 3 Operation States
 - hold
 - write
 - read
- Basic 6T (6 transistor) SRAM Cell
 - bistable (cross-coupled) INVs for storage
 - access transistors MAL & MAR
 - access to stored data for read and write
 - word line, WL, controls access
 - WL = 0, hold operation
 - WL = 1, read or write operation

 


SRAM Operations

- Hold
 - word line = 0, access transistors are OFF
 - data held in latch
- Write
 - word line = 1, access tx are ON
 - new data (voltage) applied to bit and bit_bar
 - data in latch overwritten with new value
- Read
 - word line = 1, access tx are ON
 - bit and bit_bar read by a sense amplifier
- Sense Amplifier
 - basically a simple differential amplifier
 - comparing the difference between bit and bit_bar
 - if bit > bit_bar, output is 1
 - if bit < bit_bar, output is 0
 - allows output to be set quickly without fully charging/discharging bit line

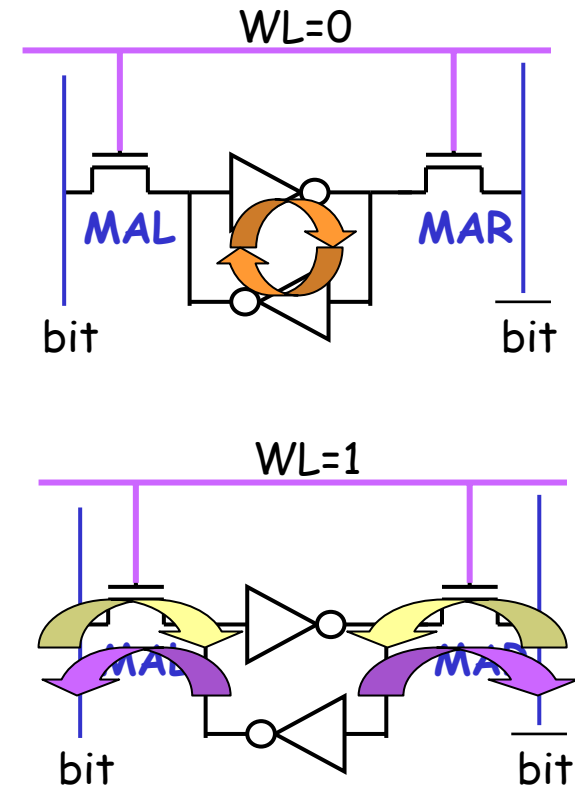


SRAM Bit Cell Circuit

 - Two SRAM cells dominate CMOS industry
 - 6T Cell
 - all CMOS transistors
 - better noise immunity
 - 4T Cell
 - replaces pMOS with high resistance ($\sim 1G\Omega$) resistors
 - slightly smaller than 6T cell
 - requires an extra high-resistance process layer



(a) 6T cell

 


 (b) 4T cell with poly resistors




6T Cell Design

- Critical Design Challenge
 - inverter sizing
 - to ensure good hold and easy/fast overwrite
 - use minimum sized transistors to save area
 - unless more robust design required
- Write Operation
 - both bit and bit_bar applied
 - inputs to inverters both change
 - unlike DFF where one INV overrides the other
 - critical size ratio, β_A/β_n
 - see resistor model
 - want R_n & R_p larger than R_A
 - » so voltage will drop across R_n, R_p
 - typical value, $\beta_A/\beta_n=2$
 - so $R_n = 2 R_A$
 - set by ratio $(W/L)_A$ to $(W/L)_n$



Write 1 Operation

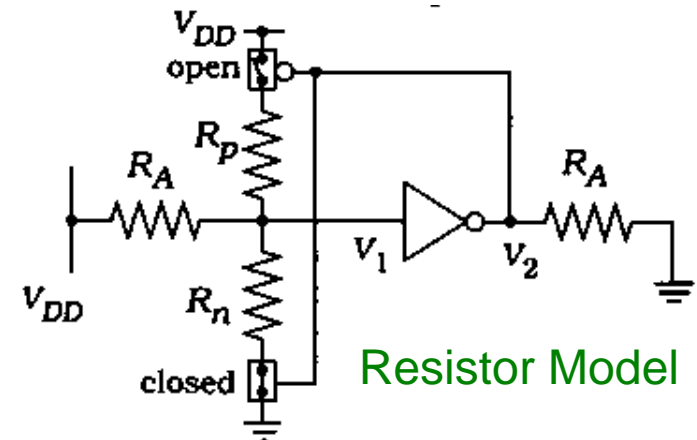


Resistor Model




SRAM Cell Layout

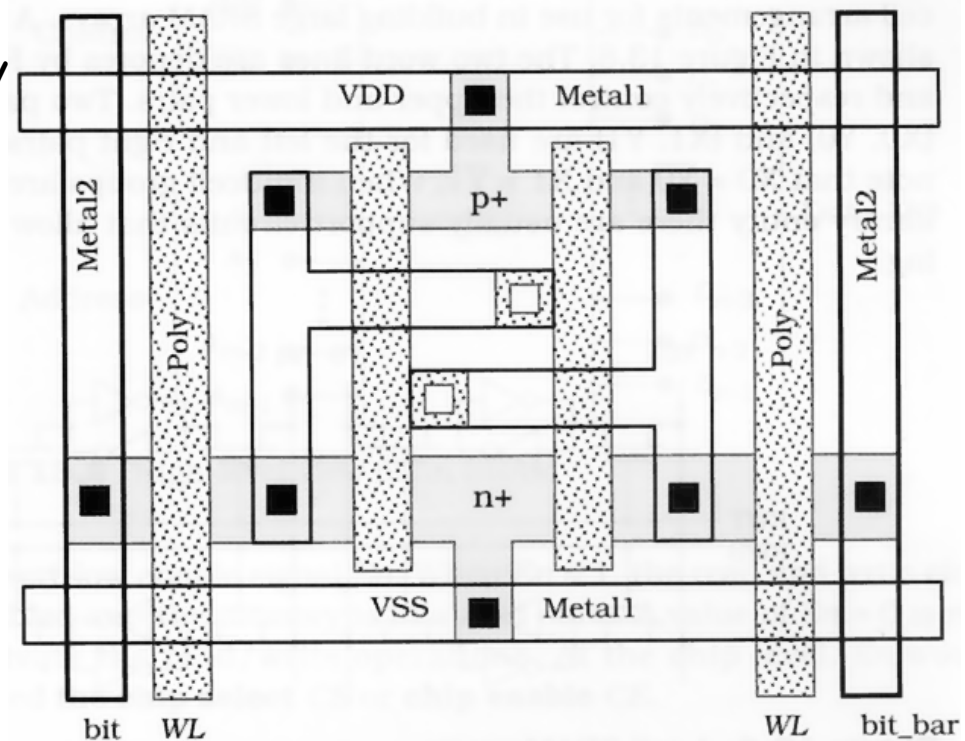- Design Challenge
 - minimum cell size (for high density SRAM array)
 - with good access to word and bit lines
- Example Layout
 - note WL routed in poly
 - will create a large RC delay for large SRAM array



Multi-Port SRAM

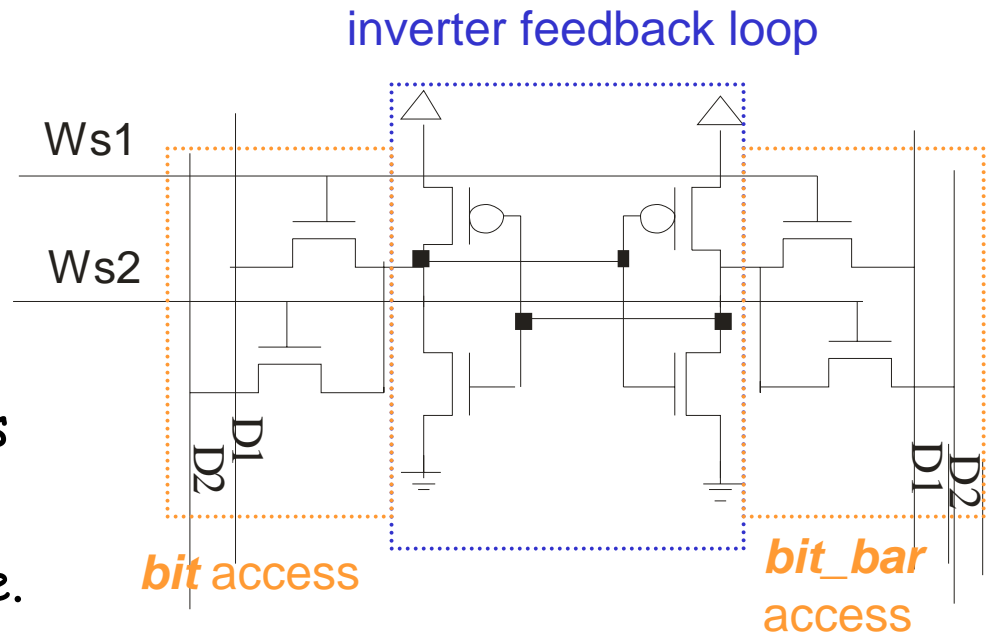- Allows multiple access to the same SRAM cell simultaneously.
 - Provide high data bandwidth.
- Applications
 - Register file
 - Cache
 - Network switch
 - ASIC etc.
- A multi-port SRAM cell schematic. Each port has
 - two access transistors
 - two bit line
 - one word selection line.
 - one address decoder




Multi-Port SRAM (cont.)

- Challenges in multi-ports SRAM.
 - layout size increases quadratically with # of ports
 - more word selection lines
 - more bitline lines
 - → lower speed and higher power consumption
- Multi-port SRAM options for ECE410 Design Project
 - Two ports
 - 1 port read and write
 - 1 port read only
 - Three ports
 - 2 ports for read and 1 port for write



SRAM Arrays

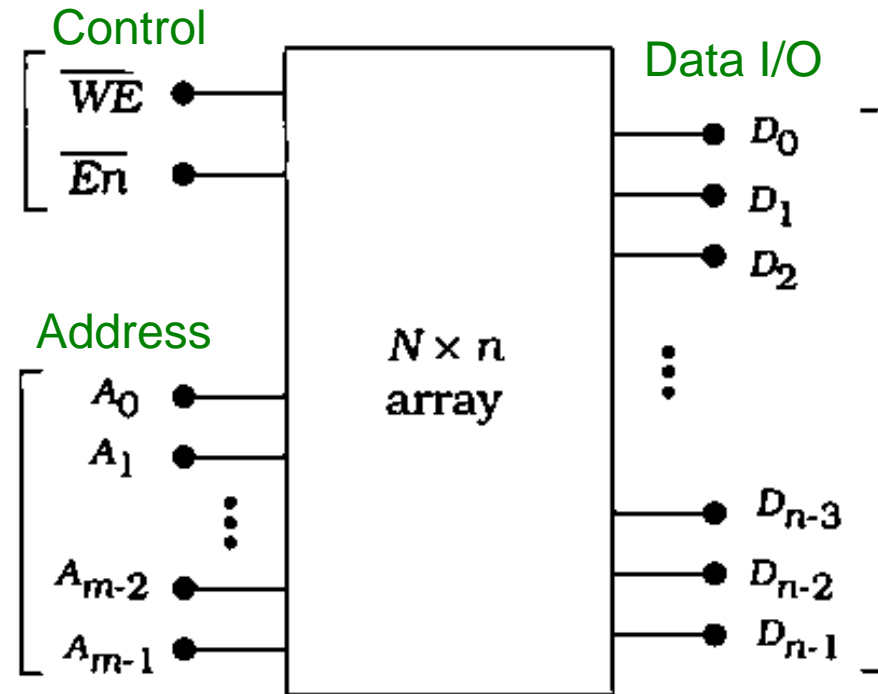
- $N \times n$ array of 1-bit cells
 - n = byte width; 8, 16, 32, etc.
 - N = number of bytes
 - m = number of address bits
 - $\max N = 2^m$
- Array I/O
 - data, in and out
 - D_{n-1} - D_0
 - address
 - A_{m-1} - A_0
 - control
 - varies with design
 - WE = write enable (assert low)
 - $WE=1$ =read, $WE=0$ =write
 - En = block enable (assert low)
 - used as chip enable (CE) for an SRAM chip



SRAM Block Architecture

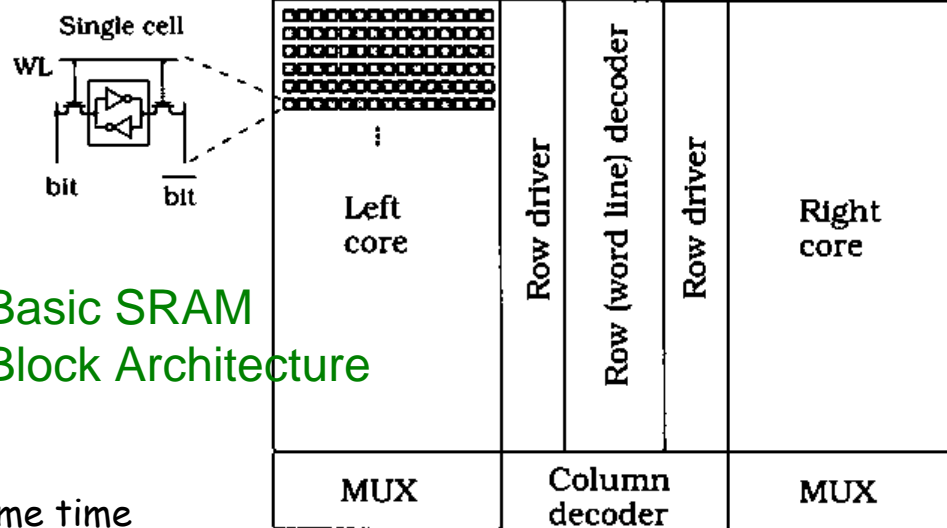- Example: 2-Core design

- core width = $k \cdot n$
 - n = SRAM word size; 8, 16, etc.
 - k = multiplier factor, 2,3,4,etc.
- shared word-line circuits
 - horizontal word lines
 - WL set by **row decoder**
 - placed in center of 2 cores
 - WL in both cores selected at same time




Basic SRAM Block Architecture

- Addressing Operation

- address word determines which row is active (which WL = 1) via **row decoder**
- row decoder outputs feed **row drivers**
 - buffers to drive large WL capacitance

- Physical Design

 - layout scheme matches regular patterning shown in schematic
 - horizontal and vertical routing




Expanded Core View





SRAM Array Addressing

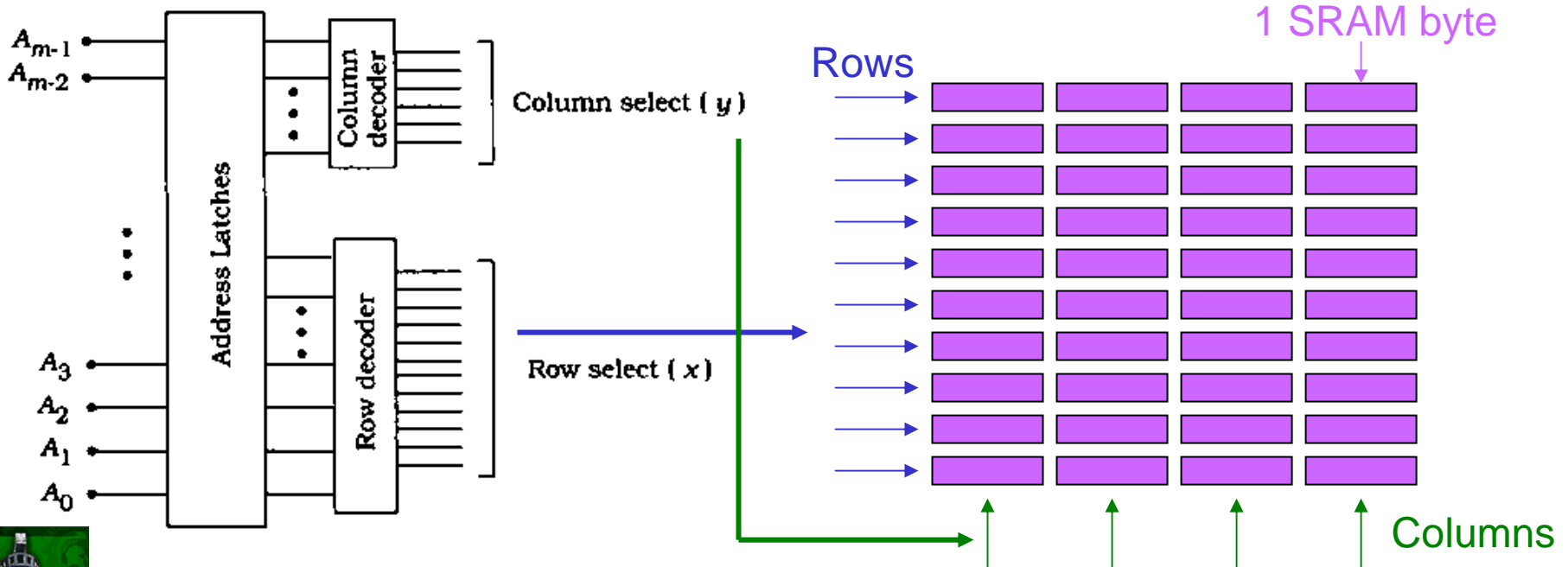- Standard SRAM Addressing Scheme
 - consider a $N \times n$ SRAM array
 - N = number of bytes, e.g., 512, 2k
 - n = byte size, e.g., 8 or 16
 - m address bits are divided into x row bits and y column bits ($x+y=m$)
 - address bits are encoded so that $2^m = N$
 - array organized with both both vertical and horizontal stacks of bytes




SRAM Array Addressing

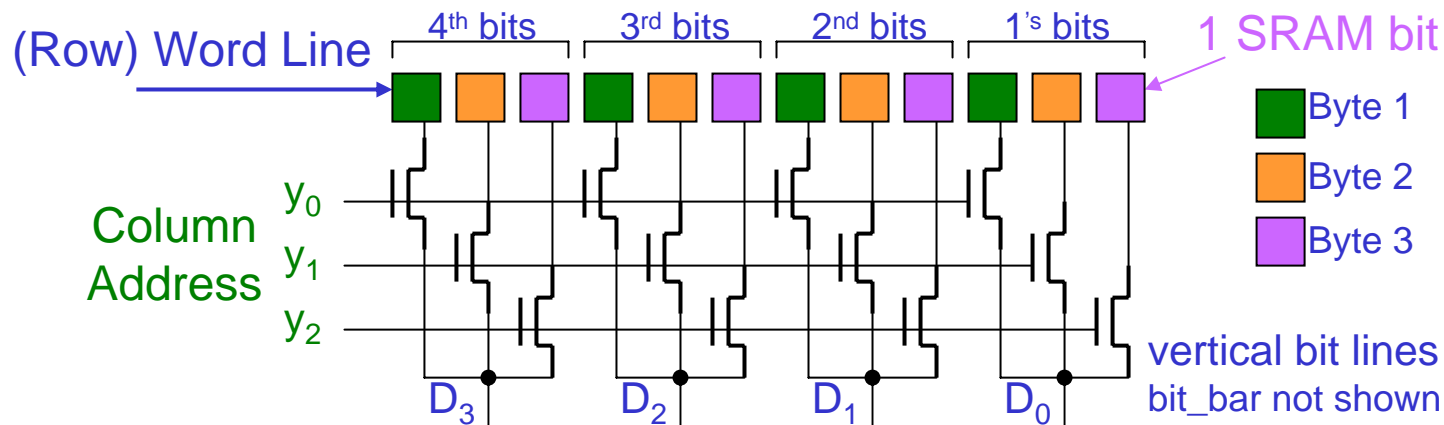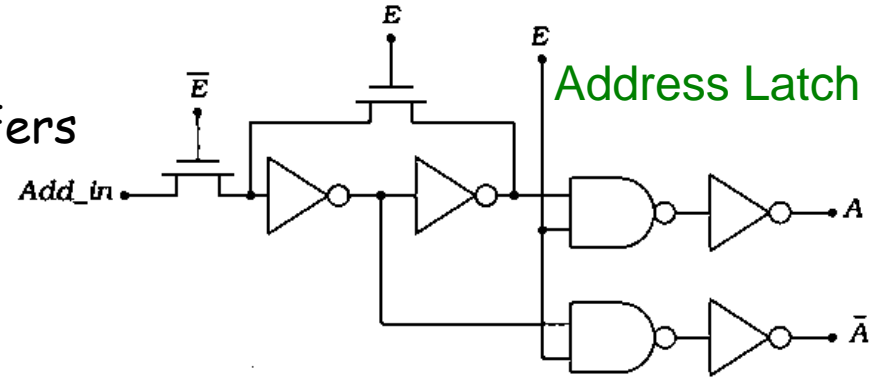- Address Latch
 - D-latch with enable and output buffers
 - outputs both A and A_{bar}
- Address Bits
 - Row address bits = Word Lines, WL
 - Column address bits select a subset of bits activated by WL
- Column Organization
 - typically, organized physically by bits, not by bytes
 - Example, SRAM with 4-bit bytes in 3 columns ($y=3$)
 - 3 4-bit bytes in each row





SRAM Array Column Circuits

- SRAM Row Driver
 - decoder output, Dec_out
 - enable, En, after address bits decoded
- Row Decoder/Driver activate a row of cells
 - each 2-core row contains 2k bytes (2k·n bits)
- Column Multiplexers
 - address signals select one of the k bytes as final output
not used in row decoder
 - figure shows example for k=3
 - for an 8-bit RAM (word size)
 - MUX used for Read operations
 - De MUX used for Write op.s
- Column Drivers
 - bit/bit_bar output for Write operations

 


Column MUX/DeMUXs

  

Column Circuitry

- Precharge Concept
 - common to use dynamic circuits in SRAMS
 - dynamic circuits have precharge and evaluate phases
 - precharge high capacitance on bit lines
 - avoids heavy capacitive loading on each SRAM cell
- Precharge Phase
 - all bit lines pulled to VDD
 - all bit_bar to ground
- Evaluate Phase
 - bits activated by WL connect to bit lines
 - if data = 1, keep precharged value
 - if data = 0, discharge bit line

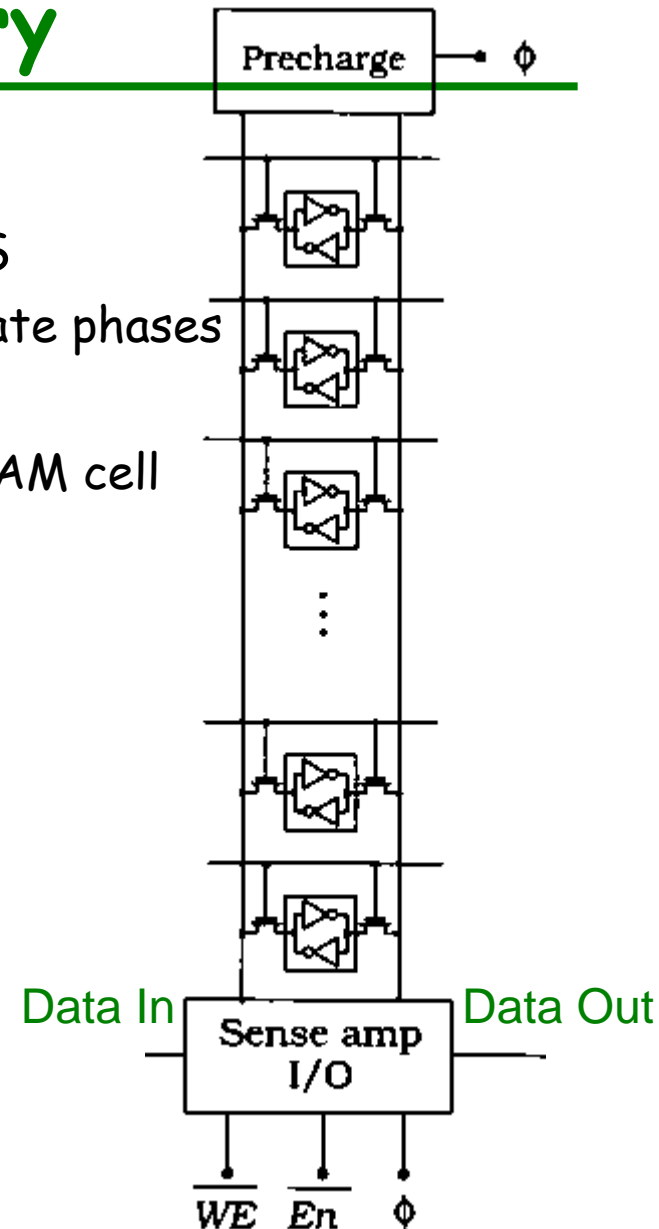


Bit line (column) Circuitry

- expanded (transistor-level) view of SRAM column

pMOS precharge loads
- charge when $\phi = 0$

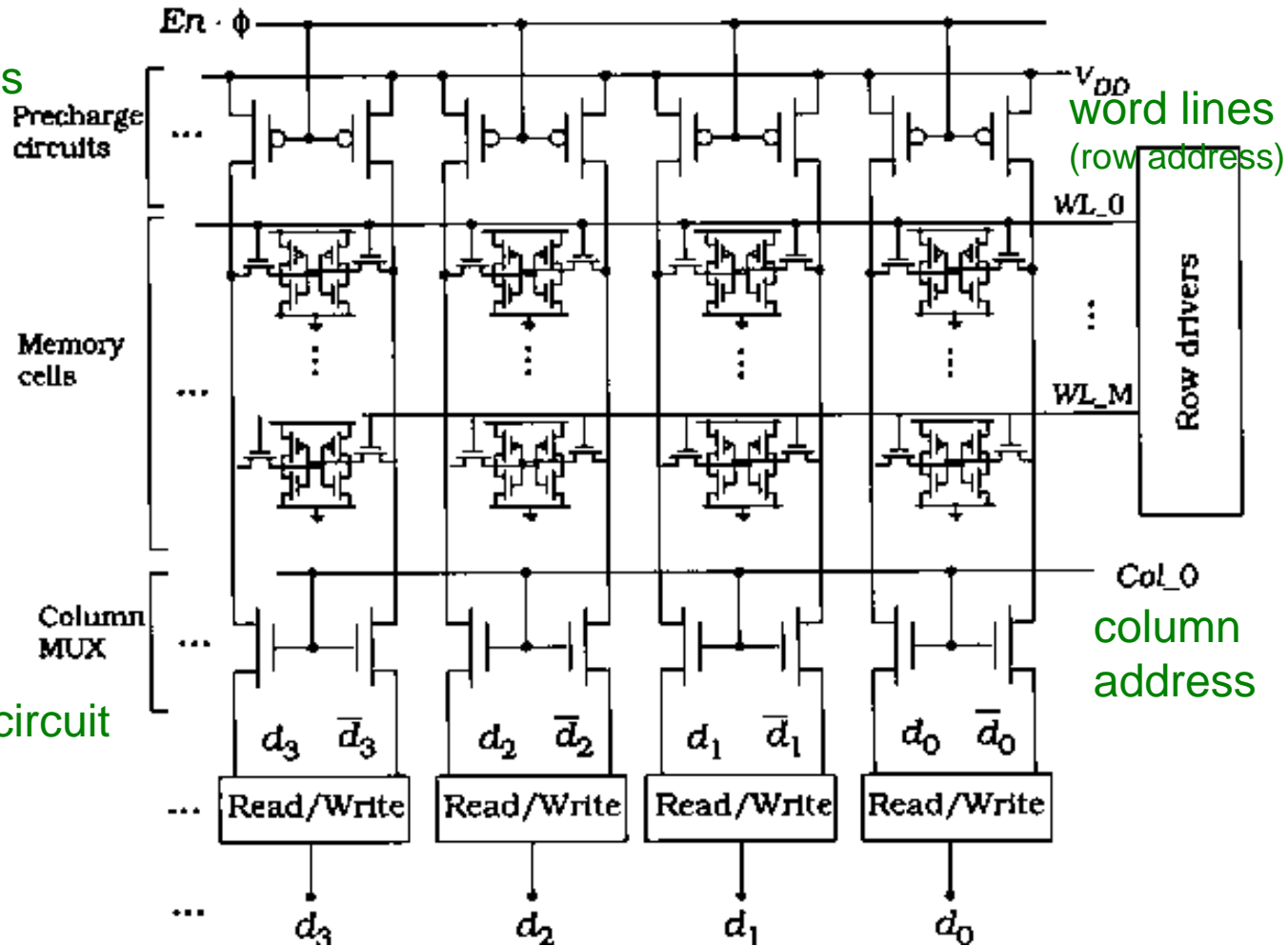nMOS switches select
which column/bit is
passed to Read/Write circuit




Sense Amplifiers

- Read sensing scheme
 - look at differential signal
 - bit and bit_bar
 - can get output before bit lines fully charge/discharge by amplifying differential signals


- Differential Amplifier

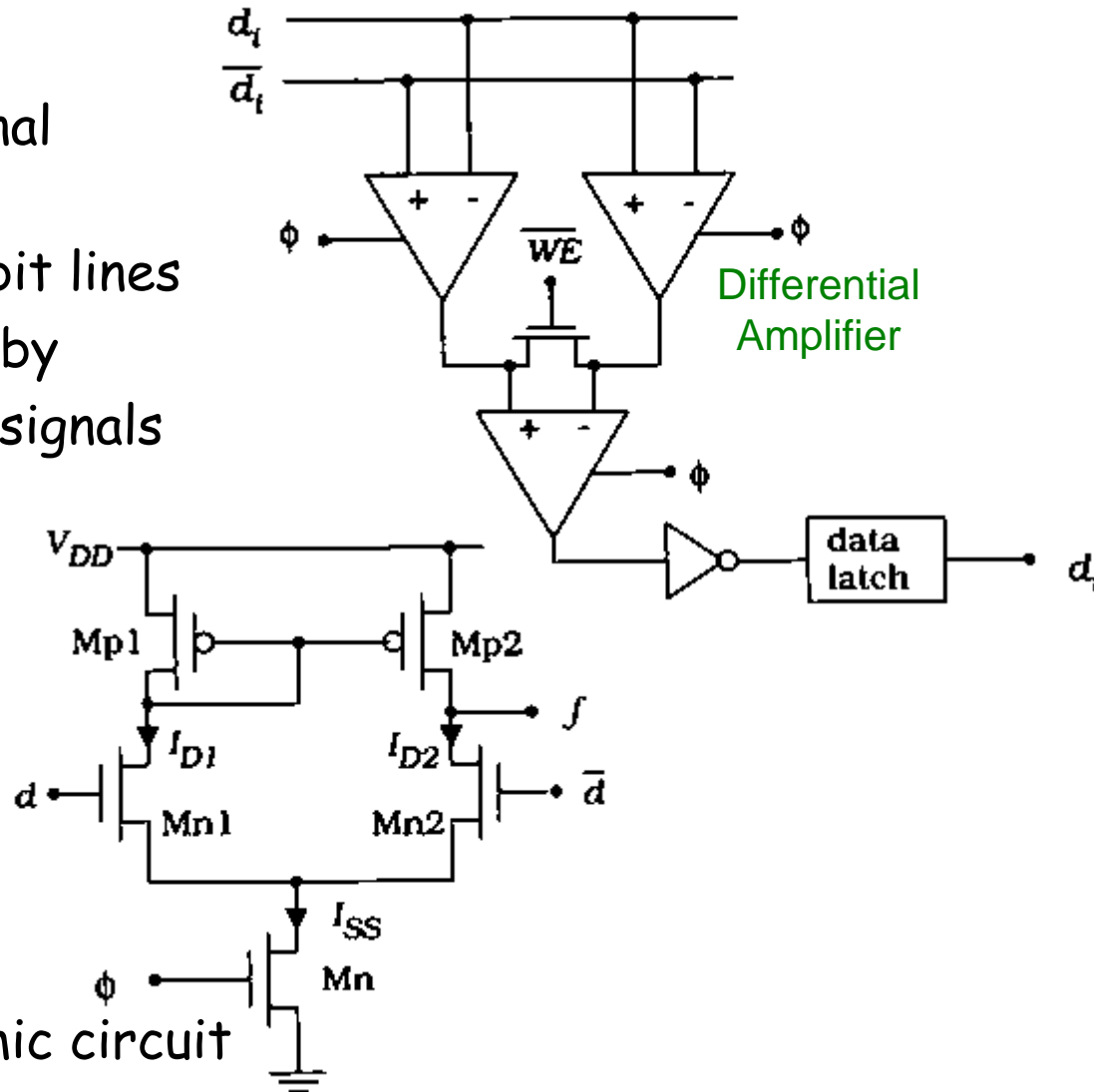- simple analog circuit
- output high
 - if bit > bit_bar
- output low
 - if bit_bar > bit
- can implement as dynamic circuit



DRAM Basics

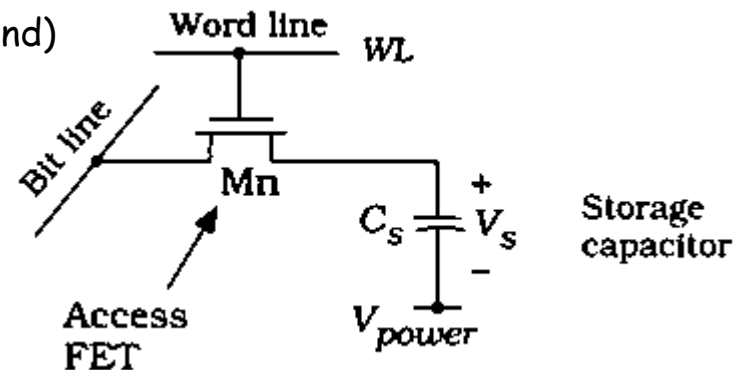- DRAM = Dynamic Random Access Memory
 - Dynamic: must be refreshed periodically
 - Volatile: loses data when power is removed
- Comparison to SRAM
 - DRAM is smaller & less expensive per bit
 - SRAM is faster
 - DRAM requires more peripheral circuitry
- 1T1R DRAM Cell
 - single access nFET
 - storage capacitor (referenced to VDD or Ground)
 - control input: word line, WL
 - data I/O: bit line



DRAM Operation


- RAM data is held on the storage capacitor
 - temporary - due to leakage currents which drain charge
- Charge Storage
 - if C_s is charged to V_s
 - $Q_s = C_s V_s$
 - if $V_s = 0$, then $Q_s = 0$: LOGIC 0
 - if $V_s = \text{large}$, then $Q_s > 0$: LOGIC 1

Write Operation


- turn on access transistor: $WL = VDD$
- apply voltage, V_d (high or low), to bit line
- C_s is charged (or discharged)
- if $V_d = 0$
 - $V_s = 0$, $Q_s = 0$, store logic 0
- if $V_d = VDD$
 - $V_s = VDD - V_{tn}$, $Q_s = C_s(VDD - V_{tn})$, logic 1

Hold Operation

 - turn off access transistor: $WL = 0$
 - charge held on C_s



(a) Write operation


 


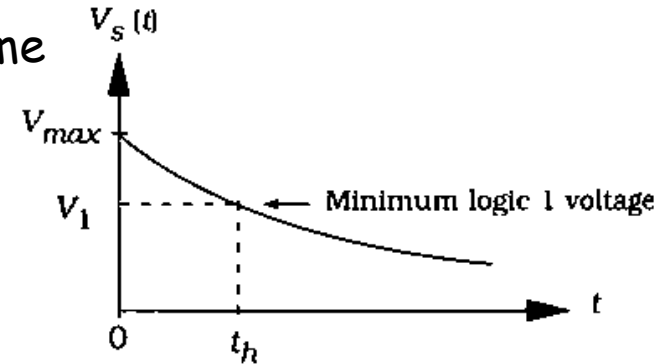 (b) Hold




Hold Time

- During Hold, leakage currents will slowly discharge C_s
 - due to leakage in the access transistor when it is OFF
 - $I_L = -\delta Q_s / \delta t = -C_s \delta V_s / \delta t$
 - if I_L is known, can determine discharge time



Hold Time, t_h

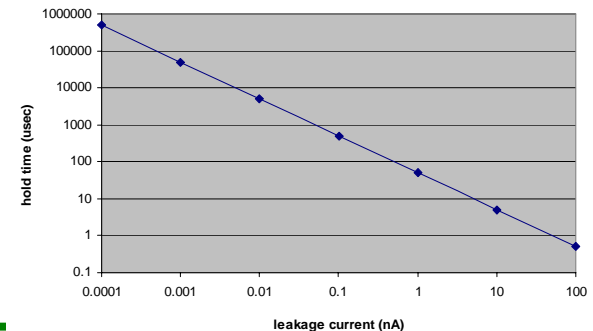- max time voltage on C_s is high enough to be a logic 1
 - = time to discharge from V_{max} to V_1 (in figure above)
- $t_h = (C_s / I_L)(\Delta V_s)$, if we estimate I_L as a constant
 - desire large hold time
 - t_h increases with larger C_s and lower I_L
 - typical value, $t_h = 50 \mu\text{sec}$
 - with $I_L = 1 \text{ nA}$, $C_s = 50 \text{ fF}$, and $\Delta V_s = 1 \text{ V}$




error in textbook, says $0.5 \mu\text{sec}$ near Eqn. 13.



Refresh Rate

 - DRAM is "Dynamic", data is stored for only short time
- Refresh Operation
 - to hold data as long as power is applied, data must be refreshed
 - periodically read every cell
 - amplify cell data
 - rewrite data to cell
- Refresh Rate, f_{refresh}
 - frequency at which cells must be refreshed to maintain data
 - $f_{\text{refresh}} = 1 / 2t_h$
 - must include refresh circuitry in a DRAM circuit



Refresh operation




DRAM Read Operation

- Read Operation
 - turn on access transistor
 - charge on C_s is redistributed on the bit line capacitance, C_{bit}
 - this will change the bit line voltage, V_{bit}
 - which is amplified to read a 1 or 0


- Charge Redistribution

 - initial charge on C_s : $Q_s = C_s V_s$
- redistributed on C_{bit} until
 - $V_{bit} = V_s = V_f$ (final voltage)
- $Q_s = C_s V_f + C_{bit} V_f$
- $C_s V_s = V_f (C_s + C_{bit})$
 - due to charge conservation
- $V_f = C_s V_s / (C_s + C_{bit})$, which is always less than V_s
 - V_f typically very small and requires a good sense amplifier



DRAM Read Operation (cont.)

- DRAM Read Operation is Destructive
 - charge redistribution destroys the stored information
 - read operation must contain a simultaneous rewrite
- Sense Amplifier
 - SA_En is the enable for the sense amplifier
 - when EQ is high both sides of the sense amp are shorted together. The circuit then holds at its midpoint voltage creating a precharge.
 - the input and output of the sense amp share the same node which allows for a simultaneous rewrite

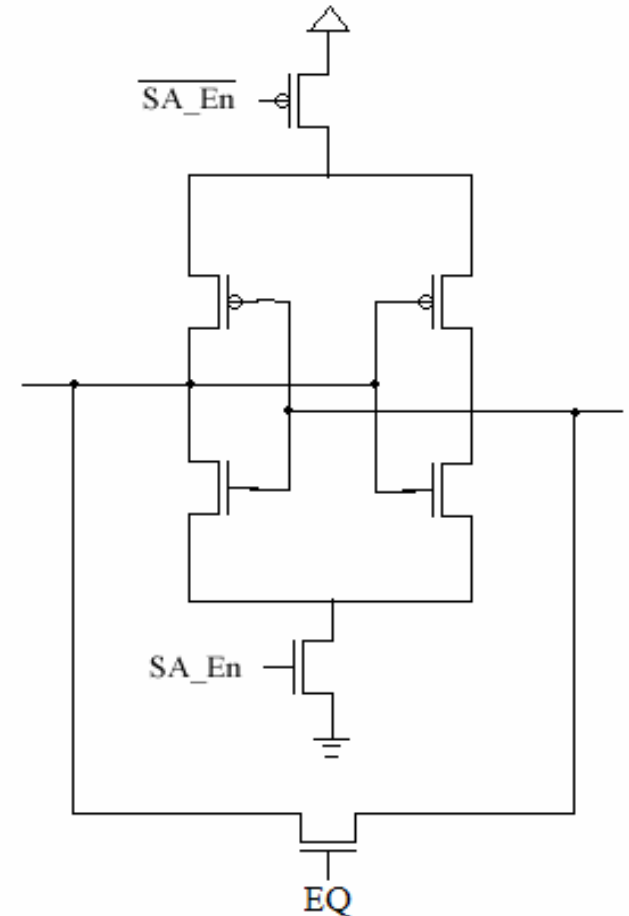


<http://jas.eng.buffalo.edu/education/system/senseamp/>




DRAM Physical Design

- Physical design (layout) is **CRITICAL** in DRAM
 - high density is required for commercial success
 - current technology provides $> 1\text{Gb}$ on a DRAM chip
- Must minimize area of the 1T DRAM cell
 - typically only 30% of the chip is needed for peripherals (refresh, etc.)
- For DRAM in CMOS, must minimize area of storage capacitor
 - but, large capacitor ($> 40\text{fF}$) is good to increase hold time, t_h
- Storage Capacitor Examples
 - **trench capacitor**
 - junction cap. with large junction area
 - using etched pit
 - **stacked capacitor**
 - cap. on top of access tx
 - using poly plate capacitor

 


A DRAM cell using a trench capacitor

 

ROM Basics

- **ROM: Read Only Memory**
 - no capabilities for "online" memory Write operations
 - data programmed
 - during fabrication: **ROM**
 - with high voltages: **PROM**
 - by control logic: **PLA**
 - **Non-volatile**: data stored even when power is removed
- **NOR-based ROM**

 - Example: 8b words stored by NOR-based ROM
- address selects an active 'row'
- each output bit connected to the active row will be high
- otherwise, output will be low




Row	Data
0	01101010
1	10010011
2	01110111
3	11011000
4	00101100




Pseudo-nMOS ROM

- Pseudo-nMOS
 - always ON active pMOS load
 - pulls output high if nMOS is off
 - controlled nMOS switch
 - pulls output low if input is high
 - competes with pMOS
 - must be sized properly
 - consumes power when output is low
- ROM Structure
 - address is decoded to choose and active 'row'
 - each row line turns on nMOS where output is zero
 - otherwise, output stays high
- Set ROM Data
 - by selectively connecting nMOS to the output lines

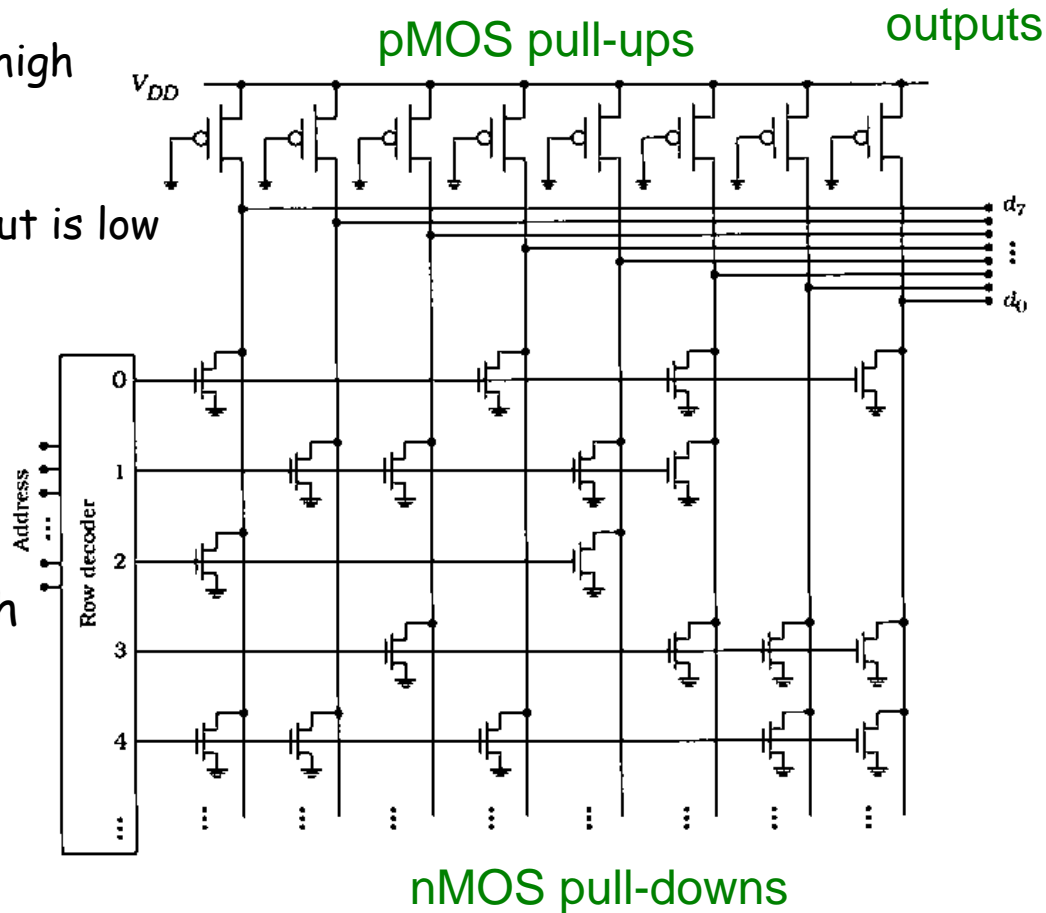


ROM Arrays

- Pseudo nMOS Arrays
 - most common style for large ROMS
- Design Concerns
 - nMOS must "overdrive" pMOS
 - need $\beta_n > \beta_p$ so that V_{OL} is low enough
 - must set $W_n > W_p$
 - but, this also increases row line capacitance
 - requires careful analog design
- Programming Methods
 - mask programmable
 - create nMOS at all points
 - define data with poly contacts
 - layout programmable
 - only place nMOS where needed
 - shown in figure →

 

ROM Array Layout

 - very "regular" layout
- high packing density
 - one tx for each data point



Programmable ROM


- PROM
 - programmable by user
 - using special program tools/modes
 - read only memory
 - during normal use
 - non-volatile
- Read Operation
 - like any ROM: address bits select output bit combinations
- Write Operation
 - typically requires high voltage (~15V) control inputs to set data
- Erase Operation
 - to change data
 - **EPROM**: erasable PROM: uses UV light to reset all bits
 - **EEPROM**: electrically-erasable PROM, erase with control voltage



PROM Storage Cells

- Physical Structure

 
- pair of stacked poly gates
 - top gate acts as normal access/control gate
 - bottom gate is 'floating', changes threshold voltage



 
(a) Symbol

- Cell Operation


- no charge on floating gate
 - transistor has normal V_{tn}
- negative charge on floating gate
 - opposes action of applied gate voltage
 - keeps transistor turned off
 - unless a high $V_{tn,H}$ is applied; $V_{tn,H} > V_{DD}$ so will not turn on with normal voltages



(b) Structure

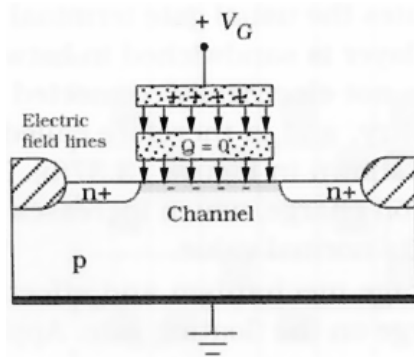

(a) Normal V_{Tn} state

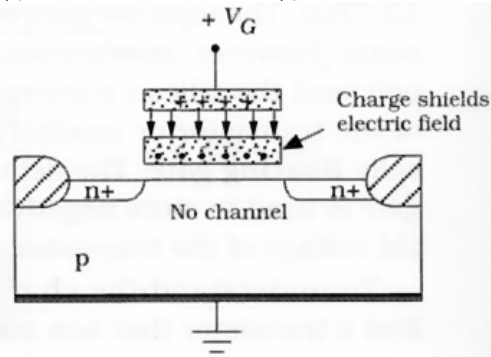


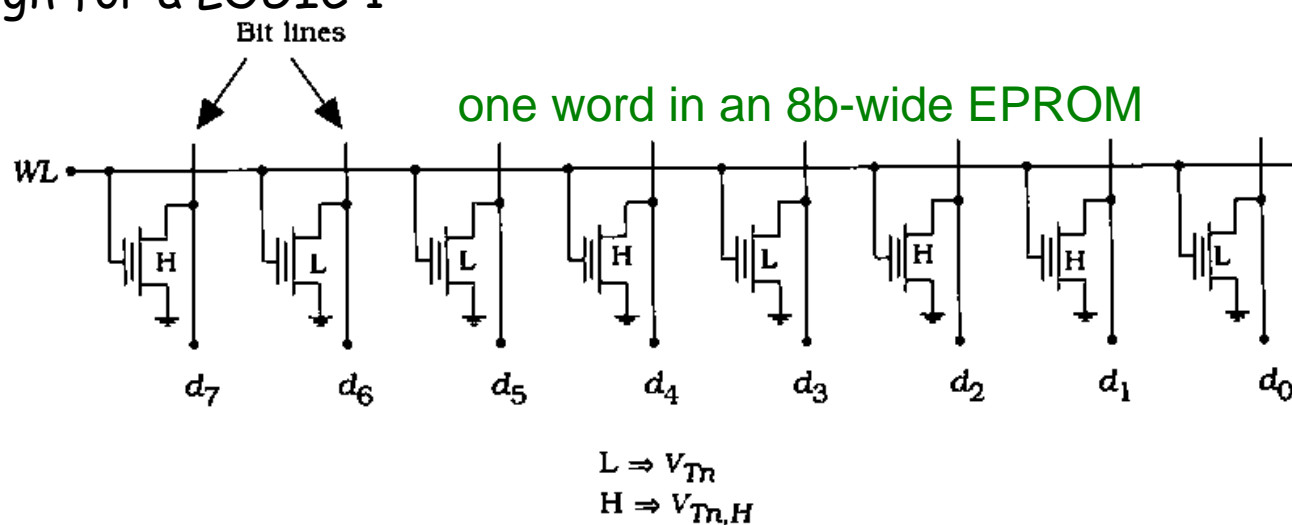(b) Increased $V_{Tn,H}$ state



EPROM Arrays

- Structure is similar to a RAM Array
- WL selects which word of data will connect to output
- When WL is high
 - each tx in the selected data byte will set the output bit line
 - if floating gate has no charge, bit line will pull down for a LOGIC 0
 - if floating gate is charged, tx will not turn on and bit line will remain high for a LOGIC 1



- Column circuitry can be used to form arrays, as in RAM



Programming & Erasing E²PROMs

- Programming techniques

- hot electron method



- charge (electrons) transferred to the floating gate by quantum mechanical tunneling of hot electrons (high energy electrons)
 - accomplished by applying a high voltage (~12-30V) to the drain node
 - charge can remain on floating gate for 10-20 years!

- Fowler-Nordheim emission

- uses modified gate geometry to allow quantum mechanical tunneling from the drain into the floating gate


- Erasure Techniques

  - bit erasure: by reversing programming voltages
 - **flash** EPROMs: erase large block simultaneously



Programmable Logic Arrays

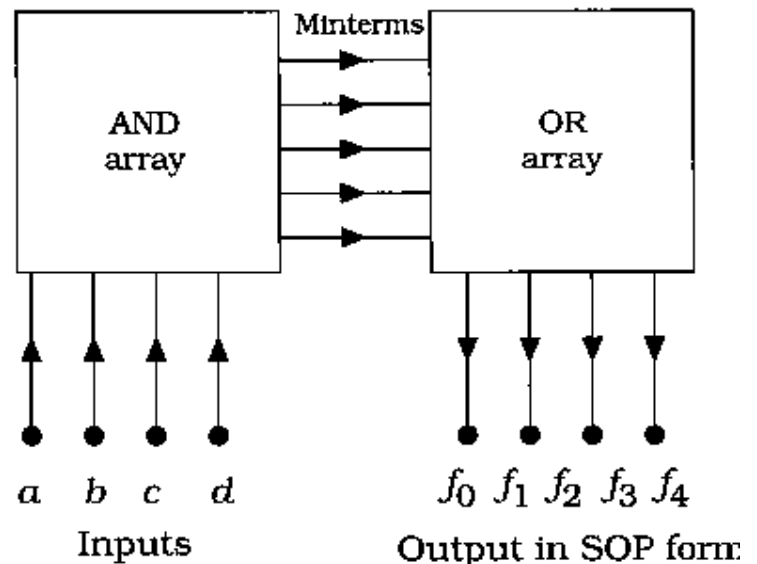- Programmable Logic Array: PLA
 - circuit which can be programmed to provide various logic functions
- Example: Sum-of-Products PLA
 - with four inputs (a, b, c, d), the possible SOP outputs are
 - $f = \sum m_i(a,b,c,d)$ [OR minterms]
 - where $m_i(a,b,c,d)$ are the minterms [AND inputs]
 - has an AND-OR structure which can be reproduced in circuits




AND-OR PLA Implementation

- Logic Array Diagram

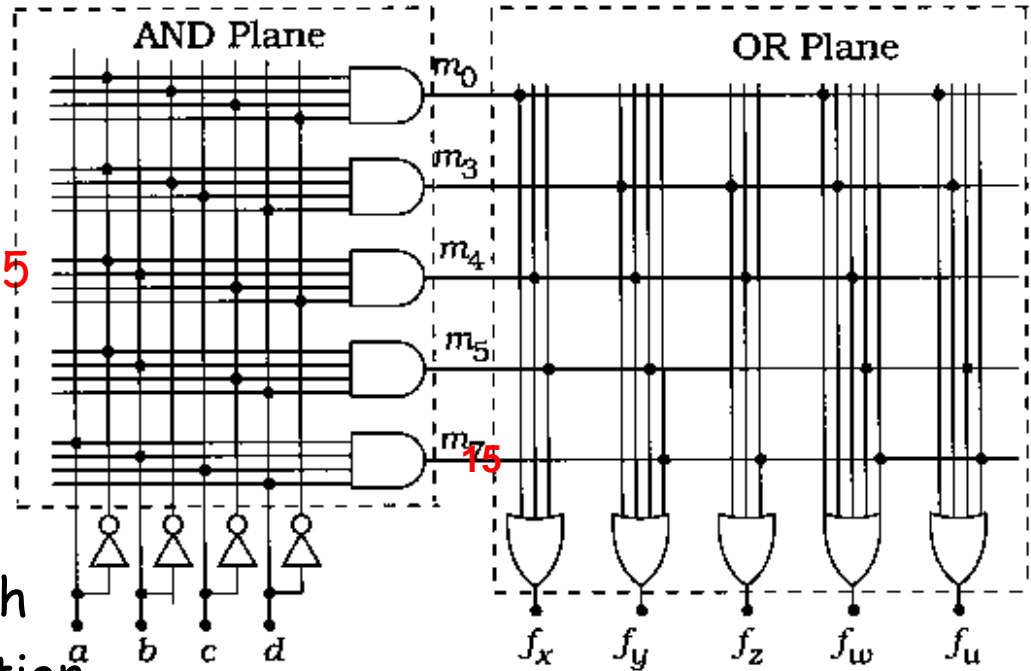- example for

- $f_x = m_0 + m_4 + m_5$
- $f_y = m_3 + m_4 + m_5 + m_{15}$
- etc.





- Programming PLA

- transistor switch at each optional connection location
- turn tx on to make connection

error in text

- VLSI Implementation

- replace AND-OR with NOR gates

  

Gate Arrays

- Gate array chip contains
 - a huge array of logic gates
 - programmable connections
 - allows gates to be combined to make larger functions (e.g., DFF)
- **Field Programmable Gate Array (FPGA)**
 - connections can be programmed easily to redefine function
 - can have more than 100,000 logic gates on an FPGA
 - capable of emulating complex functions, like a 32-bit microprocessor
 - program techniques: the antifuse concept
 - physical design: built-in fuses where connections might be wanted
 - high current short-circuits the fuse to create low resistance path

