

Cadence Tutorial C: Simulating DC and Timing Characteristics

Created for the MSU VLSI program by Professor A. Mason and the AMSaC lab group
rev S06 (convert to *spectre* simulator)

Document Contents


Introduction
Layout Extraction with Parasitic Capacitances
Timing Analysis
DC Analysis

Introduction


This document is the third of a three-part tutorial for using CADENCE Custom IC Design Tools (IC445) for a typical bottom-up circuit design flow with the AMI/C5N process technology and NCSU design kit. Tutorial A and B cover the use of the Virtuoso schematic entry tool, Affirma analog simulation tool and Virtuoso layout tool. This tutorial covers the timing analysis on the schematic and extracted view. It is assumed you have followed Tutorials A and B and have the schematic and layout views of a CMOS inverter.

Layout Extraction with Parasitic Capacitances

- Launch Cadence and open the layout view for the inverter cell.
- In the **Command Interpreter Window (CIW)**, set the capacitance-ignore-threshold by entering *NCSU_parasiticCapIgnoreThreshold=1e-18* in the prompt at the bottom of the **CIW** and pressing **Enter**. Although this was not needed for functional simulations, it will make timing analysis more accurate.
- In the **Virtuoso Layout Editing** window select **Verify => Extract**. A new window (below) with extraction options will appear.
- Click on **Set Switches** and select *Extract_parasitic_caps*. Click on **OK** to extract parasitic elements from the layout with the new parasitic capacitance threshold.
- After extraction, check the **CIW** to make sure there are no errors.
- Load the extracted cellview from the **Library Manager** window. This will open up a layout should look similar to the one below. Press **shift+f** to see all the device parameters.

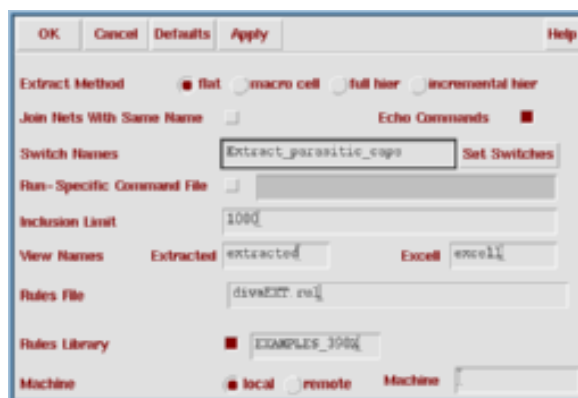

Extract Window

 


Extracted Layout View

Timing Analysis


STEP 1. Start Analog Environment

- With the extracted view open, in the **Virtuoso Layout Editing** window select **Tools => Analog Environment** to open the **Affirma Analog Circuit Design Environment** window.
 - You can also launch this tool from the **CIW** by selecting **Tools => Analog Environment => Simulation** in the **CIW**. When the **Affirma Analog Circuit Design Environment** opens you have click on the **Setup => Design** to specify the library and cell, for example “tutorial” and “inv”.

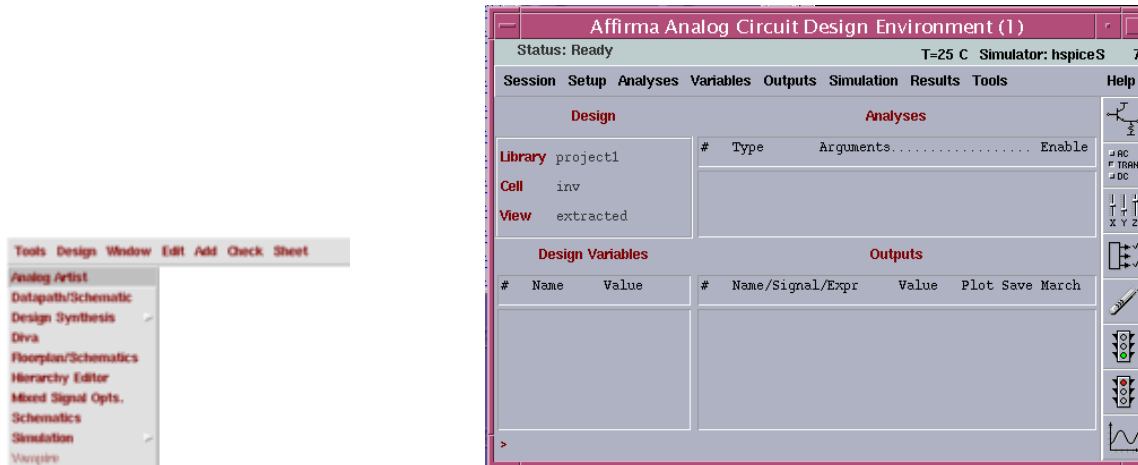


STEP 2. Setup Analog Simulator

- In **Affirma Analog Circuit Design Environment**, click on **Setup => Simulator/Directory/Host**.
- Choose **spectre** as the Simulator.
- Enter a path for your simulations files and results. You may set this to any valid path, but you might find it useful to keep all simulations in one directory. If you don't specify the whole path, the simulation files and results will be created under the directory you launched cadence. The following example saves the simulation file and results at `/egr/courses/personal/ece410/<username>/simulation` assuming you launched Cadence from your root 410 class directory. If you need to run multiple simulations on the same cell, you can even use different paths for each simulation.

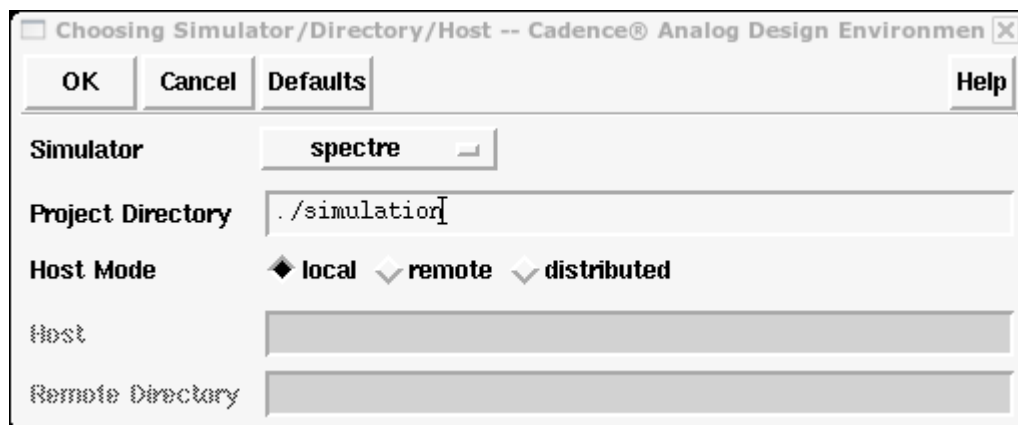

STEP 3. Set up Analog Environment to use Extracted View

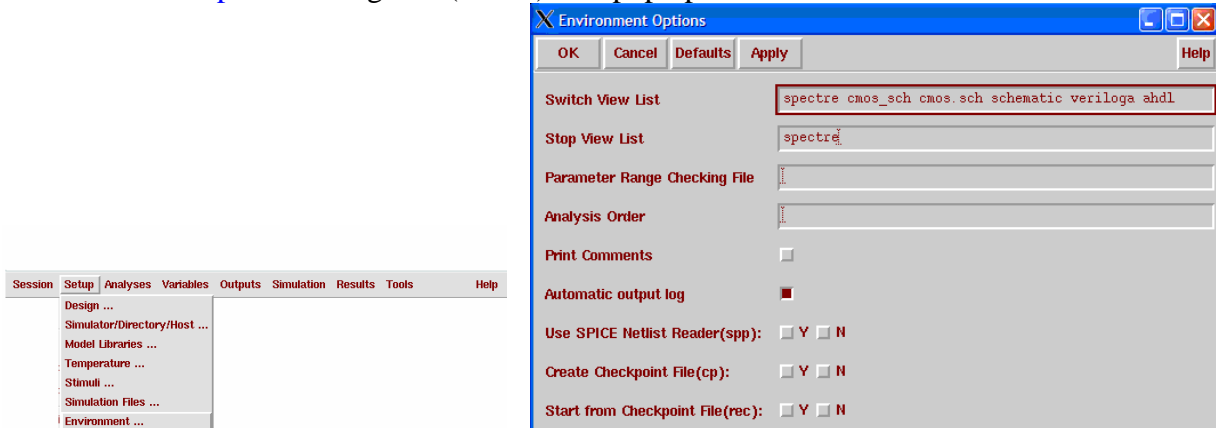- In **Affirma Analog Circuit Design Environment**, click on **Setup => Environment**. The **Environment Options** dialog box (below) will pop up.



- In the **Environment Options** window, under the line *Switch View List*, type the word “**extracted**” before the word “schematic” (see below). Then click on **OK**.

This entry is an ordered list of cell views which contain information that can be simulated. The simulator (in fact the netlister) will search until it finds one of these cellviews. The default entry does not contain an *extracted* cellview. As a result of this modification, the simulator will use the extracted cellview instead of the schematic cellview to include the effect of parasitic capacitance in the simulation.



- Make sure to check the **Y** for **Use SPICE Netlist Reader(spp)**, since the default transistor model files are written in SPICE syntax.

STEP 4. Set up stimulus file


- Create a new stimulus file by opening any text editor. Make sure to give the file a name either when you create it or when you save it, depending on your text editor (“stimulus.txt”, for example).
- Enter the following text, save the file and exit the text editor. (*Note: each circle bulleted item below represents one full line in the stimulus file; be careful if you cut and paste this text. You also need to be sure to hit Enter after the last line to insert a line return in the text file.*)
 - o simulator lang=spectre
 - o Vdd (vdd! 0) vsource dc=3
 - o v1 (A 0) vsource type=pulse val0=0 val1=3 rise=0.05n fall=0.05n width=10n period=20n
 - o c0 (0 Y) capacitor c=3f

This assumes your input and output node are called ‘A’ and ‘Y’ and attaches a load capacitance to the output that simulates the input capacitance of gates attached to the output node. For additional information about stimulus files, including notes on creating files with multiple inputs, see the [Guide to Writing Stimulus Files](#).

- In the **Affirma Analog Circuit Design Environment**, include this new stimulus file by clicking **Setup => Simulation Files** and adding the name of the file in the “Stimulus File” box.



STEP 5. Setup Analysis

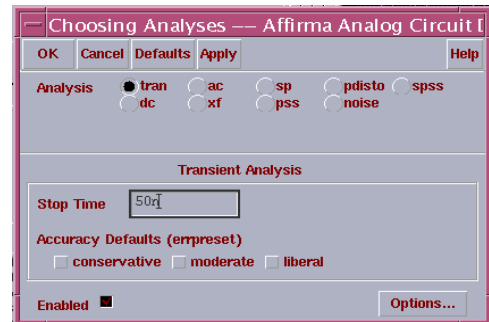- In **Affirma Analog Circuit Design Environment** window, select **Analyses => Choose**.
- In the window that pops up, select **tran** to choose a transient analysis.
- Enter the time limits for simulation: Set the *Stop Time* to “**50n**”.
- Choose **Enabled** at the bottom of the screen and press **OK**.



STEP 6. Setup output traces


- In **Affirma Analog Circuit Design Environment** window, select **Outputs => to be plotted => Select on Schematic**. This will activate the **Layout Editing** window with the extracted view of the inverter, allowing you to pick which signals (nets/wires) you would like to have plotted during the simulation.
- In the **Layout Editing** window select input gate **poly** and output **metal1** (see example below).
- This will complete the simulation setup. Now your **Affirma Analog Circuit Design Environment** window should look as follows (*names may vary*):

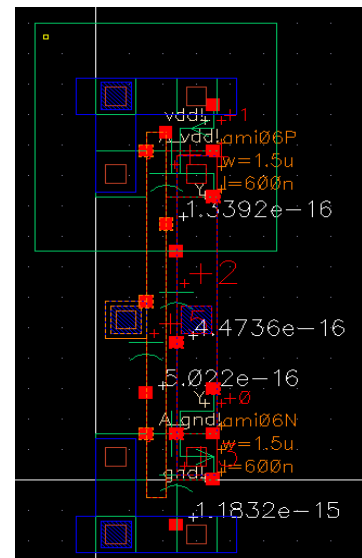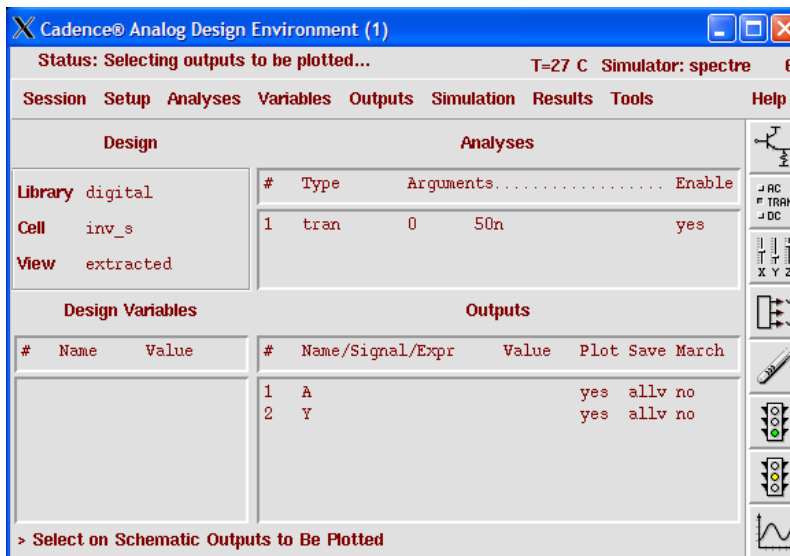

STEP 7. Run Simulation

- In the **Affirma Analog Circuit Design Environment** window select **Simulation => Netlist and Run**.
- When the simulation is complete, the **CIW** should show "Reading Simulation Data Successful". If the simulation was not successful, go to **Simulation => Output Log** in your **Affirma Analog Circuit Design Environment** to find out what the problem was.

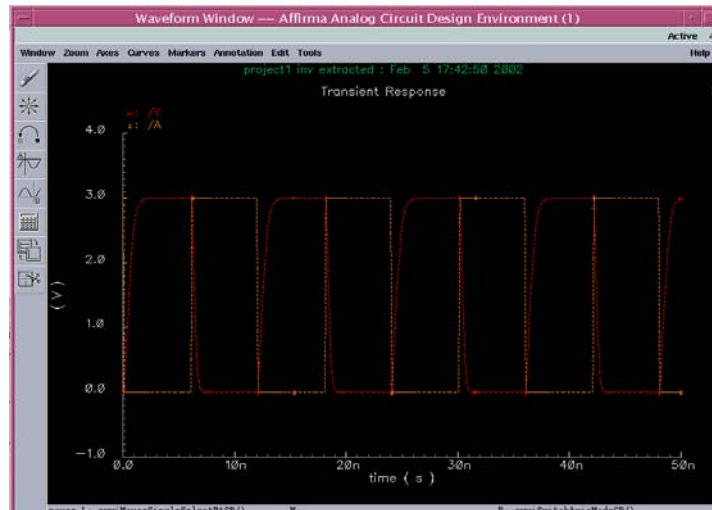After a successful simulation, an output signal plot will pop up. As shown in the plot here, you should now see delays in the output signal due to the parasitics. If the simulated output waveform looks like the function you are expecting, you have probably done everything correctly. If not, check your steps and repeat until the correct output is obtained.




STEP 8. Measure Propagation Delay

- In the **Waveform Window** click on **Axes => To Strip** to separate input and output signals.
- Click on **Markers => Crosshair Marker A / Crosshair Marker B** (hotkey: a, b) and use them to measure the rising propagation delay and falling propagation delay.
- To obtain a plot with higher resolution, you can run the simulation again showing only 1 or 2 cycles, say with a stop time of 25nsec.
- To make measurements with the markers, first you should select *Crosshair Marker A* and locate where input signal (A) raises to 1.5V (half of VDD). Then select *Crosshair Marker B* and locate where output signal (Y) falls to 1.5V. Finally, the **delta** values shown at the left-bottom corner of the window is falling propagation delay time of your inverter. Use same method find out what the rising propagation delay time is. Record these values and use them to calculate the total propagation delay.

STEP 9. Measure Rise and Fall Times

- Measure and record the output rise time and fall time using the crosshair markers A and B as in Step 8.

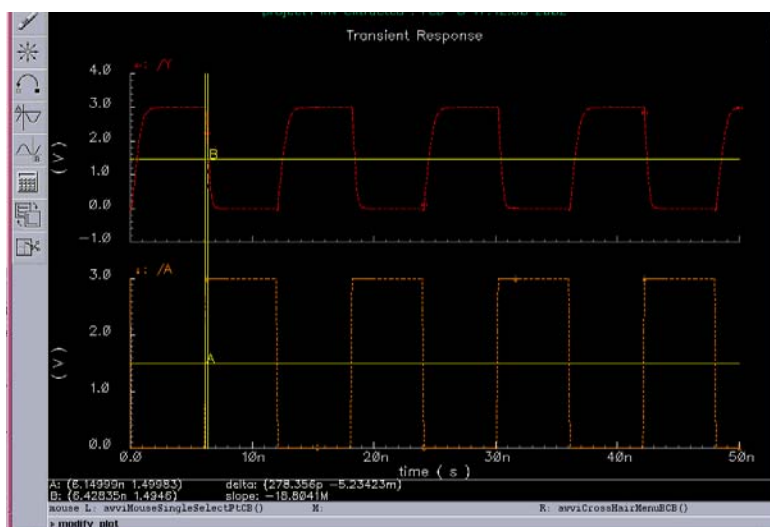Rise time of the output is defined as the time taken for the output to rise from 10% of the final value to 90% of the final value (If the output rises from 0v to 3v, then rise time is the time for the voltage to change from 0.3v to 2.7v).



Similarly the fall time of the output is defined as the time for the output signal to fall from 90% of the final value to 10% of the final value (If the output falls from 3v to 0v, then fall time is the time for the voltage to change from 2.7v to 0.3v).

DC Analysis

STEP 10. Setup Simulation

- Open a new text file (any file name is fine). Enter the following text, save the file and exit the text editor.
 - simulator lang=spectre
 - parameters vs=0
 - vdd (vdd! 0) vsource dc=3
 - v1 (A 0) vsource dc=vs
 - dcs dc param=vs start=0 stop=3 step=0.01

This assumes your input node is called ‘A’. Note an output capacitance is not needed since we are doing a DC analysis and timing will not be considered. Instead a DC statement is needed.

line 2: the “parameters” statement declares a simulation variable called “vs”, which is initialized to 0. This parameter will be used to sweep the dc value of the voltage at input node A. You can give this any name and starting value.

line 3: the standard definition of dc voltage “vdd!”

line 4: definition of a voltage source at the input node A. Notice that the dc voltage value is set to the variable “vs” as defined in line 2. This allows the value to be swept instead rather than being constant.

line 5: the DC sweep statement. The first field “dcs” is the name of the dc sweep (can be any alphanumeric name). The second field “dc” is required to specify the command. The third field “param=vs” specifies the parameter to be swept; in this case, it is the voltage at the inverter input. The fourth and fifth fields (“start” and “stop”) specify the bounds of the sweep. The sixth field “step=0.01” specifies the sweep step interval. Decreasing/increasing this value will increase/decrease the dc operating point precision, but take more/less time to simulate.


- In the [Affirma Analog Circuit Design Environment](#), include this new stimulus file by clicking **Setup => Simulation Files**. If a file exists in the “Stimulus File” box, delete it. Then add the name of the new file in the “Stimulus File” box.

STEP 11. Setup Analysis

- In [Affirma Analog Circuit Design Environment](#) window, select **Analyses => Choose**.
- In the window that pops up, select **dc** to choose a DC analysis.
- Choose **Save DC Operating Point** and press **OK**.

STEP 12. Setup Output Traces

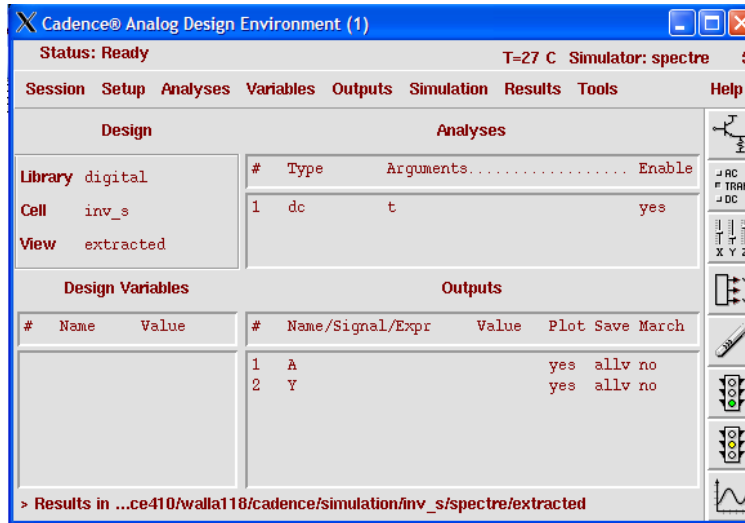- In [Affirma Analog Circuit Design Environment](#) window, select **Outputs => to be plotted => Select on Schematic** and pick the input and output nets again as you did for the transient analysis above. This will complete the simulation setup. Now your [Affirma Analog Circuit Design Environment](#) window should look like the window below.




STEP 13. Run Simulation

- In the [Affirma Analog Circuit Design Environment](#) window select **Simulation => Netlist and Run**.
- When the simulation is complete, the CIW should show "**Reading Simulation Data** **Successful**". If the simulation was not successful, go to **Simulation => Output Log** in your [Affirma Analog Circuit Design Environment](#) to find out what the problem was.

After a successful simulation, an output signal plot will pop up showing the *voltage transfer curve*. If the plot does not look like you would expect, check your steps and repeat until the correct output is obtained.

STEP 15. Measure DC Parameters

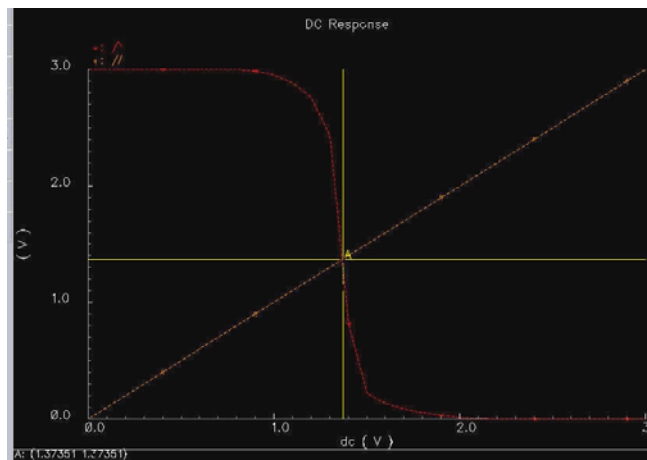
- Using the crosshair markers, measure the switching threshold (midpoint voltage), where the input voltage is equal to the output voltage.
- Measure the output high voltage and output low voltage.



OPTIONAL. Saving Simulation State

The Analog Design Environment state can be saved so that the settings do not need to be manually entered each time a design is simulated.

 - To save the simulation state, in the [Affirma Analog Circuit Design Environment](#) window select **Session => Save State**




The “Save As” field does not have to be a unique name for all designs; the state is saved within the directory of the current cell view, so you can use the same Save As name for multiple cells without overwriting each other.. For example, cells named inv and nand2 can both independently have the state “state1” saved.

- Enter a Save As name, e.g., “state1” and click on “OK”.

Saving all simulation data can take a lot of memory so you may find it useful to alter the What to Save parameters to save only the items you need to run future simulations. Saving outputs from complex cells with multiple plotted node waveforms can generate very large files.

OPTIONAL. Loading Simulation State

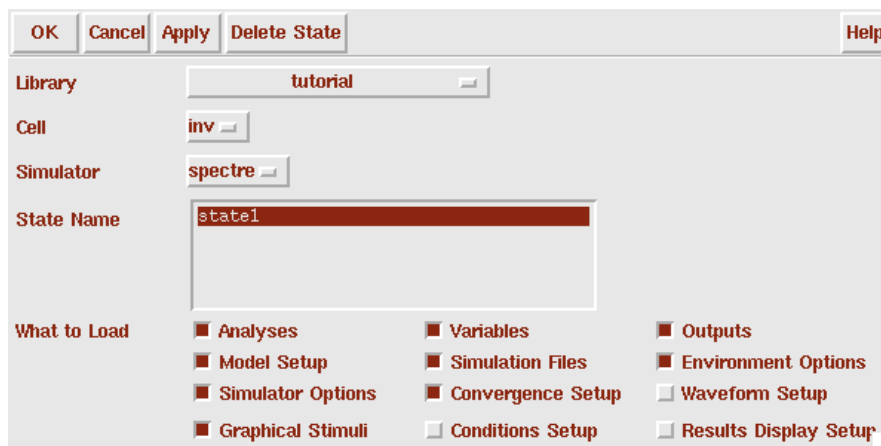- To load the saved state, after opening a specific cell, in the [Affirma Analog Circuit Design Environment](#) window select **Session => Load State**



- Select the desired State Name and click on “OK”.

THE END